

- 5 (15pt) Design a digital lock with one input and one output. The output = 1 (indicating the lock is unlocked) only when the input sequence of 1011 is observed. After unlocking, output is reset to 0 regardless of the input.
- 6 (15pt) Design a 5-to-32 line decoder using one 2-to-4 line decoder and four 3-to-8 line decoders. Enable input can be added in the decoders.

So: $x \mid x$

$$S1 = x10x$$

$$S_2 = x \mid 0 \mid x$$

$$S_3 = X \quad 1011$$

$$S_0 \begin{matrix} \nearrow 1 \\ \searrow 0 \end{matrix} \begin{matrix} S_0 \\ S_1 \end{matrix}$$

$$S_1 \xrightarrow{1} S_2$$

$$\begin{array}{ccc} S_2 & \xrightarrow{1} & S_3 \\ & \searrow & \\ 0 & & S_1 \end{array}$$

$S_3 \xrightarrow{1} S_0$
 \searrow
 S_0
 $rc_4 = 32$

$$D_A = AB'X + A'BX$$

$$p_B = B'X' + AP_1'$$

$$y = AB'x$$

