

EE 203001 Session 15

Che Lin

Institute of Communications Engineering


Department of Electrical Engineering

Ch 8.2 Graphs and Networks

Small world graphs

$$G = \{\text{nodes, edges}\}$$

= collection of nodes joined by edges

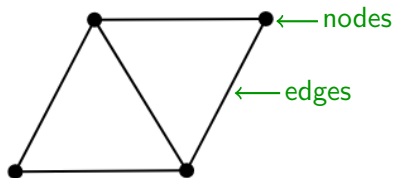

Ch 8.2 Graphs and Networks

Social Network

Each node is a person, and two nodes are connected by edge if they are friends

Q: What is the farthest distance between two people in the graph ?


Six degree of separation
⇒ It's a small world!

Other Example

www : nodes are websites
edges are links

Ch 8.2 Graphs and Networks

Electrical Network

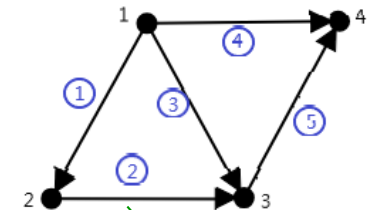

$n = 4$ nodes
 $m = 5$ edges

(direction of currents) (Directed graph)

Ch 8.2 Graphs and Networks

Incident Matrix

one col. for each node, and one row for each edge

If edge runs from node 1 \rightarrow node 2

(-1 in col 1) (+1 in col 2)

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} \text{ edge}$$


Node 1 2 3 4

(Incident matrix A if large is sparse in general
 \Rightarrow most entries are zero)

(Each row only has two non-zero entries)

Ch 8.2 Graphs and Networks

Loops :

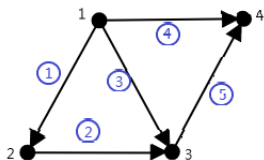

$n = 4$ nodes
 $m = 5$ edges

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

Node 1 2 3 4

edge
1
2
3
4
5

} linearly dependent
(row 3 = row 2 + row 1)

Ch 8.2 Graphs and Networks

Null space of A

$\mathbf{x} = (x_1, x_2, x_3, x_4)$: potentials at nodes

$$A\mathbf{x} = \mathbf{0} \Rightarrow A\mathbf{x} = \begin{bmatrix} x_2 - x_1 \\ x_3 - x_2 \\ x_3 - x_1 \\ x_4 - x_1 \\ x_4 - x_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \Rightarrow \mathbf{x} = c \begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix}$$

(difference of potentials)
 $\Rightarrow \dim(\mathbf{N}(A)) = 1$ with basis $\begin{bmatrix} 1 \\ 1 \\ 1 \\ 1 \end{bmatrix}$
(Nothing will move if all potentials are the same)

(or potential difference = 0)

(But potentials can only be determined up to a constant)

(If we ground node 4, $x_4 = 0 \Rightarrow x_1 = x_2 = x_3 = 0$)

Ch 8.2 Graphs and Networks

Q: What is rank(A) ?

$$\text{rank}(A) + \dim(\mathbf{N}(A)) = n = 4$$

$$\Rightarrow \text{rank}(A) = 4 - 1 = 3$$


(We can also see this via Elimination)

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \Rightarrow R = \begin{bmatrix} 1 & 0 & 0 & -1 \\ 0 & 1 & 0 & -1 \\ 0 & 0 & 1 & -1 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

$\uparrow \quad \uparrow \quad \uparrow$
basis for $\mathbf{C}(A)$ pivot col.

(Top 3 rows of R are independent
 \Rightarrow the graph it forms has no loops
 \Rightarrow It's a tree !)

(This is a tree
with no loops)

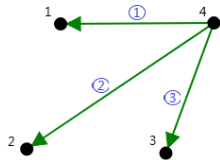

Ch 8.2 Graphs and Networks

Left nullspace $\mathbf{N}(A^T)$

$$A^T \mathbf{y} = \mathbf{0}$$

$$\begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\dim(\mathbf{N}(A^T)) = m - r = 5 - 3 = 2$$

($\mathbf{y} = (y_1, y_2, y_3, y_4, y_5)$ are currents
& $A^T \mathbf{y} = \mathbf{0}$ is Kirchhoff's current law)

(will come back to this later)


Ch 8.2 Graphs and Networks

Left nullspace $\mathbf{N}(A^T)$ (cont.)

Basis :

$$\begin{array}{llll} \text{node 1 :} & -y_1 & & -y_3 & -y_4 \\ \text{node 2 :} & y_1 & -y_2 & & \\ \text{node 3 :} & & y_2 & +y_3 & -y_5 \\ \text{node 4 :} & & & y_4 & +y_5 \end{array}$$


(current in = current out)
($-y_1$: current out, $+y_1$: current in)

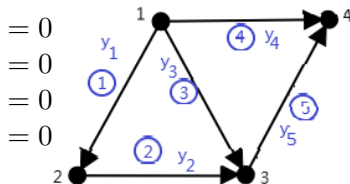

Ch 8.2 Graphs and Networks

Left nullspace $N(A^T)$ (cont.)

Basic by inspection :

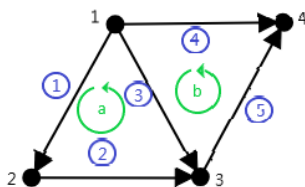

current
in loops

$$\text{loop : } \mathbf{y} = \begin{bmatrix} 1 \\ 1 \\ -1 \\ 0 \\ 0 \end{bmatrix}, \begin{bmatrix} 0 \\ 0 \\ 1 \\ -1 \\ 1 \end{bmatrix}$$

(loop a) (loop b)

($\text{Dim}(N(A^T)) = 2$ so only need these two vectors for a basis)

(Outer loop also gives a special solution $(1, 1, 0, -1, 1)$)

Ch 8.2 Graphs and Networks


Row space $C(A^T)$

$$A^T = \begin{bmatrix} -1 & 0 & -1 & -1 & 0 \\ 1 & -1 & 0 & 0 & 0 \\ 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 \end{bmatrix}$$

pivot col.s

not a pivot col. since
node 1, 2, 3 forms a loop
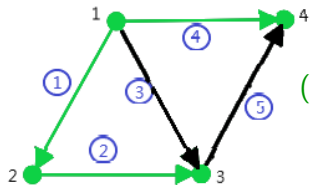
$$\text{rank}(A) = 3 \Rightarrow \dim(C(A^T)) = 3$$



(linear independent edges 1, 2, 4
form a tree)

Ch 8.2 Graphs and Networks

Complete picture

$\mathbf{x} = (x_1, x_2, x_3, x_4)$
potentials at nodes

$A^T \mathbf{y} = \mathbf{0}$
Kirchhoff's current law

$\downarrow A\mathbf{x} = \mathbf{e}$ (conductance matrix) $\uparrow A^T \mathbf{y}$

$x_2 - x_1$, etc.
potential differences

$\mathbf{y} = -\mathbf{C}\mathbf{e}$
Ohm's law

y_1, y_2, y_3, y_4, y_5
currents on edges

Ch 8.2 Graphs and Networks

Euler's Formula

$$\dim(\mathbf{N}(A^T)) = m - r$$

$$\# \text{ loops} = \# \text{ edges} - (\# \text{ nodes} - 1)$$


(rank = $n - 1$) ($\dim(\mathbf{N}(A^T))$ always = 1)

$$\Rightarrow \# \text{ nodes} - \# \text{ edges} + \# \text{ loops} = 1$$

(small loops)

(True for any connected graph)

Ex:

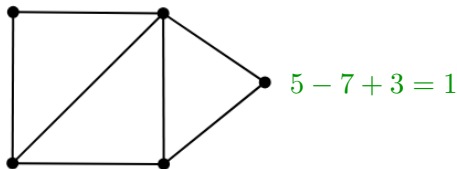

Ch 8.2 Graphs and Networks

One more thing

Still need an outside source to drive circuit

Current source \mathbf{f}


$\mathbf{x} = (x_1, x_2, x_3, x_4)$
potentials at nodes

$A^T \mathbf{y} = \mathbf{f}$
Kirchhoff's current law

$\downarrow A\mathbf{x} = \mathbf{e}$ (conductance matrix)
 $x_2 - x_1$, etc.
potential differences

$\mathbf{y} = -\mathbf{C}\mathbf{e}$
Ohm's law

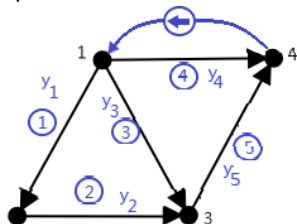$\uparrow A^T \mathbf{y}$
 y_1, y_2, y_3, y_4, y_5
currents on edges



(outside current source $\mathbf{f} = \begin{bmatrix} -s \\ 0 \\ 0 \\ 0 \end{bmatrix}$)

Ch 8.2 Graphs and Networks

Combing all 3 equations

$$A^T C A \mathbf{x} = -\mathbf{f}$$


symmetric matrix

Ch 8.2 Graphs and Networks

Ex1: in textbook (p. 427)

All conductances are $c = 1$ so $C = I$

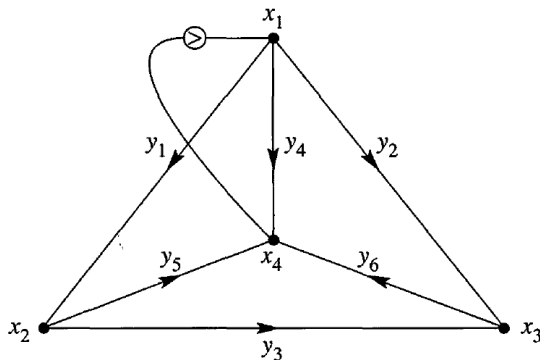


Figure 8.5: The currents in a network with a source S into node 1.

Ch 8.2 Graphs and Networks

Ex1: (cont.)

$$A = \begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$

$$\Rightarrow A^T C A = A^T A$$

$$= \begin{bmatrix} -1 & -1 & 0 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 & -1 & 0 \\ 0 & 1 & 1 & 0 & 0 & -1 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix}$$
$$= \begin{bmatrix} 3 & -1 & -1 & -1 \\ -1 & 3 & -1 & -1 \\ -1 & -1 & 3 & -1 \\ -1 & -1 & -1 & 3 \end{bmatrix}$$

Ch 8.2 Graphs and Networks

Ex1: (cont.)

Ground node 4 $\Rightarrow x_4 = 0$

\Rightarrow remove col. 4 and row 4 from $A^T C A$

Solve

$$\begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} s \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} x_1 \\ x_2 \\ x_3 \end{bmatrix} = \begin{bmatrix} \frac{s}{2} \\ \frac{s}{4} \\ \frac{s}{4} \end{bmatrix}$$

Ch 8.2 Graphs and Networks

Ex1: (cont.)

By Ohm's law $\mathbf{y} = -C\mathbf{A}\mathbf{x}$ ($x_4 = 0$)

$$\begin{bmatrix} y_1 \\ y_2 \\ y_3 \\ y_4 \\ y_5 \\ y_6 \end{bmatrix} = \begin{bmatrix} -1 & 1 & 0 & 0 \\ -1 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 \\ -1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 \\ 0 & 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \frac{s}{2} \\ \frac{s}{4} \\ \frac{s}{4} \\ 0 \end{bmatrix} = \begin{bmatrix} \frac{s}{4} \\ \frac{s}{4} \\ 0 \\ \frac{s}{2} \\ \frac{s}{4} \\ \frac{s}{4} \end{bmatrix}$$