

# Registers and Counters

---


Ch.6

# Outline

---


- . Registers
- . Parallel Data Transfer
- . Parallel Addition with Accumulator
- . Serial Data Transfer
- . Serial Addition
- . Counters
  - Ripple Counters vs Synchronous Counters
  - Binary Counter
  - BCD Counter
  - Counters for Other Sequences

# Data Path vs Control unit

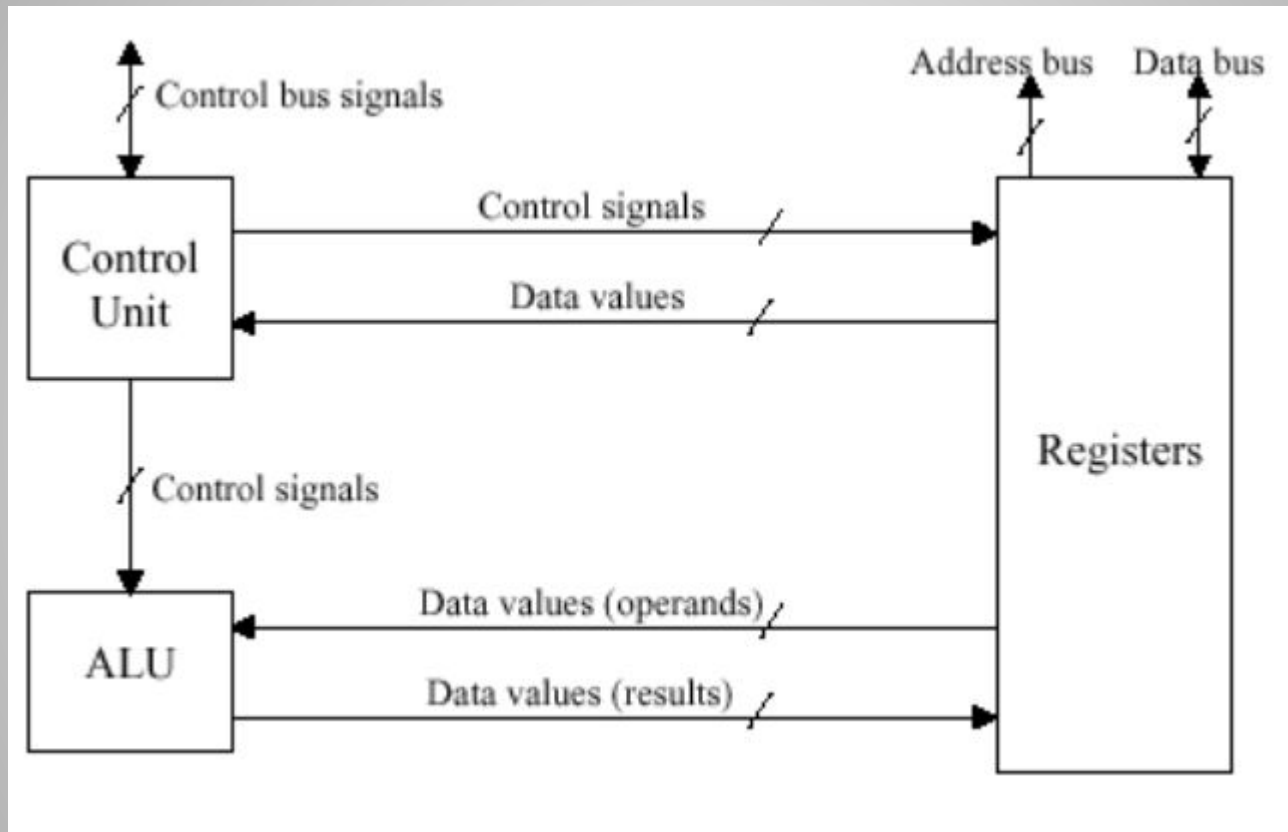

# Memory Hierarchy

---

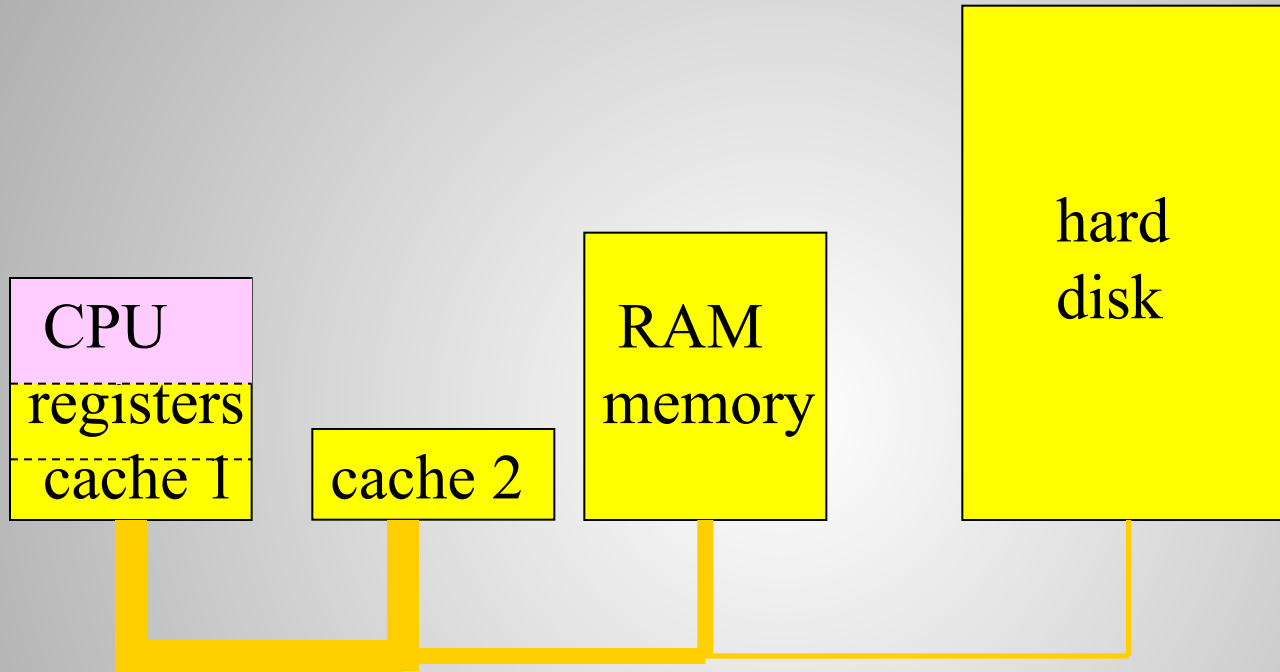

# 6.1 Registers


---

- . Clocked sequential circuits
  - a group of flip-flops and combinational gates
  - connected to form a feedback path
- Flip-flops + Combinational gates  
(essential) (optional)
- . Register:
  - a group of flip-flops
  - gates that determine how the information is transferred into the register
- . Counter:
  - a register that goes through a predetermined sequence of states

# Registers


- An  $n$ -bit register
  - $n$  flip-flops capable of storing  $n$  bits of binary information

A basic 4-bit register

 

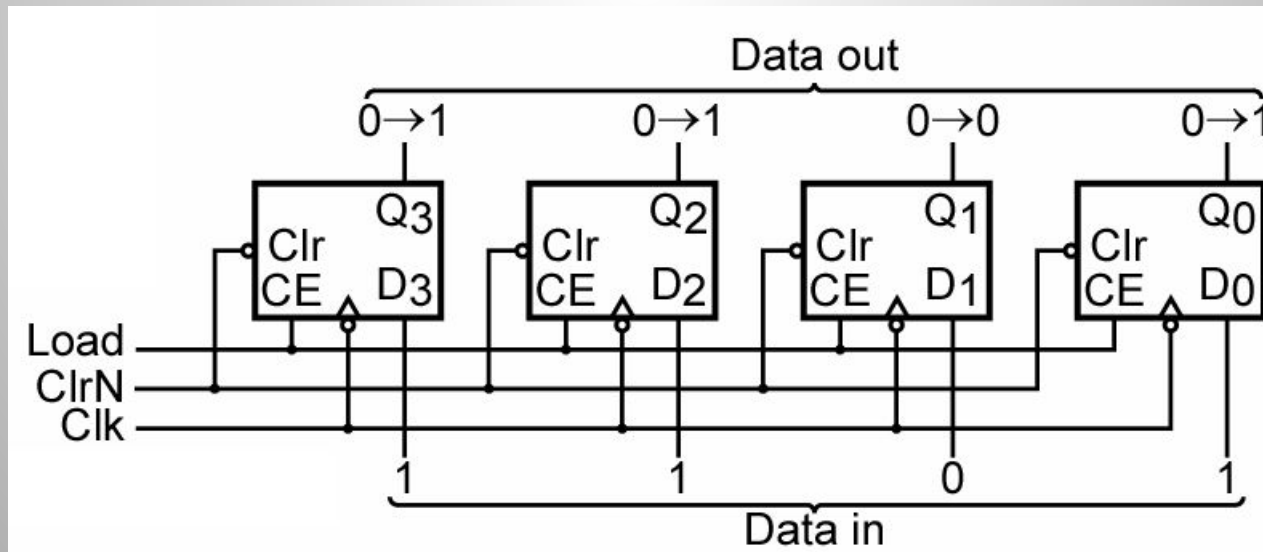
# Registers

- . To be useful, a register should keep its data until directed by a *load* control signal to read in new data
- . E.g. 4-bit register built using *D* F/Fs with enable




# 4-bit register with load control

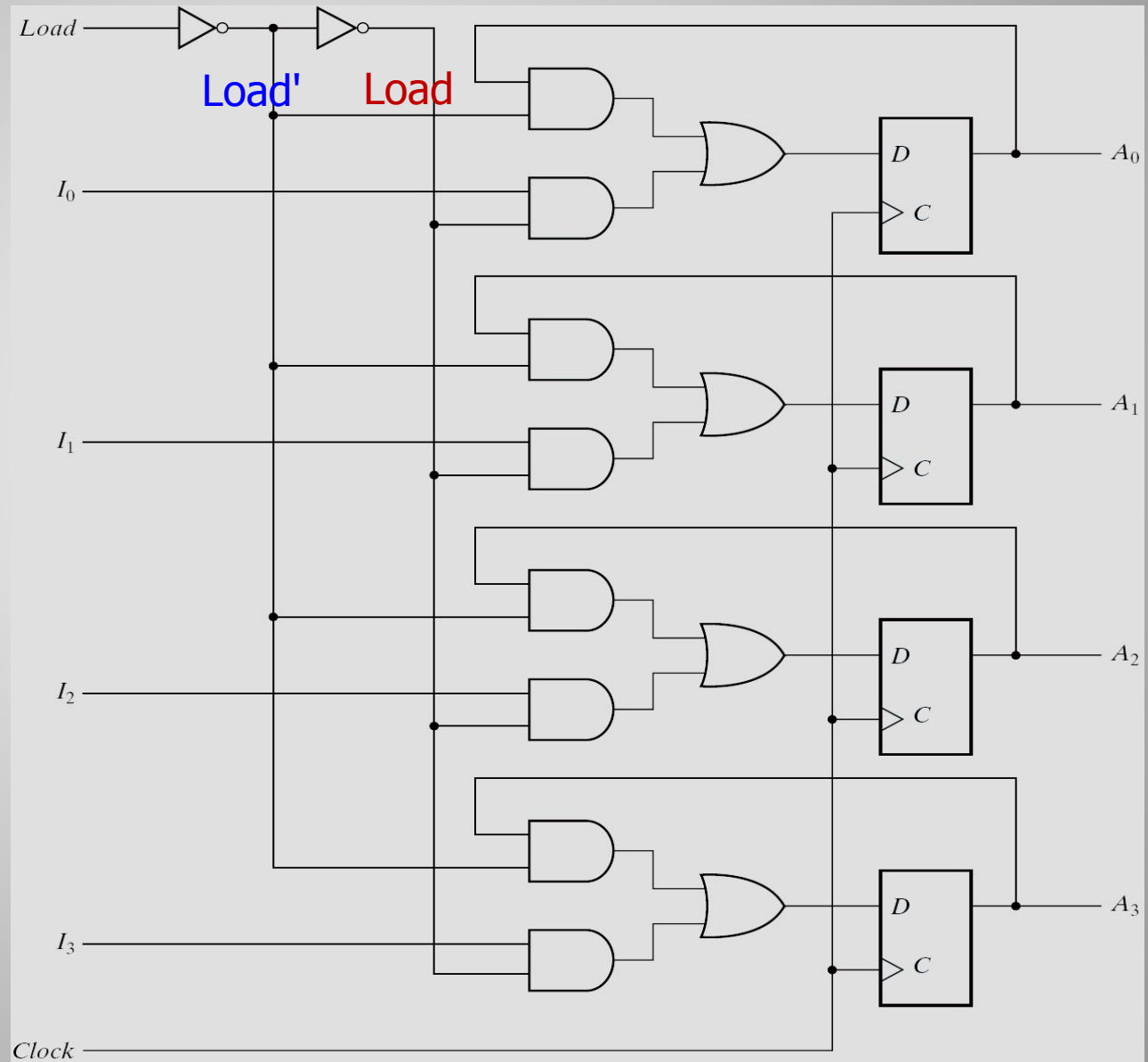



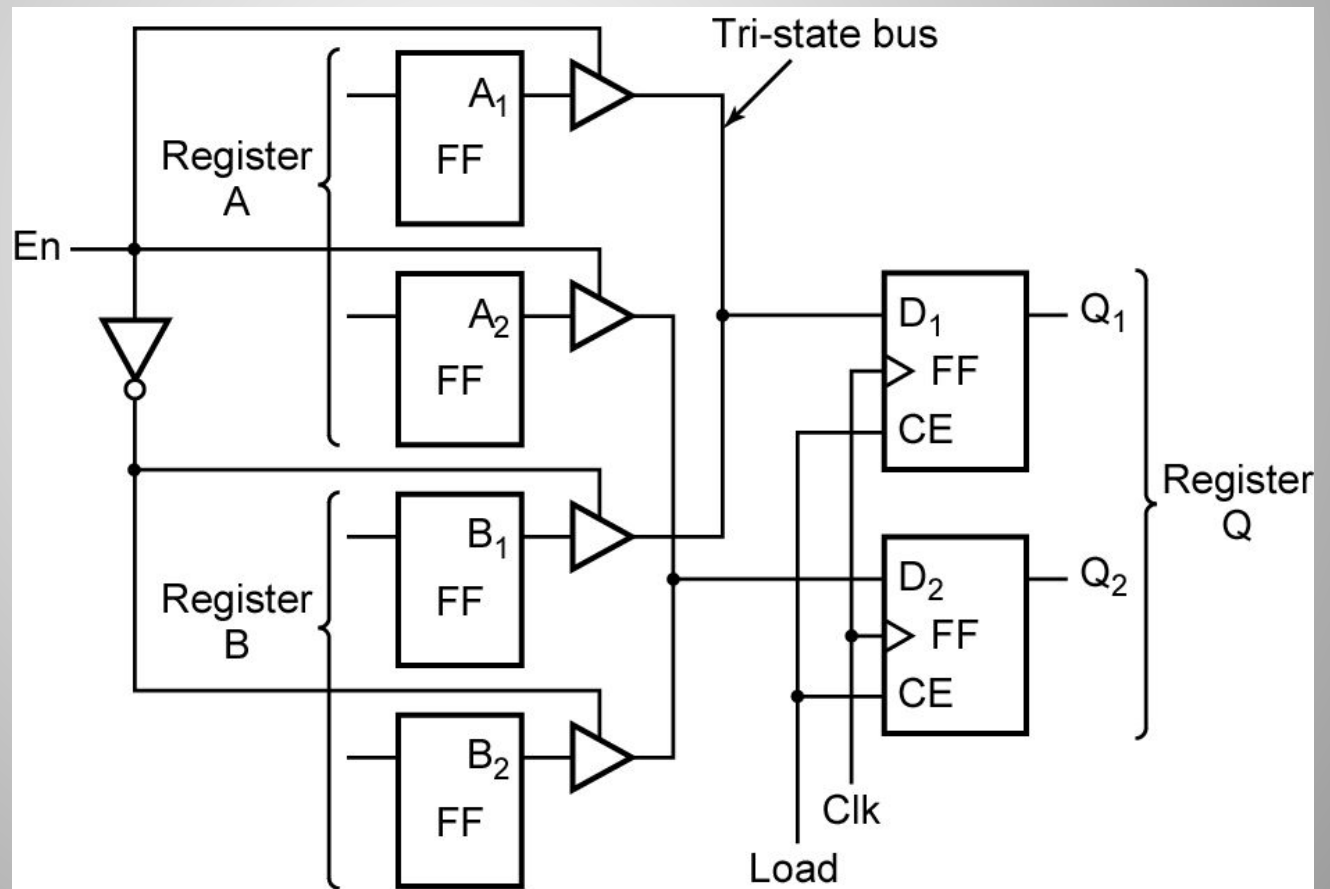
# Register Transfer

- Describe what can be done between registers A, B, Q.



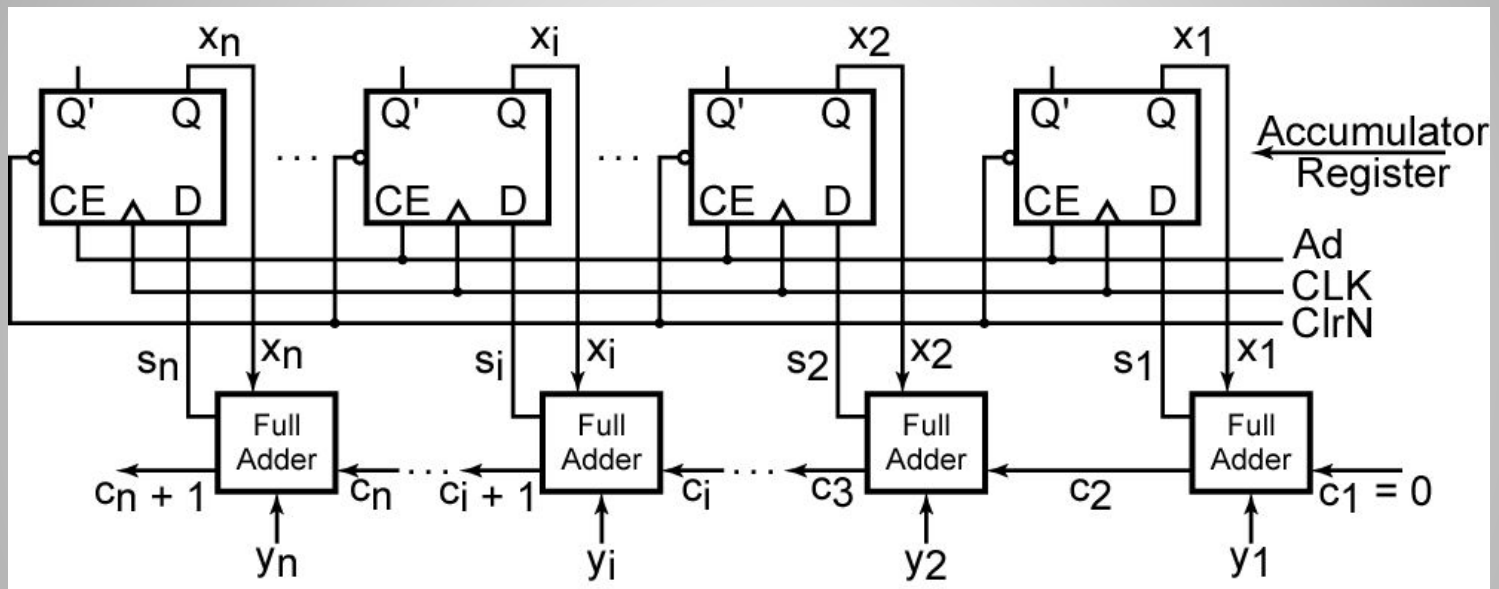
# Parallel Adder with Accumulator

- Describe the operation of the circuit below.  $X \leftarrow X + Y$ ;




Equivalent to:

 

 
# Shift Registers

- Shift registers
  - Can shift its data in one or both directions
- E.g. 4-bit serial-in, serial-out right shift registers



With shift control:

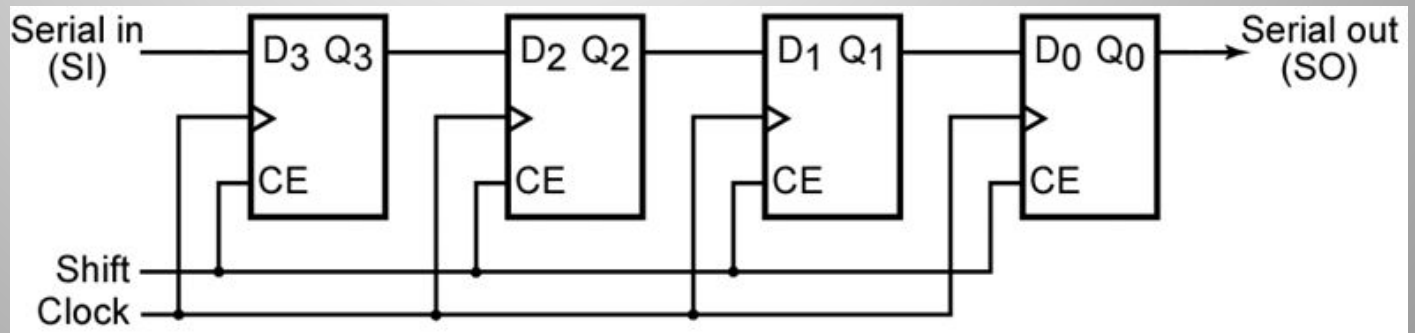



# Data Transfer

---

- . Serial transfer vs. Parallel transfer
  - Serial transfer
    - Information is transferred one bit at a time
    - Shifts the bits out of a source register into a destination register
  - Parallel transfer
    - All the bits of a register are transferred at the same time

# Serial Transfer

- E.g. Serial transfer from reg A to reg B

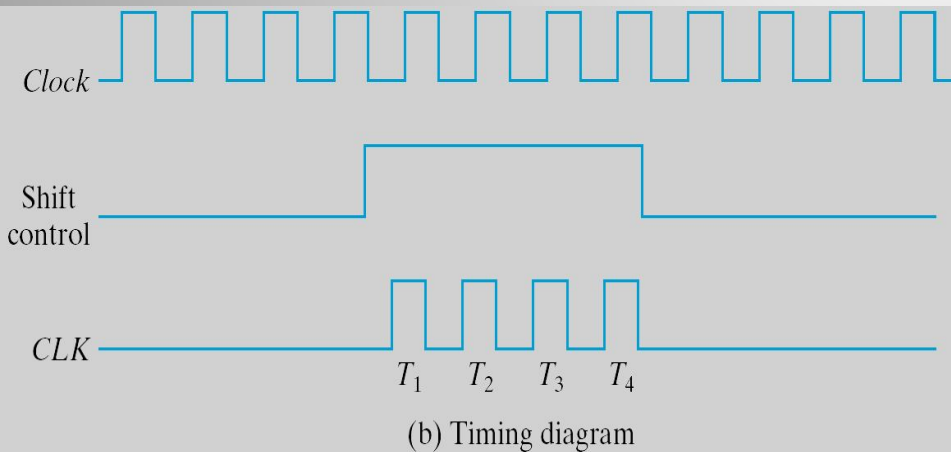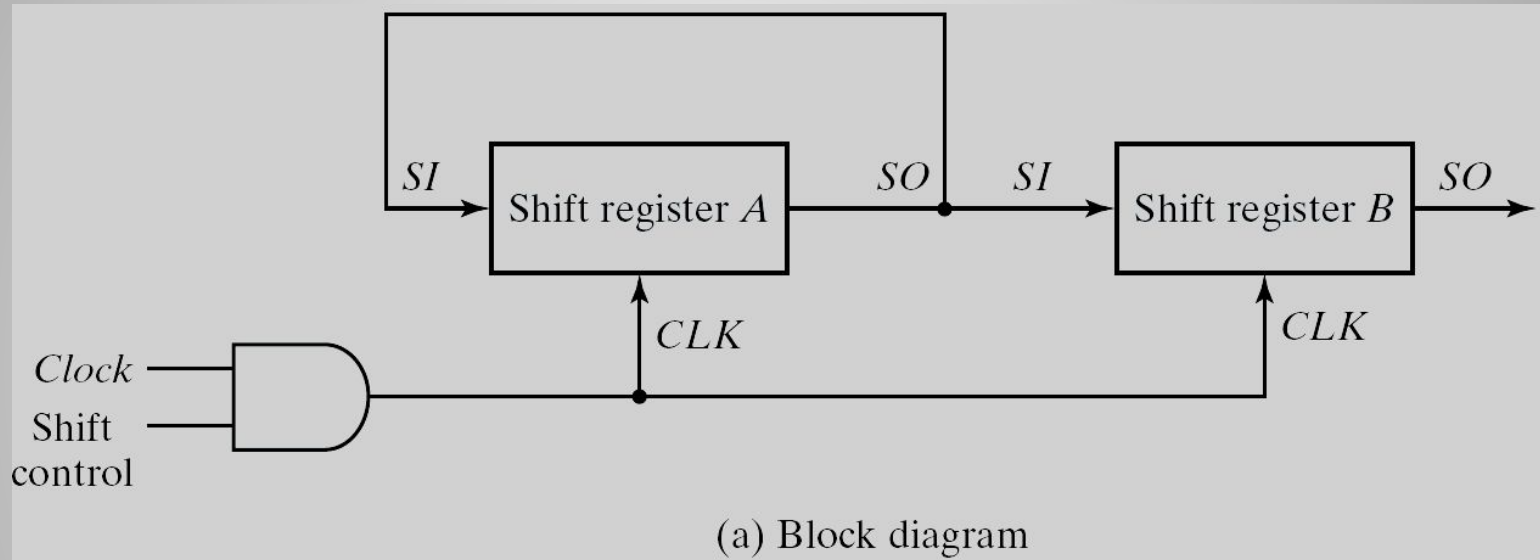

**Table 6.1**  
*Serial-Transfer Example*

Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After $T_1$	1	1	0	1	1	0	0	1
After $T_2$	1	1	1	0	1	1	0	0
After $T_3$	0	1	1	1	0	1	1	0
After $T_4$	1	0	1	1	1	0	1	1

# Serial Adder


---

- . Serial adder

- Adds two numbers *serially with a single full adder and a carry flip-flop* starting at the least significant bit (c.f.  $n$  full adders in an  $n$ -bit parallel adder)
- Takes  $n$  clock cycles to add two  $n$ -bit numbers
- It's smaller but slower than a parallel adder


# Serial addition using D flip-flop for storing carry

$$A \leftarrow A + B$$

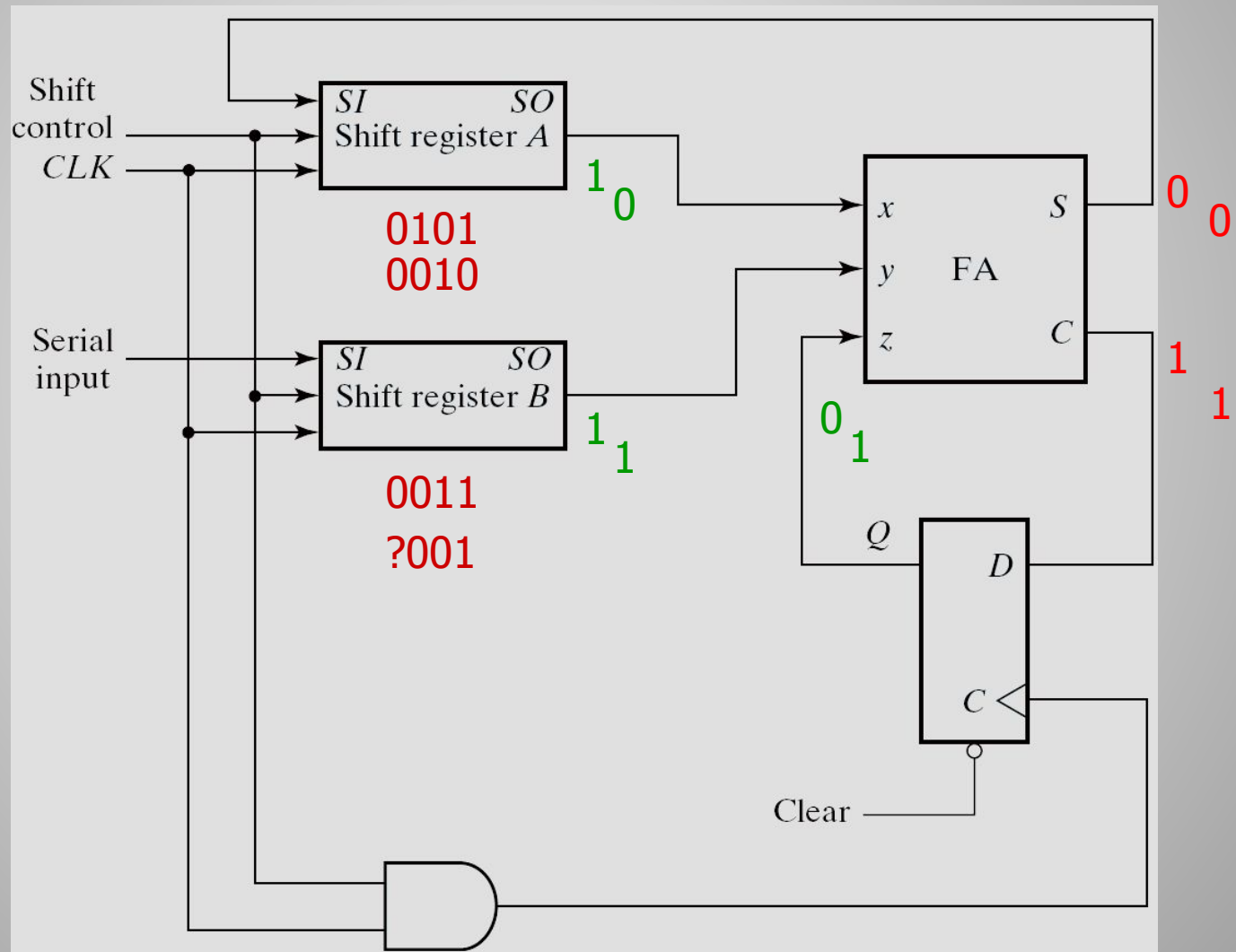

# Types of Shift Registers

- . Unidirectional shift registers
- . Bidirectional shift registers
- . Universal shift registers
  - have both direction shifts & parallel load/access capabilities

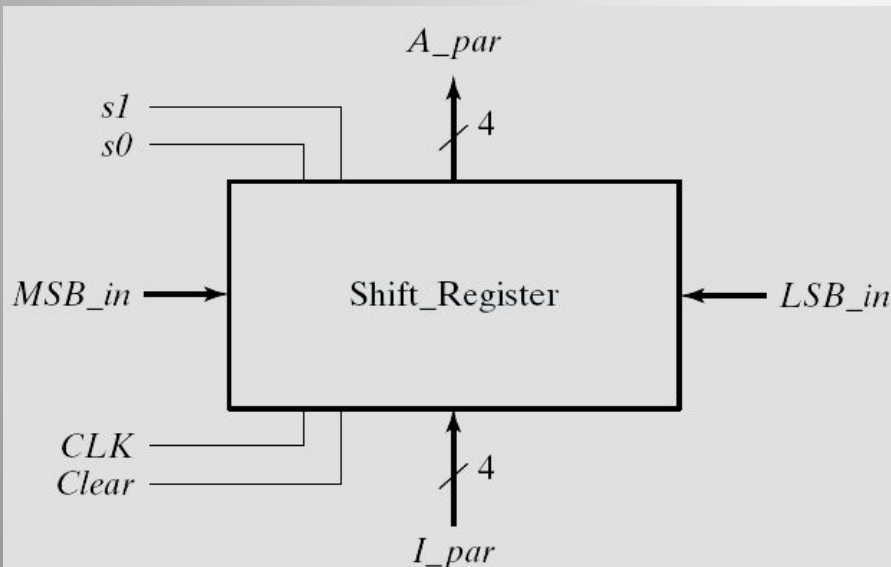


**Table 6.3**

*Function Table for the Register of Fig. 6.7*

Mode Control		Register Operation
$s_1$	$s_0$	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


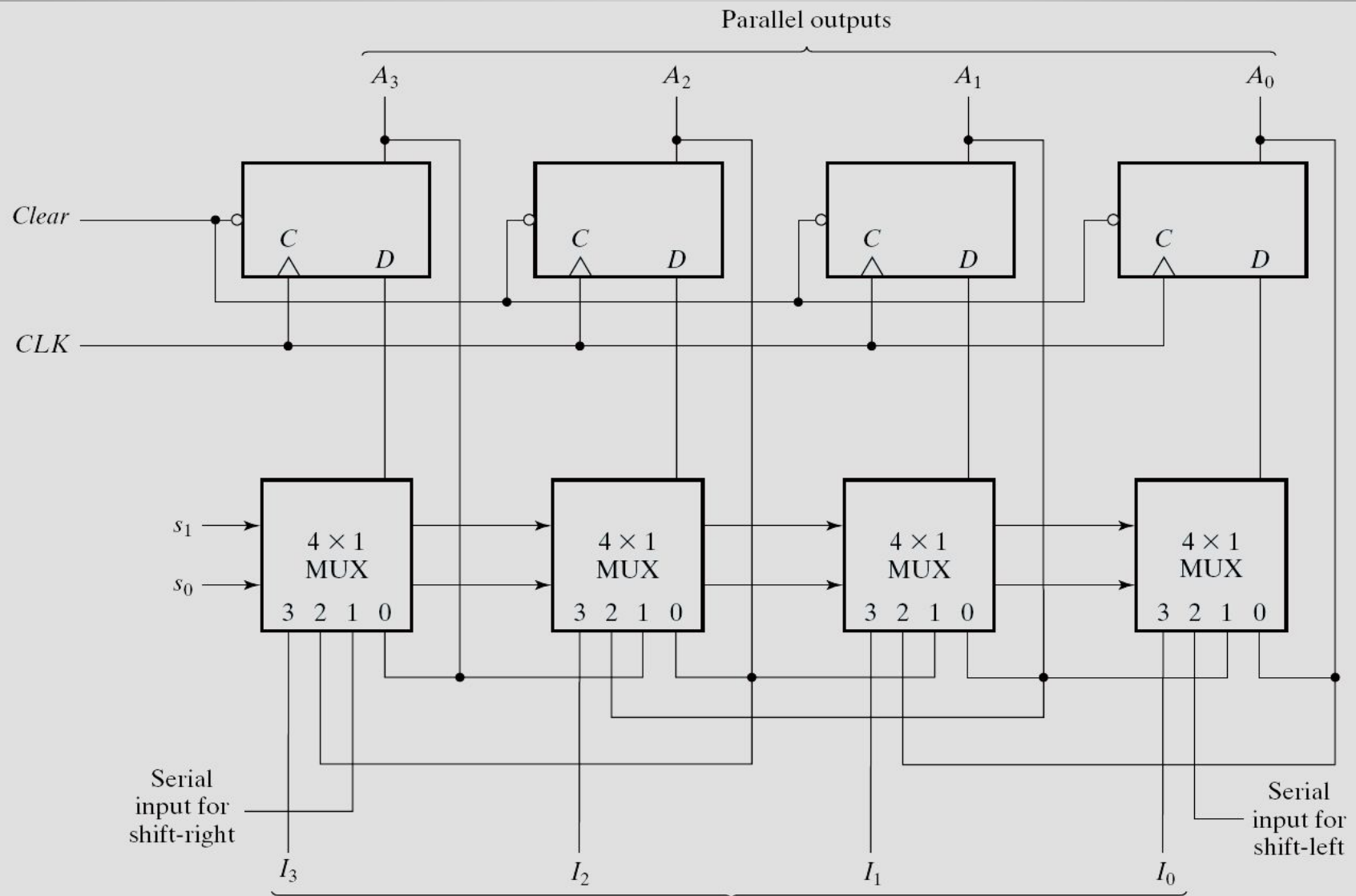
# An implementation of a 4-bit universal shift register



# Counters

---

- . Counters are special sequential circuits that sequence through some prescribed set of outputs.

- . Examples:

- Binary counter:

000 → 001 → 010 → 011 → 100 → 101 → 110 → 111

→ 000 → 001 → ...

- BCD counter:

0000 → 0001 → 0010 → ... → 1001


→ 0000 → 0001 → ...

# Ripple Counters vs Synchronous Counters

---


- . Counters are classified into two broad categories according to the way they are clocked.
- . *Ripple counter*
  - the first flip-flop is clocked by the external clock pulse and then each successive flip-flop is clocked by the output of the preceding flip-flop
  - i.e., an asynchronous sequential circuit
- . *Synchronous counter*
  - all flip-flops are clocked simultaneously by the external clock pulse.

# Binary Ripple Counter

 

- Count sequence: 0000, 0001, 0010, ..., 1111, 0000, 0001, ...
- This is a *ripple counter* because when the count is changed, the  $i+1^{\text{th}}$  bit only changes after the  $i^{\text{th}}$  bit has changed. (The flip-flops' *outputs don't change synchronously* together.)
- Note that every times  $A_i$  goes from 1 to 0, it toggles  $A_{i+1}$ .
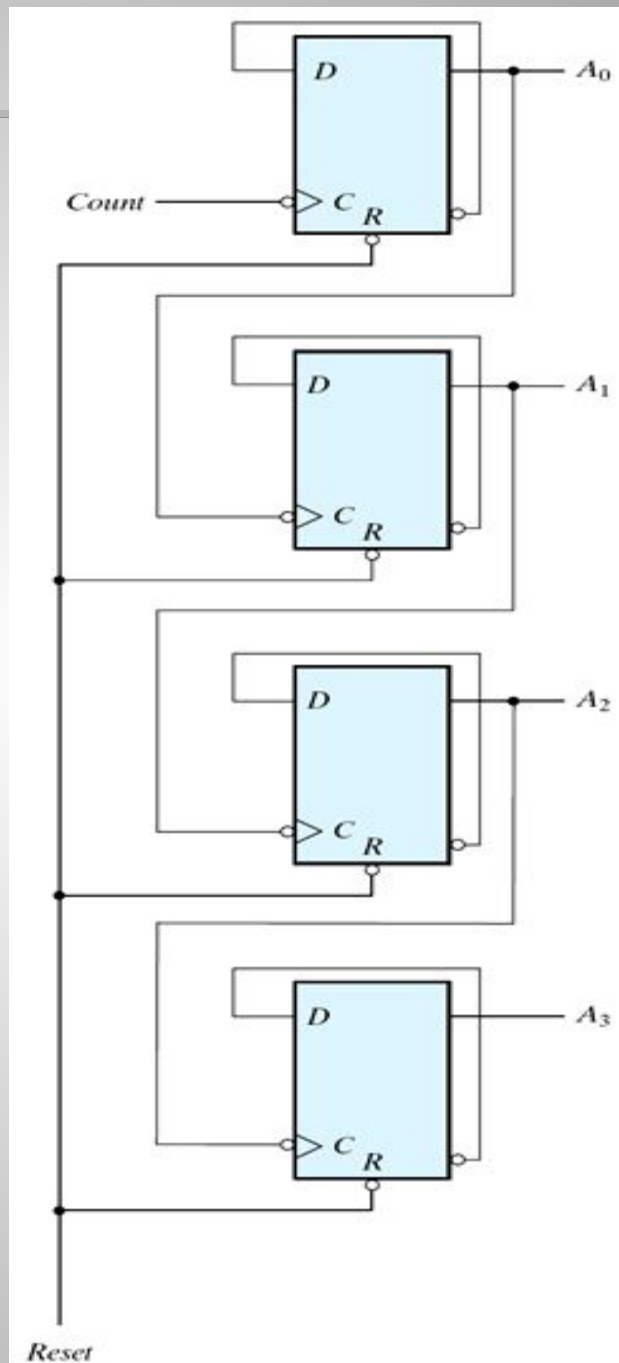
## 4-bit binary ripple counter with D flip-flops



# Synchronous Binary Counters

---


- . Synchronous counter
  - A common clock triggers all flip-flops simultaneously
- . Binary counter's counting sequence e.g. 0000, 0001, 0010, ..., 1111, 0000, 0001, ...
  - $Q_0$  is toggled every clock cycle
  - $Q_i$  needs to be toggled in the next state if  $Q_0$  to  $Q_{i-1}$  are all one in the present state (e.g. 0011  $\rightarrow$  0100)

(a) Logic Diagram-Serial Gating



# A 4-bit synchronous binary counter using JK flip-flops

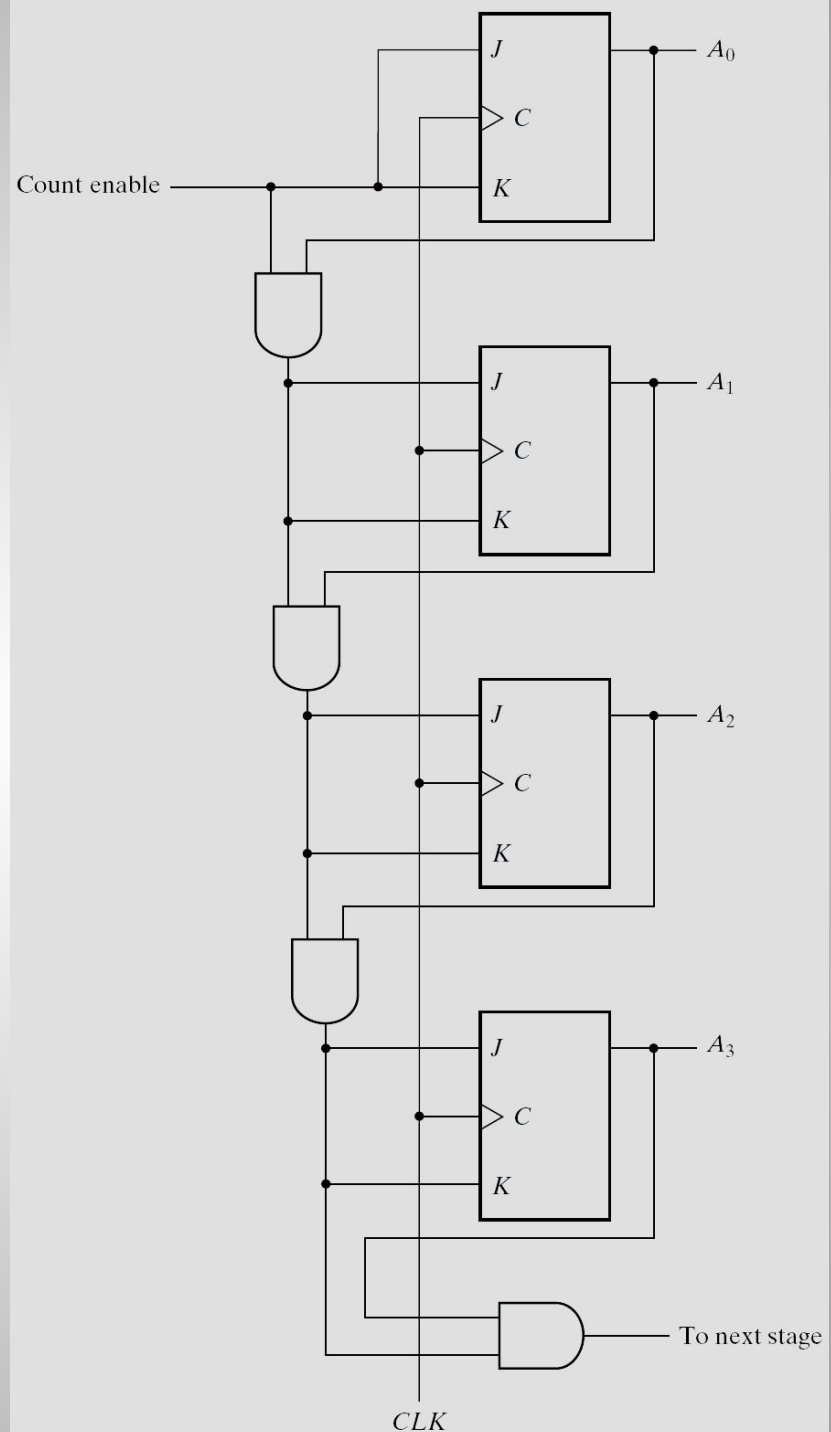
(Exercise: Construct an 8-bit synchronous binary counter using two instances of the 4-bit binary counter shown)





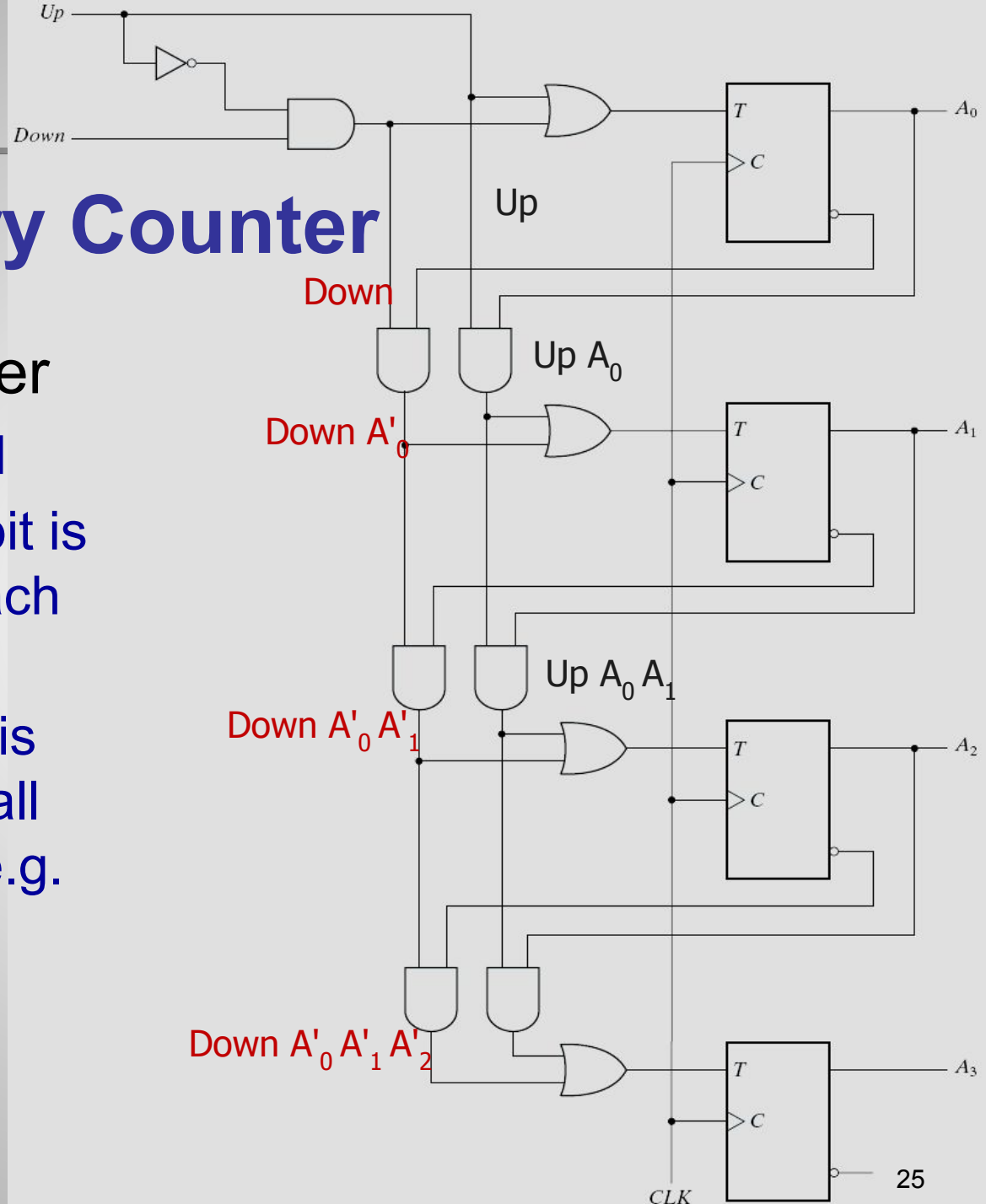
# Up-Down Binary Counter

- . For a down counter
  - Counts downward
  - Least significant bit is complemented each time
  - Other bit position is complemented if all lower bits are 0 (e.g. 1000→0111)
- . A 4-bit up-down binary counter is shown:



 
# Binary Counter with Parallel Load

- . It is desirable if we may load an initial count and/or clear a counter
- . E.g. 4-bit binary counter w/ parallel load and active-low clear




Clear_b	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

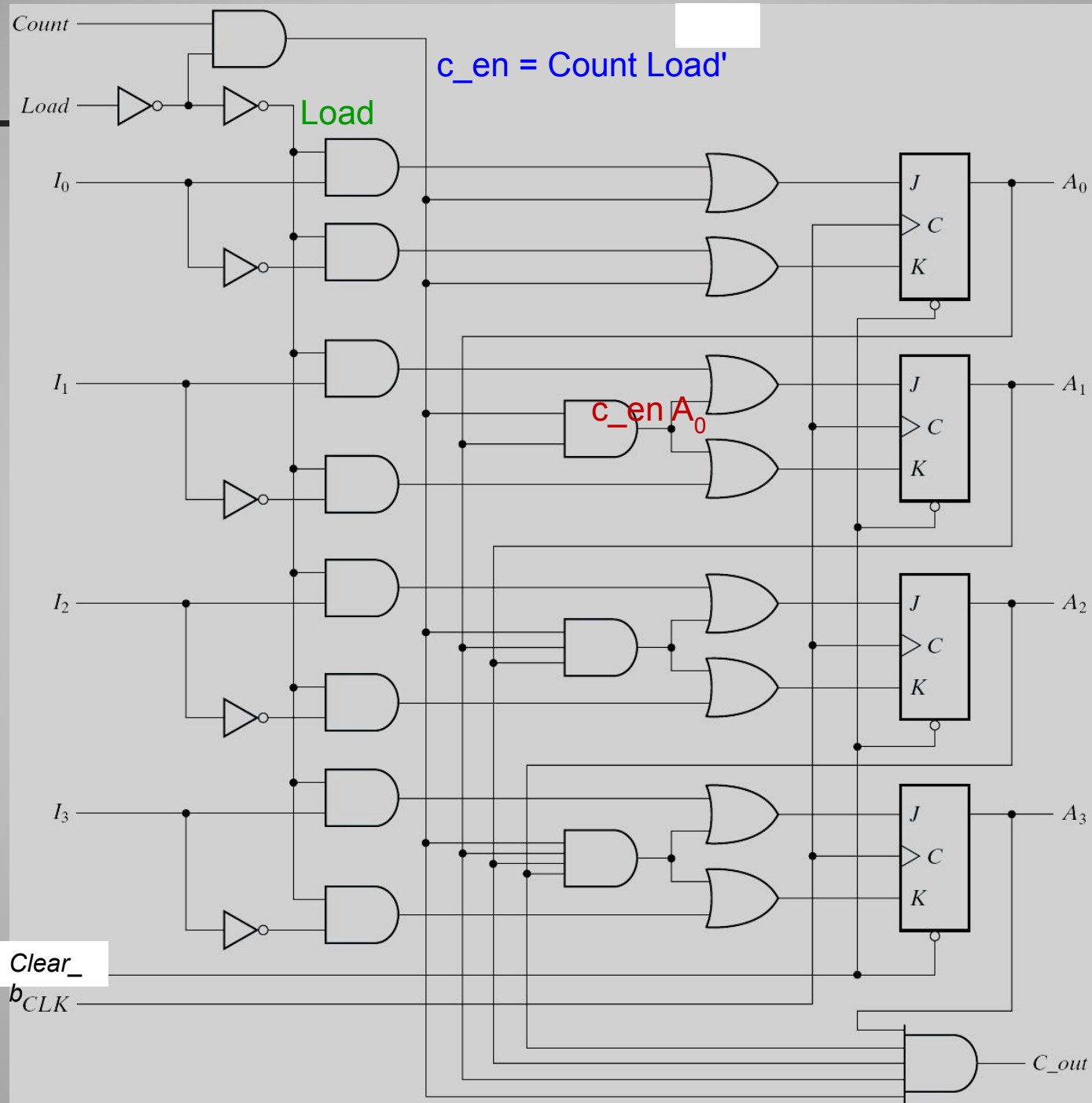
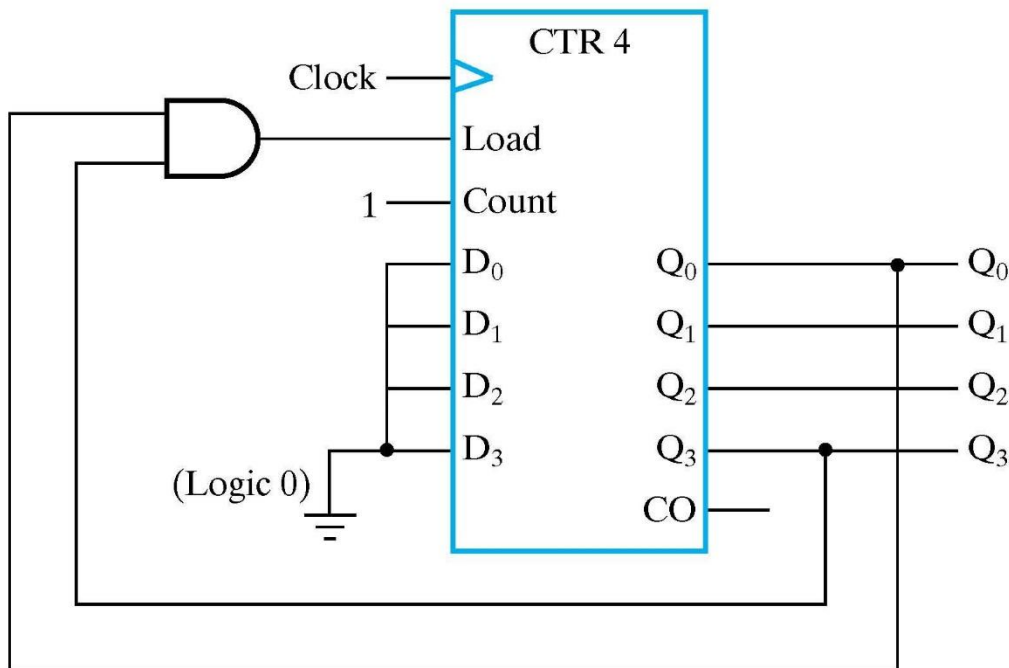
# BCD Counter

- Counts from binary 0 to 9  
(0000 → 0001 → ... → 1001 → 0000 → ...)
- Can be implemented using a 4-bit binary counter:



*Q.* Can you explain how it works?


# BCD Counter

- Alternatively, we can construct a BCD counter from scratch following the standard procedure.

Exercise: Finish the design of a BCD counter using D flip-flops.
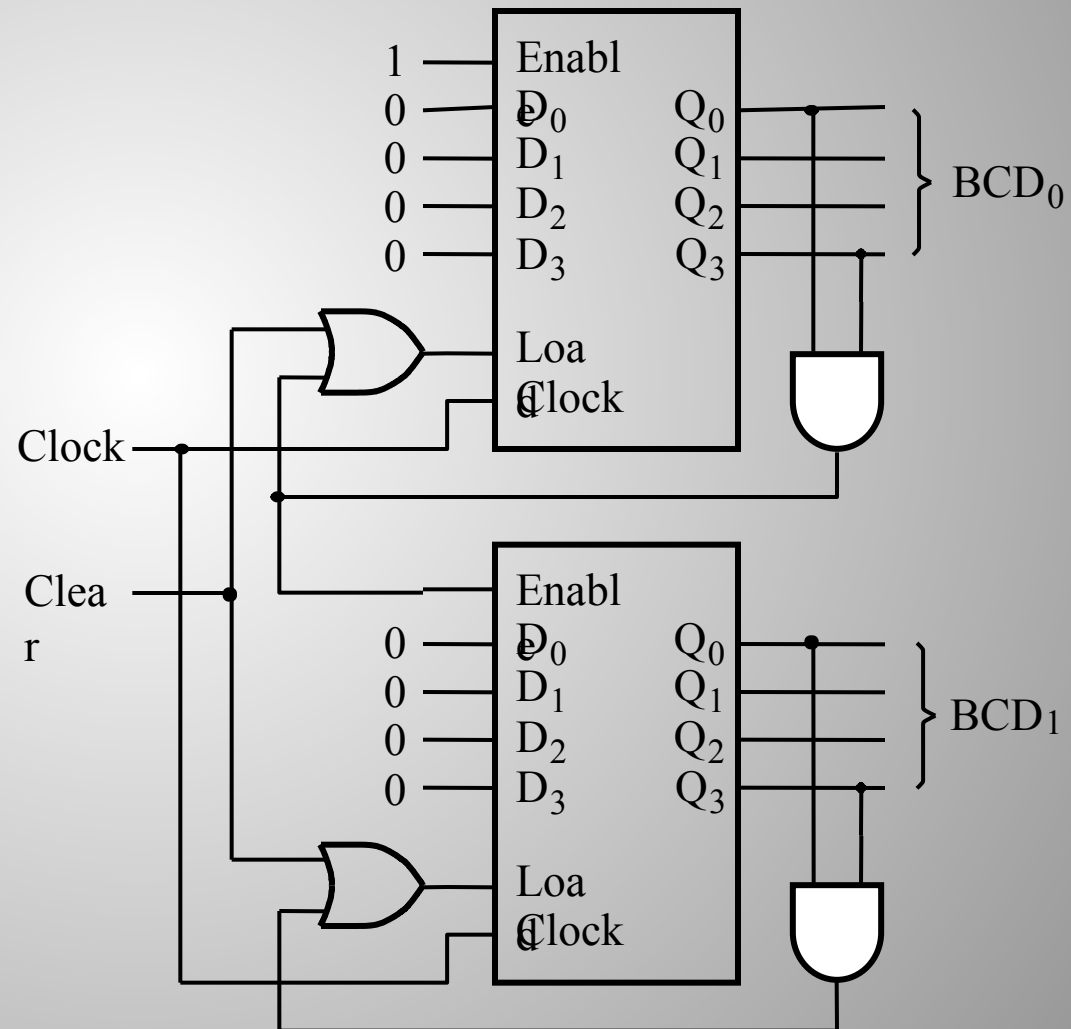
# Example

- Construct a 2-digit BCD counter using two 4-bit binary counters



# Counter for Arbitrary Count Sequence



- Constructed by following standard procedure for sequential circuit design.
- E.g. Construct a counter that counts in the sequence 000, 001, 010, 100, 101, 110 repeatedly.

**Table 6.7**  
*State Table for Counter*

Present State			Next State			Flip-Flop Inputs					
<i>A</i>	<i>B</i>	<i>C</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>J<sub>A</sub></i>	<i>K<sub>A</sub></i>	<i>J<sub>B</sub></i>	<i>K<sub>B</sub></i>	<i>J<sub>C</sub></i>	<i>K<sub>C</sub></i>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

States 011 and 111 are unused.

  
If we simplify assuming don't care conditions for their next states, we get:




 
# Synchronization Pitfall

- . A student designed a counter which is supposed to count 0,1,2,3,4,5,6,0,...
- . What is the potential problem of this design?



This is an asynchronous circuit

```
// 4-bit Left Shift Register with Reset
```

```
module srg_4_r_v (CLK, RESET, SI, Q,SO);  
    input CLK, RESET, SI;  
    output [3:0] Q;  
    output SO;
```

```
reg [3:0] Q;
```

```
assign SO = Q[3];
```

```
always@(posedge CLK or posedge RESET)  
begin  
    if (RESET)  
        Q <= 4'b0000;  
    else  
        Q <= {Q[2:0], SI};  
end  
endmodule
```

```
// 4-bit Binary Counter with Reset
```

```
module count_4_r_v (CLK, RESET, EN, Q, CO);
```

```
    input CLK, RESET, EN;
```

```
    output [3:0] Q;
```

```
    output CO;
```

```
reg [3:0] Q;
```

```
assign CO = (count == 4'b1111 && EN == 1'b1) ? 1 : 0;
```

```
always@(posedge CLK or posedge RESET)
```

```
    begin
```

```
        if (RESET)
```

```
            Q <= 4'b0000;
```

```
        else if (EN)
```

```
            Q <= Q + 4'b0001;
```

```
        end
```

```
endmodule
```