



#### Problem1

 

 

 

 


## Problem3


3a) Find and report the optimal width for PMOS for a balanced trigger point of inverter at TT corner and 25°C. The meaning of a balanced trigger point is as the following. Vin = Vout =  $0.5 \times VDD$  (That is to say, Vout equals to Vin when Vin is set to half of VDD.)

PMOS width = 1.12um

 3b) Perform DC sweep and plot Vout vs. Vin as Vin sweeps from 0 V to VDD with the step of 0.05 V in five different process/temperature corners.



 
3c) Repeat 3b) with the NMOS width set to 5X of minimum channel width. Then complete the following table. (Report Vout value when Vin is set to half of VDD.)




		NMOS width 1X	NMOS width 5X	
		Vout	Vout	
Process	Temperature	at Vin=0.5×VDD	at Vin=0.5×VDD	
ТТ	25°C	0.893V	0.0715V	
FF	−40°C	0.553V	0.056V	
SS	125°C	1.54V	0.088V	
SF	25°C	1.74V	1.19V	
FS	25°C	1.48V	0.111V	

# Problem4

## NMOS width 1X

 

### NMOS width 5x

 

Process	Temperature	NMOS width 1X		NMOS width 5X	
		Fall Delay	Rise Delay	Fall Delay	Rise Delay
Π	25°C	943.8836ps	708.5825ps	335.2387ps	707.1004ps
FF	–40°C	682.9803ps	596.8875ps	269.8264s	6599.0176ps
SS	125°C	2.3957ns	1.3317ns	633.3349ps	1.3249ns
SF	25°C	1.9824ns	600.0654ps	557.7148ps	617.1248ps
FS	25°C	1.0699ns	657.0862ps	367.5949ps	679.5118ps