

10920EECS101001 Logic Design


小考

solution


10920EECS101001 Logic Design

小考

 
1. (10%) Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter. (Hint JK flip-flop : $Q(t+1) = JQ' + K'Q$)



 2. (20%) A sequential circuit has one flip-flop Q, two inputs x and y, and one output S (Sum). It consists of a full-adder circuit connected to a D flip-flop, as shown in the figure. Derive the state table (column: Present state (Q), Input, Next state (Q), Output) and state diagram (**mealy machine only**) of the sequential circuit.




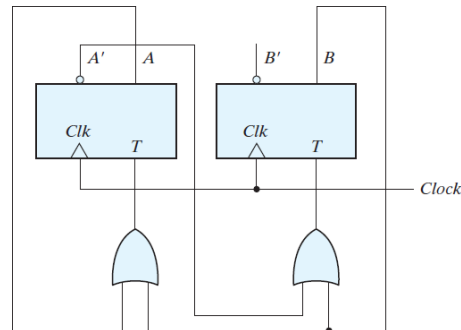3. (20%) Derive the state table (column: Present state (A,B), Next state (A,B), T_A, T_B) and the state diagram of the sequential circuit shown below. (Hint: these two flip-flops in the circuit are T flip-flop)



4. (10%) Draw the logic diagram for the sequential circuit described by the following HDL code:
- ```
always @ (posedge CLK)begin
 E <= A | B;
 Q <= E & C;
End
```

 5. (20%) Write the Verilog code for the state diagram below.




6. (10%) Draw the logic diagram of a 1-bit register with a D flip-flops and a 4 \* 1 multiplexers with mode selection inputs s1 and s0. The register operates according to the following function table.

| S1 | S0 | Register Operation    |
|----|----|-----------------------|
| 0  | 0  | Output no change      |
| 1  | 0  | Complement the output |
| 0  | 1  | Clear register to 0   |
| 1  | 1  | Load input data       |

(Hint : this register has at least three inputs S0, S1, I (input data) and outputs Q, Q'.)

7. (10%) What's the difference between blocking procedural assignment and non-blocking procedural assignment. Please give an example.

# 1.

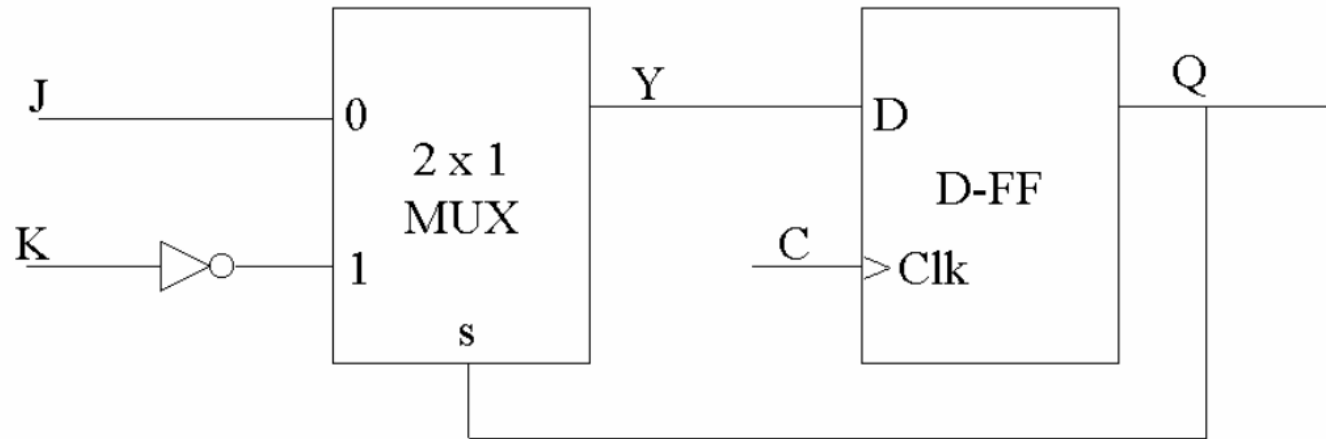


給分標準：

- 1.如果有同學MUX使用兩個and gate + 一個or gate來做我也會給對。  
但是這樣我就不知道同學是否了解mux，還是只是用題目給的 $JQ' + K'Q$ 來兜出來答案。  
希望同學能按照題目需求。
- 2.沒按題目需求(1個2-1MUX,1個inverter,1個DFF)就0分
- 3.沒有output(Q沒有凸出來)會-1分。

# 2.

| Present state | Inputs |   | Next state | Output |
|---------------|--------|---|------------|--------|
| Q             | x      | y | Q          | s      |
| 0             | 0      | 0 | 0          | 0      |
| 0             | 0      | 1 | 0          | 1      |
| 0             | 1      | 0 | 0          | 1      |
| 0             | 1      | 1 | 1          | 0      |
| 1             | 0      | 0 | 0          | 1      |
| 1             | 0      | 1 | 1          | 0      |
| 1             | 1      | 0 | 1          | 0      |
| 1             | 1      | 1 | 1          | 1      |

 


給分標準：

1. table跟state diagram各佔10分
2. table錯一行扣2分扣到歸0
3. state diagram錯一個edge扣2分扣到歸0
4. 題目有提到Derive the state table (column: Present state (Q), Input, Next state (Q), Output)  
希望同學作答能按照這個格式

# 3.

| <i>Present State</i> |          | <i>Next State</i> |          | <i>FF Inputs</i>     |                      |
|----------------------|----------|-------------------|----------|----------------------|----------------------|
| <i>A</i>             | <i>B</i> | <i>A</i>          | <i>B</i> | <i>T<sub>A</sub></i> | <i>T<sub>B</sub></i> |
| 0                    | 0        | 0                 | 1        | 0                    | 1                    |
| 0                    | 1        | 1                 | 0        | 1                    | 1                    |
| 1                    | 0        | 0                 | 0        | 1                    | 0                    |
| 1                    | 1        | 0                 | 0        | 1                    | 1                    |

 

State table(10%):

each column(5%)


1 wrong entry – 3%

State diagram(10%):

1 wrong edge -5%

1 wrong state -5%

4.

 

Missing 1 DFF -5%

Missing 2 DFF -10%

No output wire -1%

E wire disconnected -1%

Invalid form -10%

Wrong wire name -1%

1 wrong gate -5%

1 wrong gate -10%

5.

```
module mooreMachine
(
 input wire clk,
 input wire in,
 output reg out
 //output wire out
);

parameter a = 2'b00;
parameter b = 2'b01;
parameter c = 2'b10;
parameter d = 2'b11;

reg[1:0] state, next_state;

always @(posedge clk)
begin
 state <= next_state;
end
```

# 5.

```
always @*
begin
 next_state = a; // required when no case statement is satisfied. In our case, it can be a,b,c, or d.
 out = 1'b0;

 //next_state = b;
 //out = 1'b1;

 //next_state = c;
 //out = 1'b1;

 //next_state = d;
 //out = 1'b0;

 case(state)
 a:
 begin
 out = 1'b0;
 if(in)
 next_state = c;
 else
 next_state = b;
 end
 b:
 begin
 out = 1'b1;
 if(in)
 next_state = d;
 else
 next_state = c;
 end
 c:
 begin
 out = 1'b1;
 if(in)
 next_state = d;
 else
 next_state = b;
 end
 d:
 begin
 out = 1'b0;
 if(in)
 next_state = a;
 else
 next_state = c;
 end
 endcase
end

//assign out = (state == b || state == c)? 1'b1 : 1'b0; // required when output is wire type

endmodule
```



# 5.

評分規則：

墨水分數：**+10分**


**state**的轉換：**+5分** (意思有到就給分)

**Moore machine**：**+5分**

零星的錯誤：每多一個少加**1分**

總分：**20分**

6.

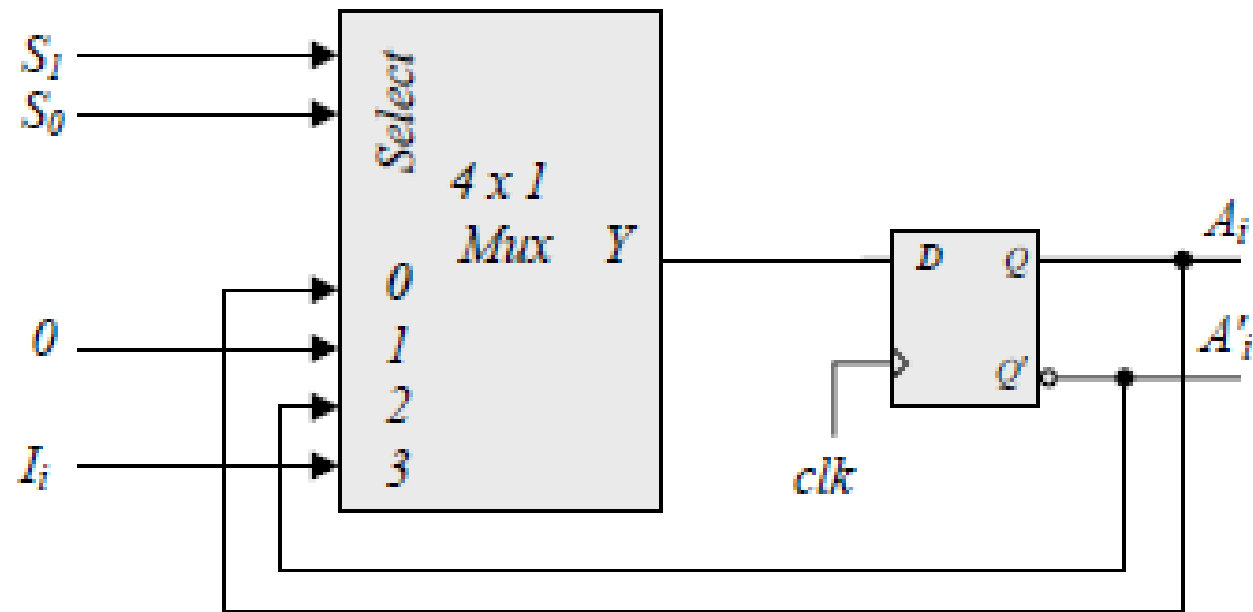

給分標準：

- 沒有使用一個題目要求的component(e.g. DFF, 4x1Mux)或有錯(e.g. 使用成其他Mux或Mux input有缺)扣4分
- 表格中4個case，錯一個扣2分

# 7.

## □ **Blocking** procedural assignment: =

- An assignment is completed before the next assignment starts.
- (assume  $a = 0$ )  
     $a = 1;$   
     $c = a; // c = 1$

## □ **Non-blocking** procedural assignment: <=

- Assignments are executed in parallel.
- (assume  $a = 0$ )  
     $a <= 1;$   
     $c <= a; // c = 0$

給分標準：

定義不同處: 5分

例子(舉例說明不同處): 5分