

Memory Basics and Programmable Logics

Hsi-Pin Ma 馬席彬

<http://lms.nthu.edu.tw/course/35472>

Department of Electrical Engineering
National Tsing Hua University

Outline

- Random-Access Memory
- Memory Decoding
- Read-Only Memory
- Programmable Logic Array
- Programmable Array Logic
- Sequential Programmable Devices

Memory Unit

- A collection of storage cells together with associated circuits needed to transfer information in and out of storage.
- RAM: Random-Access Memory
 - Volatile (memory units that lose stored information when power is turned off)
 - To accept new information for storage to be available later for use
 - read / write operation
- ROM: Read-Only Memory
 - Nonvolatile
 - The information inside can not be altered by writing
 - Programmable devices are specified by some hardware procedure

Random-Access Memory


Random-Access Memory

- Characteristics

- The time it takes to transfer data to or from any desired location is always *the same*.
- The size of the RAM is $2^k \times n$ bits. It has k address lines, n input data lines and n output data lines.
- For a commodity RAM, $16 \leq k \leq 30$, $n=1, 4, 8, 16, 32$ or 64 .

- The communication between a memory and its environment is achieved through

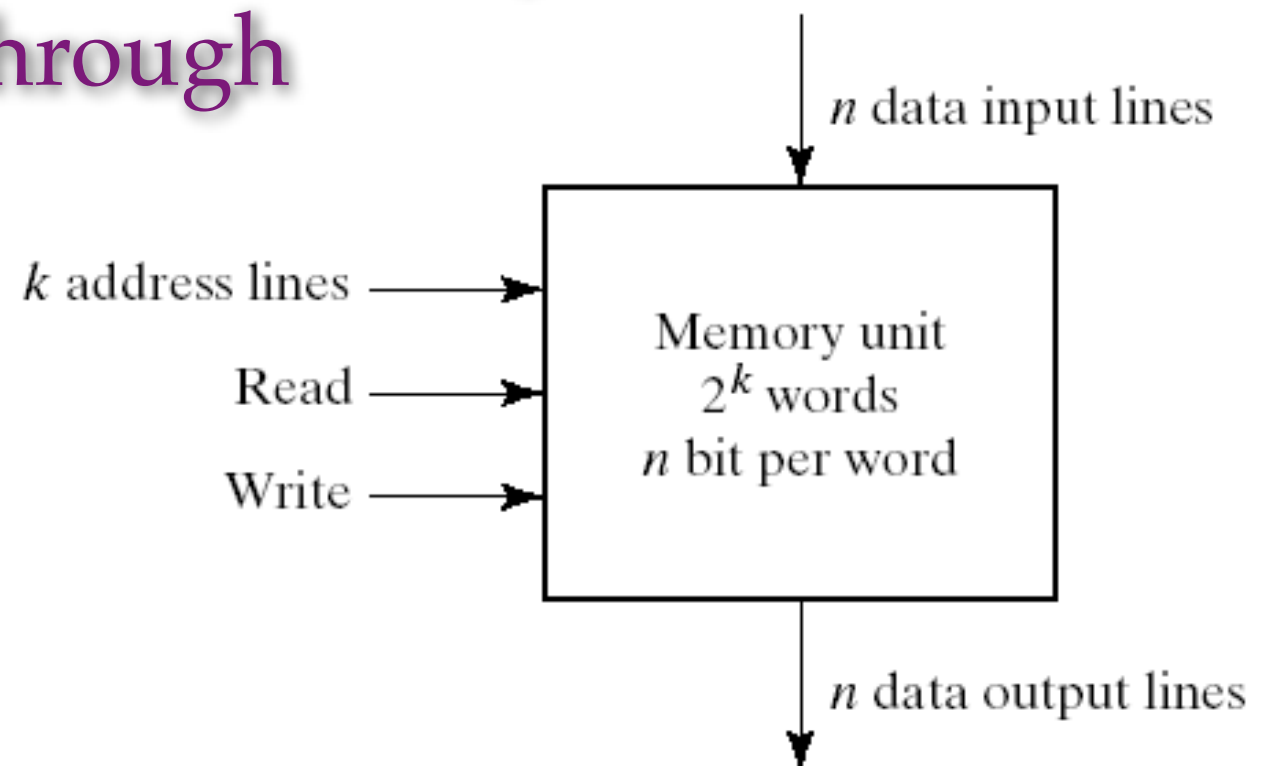- Data input lines,
- Data output lines,
- Address selection lines
- Control lines (read and write)



Memory Content Array


- A memory with k -bit address has 2^k data (depth)
 - (depth)x(width) memory
 - eg. 1K x 16 memory (1024x16 memory)

Memory address		Memory content
Binary	decimal	
0000000000	0	1011010101011101
0000000001	1	1010101110001001
0000000010	2	0000110101000110
	⋮	⋮
1111111101	1021	1001110100010100
1111111110	1022 2^{k-2}	0000110100011110
1111111111	1023 2^k-1	1101111000100101


k-bit address *n bits*

Memory Cell

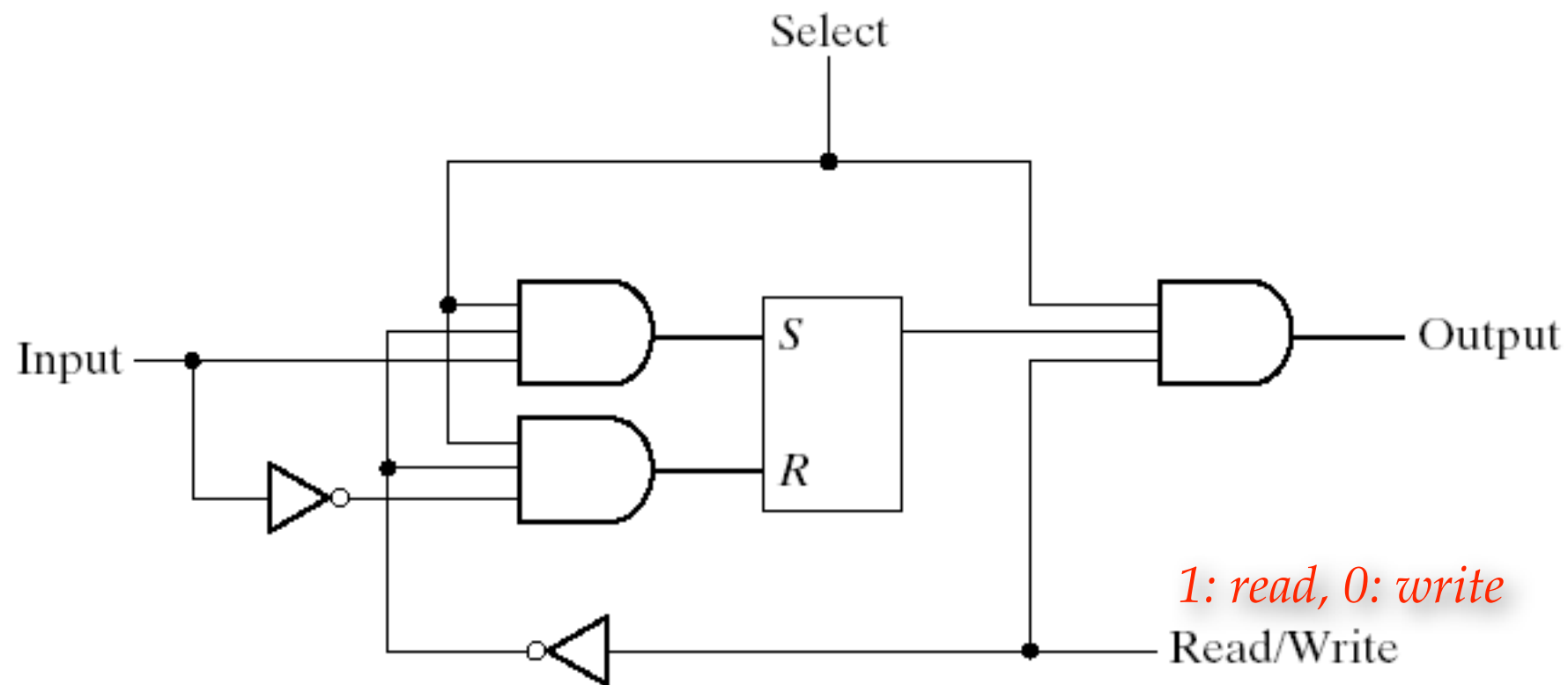
- A memory cell virtual model (binary storage cell)



(a) Logic diagram

 

(b) Block diagram

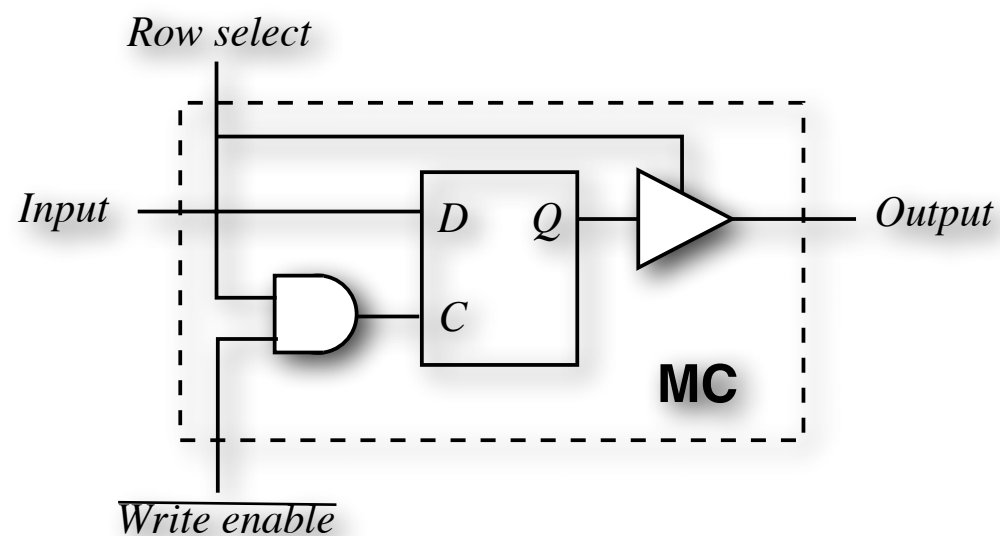

Write enable

Static RAM vs. Dynamic RAM

- A memory cell (MC) can be considered as a clocked D latch with an AND gate and an output driver
 - For a *static RAM (SRAM)*, MC is constructed by 6 transistors, using cross-coupled inverters to serve as a latch, and implementing the input AND gate and the output driver with one transistor each.
 - For a *dynamic RAM (DRAM)*, MC is constructed by only 1 transistor
 - The latch is implemented by a capacitor.
 - It needs to be refreshed periodically.
 - It has high density (therefore low cost)

Write and Read Operation


• Write operation

- Apply the binary address to the address lines
- Apply the data bits to the data input lines
- Activate the *write* input (0)

• Read operation

- Apply the binary address to the address lines
- Activate the *read* input (1)

Chip select CS	Read/ $\overline{\text{Write}}$ R/ $\overline{\text{W}}$	Memory operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

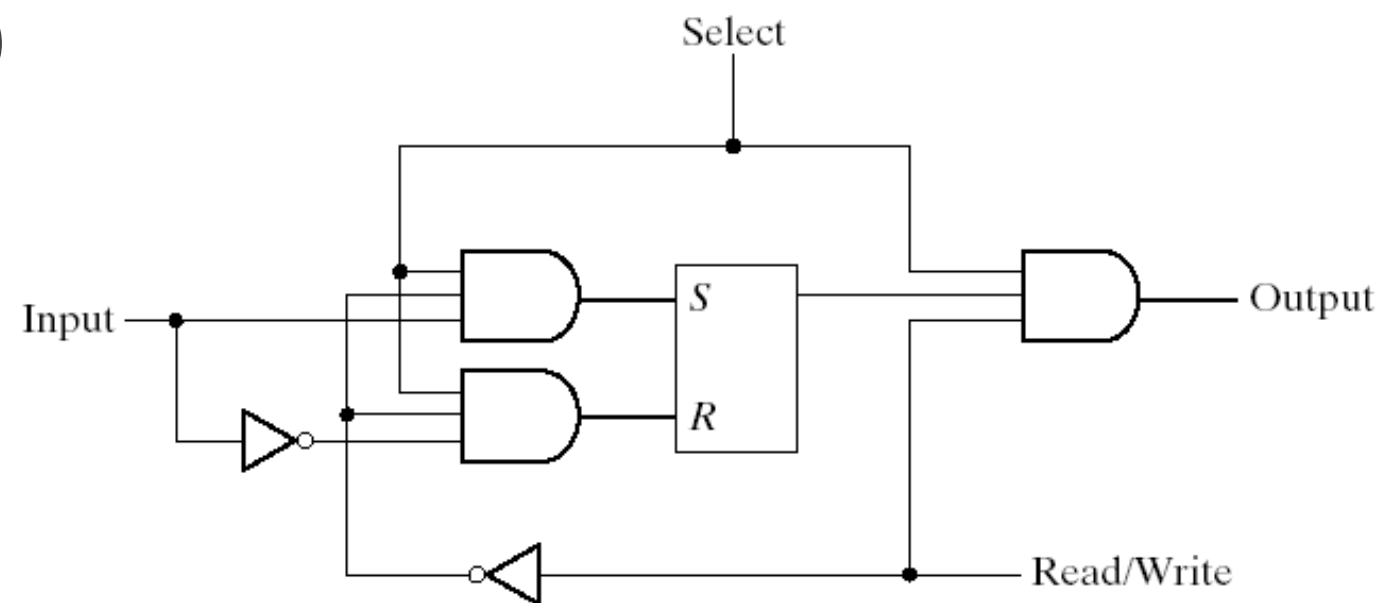


Timing Waveforms (1 / 3)

- The operation of the memory unit is controlled by an external device such as a CPU
- The access time is the time required to select a word and read it
- The write cycle time is the time required to complete a write operation
- Read and write operations must be controlled by CPU and be synchronized with an external clock.


Timing Waveforms (2/3)

 - A write cycle of *write cycle time* 75 ns



Timing Waveforms (3/3)


- A read cycle of *access time* 65 ns

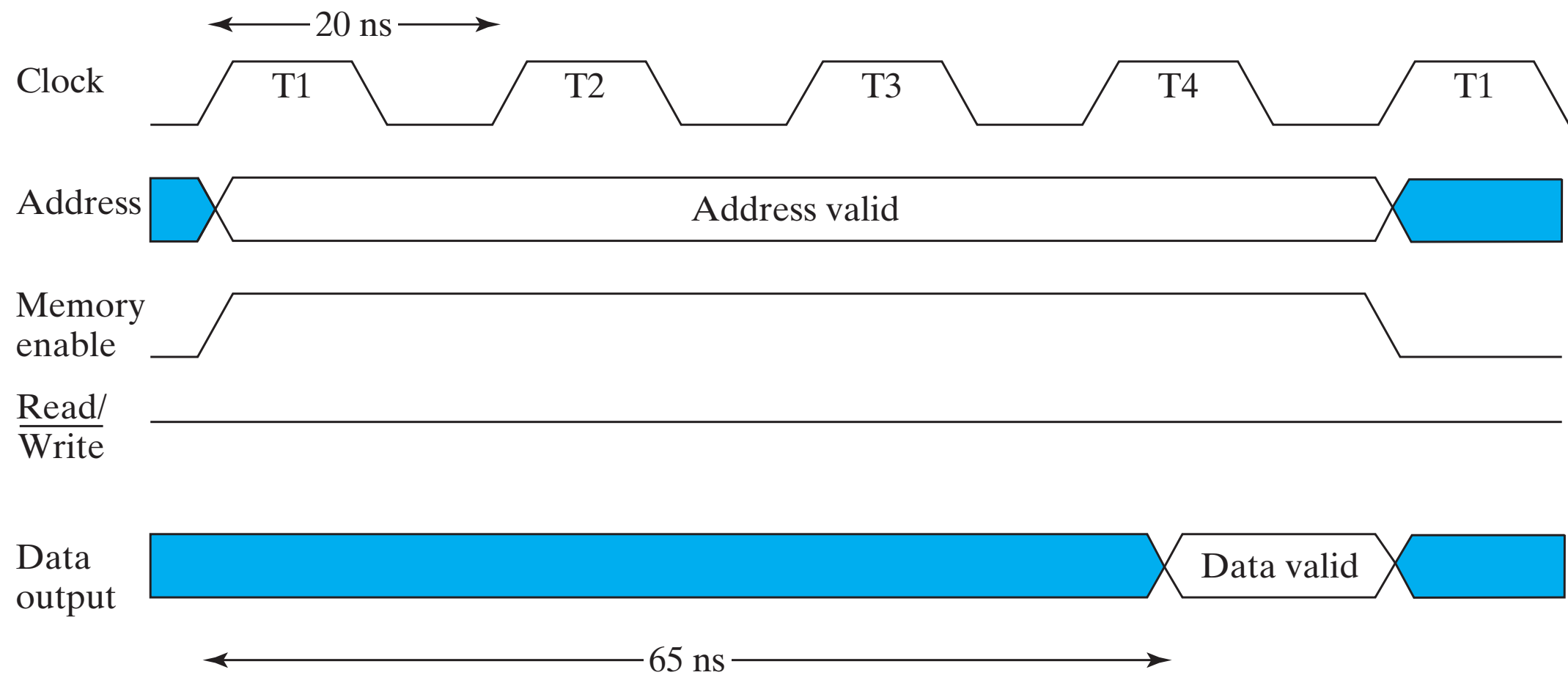

Memory Decoding


Memory Unit and Internal Construction

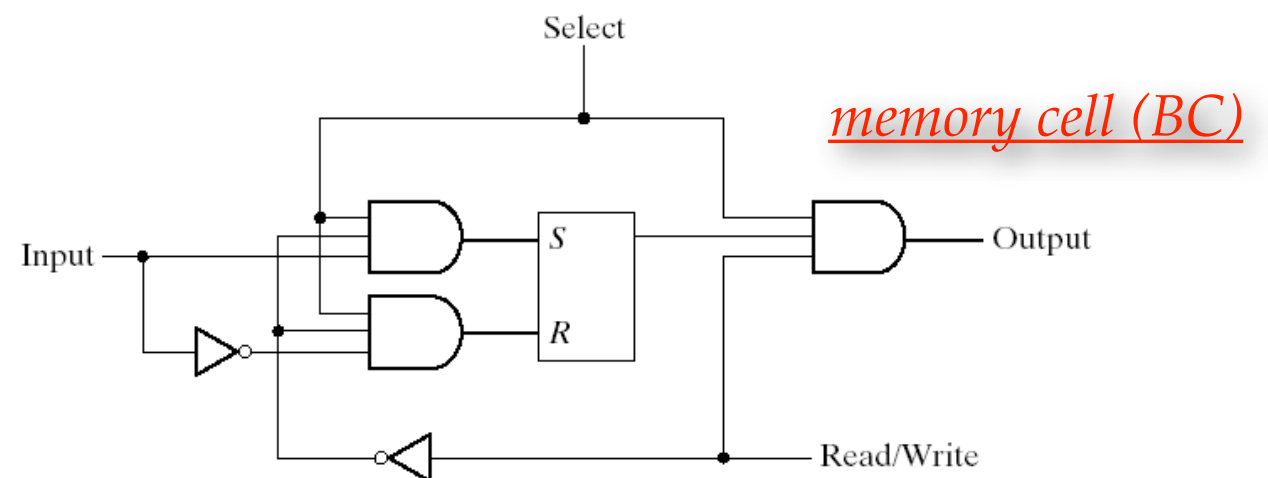- A memory unit has two parts
 - The storage components (memory cell)
 - The decoding circuits to select the memory word
- A RAM of m (2^k) words and n bits per word
 - $m \cdot n$ binary storage cells
 - Decoding circuits to select individual words
 - k -to- 2^k decoder: address input to word line
 - Read / Write control
 - Input data / Output data



4x4 RAM

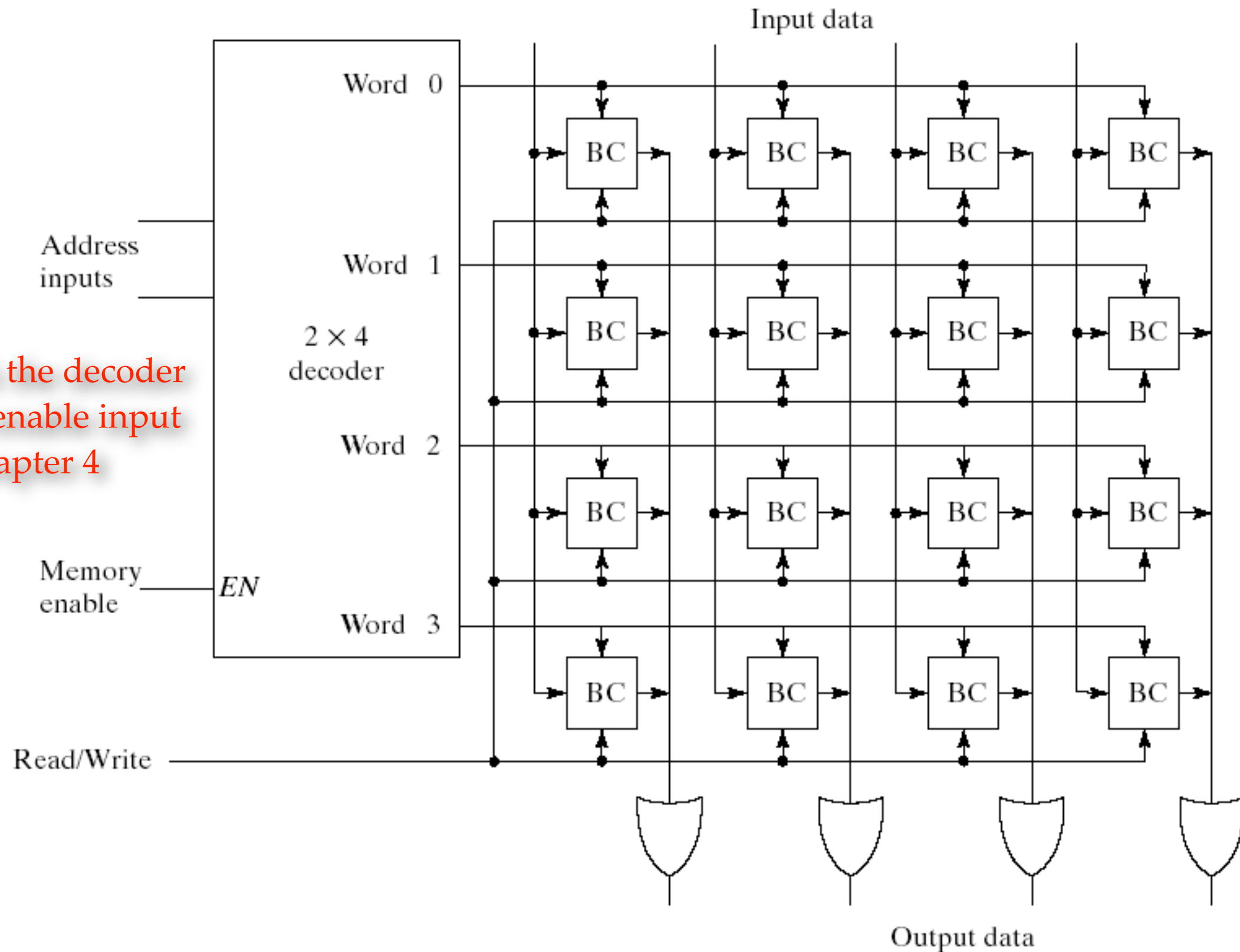
check the decoder
with enable input
in Chapter 4



Output data

Coincident Decoding (1/2)

 - *A two-dimensional selection scheme*
 - To reduce the complexity of the decoding circuits
 - To arrange the memory cells in an array that is close as possible to square



Coincident Decoding (2/2)

- Example: 1k-word memory

- A 10-to-1024 decoder

- 1024 AND gates with 10 inputs per gate


- Two 5-to-32 decoders

- $2 \times (32 \text{ AND gates with 5 inputs per gate})$
- Each word in the memory is selected by the coincidence between 1 of 32 rows and 1 of 32 columns for a total 1024 words
- Two dimensional decoding structure reduces the *circuit complexity* and the *cycle time* of the memory

Read-Only Memory

Read-Only Memory (ROM)

 
- ROM stores permanent binary information
- Once the pattern is established in the ROM, it stays within the unit, no matter power is on or off
- $2^k \times n$ ROM
 - k address input lines
 - enable input(s)
 - three-state outputs



 Example

- 32×8 ROM ($2^5 \times 8$)

- 5-to-32 decoder ($k=5$)
- $32(2^5)$ outputs of the decoder are connected to each of the eight OR gates, which have $32(2^5)$ inputs
- 32×8 internal programmable connections



ROM Programming (1/2)


- Programmable interconnections
- close [1]: connected to high voltage
- open [0]: ground left
- A fuse that can be blown by applying a high voltage pulse

ROM Truth Table (Partial)

Inputs					Outputs							
I4	I3	I2	I1	I0	A7	A6	A5	A4	A3	A2	A1	A0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮					⋮					
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

ROM Programming (2/2)

 - ROM programming according to ROM table using fusing



Combinational Circuit Implementation

- The internal operation of ROM can be interpreted in two ways
 - A memory contains a fixed pattern of *stored words*
 - A unit that implements a combinational circuit as sum of minterms in Section 4-9.
- ROM: a decoder + OR gates
 - a Boolean function = sum of minterms
 - Ex. $A_7(I_4, I_3, I_2, I_1, I_0) = \sum (0, 2, 3, \dots, 29)$ (Fig.7.11)
 - For an n -input, m -output combinational circuit
 - $2^n \times m$ ROM


Example: ROM Implementation (1 / 2)

- A combinational circuit has 3 inputs, 6 outputs and the truth table, construct the circuit

Inputs			Outputs						Decimal
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0	
0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1	1
0	1	0	0	0	0	1	0	0	4
0	1	1	0	0	1	0	0	1	9
1	0	0	0	1	0	0	0	0	16
1	0	1	0	1	1	0	0	1	25
1	1	0	1	0	0	1	0	0	36
1	1	1	1	1	0	0	0	1	49

$B_0=A_0$, $B_1=0$, leave only 8x4 ROM

Example: ROM Implementation (2/2)

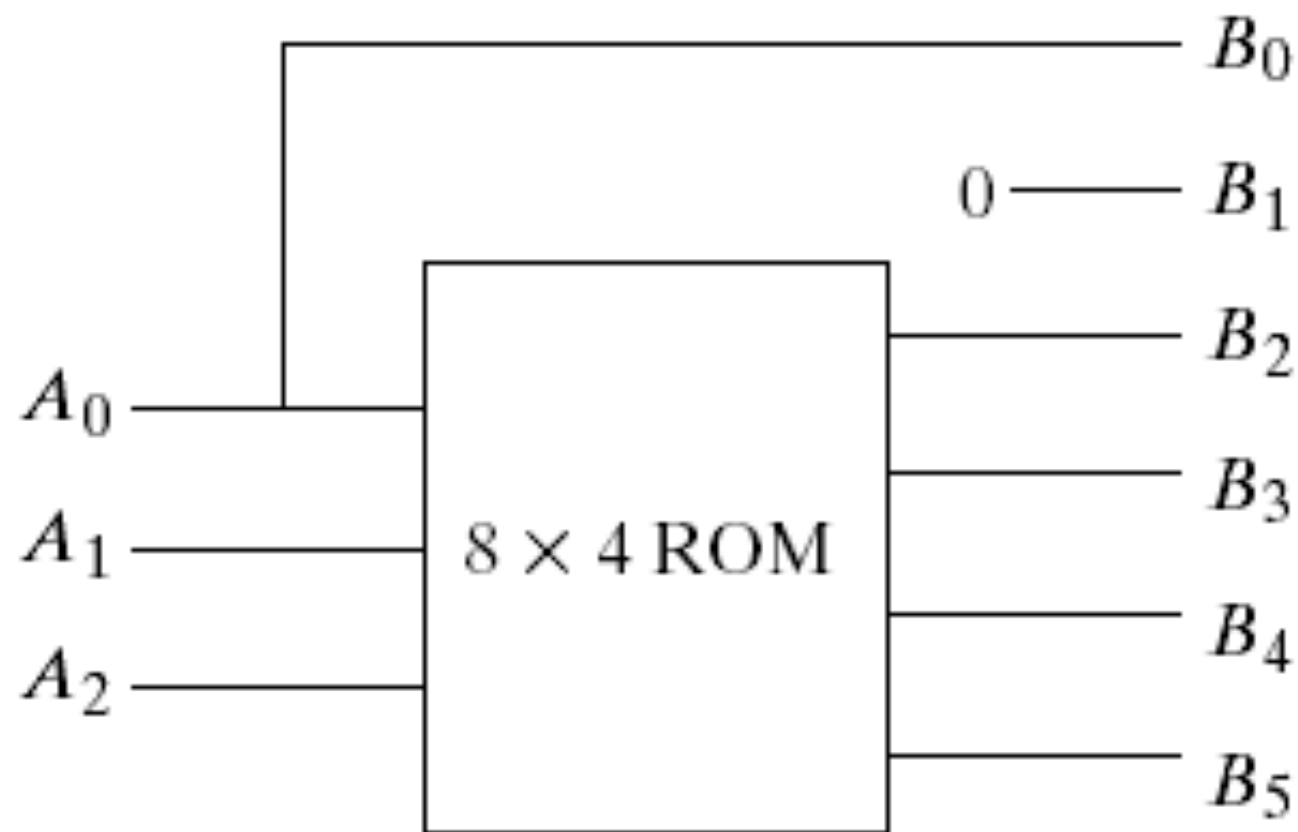

(a) Block diagram

A_2	A_1	A_0	B_5	B_4	B_3	B_2
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0




(b) ROM truth table

Types of ROM

- Mask programmable ROM
 - Data is programmed by IC manufacturers
 - Economical if a large quantity of the same ROM
- PROM: Programmable ROM
 - Fuses in the ROM are blown by high-voltage pulse
 - Universal programmer can program PROM on time
- EPROM: erasable PROM
 - Floating gate
 - The data in the ROM can be erased by UV light
- EEPROM: electrically erasable PROM
 - Longer time is needed to write
 - Flash ROM
 - Limited times of write operations

Combinational PLDs

   - PLD: Programmable logic device
- Programmable two-level logic
 - sum of products
 - an AND array and an OR array




Programmable Logic Array

Programmable Logic Array (PLA)

- PLA has two main parts
 - An array of programmable AND gates
 - Can generate any product terms of the inputs
 - An array of programmable OR gates
 - Can generate the sums of the products
- PLA is more flexible than PROM
 - PLA uses any combination of products while PROM uses sum of minterms
- PLA uses less circuits than PROM
 - Only the needed product terms are generated in PLA while all minterms must be generated in PROM

Example (1 / 2)

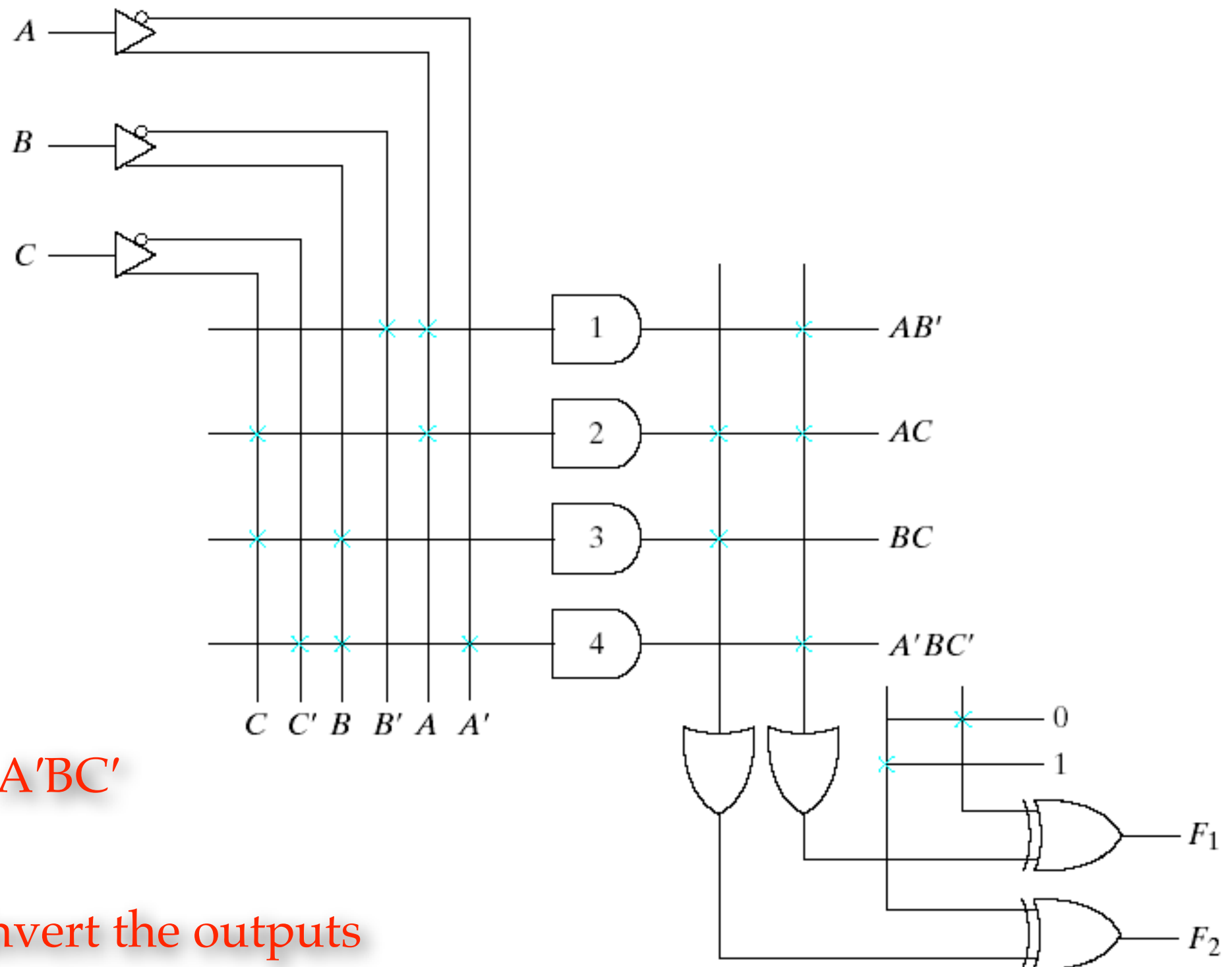

$$F_1 = AB' + A'BC'$$

$$F_2 = (AC + BC)'$$

XOR gates can invert the outputs

Example (2/2)

- Specify the fuse map
 - 1st col: list the product terms numerically
 - 2nd col: specify the required paths between inputs and AND gates
 - 3rd col: specify the required paths between AND gates and OR gates
 - (T)(C) stand for true or complement for programming XOR

PLA Programming Table

		Inputs			Outputs	
					(T)	(C)
		A	B	C	F_1	F_2
Product Term						
AB'	1	1	0	–	1	–
AC	2	1	–	1	1	1
BC	3	–	1	1	–	1
A'BC'	4	0	1	0	1	–

Characteristics of PLA

- The size of a PLA is determined by
 - the number of inputs
 - the number of product terms (AND gates)
 - the number of outputs (OR gates)
- When implementing with a PLA
 - Must reduce the number of distinct product terms before implementation
 - The number of terms in a product is not important

Example 7.2 (1/2)

• Implement $F_1(A, B, C) = \Sigma (0, 1, 2, 4)$; $F_2(A, B, C) = \Sigma (0, 5, 6, 7)$ with a PLA

- Both true and complement of the function should be simplified to check

		BC		B	
		00	01	11	10
A	0	1	1	0	1
	1	1	0	0	0

C

$$F_1 = A'B' + A'C' + B'C'$$

$$F_1 = (AB + AC + BC)'$$

		BC		B	
		00	01	11	10
A	0	1	0	0	0
	1	0	1	1	1

C

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$

Example 7.2 (2/2)

$$F_1 = (AB + AC + BC)'$$

$$F_2 = AB + AC + A'B'C'$$

PLA programming table

	Product term	Inputs			Outputs	
					(C)	(T)
		<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i> ₁	<i>F</i> ₂
<i>AB</i>	1	1	1	–	1	1
<i>AC</i>	2	1	–	1	1	1
<i>BC</i>	3	–	1	1	1	–
<i>A'B'C'</i>	4	0	0	0	–	1

Programmable Array Logic

Programmable Array Logic (PAL)

- A programmable AND array and a fixed OR array
 - The PAL is easier to program, but is not as flexible as the PLA




(b) Programmable array logic (PAL)

PAL Structure


• Example

- product term cannot be shared

 

 Example (1/2)

- $w(A,B,C,D) = \Sigma(2,12,13)$
- $x(A,B,C,D) = \Sigma(7,8,9,10,11,12,13,14)$
- $y(A,B,C,D) = \Sigma(0,2,3,4,5,6,7,8,10,11,15)$
- $z(A,B,C,D) = \Sigma(1,2,8,12,13)$




- $w = ABC' + A'B'CD'$
- $x = A + BCD$
- $y = A'B + CD + B'D'$
- $z = ABC' + A'B'CD' + AC'D' + A'B'C'D$
 $= w + AC'D' + A'B'C'D$

Product Term	AND Inputs				W	Outputs
	A	B	C	D		
1	1	1	0	–	–	$w = ABC'$ $+ A'B'CD'$
2	0	0	1	0	–	
3	–	–	–	–	–	
4	1	–	–	–	–	$x = A$ $+ BCD$
5	–	1	1	1	–	
6	–	–	–	–	–	
7	0	1	–	–	–	$y = A'B$ $+ CD$ $+ B'D'$
8	–	–	1	1	–	
9	–	0	–	0	–	
10	–	–	–	–	1	$z = w$ $+ AC'D'$ $+ A'B'C'D$
11	1	–	0	0	–	
12	0	0	0	1	–	

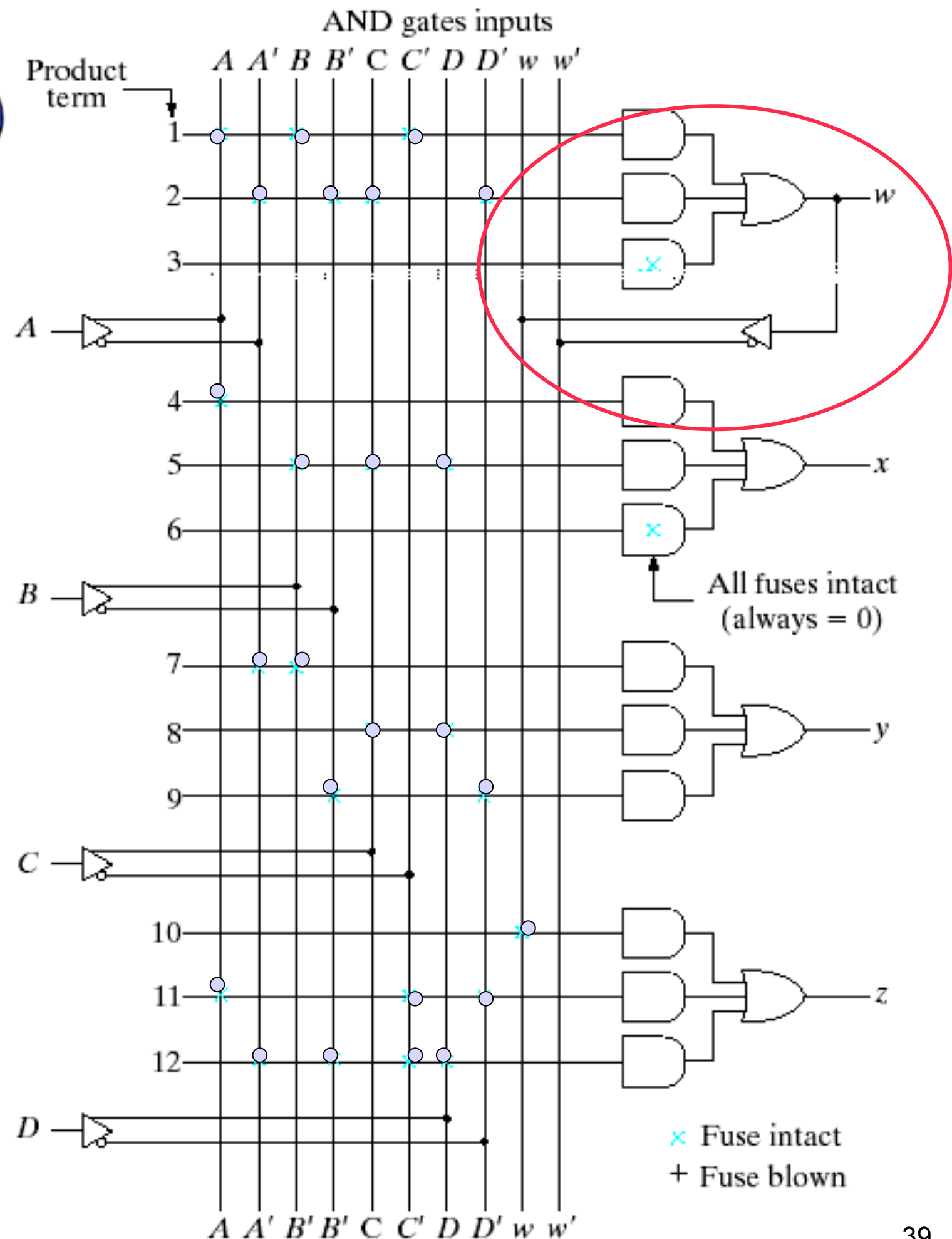Example (2/2)

- Programmed PLA


- $w = ABC' + A'B'CD'$
- $x = A + BCD$
- $y = A'B + CD + B'D'$
- $z = w + AC'D' + A'B'C'D$



Sequential Programmable Devices


Sequential Programmable Devices

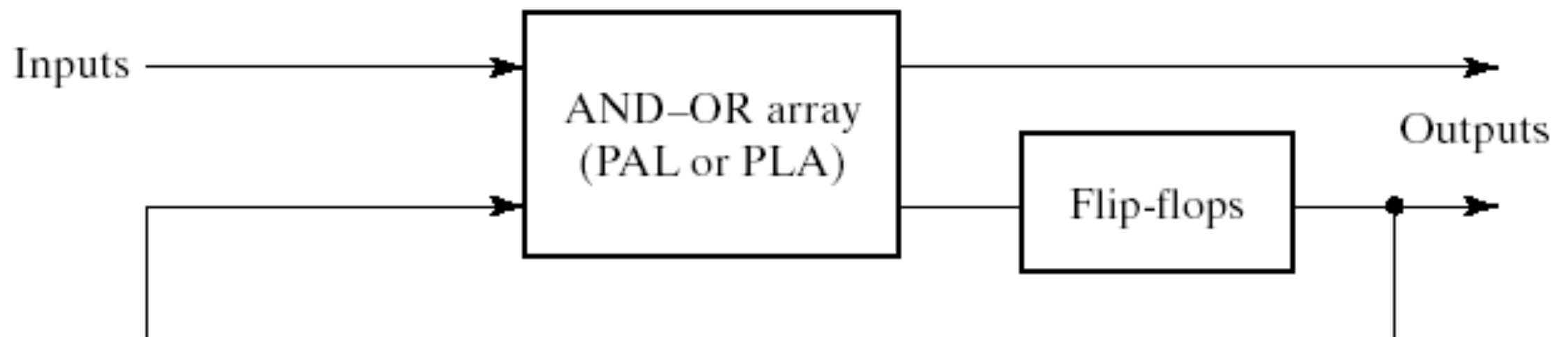- Sequential programmable devices include both programmable gates and flip-flop
- Three major types of sequential programmable devices
 - SPLD: Sequential (or simple) PLD
 - CPLD: Complex PLD
 - FPGA: Field Programmable Gate Array



SPLD

 
- A PAL or PLA is modified by including a number of flip-flops



CPLD

- Complex PLD

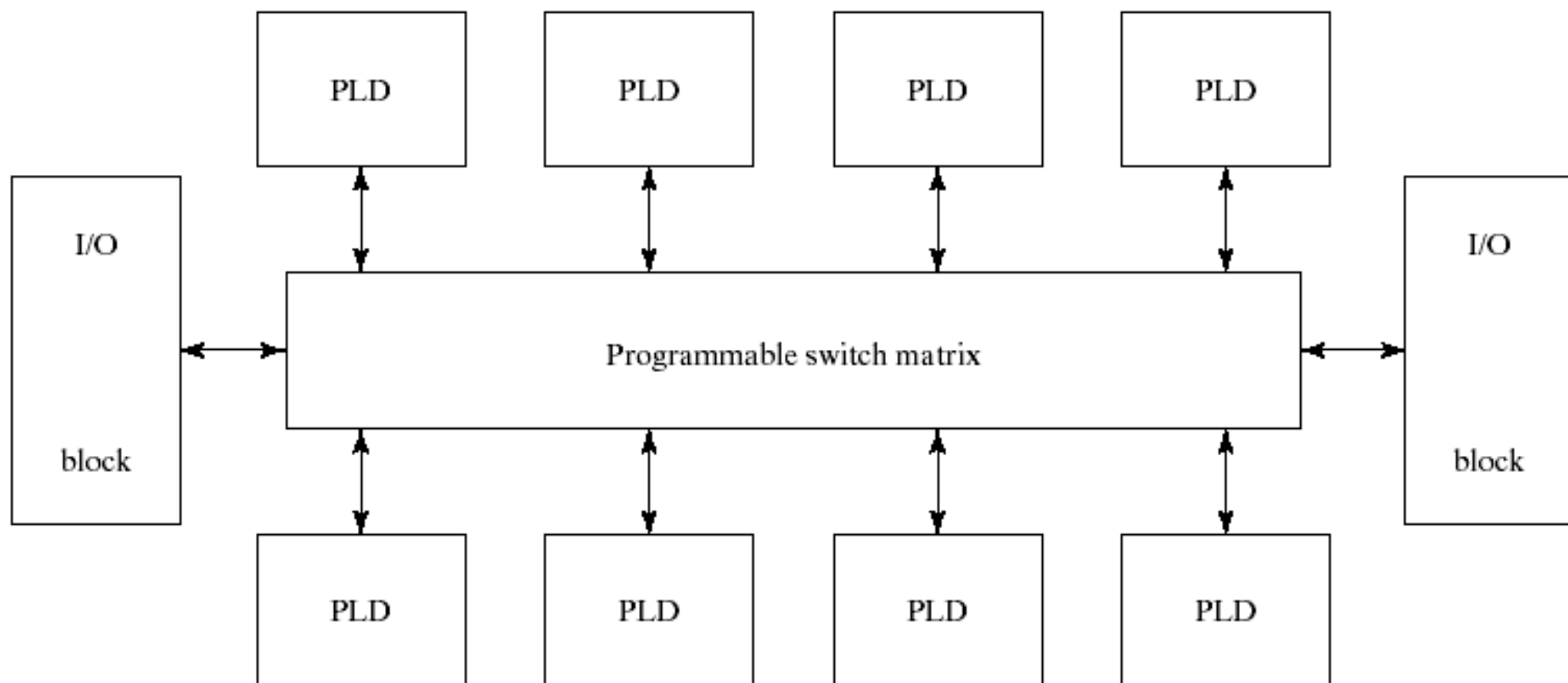
- Put a lot of PLDs on a chip
- Adds wires between PLDs whose connections can be programmed
- Use fuse / EEPROM technology




FPGA

- What is in the array? All sorts of stuff...

 - I/O Cells.
- Logic Cells.
- Memories.
- Microprocessors.
- Clock Management.
- High Speed I/O Transceivers.
- Programmable routing.




Simple FPGA Logic Cell (1 / 2)

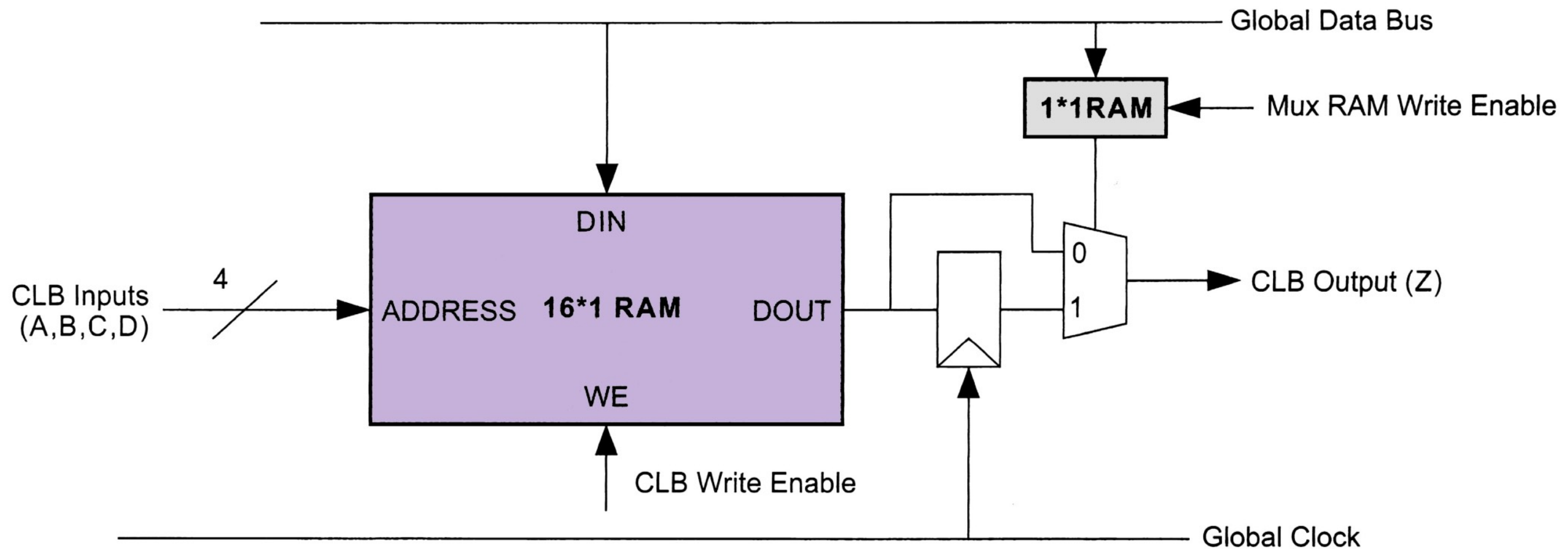


Simple FPGA Logic Cell (2/2)

Table 8.2 RAM CLB functions				
Address	<i>ABCD</i>	$A \bullet B \bullet C \bullet D$	$\sim A$	SUM(A,B,C)
0	0000	0	1	0
1	1000	0	0	1
2	0100	0	1	1
3	1100	0	0	0
4	0010	0	1	1
5	1010	0	0	0
6	0110	0	1	0
7	1110	0	0	1
8	0001	0	1	0
9	1001	0	0	1
10	0101	0	1	1
11	1101	0	0	0
12	0011	0	1	1
13	1011	0	0	0
14	0111	0	1	0
15	1111	1	0	1

Simple FPGA Routing Cell (1/2)

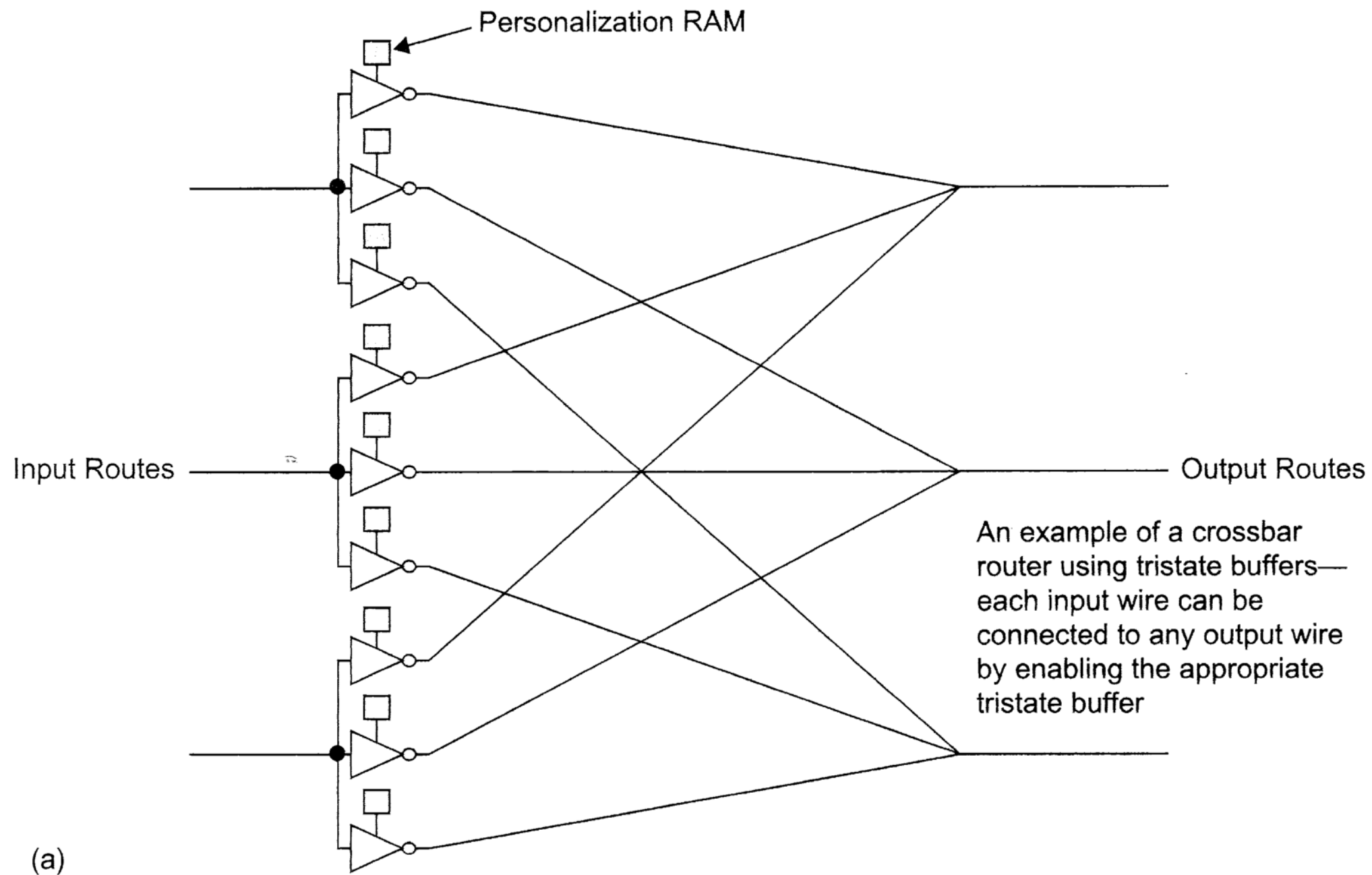

Simple FPGA Routing Cell (2/2)

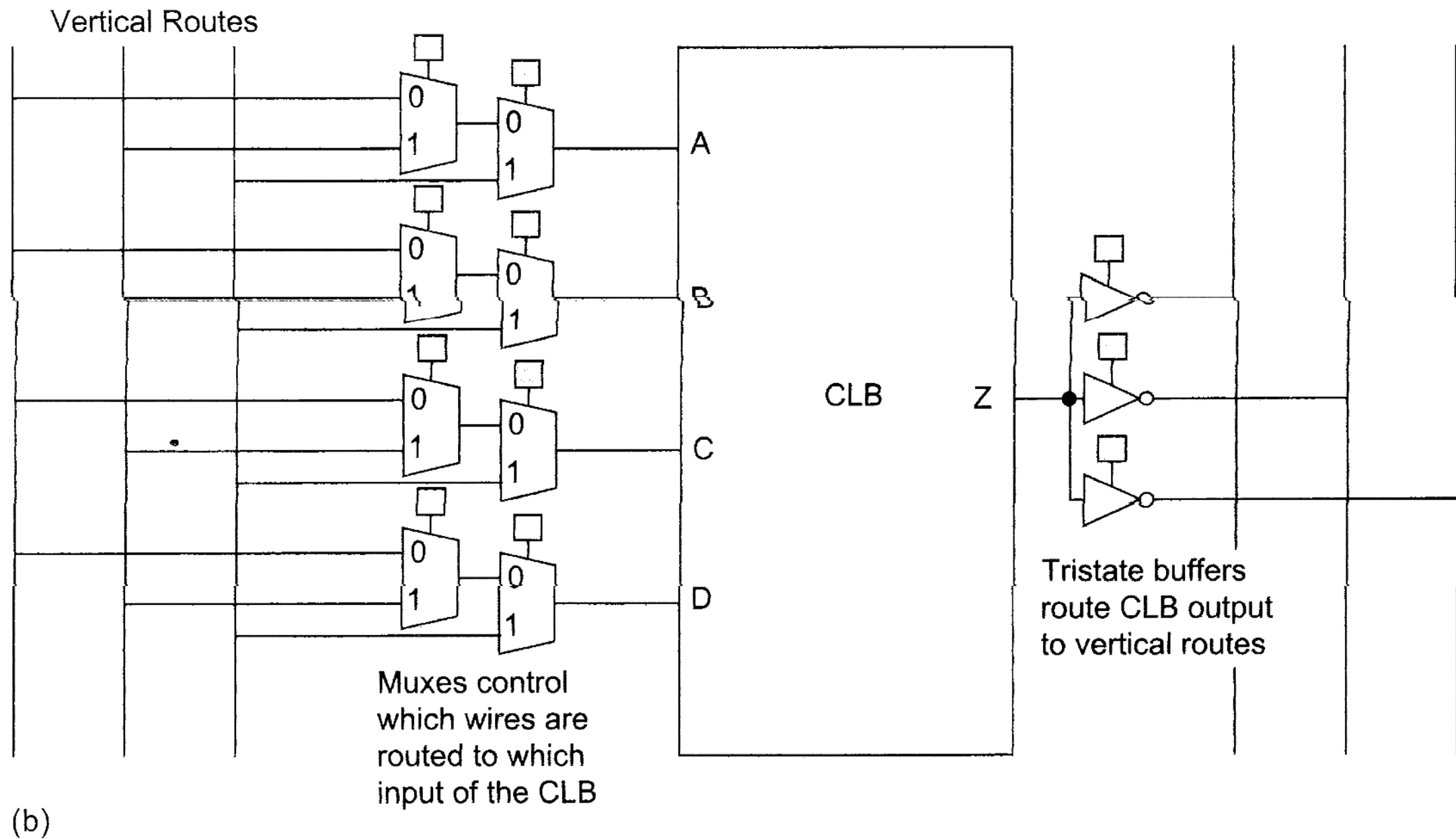

Routed FPGA

