

# Problems and Solutions

---

Ch. 5 6 7

# Problem

---

- . The memory units that follow are specified by the number of words times the number of
- . bits per word. How many address lines and input–output data lines are needed in each case?

(a)  $8\text{ K} * 32$

(b)  $2\text{ G} * 8$

# Solutions

---

.  $8k \times 32 = 2^{13} \times 32$  A=13, D= 32

.  $2G \times 8 = 2^{31} \times 8$

# Problems

---

- a) How many 32 K \* 8 RAM chips are needed to provide a memory capacity of 256 K bytes?
- b) How many lines of the address must be used to access 256 K bytes? How many of these lines are connected to the address inputs of all chips?
- c) How many lines must be decoded for the chip select inputs? Specify the size of the decoder.

# Solutions

---

- .  $256k / 32k = 8$  chips
- .  $256k = 2^{18}$  (18 address lines for memory);
- .  $32 K = 2^{15}$  (15 address pins / chip)
- .  $18 - 15 = 3$  lines; must decode with  $3 \times 8$  decoder

# Problem

---

Specify the size of a ROM (number of words and number of bits per word) that will accommodate the truth table for the following combinational circuit components:

- a) a binary multiplier that multiplies two 4-bit binary words,
- b) a 4-bit adder–subtractor, with one carry-in and one carry out

# Solutions


---


- . 8 inputs 8 outputs  $2^8 \times 8$  256 x 8 ROM
- . 9 inputs 5 outputs  $2^9 \times 5$  512 x 5 ROM

- 
- . Tabulate the PLA programming table and the truth table for an 8x2 ROM for the two Boolean functions listed below.
  - .  $A(x, y, z) = (1, 3, 5, 6)$
  - .  $B(x, y, z) = (1, 3, 6, 7)$



# Solutions

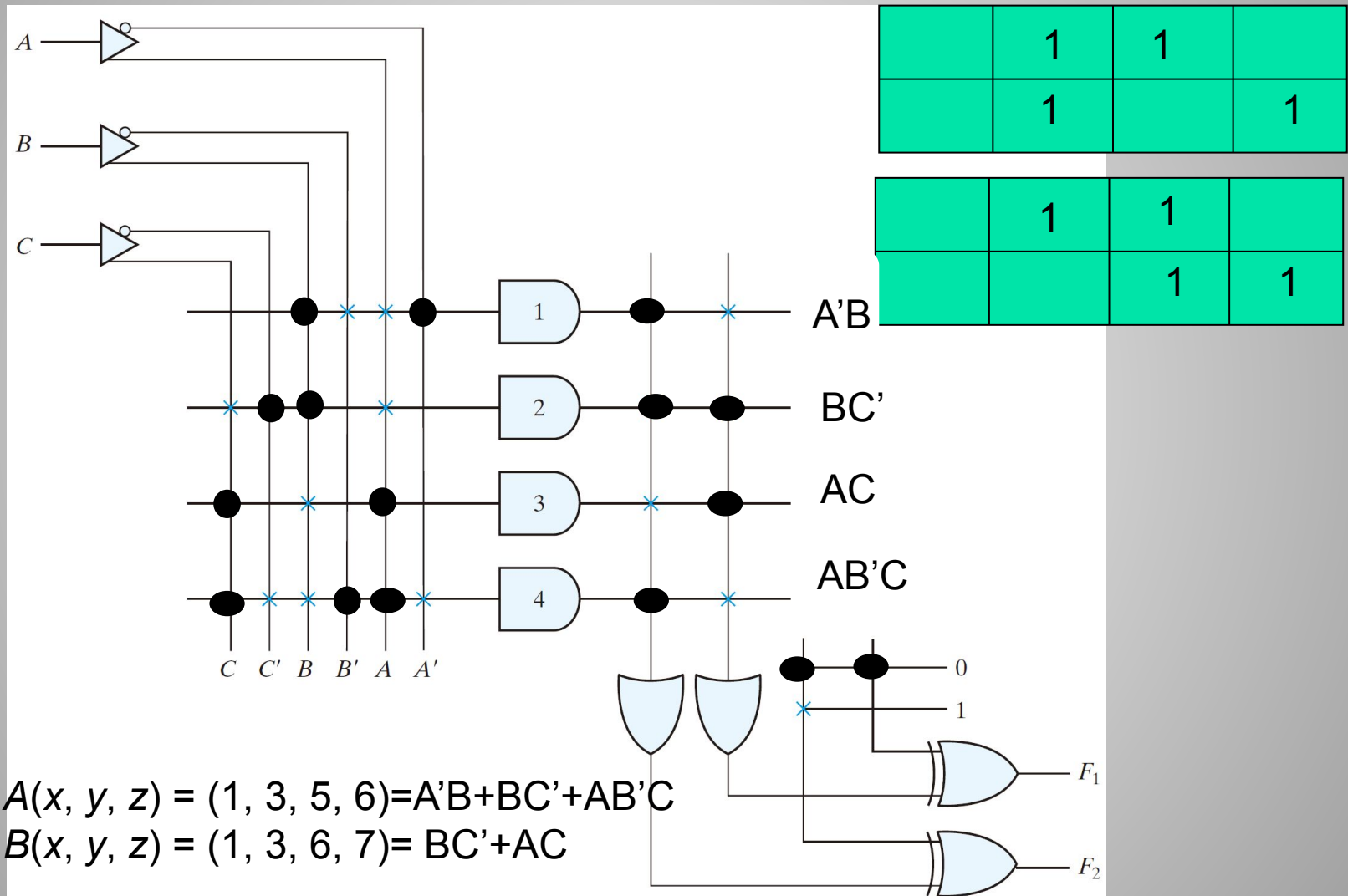

 

$$A(x, y, z) = (1, 3, 5, 6)$$

$$B(x, y, z) = (1, 3, 6, 7)$$

# Problems

---

- . Compare the price and performance of SRAM, DRAM, magnetic disk, and flash

# Solution

---

. \$/GB

SRAM > DRAM > flash > magnetic disk

Performance

fast to slow :

SRAM , DRAM , flash , magnetic disk

# Problems


---

- . Develop the state diagram for a Mealy state machine that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line.
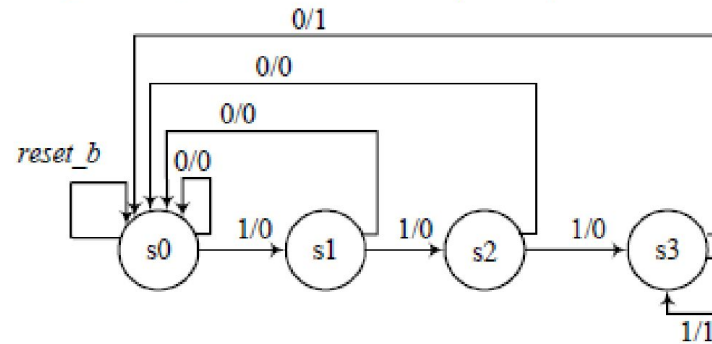
# Solution

Assumption: Synchronous active-low reset

Mealy machine, links for reset on-the-fly are implicit and not shown



# Solutions


```
module Prob_5_55 (input x_in, clk, reset_b, output reg y);  
  parameter s0 = 2'd0;  
  parameter s1 = 2'd1;  
  parameter s2 = 2'd2;  
  parameter s3 = 2'd3;  
  reg [1: 0] state, next_state;
```

```
  always @ (posedge clk, negedge reset_b)  
    if (reset_b == 1'b0) state <= s0;  
    else state <= next_state;
```

```
  always @ (state, x_in) begin  
    y = 1'b0;  
    next_state = s0;
```

```
    case (state)      // Mealy machine  
    s0:  if (x_in) begin y = 1'b0; next_state = s1; end  
         else begin y = 1'b0; next_state = s0; end  
    s1:  if (x_in) begin y = 1'b0; next_state = s2; end  
         else y = 1'b0; next_state = s0; end  
    s2:  if (x_in) begin y = 1'b0; next_state = s3; end  
         else begin y = 1'b0; next_state = s0; end  
    s3:  if (x_in) begin y = 1'b1; next_state = s3; end  
         else begin y = 1'b1; next_state = s0; end  
    default:  begin y = 1'b0; next_state = s0; end  
  endcase
```

 Assumption: Synchronous active-low reset  
Mealy machine, links for reset on-the-fly are implicit and not shown



# Problems

---

- . A synchronous Moore machine has two inputs  $x_1$  and  $x_2$ , and an output  $y_{out}$ . If both inputs have the same value, the output is asserted for one cycle; otherwise, the output is 0. Develop a state diagram



