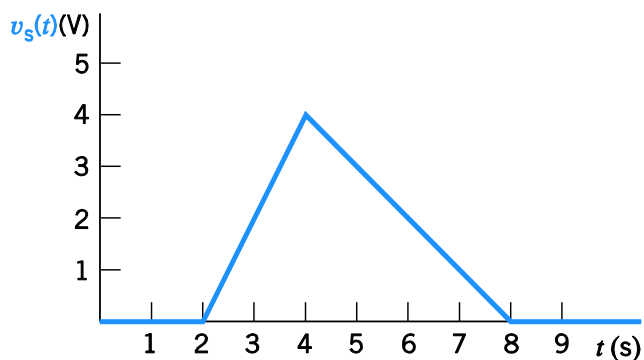



Chapter 7 Exercises

Exercise 7.2-1 Determine the current $i(t)$ for $t > 0$ for the circuit of Figure E 7.2-1b when $v_s(t)$ is the voltage shown in Figure E 7.2-1a.

Hint: Determine $i_C(t)$ and $i_R(t)$ separately, then use KCL.



(a)

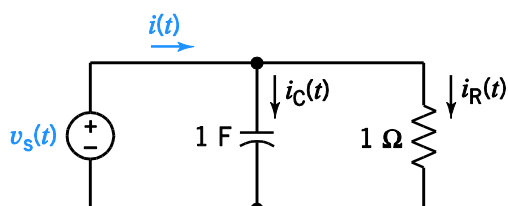

(b)

Figure E 7.2-1

Answer:

$$v(t) = \begin{cases} 2t - 2 & 2 < t < 4 \\ 7 - t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

Solution:

$$i_C(t) = 1 \frac{d}{dt} v_s(t) = \begin{cases} 2 & 2 < t < 4 \\ -1 & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases} \quad \text{and} \quad i_R(t) = 1 v_s(t) = \begin{cases} 2t - 4 & 2 < t < 4 \\ 8 - t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

so

$$i(t) = i_C(t) + i_R(t) = \begin{cases} 2t - 2 & 2 < t < 4 \\ 7 - t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

Exercise 7.3-1 A $200\text{-}\mu\text{F}$ capacitor has been charged to 100 V . Find the energy stored by the capacitor. Find the capacitor voltage at $t = 0^+$ if $v(0^-) = 100\text{ V}$.

Answer: $w(1) = 1\text{ J}$ and $v(0^+) = 100\text{ V}$

Solution:

$$w = \frac{Cv^2}{2} = \frac{1}{2}(2 \times 10^{-4})(100)^2 = \underline{1\text{ J}}$$

$$v_c(0^+) = v_c(0^-) = \underline{100\text{ V}}$$

Exercise 7.3-2 A constant current $i = 2\text{ A}$ flows into a capacitor of $100\mu\text{F}$ after a switch is closed at $t = 0$. The voltage of the capacitor was equal to zero at $t = 0^-$. Find the energy stored at (a) $t = 1\text{ s}$ and (b) $t = 100\text{ s}$.

Answer: $w(1) = 20\text{ kJ}$ and $w(100) = 200\text{ MJ}$

Solution:

(a) $w(t) = w(0) + \int_0^t vi\,dt$

First, $w(0) = 0$ since $v(0) = 0$

Next, $v(t) = v(0) + \frac{1}{C} \int_0^t i\,dt = 10^4 \int_0^t 2\,dt = \underline{2 \times 10^4 t}$

$\therefore w(t) = \int_0^t (2 \times 10^4)t(2)\,dt = 2 \times 10^4 t^2$

$w(1\text{s}) = 2 \times 10^4 \text{ J} = \underline{20\text{ kJ}}$

(b)

$w(100\text{s}) = 2 \times 10^4 (100)^2 = 2 \times 10^8 \text{ J} = \underline{200\text{ MJ}}$

Exercise 7.4-1 Find the equivalent capacitance for the circuit of Figure E 7.4-1

Answer: $C_{\text{eq}} = 4\text{ mF}$


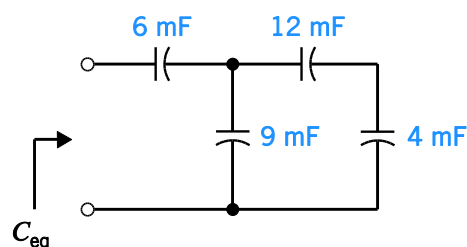


Figure E 7.4-1

Solution:

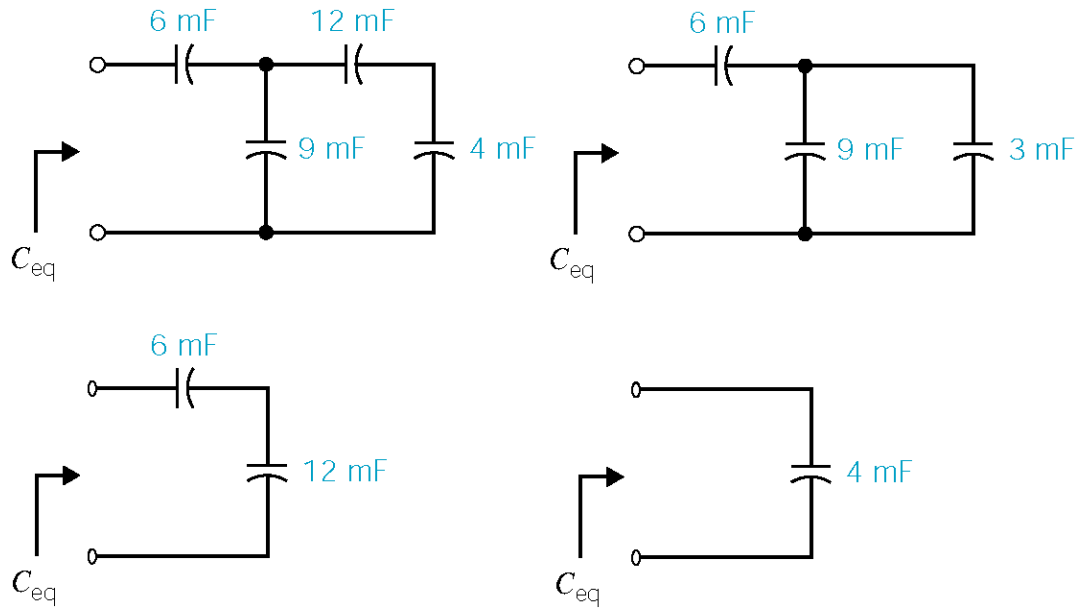

Exercise 7.4-2 Determine the equivalent capacitance C_{eq} for the circuit shown in Figure E 7.4-2.

Answer: 10/19 mF

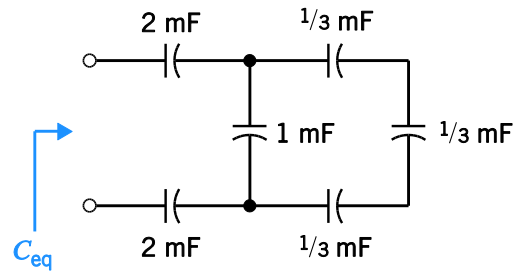


Figure E 7.4-2

Solution:

$$C_{eq1} = \frac{1}{\frac{1}{1/3} + \frac{1}{1/3} + \frac{1}{1/3}} = \frac{1}{9}, \quad C_{eq2} = 1 + C_{eq1} = \frac{10}{9}, \quad C_{eq} = \frac{1}{\frac{1}{2} + \frac{1}{2} + \frac{1}{C_{eq2}}} = \frac{1}{\frac{1}{2} + \frac{1}{2} + \frac{9}{10}} = \frac{1}{19} = \frac{10}{19} \text{ mF}$$

Exercise 7.5-1 Determine the voltage $v(t)$ for $t > 0$ for the circuit of Figure E 7.5-1b when $i_s(t)$ is the current shown in Figure E 7.5-1a.

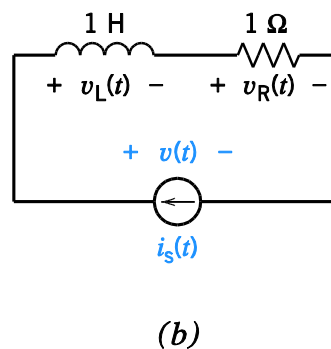
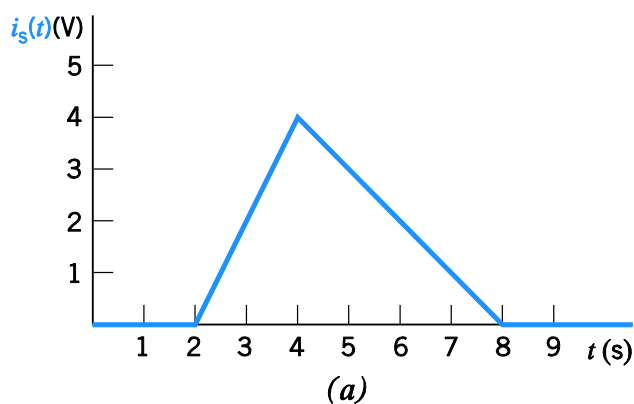


Figure E 7.5-1b

Hint: Determine $v_L(t)$ and $v_R(t)$ separately, then use KVL.

Answer:
$$v(t) = \begin{cases} 2t-2 & 2 < t < 4 \\ 7-t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

Solution:

$$v_L(t) = 1 \frac{d}{dt} i_s(t) = \begin{cases} 2 & 2 < t < 4 \\ -1 & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases} \quad \text{and} \quad v_R(t) = 1 i_s(t) = \begin{cases} 2t-4 & 2 < t < 4 \\ 8-t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

so

$$v(t) = v_L(t) + v_R(t) = \begin{cases} 2t-2 & 2 < t < 4 \\ 7-t & 4 < t < 8 \\ 0 & \text{otherwise} \end{cases}$$

Exercise 7.7-1 Find the equivalent inductance of the circuit of Figure E 7.7-1.

Answer: $L_{eq} = 14 \text{ mH}$


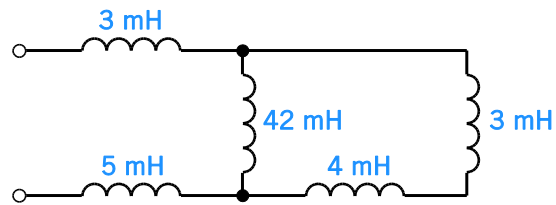


Figure E 7.7-1

Solution:

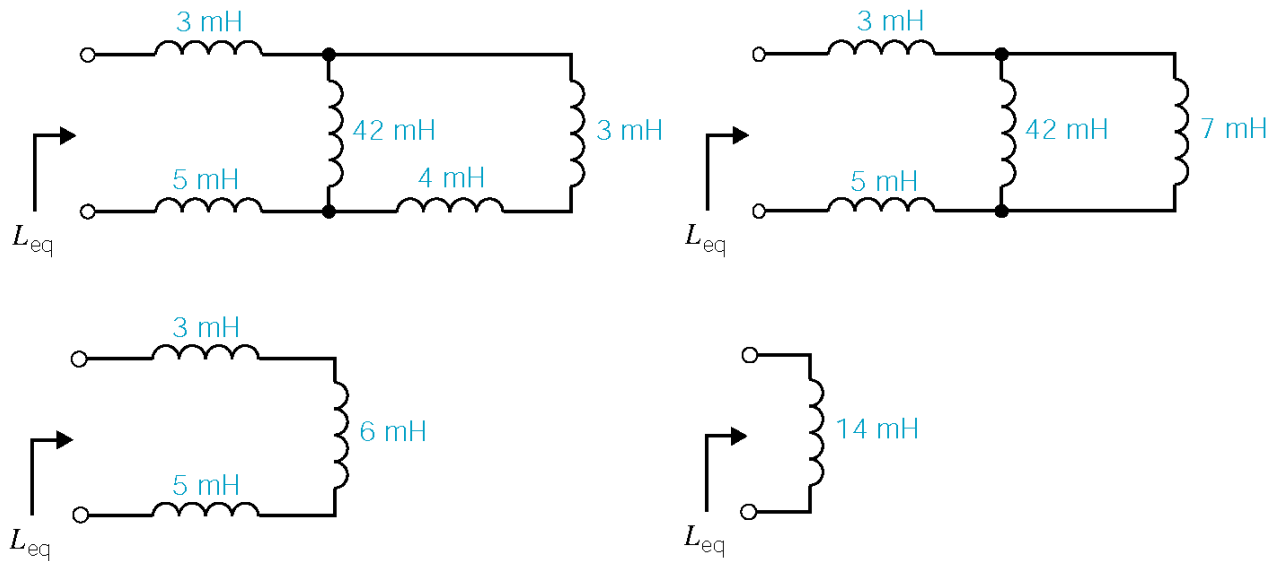

Exercise 7.7-2 Find the equivalent inductance of the circuit of Figure E 7.7-2.


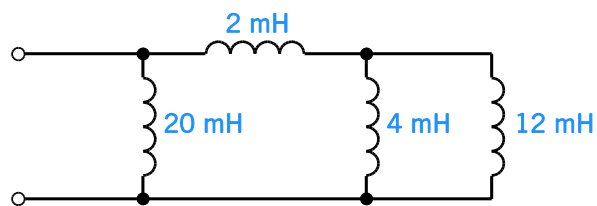


Figure E 7.7-2

Solution:

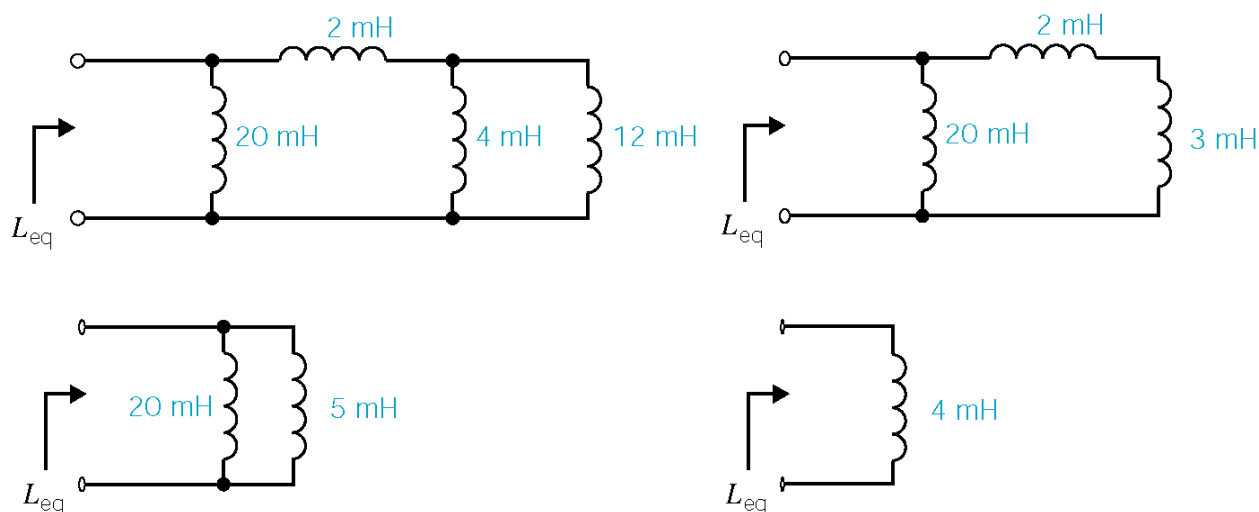

Section 7-2: Capacitors

P 7.2-1

Solution:

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau \quad \text{and} \quad q = Cv$$

In our case, the current is constant so $\int_0^t i(\tau) d\tau = it$.

$$\therefore Cv(t) = Cv(0) + it$$

$$\therefore t = \frac{q - Cv(0)}{i} = \frac{180 \times 10^{-6} - (20 \times 10^{-6})(5)}{30 \times 10^{-3}} = \underline{2.7 \text{ ms}}$$

P 7.2-2

Solution:

$$i(t) = C \frac{d}{dt} v(t) = \frac{1}{8} \frac{d}{dt} 12 \cos(2t + 30^\circ) = \frac{1}{8} (12) (-2) \sin(2t + 30^\circ) = 3 \cos(2t + 120^\circ) \text{ A}$$

P 7.2-3**Solution:**

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0) = \frac{1}{2 \times 10^{-12}} \int_0^t i(\tau) d\tau - 10^{-3}$$

$$0 < t < 2 \times 10^{-9}$$

$$i_s(t) = 0 \Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_0^t 0 d\tau - 10^{-3} = -10^{-3}$$

$$2 \times 10^{-9} < t < 3 \times 10^{-9}$$

$$i_s(t) = 4 \times 10^{-6} \text{ A}$$

$$\Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{2\text{ms}}^t (4 \times 10^{-6}) d\tau - 10^{-3} = -5 \times 10^{-3} + (2 \times 10^6) t$$

$$\text{In particular, } v(3 \times 10^{-9}) = -5 \times 10^{-3} + (2 \times 10^6)(3 \times 10^{-9}) = 10^{-3}$$

$$3 \times 10^{-9} < t < 5 \times 10^{-9}$$

$$i_s(t) = -2 \times 10^{-6} \text{ A}$$

$$\Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{3\text{ms}}^t (-2 \times 10^{-6}) d\tau + 10^{-3} = 4 \times 10^{-3} - (10^6) t$$

$$\text{In particular, } v(5 \times 10^{-9}) = 4 \times 10^{-3} - (10^6)(5 \times 10^{-9}) = -10^{-3} \text{ V}$$

$$5 \times 10^{-9} < t$$

$$i_s(t) = 0 \Rightarrow v(t) = \frac{1}{2 \times 10^{-12}} \int_{5\text{ms}}^t 0 d\tau - 10^{-3} = -10^{-3} \text{ V}$$

P 7.2-4**Solution:**

$$(a) \quad i(t) = C \frac{d}{dt} v(t) = \begin{cases} 0 & 0 < t < 2 \\ x(t) & 2 < t < 6 \\ 0.8 & 6 < t \end{cases}$$

$$(b) \quad v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0) = 2 \int_0^t i(\tau) d\tau$$

$$\text{For } 0 < t < 2, i(t) = 0 \text{ A so } v(t) = 2 \int_0^t 0 d\tau + 0 = 0 \text{ V}$$

$$\text{For } 2 < t < 6, i(t) = 0.2 t - 0.4 \text{ V so}$$


$$v(t) = 2 \int_1^t (0.2\tau - 0.4) d\tau + 0 = (0.2\tau^2 - 0.8\tau) \Big|_2^t = 0.2t^2 - 0.8t + 0.8 \text{ V}$$

$$v(6) = 0.2(6^2) - 0.8(6) + 0.8 = 3.2 \text{ V.}$$

$$\text{For } 6 < t, i(t) = 0.8 \text{ A so } v(t) = 2 \int_6^t 0.8 d\tau + 3.2 = 1.6t - 6.4 \text{ V}$$

P 7.2-5**Solution:**

$$\begin{aligned}
 v(t) &= v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau = 30 + 2.5 \times 10^4 \int_0^t (6 \times 10^{-3}) e^{-6\tau} d\tau \\
 &= 30 + 150 \int_0^t e^{-6\tau} d\tau \\
 &= 30 + 150 \left[-\frac{1}{6} e^{-6\tau} \right]_0^t = \underline{55 - 25e^{-6t} \text{ V}}
 \end{aligned}$$

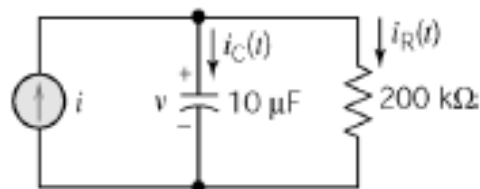P 7.2-6**Solution:**

$$\begin{aligned}
 i_R &= \frac{v}{200 \times 10^3} = \frac{1}{40} (1 - 2e^{-2t}) \times 10^{-3} = 25(1 - 2e^{-2t}) \mu\text{A} \\
 i_C &= C \frac{dv}{dt} = (10 \times 10^{-6}) (-2) (-10 e^{-2t}) = 200 e^{-2t} \mu\text{A} \\
 i &= i_R + i_C = 200 e^{-2t} + 25 - 50 e^{-2t} \\
 &= \underline{25 + 150 e^{-2t} \mu\text{A}}
 \end{aligned}$$

P 7.2-7**Solution:**

$$\begin{aligned}
 v(t) &= 1 \int_0^t i(t) dt + 2 \\
 &= 2 \quad \text{for} \quad 0 \leq t \leq 2 \\
 &= 1 \int_2^t 4 dt + 2 = 4(t - 2) + 2 = 4t - 6 \quad \text{for} \quad 2 \leq t \leq 3 \\
 &= 1 \int_2^3 4 dt + 1 \int_3^t -4 dt + 2 = 4 - 4(t - 3) + 2 = -4t + 18 \quad \text{for} \quad 3 \leq t \leq 4 \\
 &= 1 \int_2^3 4 dt + 1 \int_3^4 -4 dt + 2 = 2 \quad \text{for} \quad t \geq 4
 \end{aligned}$$

In summary

$$v(t) = \begin{cases} 2 & 0 \leq t \leq 2 \\ 4t - 6 & 2 \leq t \leq 3 \\ -4t + 18 & 3 \leq t \leq 4 \\ 2 & 4 \leq t \end{cases}$$

P 7.2-8**Solution:**

$$v(t) = v(0) + \frac{1}{C} \int_0^t i_s(t) dt = -6 + 5 \int_0^t i_s(t) dt$$

For $0 \leq t \leq 0.5$ ($i_s(t) = 8t$ for $0 \leq t \leq 0.5$)

$$v(t) = -6 + 5 \int_0^t 8\tau d\tau = -6 + 40 \left(\frac{\tau^2}{2} \right) \Big|_0^t = -6 + 20t^2$$

For example $v(0) = -6$, $v\left(\frac{1}{4}\right) = -4.75$, $v\left(\frac{1}{2}\right) = -1$ For $0.5 \leq t \leq 1$

$$v(t) = -1 + 5 \int_{0.5}^t 4 d\tau = -1 + 20(t - 0.5) = 20t - 11$$

For example $v(0.5) = -1$, $v(1) = 9$ For $t \geq 1$

$$v(t) = 9 + 5 \int_1^t 0 d\tau = 9$$

In summary

$$v(t) = \begin{cases} -6 + 20t^2 & 0 \leq t \leq 0.5 \text{ s} \\ 20t - 11 & 0.5 \leq t \leq 1 \text{ s} \\ 9 & t \geq 1 \text{ s} \end{cases}$$

P 7.2-9**Solution:**Representing $v_s(t)$ using equations of the straight line segments gives

$$v_s(t) = \begin{cases} 0 & t \leq 1 \\ 32t - 32 & 1 \leq t \leq 2 \\ -16t + 64 & 2 \leq t \leq 4 \\ 0 & 4 \leq t \end{cases}$$

Use KCL to get

$$i(t) = \frac{1}{2} \frac{d}{dt} v_s(t) + \frac{v_s(t)}{5} = \begin{cases} 0 & t \leq 1 \\ 16 + \frac{32t - 32}{8} & 1 \leq t \leq 2 \\ -8 + \frac{64 - 16t}{8} & 2 \leq t \leq 4 \\ 0 & t \geq 4 \end{cases}$$


$$i(t) = \begin{cases} 0 & t \leq 1 \\ 4t + 12 & 1 \leq t \leq 2 \\ -2t & 2 \leq t \leq 4 \\ 0 & t \geq 4 \end{cases}$$

P 7.2-10**Solution:**

$$\begin{aligned}
 i_C(t) &= \frac{1}{40} \frac{d}{dt} v(t) \\
 &= \frac{1}{40} (+20e^{-2t}) \\
 &= 0.5e^{-2t} \text{ A for } t > 0
 \end{aligned}$$


Apply KCL to get

$$i(t) = 4 - i_C(t) = 4 - 0.5e^{-2t} \text{ A for } t > 0$$

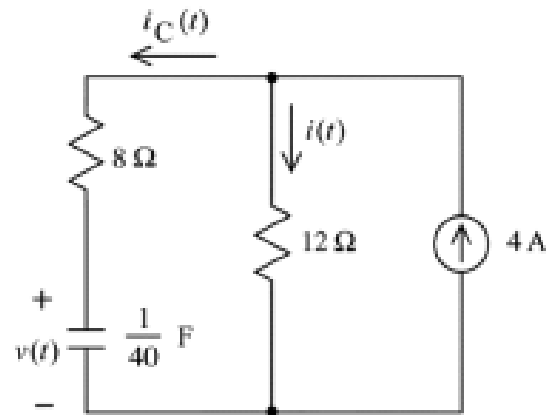**P 7.2-11****Solution:**

Apply KCL to node a to get

$$\begin{aligned}
 i(t) + \frac{v(t)}{90} + 0.030 \frac{d}{dt} v(t) &= 0 \\
 i(t) &= -\frac{10 - 8e^{-5t}}{90} - 0.030 \frac{d}{dt} (10 - 8e^{-5t}) = -\frac{1}{9} - \frac{10}{9} e^{-5t} \text{ A for } t > 0
 \end{aligned}$$

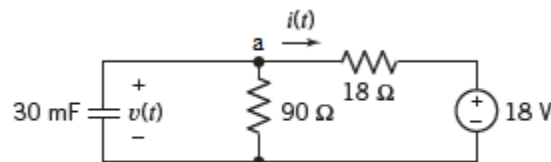**P 7.2-12****Solution:**

$$v(t) = \frac{1}{C} \int_{t_0}^t i_s(\tau) d\tau + v(t_0) = \frac{1}{\frac{1}{3}} \int_0^t i_f(\tau) d\tau - 12$$

$$v(t) = 3 \int_0^t 4 d\tau - 12 = 12t - 12 \quad \text{for } 0 < t < 4$$

In particular, $v(4) = 36 \text{ V}$.

$$v(t) = 3 \int_4^t (-2) d\tau + 36 = 60 - 6t \quad \text{for } 4 < t < 10$$

In particular, $v(10) = 0 \text{ V}$.

$$v(t) = 3 \int_{10}^t 0 d\tau + 0 = 0 \quad \text{for } 10 < t$$

P7.2-13**Solution:**

The capacitor voltage is related to the capacitor current by

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

That is:

$$4 - 1.25e^{-1.2t} = \frac{1}{C} \int_0^t 3.75e^{-1.2\tau} d\tau + v(0) = \frac{3.75}{C(-1.2)} e^{-1.2\tau} \Big|_0^t + v(0) = \frac{-3.125}{C} (e^{-1.2t} - 1) + v(0)$$

Equating the coefficients of $e^{-1.2t}$ gives

$$12.5 = \frac{3.125}{C} \Rightarrow C = \frac{3.125}{12.5} = 0.25 = 250 \text{ mF}$$

P7.2-14**Solution:**

Apply KVL to the mesh to get

$$v(t) = 8i(t) + v_C(t) = 8i(t) + \left[\frac{1}{0.1} \int_0^t i(\tau) d\tau + v(0) \right]$$

That is,

$$\begin{aligned} v(t) &= 8(3e^{-25t}) + \frac{1}{0.1} \int_0^t 3e^{-25\tau} d\tau - 2 \\ &= 24e^{-25t} + \frac{3}{0.1(-25)} (e^{-25t} - 1) - 2 \\ &= 24e^{-25t} - 1.2(e^{-25t} - 1) - 2 \\ &= 22.8e^{-25t} - 0.8 \text{ V for } t > 0 \end{aligned}$$

P7.2-15**Solution:**

Apply KVL to the mesh to get

$$v(t) = Ri(t) + v_C(t) = Ri(t) + \left[\frac{1}{C} \int_0^t i(\tau) d\tau + v(0) \right]$$

That is


$$\begin{aligned} 9.8e^{-25t} + 0.6 &= R(5e^{-25t}) + \left[\frac{1}{C} \int_0^t 5e^{-25\tau} d\tau - 2 \right] \\ &= 5Re^{-25t} + \frac{5}{C(-25)}(e^{-25t} - 1) - 2 = 5\left(R - \frac{1}{25C}\right)e^{-25t} + \frac{1}{5C} - 2 \end{aligned}$$

Equating coefficients gives

$$0.6 = \frac{1}{5C} - 2 \Rightarrow C = 0.08 = 80 \text{ mF}$$

and

$$9.8 = 5\left(R - \frac{1}{25C}\right) = 5\left(R - \frac{1}{25(0.08)}\right) = 5(R - 0.5) \quad R = 2.46 \, \Omega$$

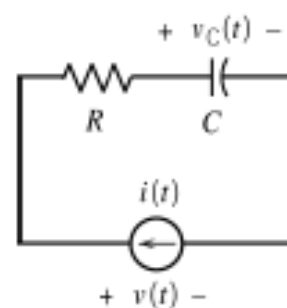**P7.2-16****Solution:**

Apply KCL at either node to get

$$\begin{aligned} 0.3 - 1.6e^{-2t} &= \frac{3 + 4e^{-2t}}{R} + C \frac{d}{dt}(3 + 4e^{-2t}) \\ &= \frac{3 + 4e^{-2t}}{R} + (-2)4Ce^{-2t} = \frac{3}{R} + \left(\frac{4}{R} - 8C\right)e^{-2t} \end{aligned}$$

Equating coefficients:

$$0.3 = \frac{3}{R} \Rightarrow R = 10 \, \Omega \quad \text{and} \quad -1.6 = \frac{4}{10} - 8C \Rightarrow C = 0.25 \text{ F}$$

P7.2-17**Solution:**At $t = 0.5$ s

$$v(0.5) = 2(0.5) + 8.6 = 9.6 \text{ V}$$

For $0.5 \leq t \leq 1.5$

$$v(t) = \frac{1}{0.25} \int_{0.5}^t 2 d\tau + 9.6 = 8\tau \Big|_{0.5}^t + 9.6 = 8(t - 0.5) + 9.6 = 8t + 5.6 \text{ V}$$

At $t = 1.5$ s

$$v(1.5) = 8(1.5) + 5.6 = 17.6 \text{ V}$$

For $t \geq 1.5$

$$v(t) = \frac{1}{0.25} \int_{1.5}^t 0 d\tau + 17.6 = 17.6$$

Checks:

At $t = 1.0$ s



$$i(t) = \frac{1}{4} \frac{d}{dt} v(t) = \frac{1}{4} \frac{d}{dt} (8t + 5.6) = \frac{1}{4} (8) = 2 \text{ A}$$

At $t = 0.5$ s

$$v(0.5) = 8(0.5) + 5.6 = 9.6 \text{ V}$$

P7.2-18

Solution:

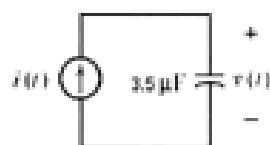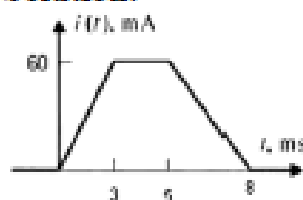

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau = v(0) + \frac{\text{"area under the curve"}}{C} = -30 + \frac{\text{"area under the curve"}}{3.5 \times 10^{-6}}$$

$$v(0.002) = -30 + \frac{\frac{1}{2}(40 \times 10^{-3})(2 \times 10^{-3})}{3.5 \times 10^{-6}} = -30 + \frac{40}{3.5} = -18.6 \text{ V}$$

(When calculating the value of $v(0.002)$, “area under the curve” indicates the area under the graph of $i(t)$ versus t corresponding to the time interval 0 to 2 ms = 0.002 s.)

$$v(0.004) = -30 + \frac{\frac{1}{2}(60 \times 10^{-3})(3 \times 10^{-3}) + (60 \times 10^{-3})(1 \times 10^{-3})}{3.5 \times 10^{-6}} = -30 + \frac{90 + 60}{3.5} = 12.9 \text{ V}$$

(When calculating the value of $v(0.004)$, “area under the curve” indicates the area under the graph of $i(t)$ versus t corresponding to the time interval 0 to 4 ms = 0.004 s.)

$$v(0.008) = -30 + \frac{\frac{1}{2}(60 \times 10^{-3})(3 \times 10^{-3}) + (60 \times 10^{-3})(2 \times 10^{-3}) + \frac{1}{2}(60 \times 10^{-3})(3 \times 10^{-3})}{3.5 \times 10^{-6}} = 55.7 \text{ V}$$

(When calculating the value of $v(0.008)$, “area under the curve” indicates the area under the graph of $i(t)$ versus t corresponding to the time interval 0 to 8 ms = 0.008 s.)

Section 7-3: Energy Storage in a Capacitor

P 7.3-1

Solution:

Given
$$i(t) = \begin{cases} 0 & t < 1 \\ 0.6(t-1) & 1 < t < 3 \\ 1.2 & t > 3 \end{cases}$$

The capacitor voltage is given by

$$v(t) = \frac{1}{0.8} \int_0^t i(\tau) d\tau + v(0) = 1.25 \int_0^t i(\tau) d\tau + v(0)$$

For $t < 1$
$$v(t) = 1.25 \int_0^t 0 d\tau + 0 = 0$$

In particular, $v(1) = 0$. For $1 < t < 3$

$$\begin{aligned} v(t) &= 1.25 \int_1^t 0.6(\tau-1) d\tau + 0 \\ &= 1.25 (0.3\tau^2 - 0.6\tau) \Big|_1^t \\ &= 1.25 (0.3t^2 - 0.6t + 0.9) \text{ V} \\ &= 0.375(t^2 - 2t + 3) \text{ V} \end{aligned}$$

In particular, $v(3) = 2.25 \text{ V}$. For $3 < t$

$$\begin{aligned} v(t) &= 1.25 \int_3^t 1.2 d\tau + 2.25 \\ &= 1.6\tau \Big|_3^t + 2.25 \\ &= (1.5t - 2.25) \text{ V} \\ &= 1.5(t - 1.5) \text{ V} \end{aligned}$$

Now the power and energy are calculated as

$$p(t) = v(t)i(t) = \begin{cases} 0 & t < 1 \\ 0.225(t-1)(t^2 - 2t + 3) & 1 < t < 3 \\ 1.8(t-1.5) & 3 < t \end{cases}$$

and


$$W(t) = \int_0^t p(\tau) d\tau = \begin{cases} 0 & t < 1 \\ 0.06(t-2)(t^3 - 2t^2 + 6t) + 5 & 1 < t < 3 \\ 0.9(t^2 - 3t) & 3 < t \end{cases}$$

P 7.3-2**Solution:**

$$i_c = C \frac{dv}{dt} = (15 \times 10^{-6})(-10)(-2000)e^{-2000t} = \underline{0.3e^{-2000t} \text{ A}} \Rightarrow \begin{cases} i_c(0) = 0.3 \text{ A} \\ i_c(15\text{ms}) = 2.8 \times 10^{-14} \text{ A} \end{cases}$$

$$W(t) = \frac{1}{2} C v^2(t) \quad \text{and} \quad v(0) = 10 - 10e^0 = 0 \Rightarrow \underline{W(0) = 0}$$

$$v(15 \times 10^{-3}) = 10 - 10e^{-30} = 10 - 9.36 \times 10^{-13} \cong 10 \Rightarrow \underline{W(10) = 7.5 \times 10^{-4} \text{ J}}$$

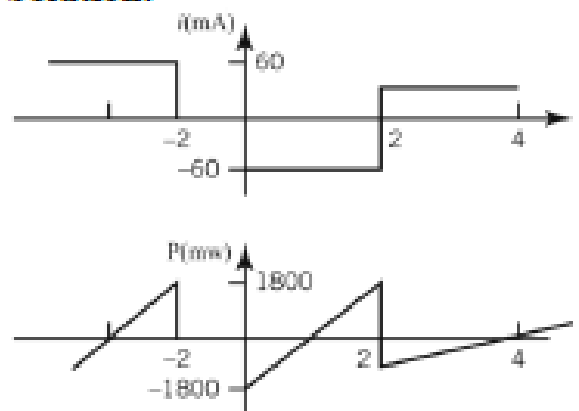P 7.3-3**Solution:**

$$i(t) = C \frac{dv_c}{dt} \text{ so read off slope of } v_c(t) \text{ to get } i(t)$$

$$p(t) = v_c(t) i(t) \text{ so multiply } v_c(t) \text{ \& } i(t) \text{ curves to get } p(t)$$

P 7.3-4**Solution:**

$$v_c(t) = v_c(0) + \frac{1}{4} \int_0^t i d\tau = v_c(0) + \frac{1}{4} \int_0^t 60 \cos\left(10\tau + \frac{\pi}{6}\right) d\tau$$

$$= \left[v_c(0) - \frac{3}{2} \sin \frac{\pi}{6} \right] + \frac{3}{2} \sin\left(10t + \frac{\pi}{6}\right)$$

$$\text{Now since } v_c(t)_{ave} = 0 \Rightarrow v_c(0) - \frac{3}{2} \sin \frac{\pi}{6} = 0$$

$$\Rightarrow v_c(t) = \frac{3}{2} \sin\left(10t + \frac{\pi}{6}\right) \text{ V}$$

$$\therefore W_{\max} = \frac{1}{2} C v_{c_{\max}}^2 = \frac{(4 \times 10^{-6})(1.5)^2}{2} = 4.5 \mu\text{J}$$

First non-negative t for max energy occurs when :

$$10t + \frac{\pi}{6} = \frac{\pi}{2} \Rightarrow \underline{t = \frac{\pi}{30} = 0.1047 \text{ s}}$$

P 7.3-5**Solution:**

$$\text{Max. charge on capacitor} = Cv = (15 \times 10^{-6})(9) = 135 \mu\text{C}$$

$$\Delta t = \frac{\Delta q}{i} = \frac{135 \times 10^{-6}}{15 \times 10^{-6}} = \underline{9 \text{ sec}} \text{ to charge}$$

$$\text{stored energy} = W = \frac{1}{2} C v^2 = \frac{1}{2} (15 \times 10^{-6})(9)^2 = \underline{607.5 \mu\text{J}}$$

P 7.3-6**Solution:**

$$\text{We have } v(0^+) = v(0^-) = 3 \text{ V}$$

$$v_c(t) = \frac{1}{C} \int_0^t i(t) dt + v_c(0) = 5 \int_0^t 3 e^{5t} dt + 3 = 3(e^{5t} - 1) + 3 = 3e^{5t} \text{ V}, \quad 0 < t < 1$$

$$\text{a) } v(t) = v_R(t) + v_c(t) = 5i(t) + v_c(t) = 15e^{5t} + 3e^{5t} = \underline{18e^{5t} \text{ V}}, \quad 0 < t < 1$$

$$\text{b) } W(t) = \frac{1}{2} C v_c^2(t) = \frac{1}{2} \times 0.2 (3e^{5t})^2 = 0.9e^{10t} \text{ J} \Rightarrow \begin{cases} W(t)|_{t=0.2s} = \underline{6.65 \text{ J}} \\ W(t)|_{t=0.8s} = \underline{2.68 \text{ kJ}} \end{cases}$$

P7.3-7**Solution:**

The capacitor acts like an open circuit when this circuit is at steady state.

(a) When the switch is closed and the circuit is at steady state, $v(t) = 6 \text{ V}$. The energy stored by the capacitor is $W = \frac{1}{2} (2.2 \times 10^{-6})(6^2) = 39.6 \mu\text{J}$.

(b) When the switch is closed and the circuit is at steady state, $v(t) = 12 \text{ V}$. The energy stored by the capacitor is $W = \frac{1}{2} (2.2 \times 10^{-6})(12^2) = 158.4 \mu\text{J}$.

Section 7-4: Series and Parallel Capacitors

P 7.4-1

Solution:

$$3\mu\text{F} \parallel 6\mu\text{F} = 9\mu\text{F}$$

$$9\mu\text{F} \text{ in series with } 6\mu\text{F} = \frac{9\mu\text{F} \cdot 6\mu\text{F}}{9\mu\text{F} + 6\mu\text{F}} = 3.6\mu\text{F}$$

$$i(t) = 3.6\mu\text{F} \frac{d}{dt}(9 \cos 100t) = (3.6 \times 10^{-6})(9)(100)(-\sin 100t) \text{ A} = \underline{-3.24 \sin 100t \text{ mA}}$$

P 7.4-2

Solution:

$$4\mu\text{F} \text{ in series with } 4\mu\text{F} = \frac{4\mu\text{F} \times 4\mu\text{F}}{4\mu\text{F} + 4\mu\text{F}} = 2\mu\text{F}$$

$$2\mu\text{F} \parallel 2\mu\text{F} = 4\mu\text{F}$$

$$4\mu\text{F} \text{ in series with } 4\mu\text{F} = 2\mu\text{F}$$

$$i(t) = (2 \times 10^{-6}) \frac{d}{dt}(5 + 3e^{-250t}) = (2 \times 10^{-6})(0 + 3(-250)e^{-250t}) \text{ A} = \underline{-1.5e^{-250t} \text{ mA}}$$

P 7.4-3

Solution:

$$C \text{ in series with } C = \frac{C \cdot C}{C + C} = \frac{C}{2}$$

$$C \parallel C \parallel \frac{C}{2} = \frac{5}{2}C$$

$$C \text{ in series with } \frac{5}{2}C = \frac{C \cdot \frac{5}{2}C}{C + \frac{5}{2}C} = \frac{5}{7}C$$

$$(25 \times 10^{-3}) \cos 250t = \left(\frac{5}{7}C \right) \frac{d}{dt}(14 \sin 250t) = \left(\frac{5}{7}C \right)(14)(250) \cos 250t$$


$$\text{so } 25 \times 10^{-3} = 2500C \Rightarrow C = 10 \times 10^{-6} = 10\mu\text{F}$$

P7.4-4**Solution:**

The 16 F capacitor is in series with a parallel combination of 4 F and 12 F capacitors. The capacitance of the equivalent capacitor is

$$\frac{16(4+12)}{16+(4+12)} = 8 \text{ F}$$

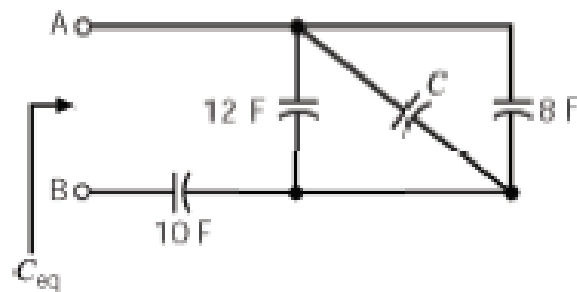The 30 F capacitor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then

$$8 = C_{\text{eq}} = \frac{10(12 + C + 8)}{10 + (12 + C + 8)} \Rightarrow C = 20 \text{ F}$$


(Checked using LNAP 6/26/04)

P 7.4-5**Solution:**

$$C_{\text{eq}} = \frac{1}{\frac{1}{70} + \frac{1}{25+20} + \frac{1}{40} + \frac{1}{50+70}} = 14.3 \text{ F}$$

P 7.4-6

Solution: First

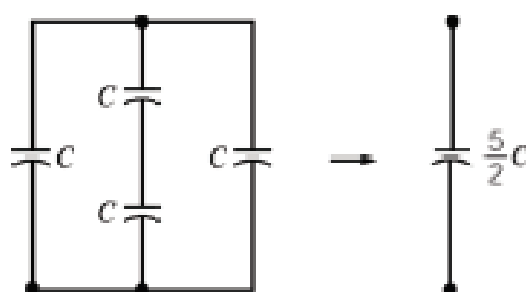

Then

$$50 = C_{\text{eq}} = \frac{1}{\frac{1}{C} + \frac{2}{5C} + \frac{2}{5C}} \Rightarrow C = 90 \text{ mF}$$

(Checked using LNAP 6/26/04)

P 7.4-7

Solution:


- (a) The energy stored in the 60 mF capacitor is $w_1 = \frac{1}{2}(0.060)3.6^2 = 0.3888 \text{ J}$ and the energy stored in the 20 mF capacitor is $w_2 = \frac{1}{2}(0.020)3.6^2 = 0.1296 \text{ J}$.
- (b) One second after the switch opens, the voltage across the capacitors is $3.6e^{-2.5} = 0.2955 \text{ V}$. Then $w_1 = 2.620 \text{ mJ}$ and $w_2 = 0.873 \text{ mJ}$.

Next $C_{\text{eq}} = 0.06 + 0.02 = 80 \text{ mF}$.

- (c) $w_{\text{eq}} = \frac{1}{2}(0.08)3.6^2 = 0.5184 \text{ J} = w_1 + w_2$
- (d) $w_{\text{eq}} = \frac{1}{2}(0.08)(0.2955)^2 = 3.493 \text{ mJ} = w_1 + w_2$

P 7.4-8

Solution:

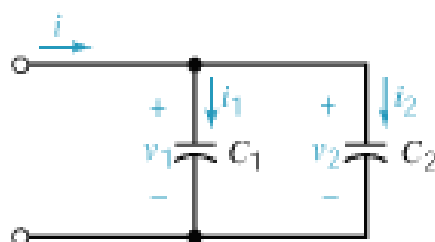

$$v_1 = v_2 \Rightarrow \frac{dv_1}{dt} = \frac{dv_2}{dt} \Rightarrow \frac{i_1}{C_1} = \frac{i_2}{C_2} \Rightarrow \underline{i_1 = \frac{C_1}{C_2} i_2}$$

$$\text{KCL: } i = i_1 + i_2 = \left(\frac{C_1}{C_2} + 1 \right) i_2 \Rightarrow \underline{i_2 = \frac{C_2}{C_1 + C_2} i}$$

Section 7-5: Inductors

P 7.5-1

Solution:

Find max. voltage across coil: $v(t) = L \frac{di}{dt} = 250[150(400) \cos 400t] \text{ V}$

$\therefore v_{\max} = 15 \times 10^6 \text{ V}$ thus have a field of $\frac{15 \times 10^6}{2} \text{ V/m} = 7.5 \times 10^6 \text{ V/m}$

which exceeds dielectric strength in air of $4 \times 10^6 \text{ V/m}$

\therefore We get a discharge as the air is ionized.

P 7.5-2

Solution:

$$v = L \frac{di}{dt} + R i = (0.2) (4e^{-t} - 4te^{-t}) + 20(4te^{-t}) = \underline{0.8e^{-t} + 79.2te^{-t} \text{ V}}$$

P 7.5-3

Solution:

$$\begin{aligned} v(t) &= (300 \times 10^{-3}) \frac{d}{dt} (150 \times 10^{-3}) \sin(500t - 30^\circ) = (0.3)(0.15)(500) \cos(500t - 30^\circ) \\ &= 22.5 \cos(500t - 30^\circ) \end{aligned}$$

P 7.5-4

Solution:

$$i_L(t) = \frac{1}{5 \times 10^{-3}} \int_0^t v_s(\tau) d\tau - 2 \times 10^{-6}$$

for $0 < t < 1 \mu\text{s}$ $v_s(t) = 4 \text{ mV}$

$$i_L(t) = \frac{1}{5 \times 10^{-3}} \int_0^t 4 \times 10^{-3} d\tau - 2 \times 10^{-6} = \left(\frac{4 \times 10^{-3}}{5 \times 10^{-3}} \right) t - 2 \times 10^{-6} = 0.8t - 2 \times 10^{-6} \text{ A}$$

$$i_L(1\mu\text{s}) = \left(\frac{4 \times 10^{-3}}{5 \times 10^{-3}} (1 \times 10^{-6}) \right) - 2 \times 10^{-6} = -\frac{6}{5} \times 10^{-6} \text{ A} = -1.2 \text{ A}$$

for $1\mu\text{s} < t < 3\mu\text{s}$ $v_s(t) = -1 \text{ mV}$

$$i_L(t) = \frac{1}{5 \times 10^{-3}} \int_{1\mu\text{s}}^t (-1 \times 10^{-3}) d\tau - \frac{6}{5} \times 10^{-6} = -\frac{1 \times 10^{-3}}{5 \times 10^{-3}} (t - 1 \times 10^{-6}) - \frac{6}{5} \times 10^{-6} = (-0.2t - 10^{-6}) \text{ A}$$

$$i_L(3\mu\text{s}) = \left(-\frac{1 \times 10^{-3}}{5 \times 10^{-3}} + 3 \times 10^{-6} \right) - 1 \times 10^{-6} = -1.6 \mu\text{A}$$

for $3\mu\text{s} < t$ $v_s(t) = 0$ so $i_L(t)$ remains $-1.6 \mu\text{A}$

P 7.5-5**Solution:**

In general

$$v(t) = (4 \times 10^3) i_s(t) + (6 \times 10^{-3}) \frac{d}{dt} i_s(t)$$

For $0.5 \mu\text{s} < t < 1 \mu\text{s}$ $i_s(t) = (1) \left(\frac{1.5 \times 10^{-3}}{1 \times 10^{-6}} \right) t = 1.5 \times 10^3 t \Rightarrow \frac{d}{dt} i_s(t) = 1.5 \times 10^3.$

Consequently

$$v(t) = (4 \times 10^3)(1.5 \times 10^3) t + 6 \times 10^{-3}(1.5 \times 10^3) = (6 \times 10^6 t + 9) \text{ V}$$

For $1 \mu\text{s} < t < 2 \mu\text{s}$ $i_s(t) = 1.5 \text{ mA} \Rightarrow \frac{d}{dt} i_s(t) = 0.$ Consequently

$$v(t) = (4 \times 10^3)(1.5 \times 10^{-3}) + (6 \times 10^{-3}) \times 0 = 6 \text{ V}$$

For $2 \mu\text{s} < t < 3 \mu\text{s}$ $i_s(t) = 6 \times 10^{-3} - \left(\frac{0.5 \times 10^{-3}}{0.5 \times 10^{-6}} \right) t \Rightarrow \frac{d}{dt} i_s(t) = -\frac{0.5 \times 10^{-3}}{0.5 \times 10^{-6}} = -10^3.$

Consequently

$$v(t) = (4 \times 10^3)(6 \times 10^{-3} - 10^3 t) + 6 \times 10^{-3}(-10^3) = 18 - (4 \times 10^6) t$$

When $3 \mu\text{s} < t < 4 \mu\text{s}$ $i_s(t) = -0.5 \times 10^{-3}$ and $\frac{d}{dt} i_s(t) = 0.$ Consequently

$$v(t) = (4 \times 10^3)(-0.5 \times 10^{-3}) = -2 \text{ V}$$

When $4 \mu\text{s} < t < 5 \mu\text{s}$ $i_s(t) = \left(\frac{0.5 \times 10^{-3}}{0.5 \times 10^{-6}} \right) t - 4 \times 10^{-3} \Rightarrow \frac{d}{dt} i_s(t) = 1 \times 10^3$

$$v(t) = (4 \times 10^3)(10^3 t - 4 \times 10^{-3}) + (6 \times 10^{-3})(10^3) = -10 + (4 \times 10^6) t$$

When $5 \mu\text{s} < t$, then $i_s(t) = 1 \text{ mA} \Rightarrow \frac{d}{dt} i_s(t) = 0.$ Consequently

$$v(t) = (4 \times 10^3)(1 \times 10^{-3}) = 4 \text{ V}.$$

P 7.5-6**Solution:**

$$(a) \quad v(t) = L \frac{d}{dt} i(t) = \begin{cases} 0 & 0 < t < 2 \\ 0.1 & 2 < t < 6 \\ 0 & 6 < t \end{cases}$$

$$(b) \quad i(t) = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0) = 2 \int_0^t v(\tau) d\tau$$

$$\text{For } 0 < t < 2, v(t) = 0 \text{ V so } i(t) = 2 \int_0^t 0 d\tau + 0 = 0 \text{ A}$$

$$\text{For } 2 < t < 6, v(t) = 0.2 t - 0.4 \text{ V so}$$

$$i(t) = 2 \int_2^t (0.2\tau - 0.4) d\tau + 0 = (0.2\tau^2 - 0.8\tau) \Big|_2^t = 0.2t^2 - 0.8t + 0.8 \text{ A}$$

$$i(6) = 0.2(6^2) - 0.8(6) + 0.8 = 3.2 \text{ A}.$$

$$\text{For } 6 < t, v(t) = 0.8 \text{ V so}$$

$$i(t) = 2 \int_6^t 0.8 d\tau + 3.2 = (1.6t - 6.4) \text{ A}$$

P 7.5-7**Solution:**

$$i(t) = \frac{1}{150} \int_0^t 0 dt + 0.03 = 0.03 \quad \text{for } 0 < t < 1$$

$$\text{so } i(1) = 0.03$$

$$i(t) = \frac{1}{150} \int_1^t -4 d\tau + 0.03 = \frac{-4(t-1)}{150} + 0.03 \quad \text{for } 1 < t < 3$$

$$\text{so } i(3) = -0.023$$

$$i(t) = \frac{1}{150} \int_3^t 2 d\tau - 0.023 = \frac{2(t-3)}{150} - 0.023 \quad \text{for } 3 < t < 9$$

$$\text{so } i(9) = 0.057$$

$$i(t) = \frac{1}{150} \int_9^t 0 d\tau + 0.057 = 0.057 \quad \text{for } t > 9$$

P 7.5-8**Solution:**

$$i(t) = \frac{1}{2} \int_0^t v(\tau) d\tau + 1 = \begin{cases} 1 & t \leq 2 \\ \int_2^t d\tau + 1 = (t-2) + 1 = t-1 & 2 \leq t \leq 4 \\ \frac{1}{2} \int_4^t d\tau + 3 = -\frac{1}{2}t + 5 & 4 \leq t \leq 6 \\ 2 & 6 \leq t \end{cases}$$

P 7.5-9**Solution:**

$$i(t) = \frac{1}{200} \int_0^t -d\tau + 0.025 = \frac{-t}{200} + 0.025 \quad \text{for } 0 < t < 1$$


$$i(t) = \frac{1}{200} \int_1^t -2 d\tau + 0.02 = \frac{-2(t-1)}{200} + 0.02 \quad \text{for } 1 < t < 4$$

$$i(t) = \frac{1}{200} \int_4^t d\tau - 0.01 = \frac{t-4}{200} - 0.01 \quad \text{for } 4 < t < 9$$

$$i(t) = 0.015 = 15 \text{ mA} \quad t < 9$$

P 7.5-10**Solution:**
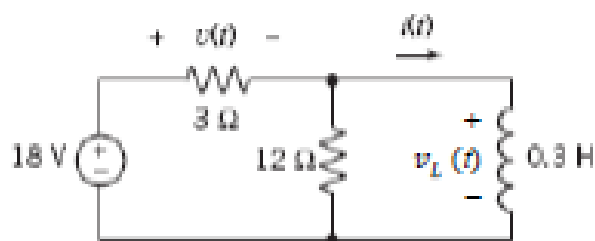
$$\begin{aligned} v_L(t) &= 0.3 \frac{d}{dt} i(t) \\ &= -9.6e^{-8t} \text{ V} \quad \text{for } t > 0 \end{aligned}$$



Use KVL to get

$$v(t) = 18 - (-9.6e^{-8t}) = 18 + 9.6e^{-8t} \text{ V} \quad \text{for } t > 0$$

P 7.5-11**Solution:**

Apply KVL to get

$$v(t) = 9i(t) + 7.5 \frac{d}{dt} i(t) = 9(3 + 2e^{-3t}) + 7.5 \frac{d}{dt} (3 + 2e^{-3t}) = 27(1 - e^{-3t}) \text{ V for } t > 0$$

P 7.5-12**Solution:**

$$i(t) = \frac{1}{L} \int_{t_0}^t v_s(\tau) d\tau + i(t_0) = \frac{1}{\frac{1}{3}} \int_0^t v_s(\tau) d\tau - 12$$

$$i(t) = 3 \int_0^t 4 d\tau - 12 = 12t - 12 \quad \text{for } 0 < t < 4 \quad \text{In particular, } i(4) = 36 \text{ A.}$$

$$i(t) = 3 \int_4^t (-2) d\tau + 36 = 60 - 6t \quad \text{for } 4 < t < 10 \quad \text{In particular, } i(10) = 0 \text{ A.}$$

$$i(t) = 3 \int_{10}^t 0 d\tau + 0 = 0 \quad \text{for } 10 < t$$

P7.5-14**Solution:**

Apply KCL at either node to get

$$i(t) = \frac{v(t)}{R} + i_L(t) = \frac{v(t)}{R} + \left[\frac{1}{L} \int_0^t v(\tau) d\tau + i(0) \right]$$

That is

$$\begin{aligned} -1.2e^{-20t} - 1.5 &= \frac{4e^{-20t}}{R} + \frac{1}{L} \int_0^t 4e^{-20\tau} d\tau - 3.5 = \frac{4e^{-20t}}{R} + \frac{4}{L(-20)}(e^{-20t} - 1) - 3.5 \\ &= \left(\frac{4}{R} - \frac{1}{5L} \right) e^{-20t} + \frac{1}{5L} - 3.5 \end{aligned}$$

Equating coefficients gives

$$-1.5 = \frac{1}{5L} - 3.5 \Rightarrow L = 0.1 \text{ H}$$

and

$$-1.2 = \frac{4}{R} - \frac{1}{5L} = \frac{4}{R} - \frac{1}{5(0.1)} = \frac{4}{R} - 2 \Rightarrow R = 5 \Omega$$

P7.5-15**Solution:**At $t = 0.2$ s

$$i(0.2) = 5(0.2) - 4.6 = -3.6 \text{ A}$$

For $0.2 \leq t \leq 0.5$

$$i(t) = \frac{1}{2.5} \int_{0.2}^t 25 d\tau - 3.6 = 10\tau \Big|_{0.2}^t - 3.6 = 10(t - 0.2) - 3.6 = 10t - 5.6 \text{ A}$$

At $t = 0.5$ s

$$i(0.5) = 10(0.5) - 5.6 = -0.6 \text{ A}$$

For $t \geq 0.5$

$$i(t) = \frac{1}{2.5} \int_{0.5}^t 0 d\tau - 0.6 = -0.6$$

Checks:At $t = 0.2$ s

$$i(0.2) = 10(0.2) - 5.6 = -3.6 \text{ A}$$

$$\text{For } 0.2 \leq t \leq 0.5 \quad v(t) = 2.5 \frac{d}{dt} i(t) = 2.5 \frac{d}{dt} (10t - 5.6) = 2.5(10) = 25 \text{ V}$$

$$-0.6 - (-3.6) = i(0.5) - i(0.2) = \frac{1}{2.5} \int_{0.2}^{0.5} 25 d\tau = 10(0.5 - 0.2) = 3 \text{ A}$$

P7.5-16**Solution:**

$$i(t) = i(0) + \frac{1}{L} \int_0^t v(\tau) d\tau = i(0) + \frac{\text{"area under the curve"}}{L} = 0.045 + \frac{\text{"area under the curve"}}{0.250}$$

$$i(0.001) = 0.045 + \frac{20(0.001)}{0.250} = 0.125 \text{ A} = 125 \text{ mA},$$

$$i(0.004) = 0.045 + \frac{20(0.002) + \frac{1}{2} 20(0.002)}{0.250} = 0.285 \text{ A} = 285 \text{ mA}$$

$$i(0.006) = 0.045 + \frac{20(0.002) + \frac{1}{2} 20(0.002) + 0}{0.250} = 0.285 \text{ A} = 285 \text{ mA}$$

P7.5-17**Solution:**

First,
$$\frac{d}{dt}i(t) = \frac{d}{dt}(0.3 \cos(2t)) = -(0.3)(2) \sin(2t) = -0.6 \sin(2t)$$

The voltage of an inductor is proportional to the derivative of the current. The constant of proportionality is the inductance. We see that $v_a(t)$ is proportional to $\frac{d}{dt}i(t)$ and the constant of proportionality is positive. Consequently, element a is the inductor. Then

$$L = \frac{v_a(t)}{\frac{d}{dt}i(t)} = \frac{-10 \sin(2t)}{-0.6 \sin(2t)} = 16.7 \text{ H}$$

Next
$$\int_{-\infty}^t i(\tau) d\tau = \int_{-\infty}^t 0.3 \cos(2\tau) d\tau = \frac{0.3 \sin(2\tau)}{2} = 0.15 \sin(2\tau)$$

The voltage of a capacitor is proportional to the integral of the current. The constant of proportionality is the reciprocal of the capacitance. We see that $v_b(t)$ is proportional to $\int_{-\infty}^t i(\tau) d\tau$ and the constant of proportionality is positive. Consequently, element b is the capacitor. Then

$$\frac{1}{C} = \frac{v_b(t)}{\int_{-\infty}^t i(\tau) d\tau} = \frac{10 \sin(2t)}{0.15 \sin(2t)} = 66.7 \Rightarrow C = \frac{1}{66.7} = 0.015 \text{ F}$$

Finally, the voltage of element c is proportional to the current and the constant of proportionality is positive. Consequently, element c is the resistor and $R = \frac{v_c(t)}{i(t)} = 33.3 \Omega$.

Section 7-6: Energy Storage in an Inductor**P 7.6-1****Solution:**

$$v(t) = 100 \times 10^{-3} \frac{d}{dt} i(t) = \begin{cases} 0 & t < 0 \\ 0.4 & 0 \leq t \leq 1 \\ 0 & t > 1 \end{cases}$$

$$p(t) = v(t)i(t) = \begin{cases} 0 & t < 0 \\ 1.6t & 0 \leq t \leq 1 \\ 0 & t > 1 \end{cases}$$

$$W(t) = \int_0^t p(\tau) d\tau = \begin{cases} 0 & t < 0 \\ 0.8t^2 & 0 < t < 1 \\ 0.8 & t > 1 \end{cases}$$

P 7.6-2**Solution:**

$$\begin{aligned}
 p(t) &= v(t) i(t) = \left[5 \frac{d}{dt}(4 \sin 2t) \right] (4 \sin 2t) \\
 &= 5 (8 \cos 2t) (4 \sin 2t) \\
 &= 80 [2 \cos 2t \sin 2t] \\
 &= 80 [\sin(2t+2t) + \sin(2t-2t)] = 80 \sin 4t \text{ W}
 \end{aligned}$$

$$w(t) = \int_0^t p(\tau) d\tau = 80 \int_0^t \sin 4\tau d\tau = -\frac{80}{4} [\cos 4\tau]_0^t = 20 (1 - \cos 4t)$$

$$i(t) = \frac{1}{25 \times 10^{-3}} \int_0^t 6 \cos 100\tau d\tau + 0 = \frac{1}{(25 \times 10^{-3})(100)} [\sin 100\tau]_0^t = 2.4 \sin 100t$$

$$\begin{aligned}
 p(t) &= v(t) i(t) = (6 \cos 100t)(2.4 \sin 100t) = 7.2 [2(\cos 100t)(\sin 100t)] \\
 &= 7.2 [\sin 200t + \sin 0] = 7.2 \sin 200t
 \end{aligned}$$

$$\begin{aligned}
 W(t) &= \int_0^t p(\tau) d\tau = 7.2 \int_0^t \sin 200\tau d\tau = -\frac{7.2}{200} [\cos 200\tau]_0^t \\
 &= 0.036[1 - \cos 200t] \text{ J} = 36 [1 - \cos 200t] \text{ mJ}
 \end{aligned}$$

P 7.6-4**Solution:**

$$v(t) = L \frac{di}{dt} = \frac{1}{2} \frac{di}{dt} \quad \text{and} \quad i(t) = \begin{cases} 0 & t < 0 \\ 2t & 0 < t < 1 \\ -2(t-2) & 1 < t < 2 \\ 0 & t > 2 \end{cases} \Rightarrow v(t) = \begin{cases} 0 & t < 0 \\ 1 & 0 < t < 1 \\ -1 & 1 < t < 2 \\ 0 & t > 2 \end{cases}$$

$$p(t) = v(t)i(t) = \begin{cases} 0 & t < 0 \\ 2t & 0 < t < 1 \\ 2(t-2) & 1 < t < 2 \\ 0 & t > 2 \end{cases}$$

$$w(t) = w(t_0) + \int_{t_0}^t p(\tau) d\tau$$

$$i(t) = 0 \text{ for } t < 0 \Rightarrow p(t) = 0 \text{ for } t < 0 \Rightarrow w(t_0) = 0$$

$$0 < t < 1: w(t) = \int_0^t 2\tau d\tau = t^2$$

$$1 < t < 2: w(t) = w(1) + \int_1^t 2(\tau-2) d\tau = t^2 - 4t + 4$$

$$\underline{t > 2: w(t) = w(2) = 0}$$

Section 7-7: Series and Parallel Inductors

P 7.7-1

Solution:

$$12 \text{ H} \parallel 6 \text{ H} = \frac{12 \times 6}{12 + 6} = 4 \text{ H} \quad \text{and} \quad 4 \text{ H} + 4 \text{ H} = 8 \text{ H}$$

$$i(t) = \frac{1}{8} \int_0^t 6 \cos 100\tau \, d\tau = \frac{6}{8 \times 100} [\sin 100\tau]_0^t = 0.0075 \sin 100t \text{ A} = 7.5 \sin 100t \text{ mA}$$

P 7.7-2

Solution:

$$6 \text{ mH} + 6 \text{ mH} = 12 \text{ mH} \quad , \quad 12 \text{ mH} \parallel 12 \text{ mH} = \frac{(12 \times 10^{-3}) \times (12 \times 10^{-3})}{12 \times 10^{-3} + 12 \times 10^{-3}} = 6 \text{ mH}$$

$$\text{and } 6 \text{ mH} + 6 \text{ mH} = 12 \text{ mH}$$

$$v(t) = (12 \times 10^{-3}) \frac{d}{dt} (5 + 3e^{-250t}) = (12 \times 10^{-3}) (0 + 3(-250)e^{-250t}) = -9e^{-250t} \text{ V}$$

P 7.7-3

Solution:

$$L \parallel L = \frac{L \cdot L}{L + L} = \frac{L}{2} \quad \text{and} \quad L + L + \frac{L}{2} = \frac{5}{2} L$$

$$25 \cos 250t = \left(\frac{5}{2} L \right) \frac{d}{dt} ((14 \times 10^{-3}) \sin 250t) = \left(\frac{5}{2} L \right) (14 \times 10^{-3}) (250) \cos 250t$$

$$\text{so } L = \frac{25}{\frac{5}{2} (14 \times 10^{-3}) (250)} = 2.86 \text{ H}$$

P 7.7-4

Solution:

$$\text{The equivalent inductance is: } \frac{\left(\frac{L \times 2L}{L + 2L} + L \right) \times L}{\left(\frac{L \times 2L}{L + 2L} + L \right) + L} + 2L = \frac{21}{8} L$$

$$\text{Then } i(t) = \frac{1}{\frac{21}{8} L} \int_{-\infty}^t 4 \cos(3\tau) \, d\tau = \frac{8}{21 \times 4} \times \frac{4}{3} \sin(3t) = 127 \sin(3t) \text{ mA}$$


(Checked using LNAP 6/26/04)

P 7.7-5**Solution:**

The 30 H inductor is in series with a parallel combination of 30 H and 70 H inductors. The inductance of the equivalent inductor is

$$30 + \frac{70 \times 30}{70 + 30} = 51 \text{ H}$$

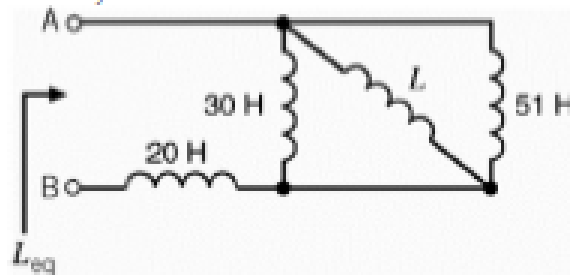The 40 H inductor is in parallel with a short circuit, which is equivalent to a short circuit. After making these simplifications, we have



Then


$$28 = L_{eq} = 20 + \frac{1}{\frac{1}{30} + \frac{1}{L} + \frac{1}{51}} \Rightarrow \frac{1}{30} + \frac{1}{L} + \frac{1}{51} = \frac{1}{8} \Rightarrow L = 13.88 \text{ H}$$

P 7.7-6**Solution:**

$$L_{eq} = 70 + \frac{25 \times 20}{25 + 20} + 40 + \frac{50 \times 70}{50 + 70} = 70 + 11.1 + 40 + 29.2 = 150.3 \text{ H}$$

P 7.7-7**Solution:**

First

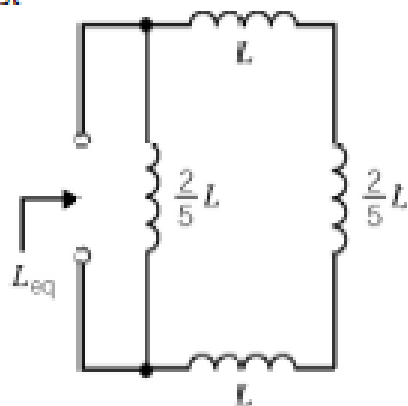

Then

$$12 = L_{eq} = \frac{\left(\frac{2}{5}L\right) \times \left(\frac{2}{5}L + 2L\right)}{\left(\frac{2}{5}L\right) + \left(\frac{2}{5}L + 2L\right)} = \frac{12}{35}L \Rightarrow L = 35 \text{ mH}$$

(Checked using LNAP 6/26/04)

P 7.7-8**Solution:**

(a) The energy stored by the 0.5 H inductor is $w_1 = \frac{1}{2}(0.5)(0.8^2) = 0.16 \text{ J}$ and the energy stored by the 2 H inductor is $w_2 = \frac{1}{2}(2)(0.8^2) = 0.64 \text{ J}$.

(b) 200 ms after the switch opens the current in the inductors is $0.8e^{-0.4} = 0.536 \text{ A}$. Then $w_1 = \frac{1}{2}(0.5)(0.536^2) = 71.8 \text{ mJ}$ and $w_2 = \frac{1}{2}(2)(0.535^2) = 287.3 \text{ mJ}$.

Next, $L_{\text{eq}} = 2 + 0.5 = 2.5 \text{ H}$.

(c) $w_{\text{eq}} = \frac{1}{2}(2.5)(0.8^2) = 0.8 \text{ J} = w_1 + w_2$

(d) $w_{\text{eq}} = \frac{1}{2}(2.5)(0.536^2) = 359.12 \text{ mJ} = w_1 + w_2$

P 7.7-9**Solution:**

$$i_1 = \frac{1}{L_1} \int_{t_0}^t v \, dt + i_1(t_0), \quad i_2 = \frac{1}{L_2} \int_{t_0}^t v \, dt + i_2(t_0) \quad \text{but } i_1(t_0) = 0 \text{ and } i_2(t_0) = 0$$

$$i = i_1 + i_2 = \frac{1}{L_1} \int_{t_0}^t v \, dt + \int_{t_0}^t v \, dt = \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int_{t_0}^t v \, dt = \frac{1}{L_p} \int_{t_0}^t v \, dt$$

$$\therefore \frac{i_1}{i} = \frac{\frac{1}{L_1} \int_{t_0}^t v \, dt}{\frac{1}{L_p} \int_{t_0}^t v \, dt} = \frac{\frac{1}{L_1}}{\frac{1}{L_1} + \frac{1}{L_2}} = \frac{L_2}{L_1 + L_2}$$

P7.7-10**Solution:**


$$(a) \ C_{\text{eq}} = \frac{30(10)}{30+10} + 30 = 37.5 \ \mu\text{F} \quad (b) \ L_{\text{eq}} = \frac{(60+40)(30)}{(60+40)+30} = 23.08 \text{ mH}$$

$$(c) \ R_{\text{eq}} = \frac{(10+8)(10)}{(10+8)+10} = 6.4 \text{ k}\Omega$$

P7.7-11**Solution:**

$$(a) C_{eq} = \frac{(10+20)(15)}{(10+20)+15} = 10 \mu F \quad (b) L_{eq} = \frac{(30)(6)}{30+6} + 10 = 15 \text{ mH}$$



$$(c) R_{eq} = \frac{(30)(40)}{30+40} + 16 = 33.14 \text{ k}\Omega$$

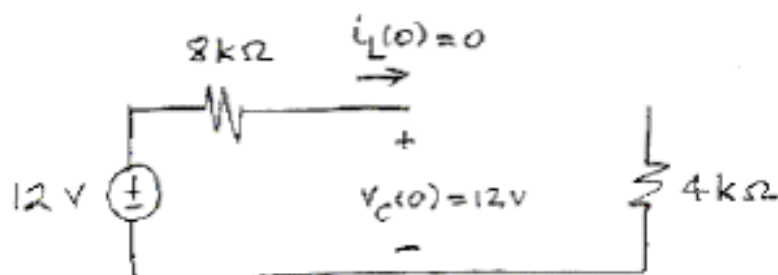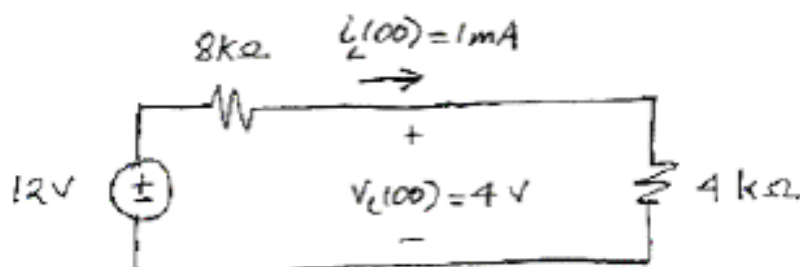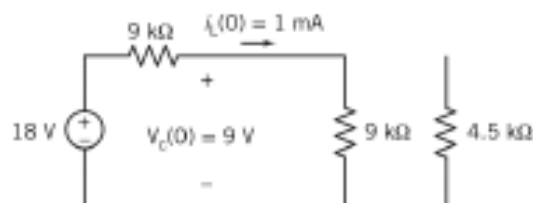Section 7-8: Initial Conditions of Switched Circuits**P 7.8-1****Solution:**

Then

$$i_L(0^+) = i_L(0^-) = 0 \quad \text{and} \quad v_C(0^+) = v_C(0^-) = 12\text{V}$$


Next

**P 7.8-2****Solution:**

Then


$$i_L(0^+) = i_L(0^-) = 1\text{mA} \quad \text{and} \quad v_C(0^+) = v_C(0^-) = 9\text{V}$$

Next

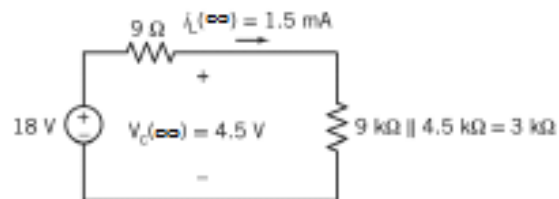

P 7.8-3


Solution:

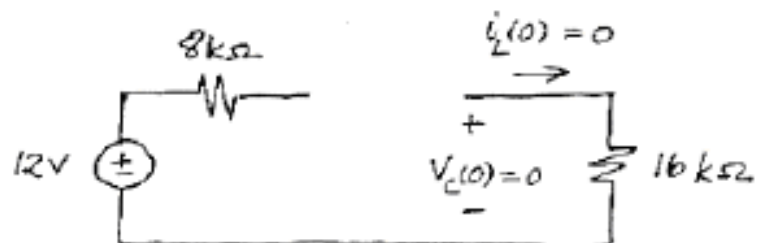

Then

$$i_L(0^+) = i_L(0^-) = 0 \text{ and } v_C(0^+) = v_C(0^-) = 0\text{ V}$$


Next

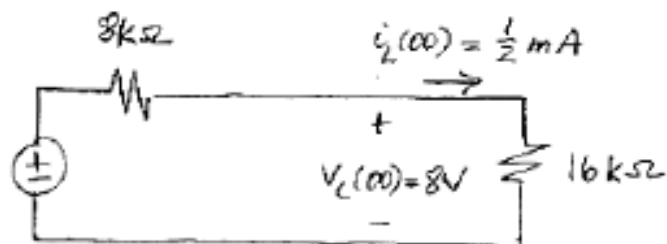

P7.8-4

Solution:

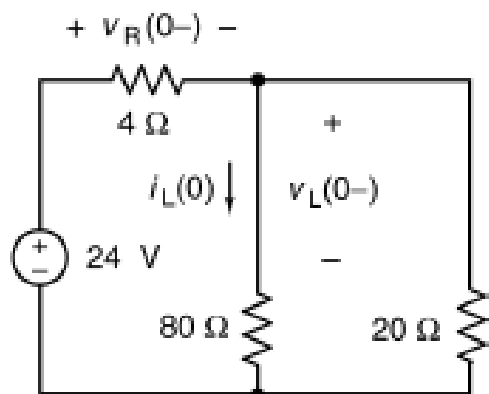The circuit is at steady state immediately before the switch opens. We have



The inductor acts like a short circuit so $v_L(0-) = 0$.


Noticing that the $80\ \Omega$ and $20\ \Omega$ are connected in parallel and using voltage division:

$$v_R(0-) = \frac{4}{4 + (80 \parallel 20)} (24) = \frac{4}{4 + 16} (24) = 4.8\text{ V}$$

Using current division:

$$i_L(0) = \left(\frac{20}{80 + 20} \right) \frac{24}{4 + (80 \parallel 20)} = \frac{1}{5} \left(\frac{24}{4 + 16} \right) = 0.24\text{ A}$$

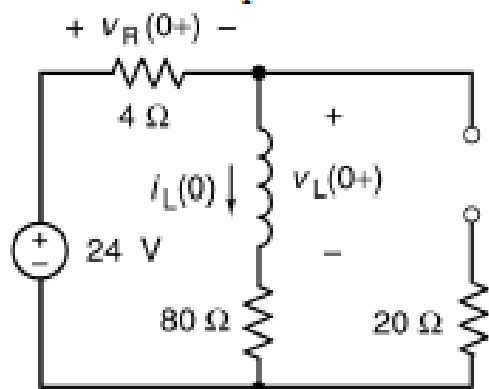The inductor current does not change instantaneously so $i_L(0+) = i_L(0-) = i_L(0)$. Immediately after the switch opens we have:



$$v_R(0+) = 4i_L(0) = 4(0.24) = 0.96\text{ V}$$

Using KVL:

$$v_R(0+) + v_L(0+) + 80i_L(0) - 24 = 0$$

$$0.96 + v_L(0+) + 80(0.24) - 24 = 0$$

$$v_L(0+) = 3.84\text{ V}$$

$$\begin{aligned} v(t) &= 75 - 82e^{-7t} = R(5 + 2e^{-7t}) + L \frac{d}{dt}(5 + 2e^{-7t}) \\ &= R(5 + 2e^{-7t}) + L((-7)2e^{-7t}) = 5R + (2R - 14L)e^{-7t} \end{aligned}$$

Equation coefficients gives

$$75 = 5R \Rightarrow R = 15\ \Omega \text{ and}$$


and

$$-82 = 2R - 14L = 30 - 14L \Rightarrow L = \frac{82 + 30}{14} = 8\text{ H}$$

P7.8-5

Solution:

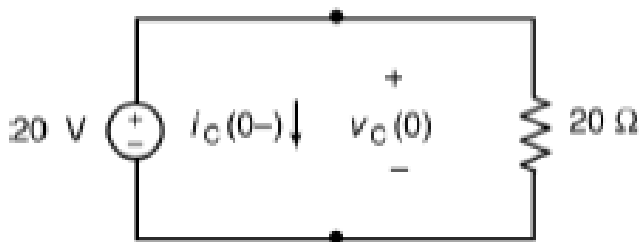The circuit is at steady state immediately before the switch opens. We have




The capacitor acts like an open circuit so

$$i_C(0-) = 0.$$

The capacitor voltage is equal to the voltage source voltage:

$$v_C(0) = 20 \text{ V}$$

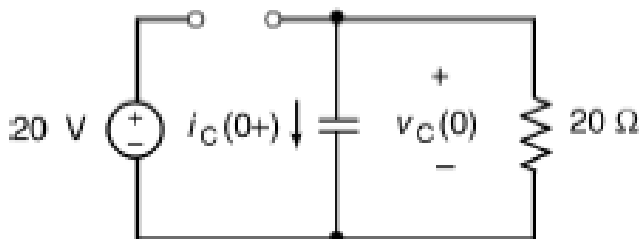The capacitor does not change instantaneously so $v_C(0+) = v_C(0-) = v_C(0)$. Immediately after the switch opens we have:



Applying KCL at the top node of the capacitor, we see that:

$$i_C(0+) + \frac{v_C(0)}{20} = 0$$


$$i_C(0+) = -\frac{v_C(0)}{20} = -1 \text{ A}$$

P7-8.6

Solution:

The capacitor voltage and inductor current don't change instantaneously and so are the keys to solving this problem.

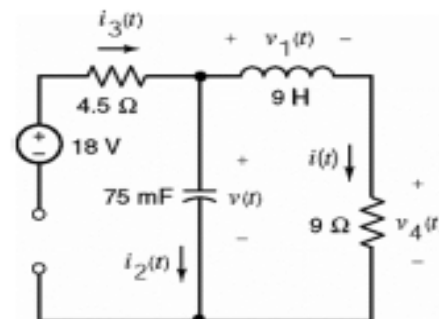Label the capacitor voltage and inductor current as shown.



Before $t = 0$, with the switch closed and the circuit at steady state, the inductor acts like a short circuit and the capacitor acts like an open circuit.


$$i_3(0-) = i(0-) = \frac{18}{13.5} = 1.33 \text{ A}$$

$$v_4(0-) = v(0-) = 9i(0-) = 12 \text{ V}$$

$$v_1(0-) = 0 \text{ V and } i_2(0-) = 0 \text{ A}$$

The capacitor voltage and inductor current don't change instantaneously so
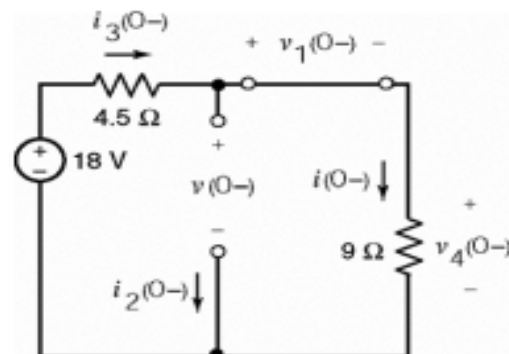
$$v(0+) = v(0-) = 12 \text{ V and } i(0+) = i(0-) = 1.33 \text{ A}$$



After the switch opens the circuit looks like this:

From KCL:

$$i_3(t) = 0 \text{ A and } i_2(t) = -i(t)$$

From KVL:

$$v_1(t) + 9i(t) = v(t)$$

From Ohm's Law:


$$v_4(t) = 9i(t)$$

At $t = 0+$

$$i_3(0+) = 0 \text{ A and } i_2(0+) = -i(0+) = -1.33 \text{ A}$$

$$v_1(0+) = v(0+) - 9i(0+) = 12 - 9(1.333) = 0 \text{ V}$$

$$v_4(0+) = 9i(0+) = 12 \text{ V}$$

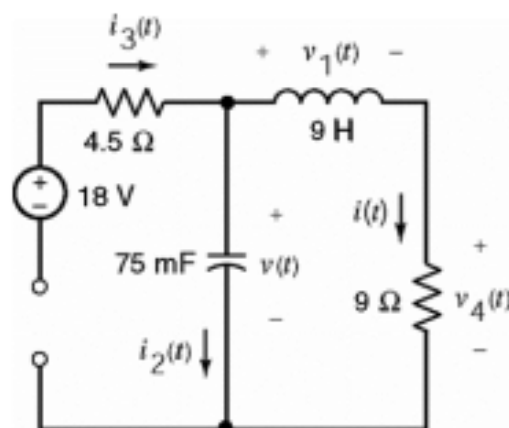


P 7.8-7

Solution:

The capacitor voltage and inductor current don't change instantaneously and so are the keys to solving this problem.

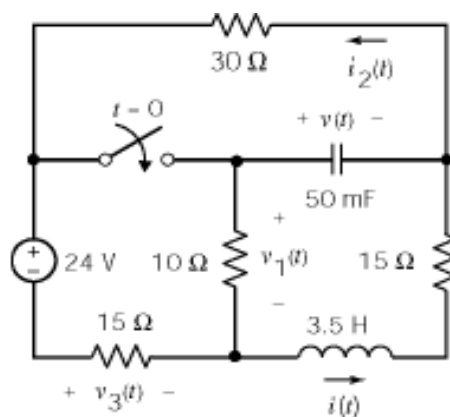Label the capacitor voltage and inductor current as shown.



Before $t = 0$, with the switch open and the circuit at steady state, the inductor acts like a short circuit and the capacitor acts like an open circuit.

$$i_2(0-) = i(0-) = \frac{24}{60} = -0.4 \text{ A}$$


$$v_1(0-) = 0 \text{ V}$$

$$v(0-) - 15i(0-) = v_1(0-) \Rightarrow v(0-) = -6 \text{ V}$$

$$v_3(0-) = 15i(0-) = -6 \text{ V}$$

The capacitor voltage and inductor current don't change instantaneously so
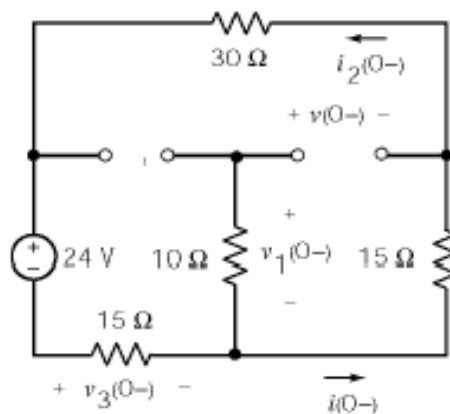
$$v(0+) = v(0-) = -6 \text{ V and } i(0+) = i(0-) = -0.4 \text{ A}$$



After the switch closes the circuit looks like this:

From Ohm's Law:

$$i_2(t) = -\frac{v(t)}{30}$$

From KVL:

$$v_1(t) = v_3(t) + 24$$


From KCL:

$$\frac{v_1(t)}{10} + \frac{v_3(t)}{15} = i(t)$$

At $t = 0+$

$$i_2(0+) = -\frac{v(0+)}{30} = 0.2 \text{ A}$$
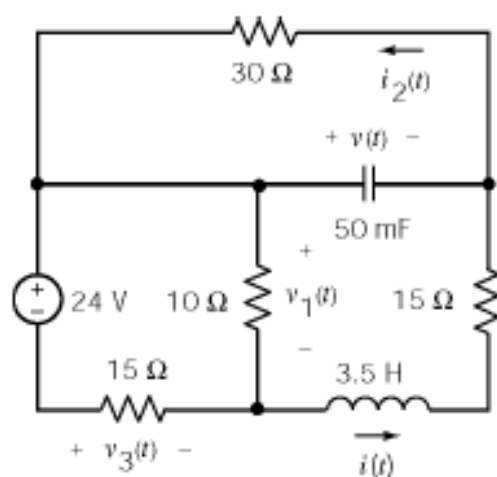
$$\left. \begin{array}{l} v_1(0+) = v_3(0+) + 24 \\ \frac{v_1(0+)}{10} + \frac{v_3(0+)}{15} = i(0+) \end{array} \right\} \Rightarrow v_1(0+) = 7.2 \text{ V and } v_3(0+) = -16.8 \text{ V}$$



P7.8-8

Solution:

Because

- This circuit has reached steady state before the switch opens at time $t = 0$.
- The only source is a constant voltage source.

At $t=0^-$, the capacitor acts like an open circuit and the inductor acts like a short circuit. From the circuit

$$i_1(0^-) = \frac{37.5}{6 + (30 \parallel 120)} = \frac{37.5}{6 + 24} = 1.25 \text{ A},$$

$$i_L(0^-) = \left(\frac{120}{30 + 120} \right) i_1(0^-) = 1 \text{ A},$$

$$v_C(0^-) = 30i_L(0^-) = 30 \text{ V}$$

and

$$v_R(0^-) = 6i_1(0^-) = 7.5 \text{ V}$$

The capacitor voltage and inductor current don't change instantaneously so

$$v_C(0^+) = v_C(0^-) = 30 \text{ V} \text{ and}$$

$$i_L(0^+) = i_L(0^-) = 1 \text{ A}$$



Apply KCL at the top node to see that

$$i_1(0^+) = i_L(0^+) = 1 \text{ A}$$

From Ohm's law

$$v_R(0^+) = 6i_1(0^+) = 6 \text{ V}$$

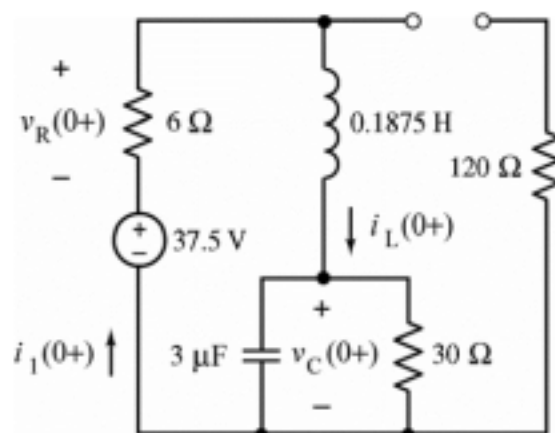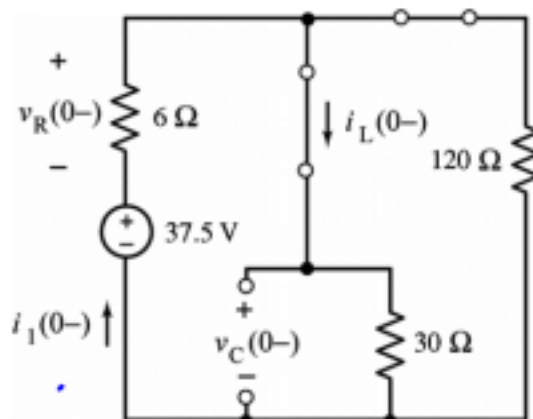(Notice that the resistor voltage did change instantaneously.)




P7.8-9

Solution:

Because

- This circuit has reached steady state before the switch closes at time $t = 0$.
- The only source is a constant voltage source.

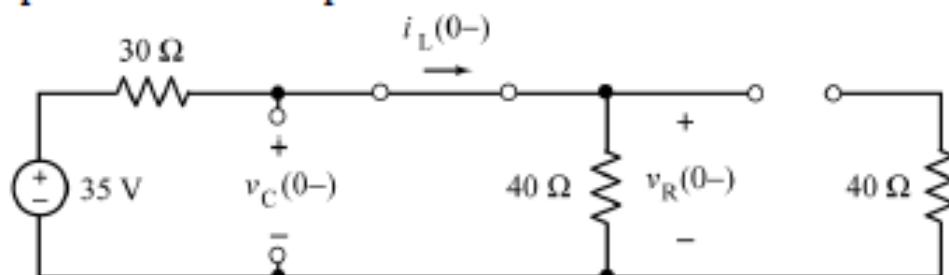At $t=0^-$, the capacitor acts like an open circuit and the inductor acts like a short circuit.




From the circuit $i_L(0^-) = \frac{35}{30+40} = 0.5 \text{ A}$, $v_R(0^-) = 40i_L(0^-) = 20 \text{ V}$,

And $v_C(0^-) = v_R(0^-) = 20 \text{ V}$

The capacitor voltage and inductor current don't change instantaneously so
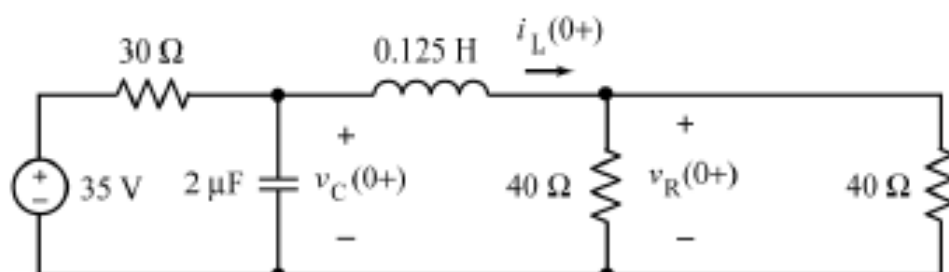
$$v_C(0^+) = v_C(0^-) = 20 \text{ V} \text{ and } i_L(0^+) = i_L(0^-) = 0.5 \text{ A}$$



$$v_R(0^+) = 40 \left(\frac{40}{40+40} \right) i_L(0^+) = 10 \text{ V}$$

(Notice that the resistor voltage did change instantaneously.)

P 7.8-10

Solution: Apply KVL to the left mesh to obtain

$$v_s(t) = 100(i_1(t) + i_2(t)) + 0.005 \frac{d}{dt} i_1(t)$$

Apply KVL to the outside loop to obtain

$$v_s(t) = 100(i_1(t) + i_2(t)) + 250i_2(t) + 0.002 \frac{d}{dt} i_2(t)$$


Immediately after $t = 0$, at $t = 0+$, we have

$$\frac{d}{dt} i_1(0+) = \frac{8 - 100(i_1(0+) + i_2(0+))}{0.005}$$

and

$$\frac{d}{dt} i_2(0+) = \frac{8 - (100i_1(0+) + 250i_2(0+))}{0.002}$$

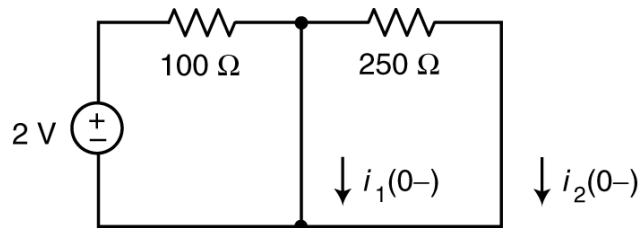where $8 = v_s(0+)$. The initial inductor currents can be calculated from:



Inductor currents must be continuous so

$$i_1(0+) = i_1(0-) = \frac{2}{100} = 0.02 \text{ A} \quad \text{and} \quad i_2(0+) = i_2(0-) = 0$$


Substituting these values into the equations for $\frac{d}{dt} i_1(0+)$ and $\frac{d}{dt} i_2(0+)$ gives

$$\frac{d}{dt} i_1(0+) = \frac{8 - 100(0.02 + 0)}{0.005} = 1200 \frac{\text{A}}{\text{s}} \quad \text{and} \quad \frac{d}{dt} i_2(0+) = \frac{8 - (100(0.02) + 0)}{0.002} = 3000 \frac{\text{A}}{\text{s}}$$

Section 7-9: Operational amplifier Circuits and Linear Differential Equations


P 7.9-1

Solution:

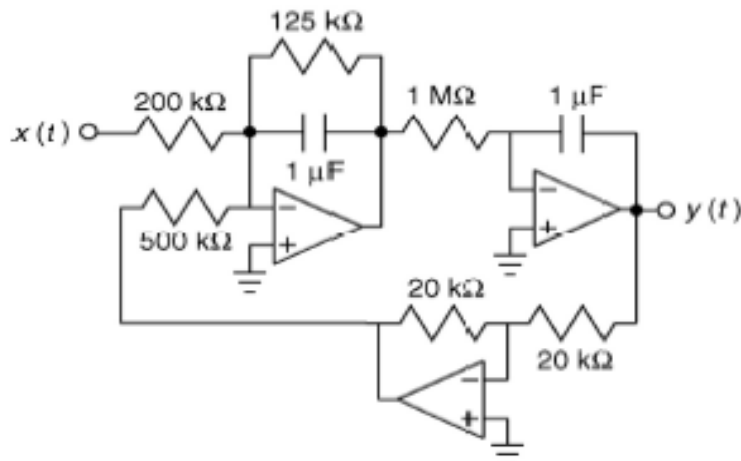


P 7.9-2

Solution:

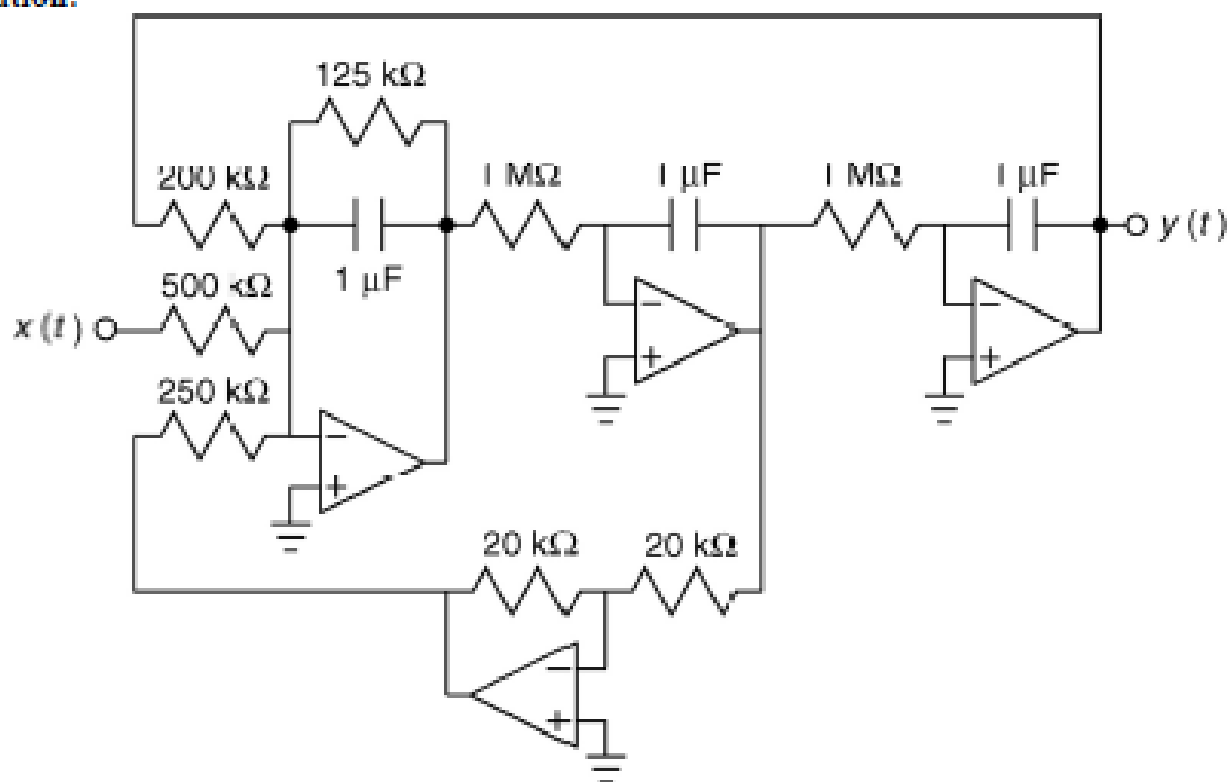

P 7.9-3

Solution:

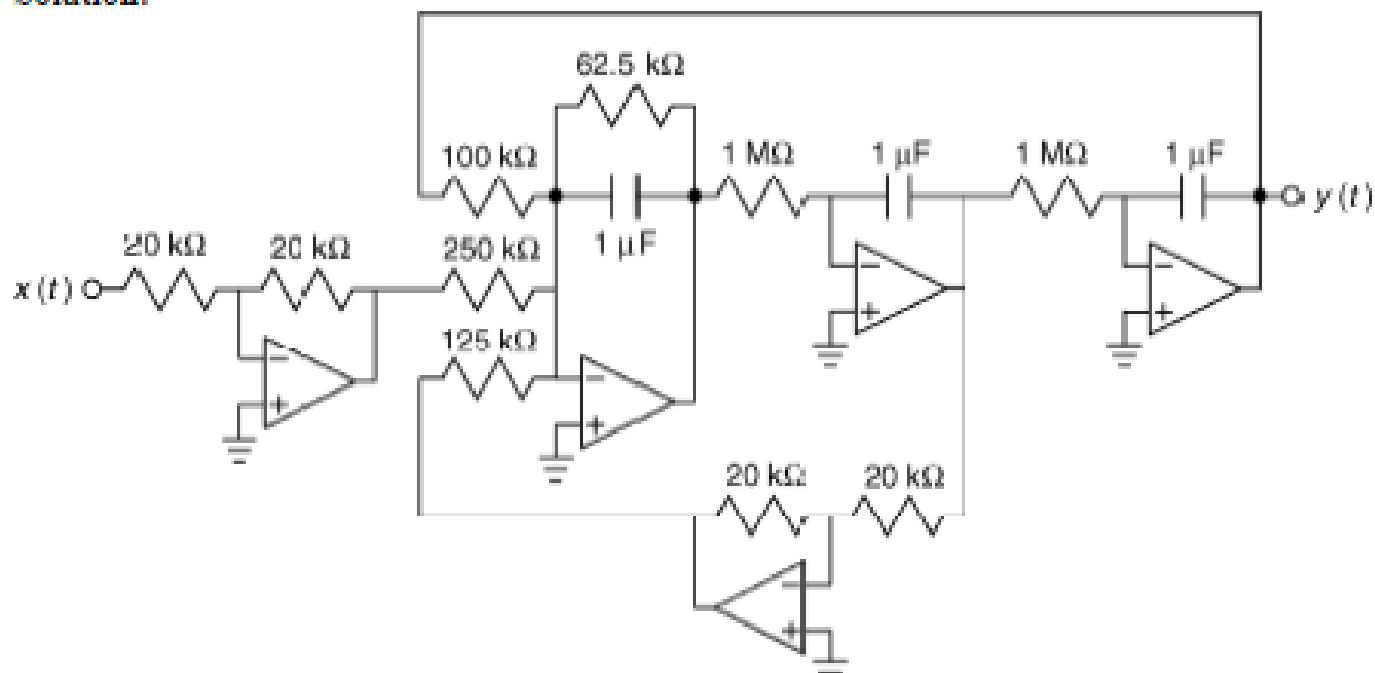

Section 7.11 How Can We Check...?

P 7.11-1

Solution: We need to check the values of the inductor current at the ends of the intervals.

$$\text{at } t=1 \quad 0.025 \stackrel{?}{=} -\frac{1}{25} + 0.065 = 0.025 \quad (\text{Yes!})$$

$$\begin{aligned} \text{at } t=3 \quad -\frac{3}{25} + 0.065 &\stackrel{?}{=} \frac{3}{50} - 0.115 \\ -0.055 &= -0.055 \quad (\text{Yes!}) \end{aligned}$$

$$\begin{aligned} \text{at } t=9 \quad \frac{9}{50} - 0.115 &\stackrel{?}{=} 0.065 \\ 0.065 &= 0.065 \quad (\text{Yes!}) \end{aligned}$$

The given equations for the inductor current describe a current that is continuous; as must be the case since the given inductor voltage is bounded.

P 7.11-2

Solution:

We need to check the values of the inductor current at the ends of the intervals.

$$-\frac{1}{300} + 0.0375 \stackrel{?}{=} -\frac{1}{150} + 0.045 \quad (\text{No!})$$

$$-\frac{4}{150} + 0.045 \stackrel{?}{=} \frac{4}{150} - 0.045 \quad (\text{No!})$$

The equation for the inductor current indicates that this current changes instantaneously at $t = 4\text{s}$. This equation cannot be correct.

Design Problems

DP 7-1

Solution:

a) $\frac{d}{dt}v(t) = -13.5 e^{-4.5t}$ is proportional to $i(t)$ so the element is a capacitor. $C = \frac{i(t)}{\frac{d}{dt}v(t)} = 0.3 \text{ F}.$

b) $\frac{d}{dt}i(t) = -13.5 e^{-1.5t}$ is proportional to $v(t)$ so the element is an inductor. $L = \frac{v(t)}{\frac{d}{dt}i(t)} = 0.3 \text{ H}.$

c) $v(t)$ is proportional to $i(t)$ so the element is a resistor. $R = \frac{v(t)}{i(t)} = 2 \Omega.$

DP 7-2

Solution:

(a)


$$1.131 \cos(2t + 45^\circ) = 1.131 [\cos(45^\circ) \cos(2t) - \sin(45^\circ) \sin(2t)] \\ = 0.8 \cos 2t - 0.8 \sin 2t$$

The first term is proportional to the voltage. Associate it with the resistor. The noticing that

$$\int_{-\infty}^t v(\tau) d\tau = \int_{-\infty}^t 4 \cos 2\tau d\tau = 2 \sin 2t \\ \frac{d}{dt}v(t) = \frac{d}{dt} 4 \cos 2t = -8 \sin 2t$$

associate the second term with a capacitor to get the minus sign. Then
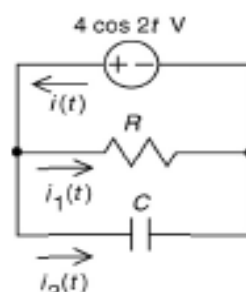
$$R = \frac{4 \cos 2t}{i_1(t)} = \frac{4 \cos 2t}{0.8 \cos 2t} = 5 \Omega \text{ and} \\ C = \frac{i_2(t)}{\frac{d}{dt} 4 \cos 2t} = \frac{-0.8 \sin 2t}{-8 \sin 2t} = 0.1 \text{ F}$$



(b)


$$1.131 \cos(2t - 45^\circ) = 1.131 [\cos(-45^\circ) \cos(2t) - \sin(-45^\circ) \sin(2t)] \\ = 0.8 \cos 2t + 0.8 \sin 2t$$

The first term is proportional to the voltage. Associate it with the resistor. Then noticing that

$$\int_{-\infty}^t v(\tau) d\tau = \int_{-\infty}^t 4 \cos 2\tau d\tau = 2 \sin 2t \\ \frac{d}{dt}v(t) = \frac{d}{dt} 4 \cos 2t = -8 \sin 2t$$

associate the second term with an inductor to get the plus sign. Then


$$R = \frac{4 \cos 2t}{i_1(t)} = \frac{4 \cos 2t}{0.8 \cos 2t} = 5 \Omega \text{ and} \\ L = \frac{\int_{-\infty}^t 4 \cos 2\tau d\tau}{i_2(t)} = \frac{2 \sin 2t}{0.8 \sin 2t} = 2.5 \text{ H}$$

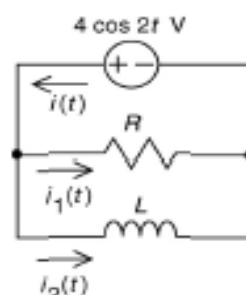

DP 7-3

Solution:

a)

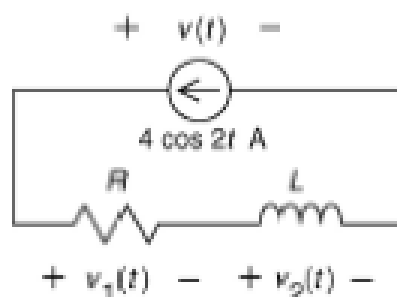

$$11.31 \cos(2t + 45^\circ) = 11.31 [\cos(45^\circ) \cos(2t) - \sin(45^\circ) \sin(2t)] \\ = 8 \cos 2t - 8 \sin 2t$$


The first term is proportional to the voltage. Associate it with the resistor. The noticing that

$$\int_{-\infty}^t i(\tau) d\tau = \int_{-\infty}^t 4 \cos 2\tau d\tau = 2 \sin 2t \\ \frac{d}{dt} i(t) = \frac{d}{dt} 4 \cos 2t = -8 \sin 2t$$

associate the second term with an inductor to get the minus sign. Then

$$R = \frac{v_1(t)}{4 \cos 2t} = \frac{8 \cos 2t}{4 \cos 2t} = 2 \Omega \text{ and } L = \frac{v_2(t)}{\frac{d}{dt} 4 \cos 2t} = \frac{-8 \sin 2t}{-8 \sin 2t} = 1 \text{ H}$$

b)

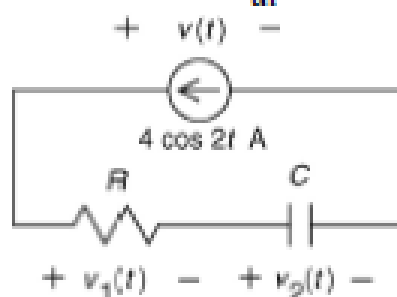


$$11.31 \cos(2t + 45^\circ) = 11.31 [\cos(-45^\circ) \cos(2t) - \sin(-45^\circ) \sin(2t)] \\ = 8 \cos 2t + 8 \sin 2t$$

The first term is proportional to the voltage. Associate it with the resistor. The noticing that

$$\int_{-\infty}^t i(\tau) d\tau = \int_{-\infty}^t 4 \cos 2\tau d\tau = 2 \sin 2t \\ \frac{d}{dt} i(t) = \frac{d}{dt} 4 \cos 2t = -8 \sin 2t$$

associate the second term with a capacitor to get the minus sign. Then


$$R = \frac{v_1(t)}{4 \cos 2t} = \frac{8 \cos 2t}{4 \cos 2t} = 2 \Omega \text{ and } C = \frac{\int_{-\infty}^t 4 \cos 2\tau d\tau}{v_2(t)} = \frac{2 \sin 2t}{8 \sin 2t} = 0.25 \text{ F}$$

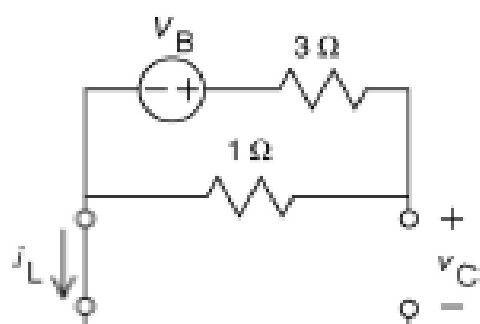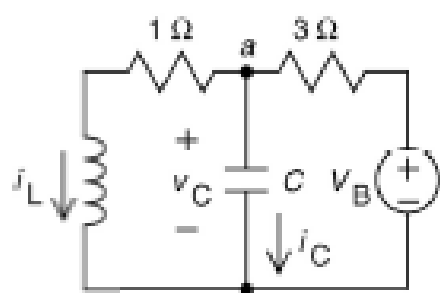DP 7-4**Solution:**at $t=0^-$ 

$$i_L(0^-) = 0$$

By voltage division: $v_C(0^-) = \frac{V_B}{4}$

We require $v_C(0^-) = 3 \text{ V}$ so $V_B = 12 \text{ V}$

at $t=0^+$ 

Now we will check $\left. \frac{dv_C}{dt} \right|_{t=0^+}$

First: $i_L(0^+) = i_L(0^-) = 0$

and $v_C(0^+) = v_C(0^-) = 3 \text{ V}$

Apply KCL at node a :

$$i_L(0^+) + i_C(0^+) = \frac{V_B - v_C(0^+)}{3}$$

$$0 + i_C(0^+) = \frac{12 - 3}{3} \Rightarrow i_C(0^+) = 3 \text{ A}$$

Finally

$$\left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{3}{0.125} = 24 \frac{\text{V}}{\text{s}}$$

as required.

DP 7-5**Solution:**


We require $\frac{1}{2} L i_L^2 = \frac{1}{2} C v_C^2$ where i_L and v_C are the steady-state inductor current and capacitor voltage. At steady state, $i_L = \frac{v_C}{R}$. Then

$$L \left(\frac{v_C}{R} \right)^2 = C v_C^2 \Rightarrow C = \frac{L}{R^2} \Rightarrow R = \sqrt{\frac{L}{C}} = \sqrt{\frac{10^{-2}}{10^{-6}}} = \sqrt{10^4} = 10^2 \Omega$$

DP 7-6

Solution:

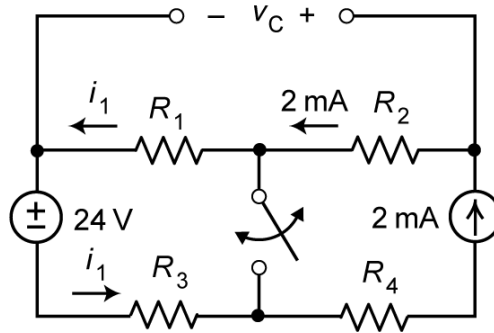A capacitor in a **steady state** circuit with constant inputs (that is, a dc circuit) acts like an open circuit:



The **steady state** current in resistor R_2 is 2 mA both when the switch is open and when it is closed. Also the **steady state** current in resistor R_3 is equal to the **steady state** current in resistor R_1 as shown in the above figure.

The current in resistor R_1 is given by

$$i_1 = \begin{cases} -2 \text{ mA} & \text{the switch is open} \\ \frac{24}{R_1 + R_3} & \text{the switch is closed} \end{cases}$$

Use Ohm's law and KVL to express the **steady state** voltage across the capacitor as

$$v_C = \begin{cases} (R_1 + R_2)0.002 & \text{the switch is open} \\ -\frac{R_1}{R_1 + R_3}24 + R_2(0.002) & \text{the switch is closed} \end{cases}$$

The specification requires

$$10 = v_C = (R_1 + R_2)0.002 \Rightarrow R_1 + R_2 = \frac{10}{0.002} = 5000$$

when the switch is open, and

$$-10 = -\frac{R_1}{R_1 + R_3}24 + R_2(0.002)$$

when the switch is closed.

Let's try $R_1 = 4 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$. The specification is satisfied when the switch is open. When the switch is closed we have

$$-10 = -\frac{4000}{4000 + R_3} 24 + 1000(0.002) \Rightarrow -12 = -\frac{4000}{4000 + R_3} 24 \Rightarrow R_3 = 4 \text{ k}\Omega$$

The specifications are satisfied when $R_1 = 4 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$ and $R_3 = 4 \text{ k}\Omega$. Any value of R_4 will do. It's hard to argue against choosing $R_4 = 0$, in which case resistor R_4 is just a wire.


In summary, the specifications are satisfied when

$$R_1 = 4 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega \text{ and } R_4 = 0$$

DP 7-7

Solution:

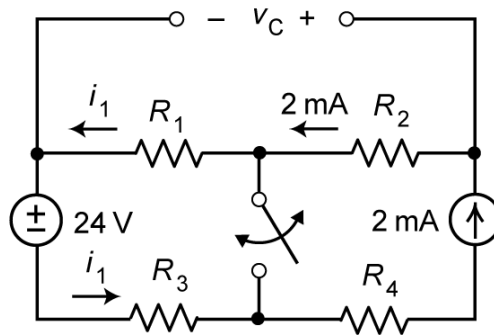A capacitor in a **steady state** circuit with constant inputs (that is, a dc circuit) acts like an open circuit:



The **steady state** current in resistor R_2 is 2 mA both when the switch is open and when it is closed. Also the **steady state** current in resistor R_3 is equal to the **steady state** current in resistor R_1 as shown in the above figure.

The current in resistor R_1 is given by

$$i_1 = \begin{cases} -2 \text{ mA} & \text{the switch is open} \\ \frac{24}{R_1 + R_3} & \text{the switch is closed} \end{cases}$$

Use Ohm's law and KVL to express the **steady state** voltage across the capacitor as

$$v_C = \begin{cases} (R_1 + R_2)0.002 & \text{the switch is open} \\ -\frac{R_1}{R_1 + R_3}24 + R_2(0.002) & \text{the switch is closed} \end{cases}$$

The specification requires


$$4 = v_C = (R_1 + R_2)0.002 \Rightarrow R_1 + R_2 = \frac{4}{0.002} = 2000$$

when the switch is open, and

$$-30 = -\frac{R_1}{R_1 + R_3}24 + R_2(0.002)$$

when the switch is closed. There is no choice of positive resistances R_1, R_2 and R_3 that will satisfy this equation. The specifications cannot be satisfied.

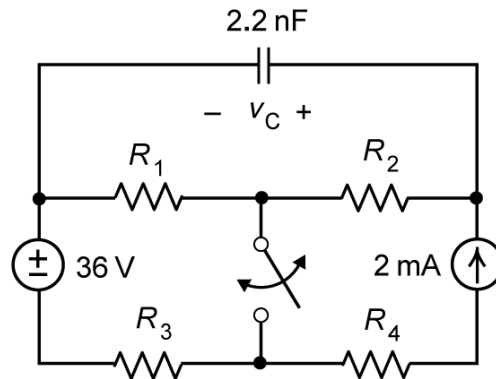We might be able to satisfy the specifications if we increased the voltage source-voltage to something a bit larger than 24 V. Let's try 36 V:



Now

$$v_C = \begin{cases} (R_1 + R_2)0.002 & \text{the switch is open} \\ -\frac{R_1}{R_1 + R_3}30 + R_2(0.002) & \text{the switch is closed} \end{cases}$$

Let's try $R_1 = 1 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$. The specification is satisfied when the switch is open. When the switch is closed we have

$$-30 = -\frac{1000}{1000 + R_3}36 + 1000(0.002) \Rightarrow -32 = -\frac{1000}{1000 + R_3}36 \Rightarrow R_3 = 125 \Omega$$

The specifications are satisfied when $R_1 = 4 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$ and $R_3 = 125 \Omega$. Any value of R_4 will do. It's hard to argue against choosing $R_4 = 0$, in which case resistor R_4 is just a wire.

In summary, if the voltage source-voltage the specifications are satisfied when


$$R_1 = 4 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 4 \text{ k}\Omega \text{ and } R_4 = 0$$

If the circuit cannot be changed, the specifications cannot be satisfied.

DP7-8

Solution:

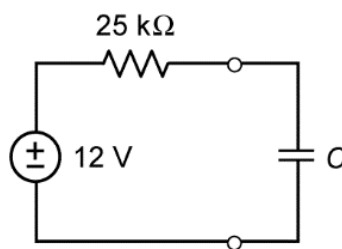Replace the part of the circuit connected to the capacitor by its Thevenin equivalent circuit (see the solution to problem DP 5-11).




We require: $2 \times 10^{-3} = 25 \times 10^3 C \Rightarrow C = \frac{2}{25} \times 10^{-6} = 80 \text{ nF}$

Consequently 80 nF is the value of the capacitance C in the circuit shown in Figure DP 7-8b that will cause the time constant to be $\tau = 2 \text{ ms}$.

DP7-9

Solution:

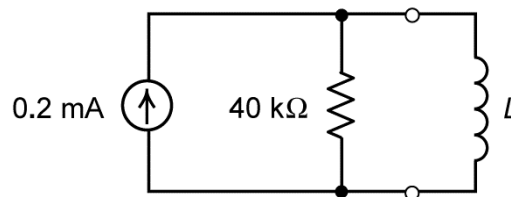Replace the part of the circuit connected to the resistor having resistance R by its Norton equivalent circuit (see the solution to problem DP5-5).



We require: $2 \times 10^{-6} = \frac{L}{40000} \Rightarrow L = 80 \times 10^{-3} = 80 \text{ mH}$

Consequently 80 mH is the value of the inductance L in the circuit shown in Figure DP 7-9(b) that will cause the time constant to be $\tau = 2 \mu\text{s}$.

