

HW6 solution

1. The content of a 4-bit shift register is initially 1011. The register is shifted six times to the right with the serial input 101110 (left bit is first input). What is the content of the register after each shift?

Answer :

initial : 1011 input: 101110

shift 1 : 1101

shift 2 : 0110

shift 3 : 1011

shift 4 : 1101


shift 5 : 1110

shift 6 : 0111

2. Draw the logic diagram of a four-bit register with four D flip-flops and four 4x1 multiplexers with mode selection S1 and S0. The register operates according to the following function table.


S1	S0	Register Operation
0	0	Load parallel data
0	1	Complement the four outputs
1	0	Clear register to 0 (synchronous with the clock)
1	1	No change

Answer :

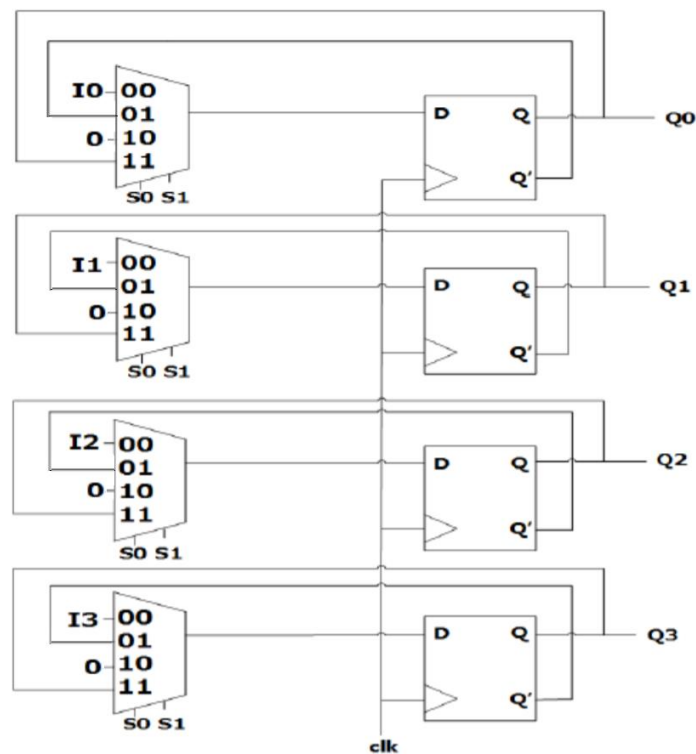

3. Johnson counter: List the 10 states produced with five flip-flops and the Boolean terms of each of the 10 AND gate outputs.

Answer :

 

	Sequence number	Flip-flop outputs					AND gate required for output
		A	B	C	E	F	
Q ₁	1	0	0	0	0	0	A'F'
Q ₂	2	1	0	0	0	0	AB'
Q ₃	3	1	1	0	0	0	BC'
Q ₄	4	1	1	1	0	0	CE'
Q ₅	5	1	1	1	1	0	EF'
Q ₆	6	1	1	1	1	1	AF
Q ₇	7	0	1	1	1	1	A'B
Q ₈	8	0	0	1	1	1	B'C
Q ₉	9	0	0	0	1	1	C'E
Q ₁₀	10	0	0	0	0	1	E'F

4. Use D flip-flops and gates to design a binary counter with each of the following repeated binary sequences:

(a) 2, 4, 7

(b) 0, 2, 4, 6

4.(a)

Present State			Next State			Flip-Flop Inputs		
A	B	C	A	B	C	A	B	C
0	1	0	1	0	0	1	0	0
1	0	0	1	1	1	1	1	1
1	1	1	0	1	0	0	1	0

For D_A :

A	BC	00	01	11	10
0		X	X	X	1
1		1	X	0	X

$D_A = C'$

For D_B :

A	BC	00	01	11	10
0		X	X	X	0
1		1	X	1	X

$D_B = A$

For D_C :

A	BC	00	01	11	10
0		X	X	X	0
1		1	X	0	X

$D_C = B'$

Second Design -

Present State			Next State			Flip-Flop Inputs		
A	B	C	A	B	C	D_A	D_B	D_C
0	0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0	1
0	1	0	1	0	0	1	0	0
0	1	1	0	0	0	0	0	0
1	0	0	1	1	1	1	1	1
1	0	1	0	1	1	0	1	1
1	1	0	1	0	0	1	0	0
1	1	1	0	1	0	0	1	0

For D_A :

A	BC	00	01	11	10
0		1	1	0	1
1		1	0	0	1

$D_A = C' + AB'$

For D_B :

A	BC	00	01	11	10
0		0	0	0	0
1		1	1	1	0

$D_B = AB' + AC$

For D_C :

A	BC	00	01	11	10
0		0	0	0	0
1		1	1	1	0

$D_C = AB'$

4.1b)

Present State			Next State			Flip-Flop Inputs		
A	B	C	A	B	C	D_A	D_B	D_C
0	0	0	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
1	0	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0	0

For D_A :

A \ BC	00	01	11	10
0	0	X	X	1
1	1	X	X	0

$$D_A = AB' + A'B$$

For D_B :


A \ BC	00	01	11	10
0	1	X	X	0
1	1	X	X	0

$$D_B = B'$$

For D_C :

A \ BC	00	01	11	10
0	0	X	X	0
1	0	X	X	0


$$D_C = 0$$

 


5. Frequency divider:

- (a) Design a frequency divider to provide the output signal with frequency as $1/8$ of the that of the original signal.
- (b) Design a frequency divider to provide the output signal with frequency as $1/6$ of the that of the original signal.



(a)

 

$$f_{Q_2} = \frac{1}{8} f_{clk}$$

 

(b)

  

$$f_Q = \frac{1}{6} f_{clk}$$