

Chapter 10

Exercise

EXERCISE 10.10-1 Find the ratio V_o/V_s for the circuit shown in Figure 10.10-2 when $R_1 = R_2 = 1 \text{ k}\Omega$, $C_2 = 0$, $C_1 = 1 \text{ }\mu\text{F}$, and $\omega = 1000 \text{ rad/s}$.

Solution

The circuit of Figure 10.10-2 is an example of the inverting amplifier shown in Figure 10.10-1a. Using Eqs. 10.10-3 and 10.10-6, we obtain

$$\frac{V_o}{V_s} = - \frac{Z_1}{Z_2} = - \frac{\frac{R_2}{1 + j\omega C_2 R_2}}{\frac{R_1}{1 + j\omega C_1 R_1}} = - \frac{R_2(1 + j\omega C_1 R_1)}{R_1(1 + j\omega C_2 R_2)}$$

Substituting the given values of R_1 ; R_2 ; C_1 ; C_2 ; and ω gives

$$\frac{V_o}{V_s} = - \frac{10^3(1 + j10^3(10^{-6})10^3)}{10^3(1 + j10^3(0)10^3)} = - \frac{1 + j}{1} = -1 - j = 45^\circ$$

Section 10.2 Sinusoidal Sources

P10.2-1

Given:

$$v_1(t) = 5 \cos(150t + 30^\circ) \text{ V}$$

$$v_2(t) = 4 \cos(150t - 60^\circ) \text{ V}$$

So,

$$\theta_1 = 30^\circ$$

$$\theta_2 = -60^\circ$$

The period of the sinusoids is given by,

$$150 = \frac{2\pi}{T}$$

$$T = 42 \text{ ms}$$

Compare $v_2(t)$ to $v_1(t)$

$$\theta_2 - \theta_1 = -60 - 30 = -90^\circ = -\frac{\pi}{2} \text{ rad}$$

The minus sign (–) indicates a delay rather than an advance,
Convert the angle to time.

$$\theta_2 - \theta_1 = 2\pi \frac{t_d}{T}$$

$$\begin{aligned} t_d &= \frac{(\theta_2 - \theta_1)T}{2\pi} \\ &= \frac{(-\pi/2)(0.042)}{2\pi} \\ &= -0.105 \text{ s} \end{aligned}$$

P10.2-2

Given:

$$v_1(t) = 12 \cos(150t - 102^\circ) \text{ V}$$

$$v_2(t) = 12 \cos(150t - 54^\circ) \text{ V}$$

So,

$$\theta_1 = -102^\circ$$

$$\theta_2 = -54^\circ$$

The period of the sinusoids is given by,

$$150 = \frac{2\pi}{T}$$

$$T = 42 \text{ ms}$$

Compare $v_2(t)$ to $v_1(t)$

$$\theta_2 - \theta_1 = -54 + 102 = 48^\circ = 0.838 \text{ rad}$$

The plus sign (+) indicates an advance rather than a delay.

Convert the angle to time.

$$\theta_2 - \theta_1 = 2\pi \frac{t_d}{T}$$


$$\begin{aligned} t_d &= \frac{(\theta_2 - \theta_1)T}{2\pi} \\ &= \frac{(0.838)(0.042)}{2\pi} \\ &= 5.6 \text{ ms} \end{aligned}$$

P10.2-3

Solution: The amplitude is $A = 45 \text{ mV}$ and the period is given by $\frac{T}{2} = 60 - 20 = 40 \text{ ms}$ so the period is T

$= 80 \text{ ms}$. The frequency is given by $\omega = \frac{2\pi}{80 \times 10^{-3}} = 78.54 \text{ rad/s}$. Noticing that $v(t)$ is 0 at time 0 and is increasing at time 0, we can write

$$v(t) = 45 \sin(78.54t) = 45 \cos(78.54t - 90^\circ) \text{ mV}$$

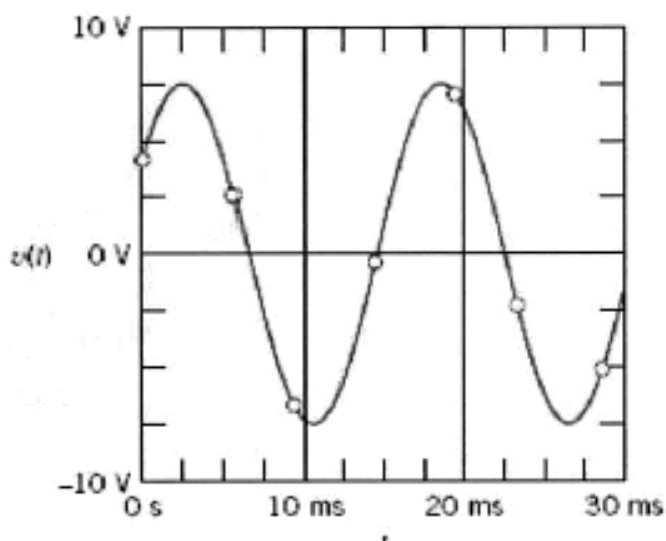P 10.2-4**Solution:**

$$A = 7.5 \text{ V}$$

$$T = 21.5 - 5.5 = 16 \text{ ms}$$

$$\omega = \frac{2\pi}{T} = \frac{2\pi}{0.016} = 392 \text{ rad/s}$$

$$\theta = -\cos^{-1}\left(\frac{4}{7.5}\right) = -58^\circ$$

$$v(t) = 7.5 \cos(392t - 58^\circ) \text{ V}$$

Section 10.3 Phasors and Sinusoids**P10.3-1****Solution:**

The current is given as,

$$i(t) = 3\cos(9t - 60^\circ) + 3\sin(9t + 120^\circ) \text{ mA}$$

Express it in the general form,

$$i(t) = A\cos(\omega t + \theta) \text{ mA}$$

First, find the Phasor form.

$$\begin{aligned} i(t) &= 3\cos(9t - 60^\circ) + 3\sin(9t + 120^\circ) \\ &= 3\cos(9t - 60^\circ) + 3\cos(9t + 120^\circ - 90^\circ) \\ &= 3\cos(9t - 60^\circ) + 3\cos(9t + 30^\circ) \\ &= 3\angle -60^\circ + 3\angle 30^\circ \\ &= 4.25\angle -15^\circ \end{aligned}$$

Now,

$$\begin{aligned} i(t) &= A\cos(\omega t + \theta) \text{ mA} \\ &= 4.25 \cos(9t - 15^\circ) \text{ mA} \end{aligned}$$

P10.3-2**Solution:**

The voltage is given as,

$$v(t) = 6\sqrt{2} \cos(10t) + 3 \sin(10t + 60^\circ) \text{ V}$$

Express it in the general form,

$$v(t) = A \cos(\omega t + \theta) \text{ V}$$

First, find the Phasor form.

$$\begin{aligned} v(t) &= 6\sqrt{2} \cos(10t) + 3 \sin(10t + 60^\circ) \\ &= 6\sqrt{2} \cos(10t) + 3 \cos(10t + 60^\circ - 90^\circ) \\ &= 6\sqrt{2} \cos(10t) + 3 \cos(10t - 30^\circ) \\ &= 6\sqrt{2} \angle 0^\circ + 3 \angle -30^\circ \\ &= 11.2 \angle -7.7^\circ \end{aligned}$$

Now,

$$\begin{aligned} v(t) &= A \cos(\omega t + \theta) \text{ V} \\ &= \underline{11.2 \cos(10t - 7.7^\circ) \text{ V}} \end{aligned}$$

P 10.3-3**Solution:**


$$\frac{(25 \angle 36.9^\circ)(80 \angle -53.1^\circ)}{(4 + j8) + (6 - j8)} = \frac{25 \cdot 80 \angle (36.9^\circ - 53.1^\circ)}{(4 + 6) + j(8 - 8)} = \frac{2000 \angle -16.2^\circ}{10} = 200 \angle -16.2^\circ$$

P 10.3-4**Solution:**

$$\begin{aligned} \frac{(60 \angle 120^\circ)(-16 + j12 + 20 \angle 15^\circ)}{5 \angle -75^\circ} &= \frac{(60 \angle 120^\circ)(-16 + j12 + 19.3185 + j5.1764)}{5 \angle -75^\circ} \\ &= \frac{(60 \angle 120^\circ)(3.3185 + j17.1764)}{5 \angle -75^\circ} \\ &= \frac{(60 \angle 120^\circ)(17.494 \angle 79.065^\circ)}{5 \angle -75^\circ} \\ &= \frac{1049.6 \angle -160.93^\circ}{5 \angle -75^\circ} = 139.95 \angle 109.07^\circ = 45.714 + j132.28 \end{aligned}$$

P10.3-5**Solution:**

The circuit is shown below.

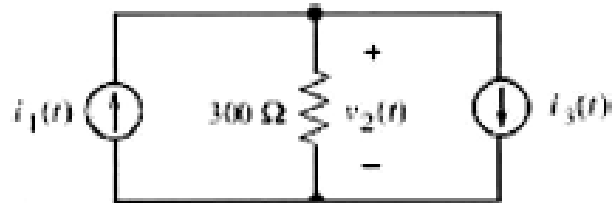

Given

$$i_1(t) = 12 \cos(30t)$$

$$i_3(t) = 12 \cos(30t + 150^\circ)$$

Now, from the circuit,

$$i_2(t) = i_1(t) - i_3(t)$$


So,

$$\begin{aligned} i_2(t) &= 12 \cos(30t) - 12 \cos(30t + 150^\circ) \\ &= 12 \angle 0^\circ - 12 \angle 150^\circ \\ &= 23.2 \angle -15^\circ \text{ mA} \end{aligned}$$

Now,

$$R = 300 \, \Omega$$

$$\begin{aligned} v_2(t) &= 300 \times 23.2 \angle -15^\circ \times 10^{-3} \\ &= 6.94 \angle -15^\circ \\ &= \underline{6.94 \cos(30t - 15^\circ) \text{ V}} \end{aligned}$$

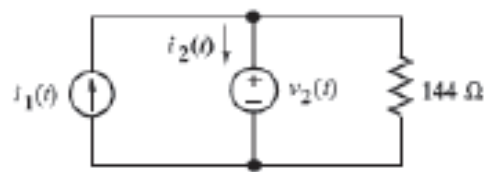P10.3-6**Solution:**

Given:

$$i_1(t) = 0.18 \cos(150t + 60^\circ) \text{ A}$$

$$i_2(t) = 36 \cos(150t + 75^\circ) \text{ A}$$

Now,

$$R = 144 \, \Omega$$

Now, from the circuit, apply the voltage law

$$144(i_1(t) - i_2(t)) - v_2(t) = 0$$

So,

$$v_2(t) = 144(0.18 \cos(150t + 60^\circ)) - 144i_2(t)$$

$$36 \cos(150t - 75^\circ) = 144(0.18 \cos(150t + 60^\circ)) - 144i_2(t)$$

$$36 \angle -75^\circ = 25.92 \angle 60^\circ - 144i_2(t)$$

$$i_2(t) = \frac{57.34 \angle 86.36^\circ}{144}$$


$$i_2(t) = 0.4 \angle 86.36^\circ \text{ A}$$

$$i_2(t) = 0.4 \cos(150t + 86.36^\circ) \text{ A}$$

P 10.3-7

Solution:

The figure below shows the RL circuit:

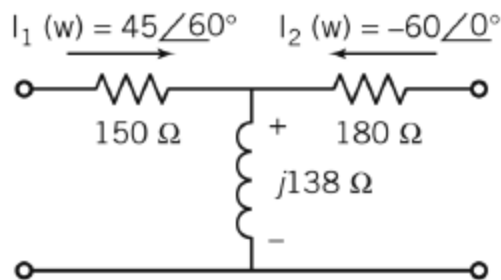

The impedance of the inductor is:

$$Z_L = j\omega L$$

Substitute 6 rad/s for ω , and 23 H for L ,

$$\begin{aligned} Z_L &= j(6 \text{ rad/s})(23 \text{ H}) \\ &= j138 \Omega \end{aligned}$$

The phasor representation of current $i_1(t) = 45 \cos(6t + 60^\circ)$ is:

$$\mathbf{I}_1(\omega) = 45 \angle 60^\circ$$

The phasor representation of current $i_2(t) = -60 \cos(6t)$ is:

$$\mathbf{I}_2(\omega) = -60 \angle 0^\circ$$

Apply KCL at node 'a',

$$\begin{aligned} \mathbf{I}(\omega) &= \mathbf{I}_1(\omega) + \mathbf{I}_2(\omega) \\ &= 45 \angle 60^\circ - 60 \angle 0^\circ \end{aligned}$$

The current through the inductor is given as:

$$\mathbf{I}(\omega) = \frac{\mathbf{V}(\omega)}{Z_L}$$

Substitute the same in equation $\mathbf{I}(\omega) = 45 \angle 60^\circ - 60 \angle 0^\circ$,

$$\begin{aligned} \frac{\mathbf{V}(\omega)}{Z_L} &= 45 \angle 60^\circ - 60 \angle 0^\circ \\ \mathbf{V}(\omega) &= Z_L (45 \angle 60^\circ - 60 \angle 0^\circ) \\ &= (j138 \Omega)(45 \cos 60^\circ \text{ mA} + j45 \sin 60^\circ \text{ mA} - 60 \cos 0^\circ \text{ mA}) \\ &= (j138 \Omega) \left((-37.5 \text{ mA}) \left(\frac{10^{-3} \text{ A}}{1 \text{ mA}} \right) + (j38.9 \text{ mA}) \left(\frac{10^{-3} \text{ A}}{1 \text{ mA}} \right) \right) \\ &= -5.17 + j5.36 \text{ V} \end{aligned}$$

The phase of voltage $V(\omega)$ is:

$$\begin{aligned}\theta &= 180^\circ - \tan^{-1} \left(\frac{5.36}{-(-5.17)} \right) \\ &= 134^\circ\end{aligned}$$

The amplitude of the voltage $V(\omega)$ is:

$$\begin{aligned}V &= \sqrt{(-5.17 \text{ V})^2 + (5.36 \text{ V})^2} \\ &= 7.44 \text{ V}\end{aligned}$$

The voltage $v(t)$ is:

$$v(t) = V \cos(\omega t + \theta)$$


Substitute 7.44 V for V , 134° for θ , and 6 rad/s for ω ,

$$v(t) = 7.44 \text{ V} \cos(6t + 134^\circ)$$

Therefore, the voltage $v(t)$ is $7.44 \text{ V} \cos(6t + 134^\circ)$.

P 10.3-8

Solution:

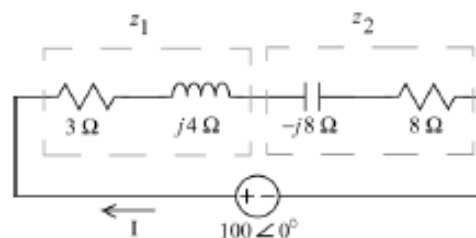


- (a) $\underline{Z_1 = 3 + j4 = 5 \angle 53.1^\circ \Omega}$ and $\underline{Z_2 = 8 - j8 = 8\sqrt{2} \angle -45^\circ \Omega}$
- (b) Total impedance = $Z_1 + Z_2 = 3 + j4 + 8 - j8 = 11 - j4 = \underline{11.7 \angle -20.0^\circ \Omega}$
- (c) $\underline{I = \frac{100 \angle 0^\circ}{Z_1 + Z_2} = \frac{100}{11.7 \angle -20^\circ} = \frac{100}{11.7} \angle 20.0^\circ \Rightarrow i(t) = 8.55 \cos(1250t + 20.0^\circ) \text{ A}}$

P 10.3-9**Solution:**

$$\begin{aligned}
 \mathbf{V}_1(\omega) &= \mathbf{V}_s(\omega) - \mathbf{V}_2(\omega) = 7.68\angle 47^\circ - 1.59\angle 125^\circ \\
 &= (5.23 + j5.62) - (-0.91 + j1.30) \\
 &= (5.23 + 0.91) + j(5.62 - 1.30) \\
 &= 6.14 + j4.32 \\
 &= 7.51\angle 35^\circ
 \end{aligned}$$

$$v_1(t) = 7.51 \cos(2t + 35^\circ) \text{ V}$$

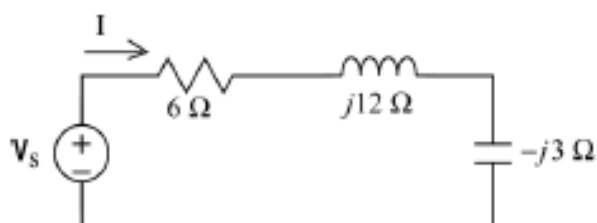P 10.3.10**Solution:**

$$\begin{aligned}
 \mathbf{V}_s &= 2\angle 30^\circ \text{ V} \\
 \text{and } \mathbf{I} &= \frac{2\angle 30^\circ}{6 + j12 + 3/j} = 0.185\angle -26.3^\circ \text{ A}
 \end{aligned}$$

$$\underline{i(t) = 0.185 \cos(4t - 26.3^\circ) \text{ A}}$$

P 10.3-11**Solution:** (a)

$$12 + v(t) - 10(0.02) = 0 \Rightarrow v(t) = 2 - 12 = -10 \text{ V}$$

(b)

$$\begin{aligned}
 12 + v(t) - 10i(t) &= 0 \Rightarrow v(t) = 10(0.020 \cos(100t + 15^\circ)) - 12 \\
 &= 0.2 \cos(100t + 15^\circ) - 12
 \end{aligned}$$

(c)

$$v_c(t) + v(t) - 10i(t) = 0$$

$$0.1 \cos(100t + 105^\circ) + v(t) - 10(0.020 \cos(100t + 15^\circ)) = 0$$

$$v(t) = 0.2 \cos(100t + 15^\circ) - 0.1 \cos(100t + 105^\circ) \text{ V}$$

$$\begin{aligned}\mathbf{V} &= 0.2\angle 15^\circ - 0.1\angle 105^\circ = (0.193 + j0.052) - (-0.0259 + j0.0966) \\ &= 0.219 - j0.045 = 0.2236\angle -11.6^\circ \text{ V}\end{aligned}$$

$$v(t) = 0.2236 \cos(100t - 11.6^\circ) \text{ V}$$

Section 10.4 Impedances

P10.4-1

Solution:

$$\begin{aligned}Z_R &= 8 \, \Omega, \quad Z_C = \frac{1}{j3\frac{1}{12}} = \frac{4}{j} = \frac{j4}{j \times j} = -j4 \, \Omega, \quad Z_{L1} = j3(2) = j6 \, \Omega, \\ Z_{L2} &= j3(4) = j12 \, \Omega \text{ and } \mathbf{I}_S = 4 \angle 15^\circ \text{ A}.\end{aligned}$$

P10.4-2

Solution:

The current $i_1(t) = 600 \cos(38t - 30^\circ)$ can be represented in phasor form as:

$$\mathbf{I}_1(\omega) = 600\angle -30^\circ$$

The current $i_2(t) = 1125 \cos(38t + 75^\circ)$ can be represented in phasor form as:

$$\mathbf{I}_2(\omega) = 1125\angle 75^\circ$$

The impedance of inductor is:

$$Z_L = j\omega L$$

Substitute 38 rad/s for ω , and 96 mH for L ,

$$\begin{aligned}Z_L &= j(38 \text{ rad/s})(96 \text{ mH}) \left(\frac{10^{-3} \text{ H}}{1 \text{ mH}} \right) \\ &= j3.64 \, \Omega\end{aligned}$$

The impedance of the capacitor is:


$$Z_C = \frac{-j}{\omega C}$$

Substitute 38 rad/s for ω , and 6 mF for C ,

$$Z_C = \frac{-j}{(38 \text{ rad/s})(6 \text{ mF}) \left(\frac{10^{-3} \text{ F}}{1 \text{ mF}} \right)}$$

$$= -j4.38 \Omega$$

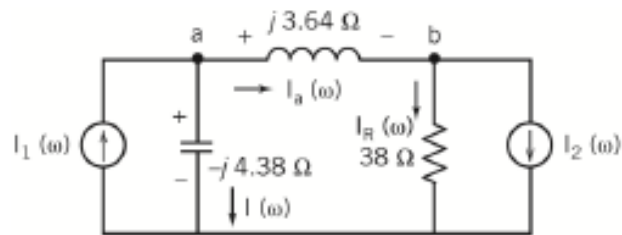The figure below shows the circuit in frequency domain:



Apply KCL at node 'a':

$$I_1(\omega) = I(\omega) + I_a(\omega) \quad \dots\dots (1)$$

Apply KCL at node 'b':

$$I_a(\omega) = I_R(\omega) + I_2(\omega) \quad \dots\dots (2)$$

KVL in middle loop gives,

$$I(\omega)Z_C - V_a(\omega) - I_R(\omega)R = 0$$

$$I(\omega)Z_C - I_a(\omega)Z_L - I_R(\omega)R = 0$$

Substitute $I_a(\omega) = I_1(\omega) - I(\omega)$ (from equation 1),

$$I(\omega)Z_C - (I_1(\omega) - I(\omega))Z_L - I_R(\omega)R = 0$$

$$I(\omega)(Z_C + Z_L) - I_1(\omega)Z_L = I_R(\omega)R$$

Substitute $\mathbf{I}_R(\omega) = \mathbf{I}_1(\omega) - \mathbf{I}_2(\omega) - \mathbf{I}(\omega)$ (from equation 3),

$$\begin{aligned}\mathbf{I}(\omega)(\mathbf{Z}_C + \mathbf{Z}_L) - \mathbf{I}_1(\omega)\mathbf{Z}_L &= (\mathbf{I}_1(\omega) - \mathbf{I}_2(\omega) - \mathbf{I}(\omega))R \\ \mathbf{I}(\omega)(\mathbf{Z}_C + \mathbf{Z}_L + R) &= \mathbf{I}_1(\omega)(\mathbf{Z}_L + R) - \mathbf{I}_2(\omega)R \\ \mathbf{I}(\omega) &= \frac{\mathbf{I}_1(\omega)(\mathbf{Z}_L + R) - \mathbf{I}_2(\omega)R}{\mathbf{Z}_C + \mathbf{Z}_L + R}\end{aligned}$$

Substitute $\mathbf{I}_1(\omega) = 600\angle -30^\circ$, $\mathbf{I}_2(\omega) = 1125\angle 75^\circ$, $\mathbf{Z}_L = j3.64\ \Omega$, $\mathbf{Z}_C = -j4.38\ \Omega$, and $R = 38\ \Omega$,

$$\begin{aligned}\mathbf{I}(\omega) &= \frac{(600\angle -30^\circ)(j3.64\ \Omega + 38\ \Omega) - (1125\angle 75^\circ)(38\ \Omega)}{-j4.38\ \Omega + j3.64\ \Omega + 38\ \Omega} \\ &= \frac{(600\cos(-30^\circ) + j600\sin(-30^\circ))(j3.64\ \Omega + 38\ \Omega) - (1125\cos(75^\circ) + j1125\sin(75^\circ))(38\ \Omega)}{-j4.38\ \Omega + j3.64\ \Omega + 38\ \Omega} \\ &= \frac{9772.8 - j50802\ \Omega\text{A}}{38 - j0.74\ \Omega} \\ &= 231 - j1331\text{ A}\end{aligned}$$

The phase of current $\mathbf{I}(\omega)$ is:

$$\begin{aligned}\theta &= \tan^{-1}\left(\frac{-1331}{231}\right) \\ &= -80^\circ\end{aligned}$$

The amplitude of current $\mathbf{I}(\omega)$ is:

$$\begin{aligned}I &= \sqrt{(231\text{ A})^2 + (-1331\text{ A})^2} \\ &= 1351\text{ A}\end{aligned}$$

Therefore, the current $\mathbf{I}(\omega)$ in frequency domain is:

$$\begin{aligned}\mathbf{I}(\omega) &= I\angle\theta \\ &= 1351\angle -80^\circ\end{aligned}$$

Substitute $\mathbf{I}(\omega)$ and $\mathbf{I}_1(\omega)$ back in equation $\mathbf{I}_a(\omega) = \mathbf{I}_1(\omega) - \mathbf{I}(\omega)$,

$$\begin{aligned}
 \mathbf{I}_a(\omega) &= \mathbf{I}_1(\omega) - \mathbf{I}(\omega) \\
 &= (600 \angle -30^\circ) - (1351 \angle -80^\circ) \\
 &= 519.6 - j300 - 234.5 + j1330.4 \\
 &= 285.1 + j1030.4 \text{ A}
 \end{aligned}$$

The voltage $\mathbf{V}_a(\omega)$ is:

$$\begin{aligned}
 \mathbf{V}_a(\omega) &= \mathbf{I}_a(\omega) \mathbf{Z}_L \\
 &= (285.1 + j1030.4 \text{ A})(j3.64 \Omega) \\
 &= -3750.6 + j1037.7 \text{ V}
 \end{aligned}$$

The phase of voltage $\mathbf{V}_a(\omega)$ is:

$$\begin{aligned}
 \phi &= 180^\circ - \tan^{-1} \left(\frac{1037.7}{3750.6} \right) \\
 &= 165^\circ
 \end{aligned}$$


The amplitude of voltage $\mathbf{V}_a(\omega)$ is:

$$\begin{aligned}
 V &= \sqrt{(-3750.6 \text{ V})^2 + (1037.7 \text{ V})^2} \\
 &= 3891 \text{ V}
 \end{aligned}$$

Therefore, the voltage $\mathbf{V}_a(\omega)$ in frequency domain is:

$$\begin{aligned}
 \mathbf{V}_a(\omega) &= V \angle \phi \\
 &= 3891 \angle 165^\circ
 \end{aligned}$$

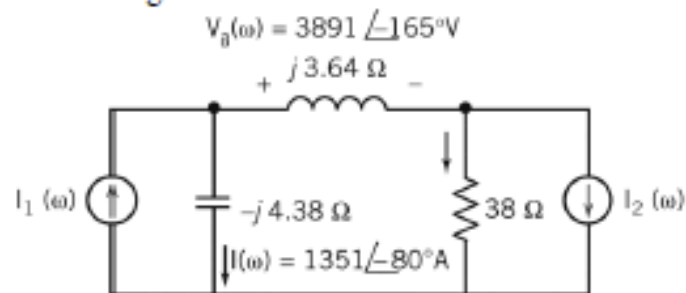The circuit in frequency domain is given as:



P10.4-3

Solution:

In order to show the given circuit in frequency- domain, proceed as follows:

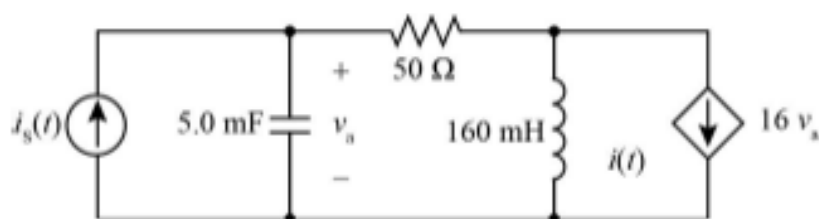


Figure 1: Depicts the circuit

As per Figure 1, the current is $i_s(t) = 2.88(\cos 100t - 48^\circ)$ mA

Resistance $R = 50 \Omega$

Capacitance $C = 5 \text{ mF}$

Inductance $L = 160 \text{ mH}$

Voltage is $16v_s$

Source current is $i_s(t)$

Now the above parameters in s -domain is are as follows:

$$\text{Current is } i_s(t) = \frac{j10^4}{j10^4 + 48}$$

Resistance $R = 50 \Omega$

Capacitance $C = 16 / j100$

Inductance $L = j250$

Voltage is $16v_s$

Source current is $i_s(s)$

As per the above s -domain parameters, the circuit diagram shown in Figure 1 is depicted as a s -domain as below:


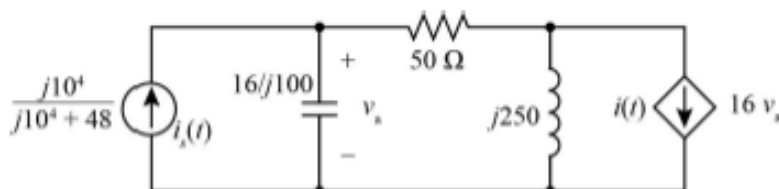


Figure 2: Depicts the s -domain circuit

P10.4-4**Solution:**

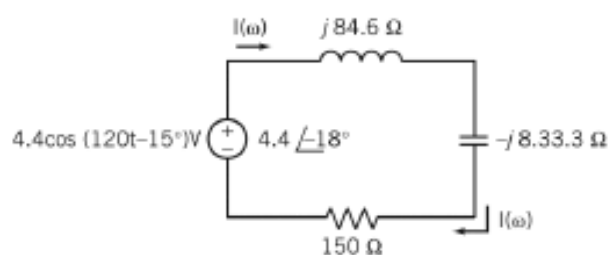The figure below shows the series LCR circuit:



The impedance of inductor is:

$$Z_L = j\omega L$$

Substitute 120 rad/s for ω , and 288 mH for L ,

$$\begin{aligned} Z_L &= j(120 \text{ rad/s})(288 \text{ mH}) \left(\frac{10^{-3} \text{ H}}{1 \text{ mH}} \right) \\ &= j34.6 \Omega \end{aligned}$$

The impedance of the capacitor is:

$$Z_C = \frac{-j}{\omega C}$$

Substitute 120 rad/s for ω , and 10 μF for C ,

$$\begin{aligned} Z_C &= \frac{-j}{(120 \text{ rad/s})(10 \mu\text{F}) \left(\frac{10^{-6} \text{ F}}{1 \mu\text{F}} \right)} \\ &= -j833.3 \Omega \end{aligned}$$

The input voltage $v(t) = 4.4 \cos(120t - 15^\circ)$ can be written in Cartesian form as:

$$\begin{aligned} V(\omega) &= 4.4 \angle -15^\circ \\ &= 4.4 \cos(-15^\circ) + j4.4 \sin(-15^\circ) \\ &= 4.25 - j1.13 \end{aligned}$$

The inductor, capacitor and the resistor are in series, and the net impedance of the three elements is:

$$\begin{aligned} Z &= Z_C + Z_L + R \\ &= -j833.3 \, \Omega + j34.6 \, \Omega + 150 \, \Omega \\ &= 150 \, \Omega - j799 \, \Omega \end{aligned}$$

The current in frequency domain is:

$$\begin{aligned} \mathbf{I}(\omega) &= \frac{\mathbf{V}(\omega)}{Z} \\ &= \frac{4.25 - j1.13 \, \text{V}}{150 - j799 \, \Omega} \\ &= \left(\frac{4.25 - j1.13}{(150)^2 - (j799)^2} \right) (150 + j799) \\ &= 2.33 - j4.88 \, \text{mA} \end{aligned}$$

The phase angle of current $\mathbf{I}(\omega)$ is:

$$\begin{aligned} \theta &= \tan^{-1} \left(\frac{-4.88}{2.33} \right) \\ &= -64.4^\circ \end{aligned}$$

The amplitude of current $\mathbf{I}(\omega)$ is:

$$\begin{aligned} I &= \sqrt{(2.33 \, \text{mA})^2 + (-4.88 \, \text{mA})^2} \\ &= 5.40 \, \text{mA} \end{aligned}$$

Therefore, the current $\mathbf{I}(\omega)$ in frequency domain is:


$$\begin{aligned} \mathbf{I}(\omega) &= I \angle \theta \\ \mathbf{I}(\omega) &= 5.40 \, \text{mA} \angle -64.4^\circ \end{aligned}$$

The current $i(t)$ is:

$$\begin{aligned} i(t) &= I \cos(120t - \theta) \\ &= 5.40 \, \text{mA} \cos(120t - 64.4^\circ) \end{aligned}$$

P10.4-5**Solution:**

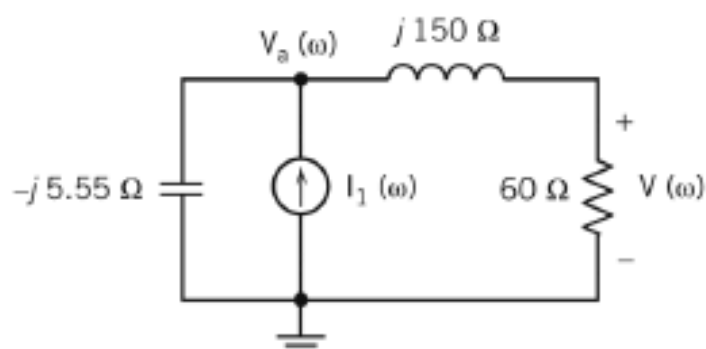The figure below shows the given circuit:



The impedance of inductor is:

$$Z_L = j\omega L$$

Substitute 6000 rad/s for ω , and 25 mH for L ,

$$\begin{aligned} Z_L &= j(6000 \text{ rad/s})(25 \text{ mH}) \left(\frac{10^{-3} \text{ H}}{1 \text{ mH}} \right) \\ &= j150 \Omega \end{aligned}$$

The impedance of the capacitor is:

$$Z_C = \frac{-j}{\omega C}$$

Substitute 6000 rad/s for ω , and 30 μF for C ,

$$\begin{aligned} Z_C &= \frac{-j}{(6000 \text{ rad/s})(30 \mu\text{F}) \left(\frac{10^{-6} \text{ F}}{1 \mu\text{F}} \right)} \\ &= -j5.55 \Omega \end{aligned}$$

The phasor representation of current $i(t) = 180 \cos(6000t)$ is:

$$\begin{aligned} \mathbf{I}(\omega) &= 180 \angle 0^\circ \\ &= 180 \cos(0^\circ) - j180 \sin(0^\circ) \\ &= 180 \text{ mA} \end{aligned}$$

Apply Nodal analysis at node 'a':

$$\begin{aligned}\frac{V_a(\omega)}{Z_c} + \frac{V_a(\omega)}{Z_L + R} &= I(\omega) \\ V_a(\omega) &= \frac{I(\omega)}{\left(\frac{1}{Z_c} + \frac{1}{Z_L + R}\right)} \\ &= \frac{I(\omega)(Z_c)(Z_L + R)}{Z_c + Z_L + R}\end{aligned}$$

Substitute the values,

$$\begin{aligned}V_a(\omega) &= \frac{(180 \text{ mA})(-j5.55 \Omega)(j150 \Omega + 60 \Omega)}{-j5.55 \Omega + j150 \Omega + 60 \Omega} \\ &= \frac{150 - j60 \text{ A}\Omega^2}{60 \Omega + j144.5 \Omega}\end{aligned}$$

The voltage division rule between the inductor and the resistor gives the voltage $V(\omega)$ as:

$$V(\omega) = \left(\frac{R}{R + Z_L}\right) V_a(\omega)$$

Substitute the values,

$$\begin{aligned}V(\omega) &= \left(\frac{60 \Omega}{60 \Omega + j150 \Omega}\right) \left(\frac{150 - j60 \text{ A}\Omega^2}{60 \Omega + j144.5 \Omega}\right) \\ &= \frac{9000 - j3600 \text{ A}\Omega^3}{-18075 + j17670 \Omega^2} \\ &= \frac{1800 - j720 \text{ A}\Omega^3}{3615 + j3534 \Omega^2} \\ &= 0.51 + j0.14 \text{ V}\end{aligned}$$

The phase angle of the voltage $V(\omega)$ is:

$$\begin{aligned}\theta &= \tan^{-1}\left(\frac{0.14}{0.51}\right) \\ &= 16^\circ\end{aligned}$$

The amplitude of voltage $V(\omega)$ is:

$$V = \sqrt{(0.14 \text{ V})^2 + (0.51 \text{ V})^2} \\ = 0.65 \text{ V}$$

The voltage across the resistor is:


$$v(t) = V \cos(6000t + \theta) \\ = 0.65 \cos(6000t + 16^\circ)$$

Therefore, the voltage across the resistor is $\boxed{0.65 \cos(6000t + 16^\circ)}$.

P10.4-6

Solution:

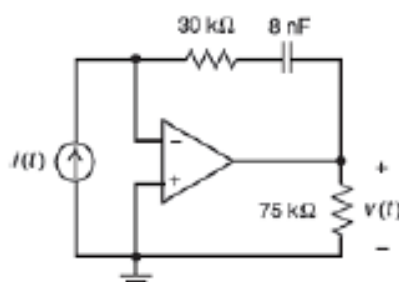The figure below shows the op-amp circuit:



The net impedance of the series RL circuit is:

$$Z = \frac{-j}{\omega C} + R$$

Substitute the given values,

$$Z = \frac{-j}{(15000 \text{ rad/s})(8 \text{ nF})\left(\frac{10^{-9} \text{ F}}{1 \text{ nF}}\right)} + 30 \text{ k}\Omega \\ = -j(8333.3 \Omega)\left(\frac{10^{-3} \text{ k}\Omega}{1 \Omega}\right) + 30 \text{ k}\Omega \\ = 30 \text{ k}\Omega - j8.33 \text{ k}\Omega$$

The phasor representation of current $i(t) = 120 \cos(15000t) \mu\text{A}$ is:

$$\begin{aligned} \mathbf{I}(\omega) &= 120 \angle 0^\circ \\ &= 120 \mu\text{A} \cos(0^\circ) + j120 \mu\text{A} \sin(0^\circ) \\ &= 120 \mu\text{A} \end{aligned}$$

KCL at node 'a' gives:

$$\mathbf{I}(\omega) = \frac{\mathbf{V}(\omega) - \mathbf{V}_a(\omega)}{\mathbf{Z}} + \mathbf{I}_-(\omega)$$

For an ideal op-amp, the voltage at the non-inverting terminal is equal to the voltage at the inverting terminal. Therefore, $\mathbf{V}_a(\omega) = 0$. Also, no current passes through these terminal and account for the fact that $\mathbf{I}_-(\omega) = 0$.

Substitute the same in equation $\mathbf{I}(\omega) = \frac{\mathbf{V}(\omega) - \mathbf{V}_a(\omega)}{\mathbf{Z}} + \mathbf{I}_-(\omega)$,

$$\begin{aligned} \mathbf{I}(\omega) &= \frac{\mathbf{V}(\omega) - 0}{\mathbf{Z}} + 0 \\ \mathbf{V}(\omega) &= \mathbf{I}(\omega) \mathbf{Z} \end{aligned}$$

Substitute $120 \mu\text{A}$ for $\mathbf{I}(\omega)$, and $30 \text{ k}\Omega - j8.33 \text{ k}\Omega$ for \mathbf{Z} ,

$$\begin{aligned} \mathbf{V}(\omega) &= 120 \mu\text{A} (30 \text{ k}\Omega - j8.33 \text{ k}\Omega) \\ &= (120 \mu\text{A}) \left(\frac{10^{-6} \text{ A}}{1 \mu\text{A}} \right) (30 \text{ k}\Omega) \left(\frac{10^3 \Omega}{1 \text{ k}\Omega} \right) - j(120 \mu\text{A}) \left(\frac{10^{-6} \text{ A}}{1 \mu\text{A}} \right) (8.33 \text{ k}\Omega) \left(\frac{10^3 \Omega}{1 \text{ k}\Omega} \right) \\ &= 3.6 \text{ V} - j0.99 \text{ V} \end{aligned}$$

The phase of the voltage $\mathbf{V}(\omega)$ is:

$$\begin{aligned} \theta &= \tan^{-1} \left(\frac{-0.99}{3.6} \right) \\ &= -15.6^\circ \end{aligned}$$

The amplitude of the voltage $\mathbf{V}(\omega)$ is:

$$V = \sqrt{(3.6 \text{ V})^2 + (-0.99 \text{ V})^2}$$

$$= 3.73 \text{ V}$$

The voltage in time domain is:

$$v(t) = V \cos(15000t + \theta)$$

$$= 3.73 \cos(15000t - 15.6^\circ) \text{ V}$$

Therefore, the voltage across the $75 \text{ k}\Omega$ resistor is $\boxed{3.73 \cos(15000t - 15.6^\circ) \text{ V}}$.

P 10.4-7

Solution:

(a) $v = 15 \cos(400t + 30^\circ) \text{ V}$

$$i = 3 \sin(400t + 30^\circ) = 3 \cos(400t - 60^\circ) \text{ V}$$

v leads i by $90^\circ \Rightarrow$ element is an inductor

$$|Z_L| = \frac{v_{\text{peak}}}{i_{\text{peak}}} = \frac{15}{3} = 5 = \omega L = 400 L \Rightarrow \underline{L = 0.0125 \text{ H} = 12.5 \text{ mH}}$$

(b) i leads v by $90^\circ \Rightarrow$ the element is a capacitor

$$|Z_C| = \frac{v_{\text{peak}}}{i_{\text{peak}}} = \frac{8}{2} = 4 = \frac{1}{\omega C} = \frac{1}{900 C} \Rightarrow \underline{C = 277.77 \text{ }\mu\text{F}}$$

(c) $v = 20 \cos(250t + 60^\circ) \text{ V}$

$$i = 5 \sin(250t + 150^\circ) = 5 \cos(250t + 60^\circ) \text{ A}$$


Since v & i are in phase \Rightarrow element is a resistor

$$\therefore R = \frac{v_{\text{peak}}}{i_{\text{peak}}} = \frac{20}{5} = \underline{4 \text{ }\Omega}$$

P10.4-8

Solution:

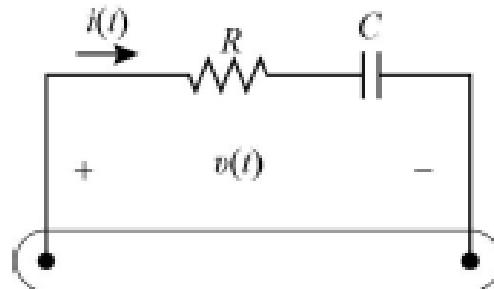In order to find the values of resistances and capacitances proceed as follows:



Impedance Z is given as follows:

$$Z = \frac{v(t)}{i(t)}$$

Here,

Voltage signal $v(t)$ is $30\cos(30t + 30^\circ)$ V

Current signal $i(t)$ is $2.2\cos(30t + 78^\circ)$ A

Substitute the corresponding values to obtain Z as follows:

$$\begin{aligned} Z &= \frac{v(t)}{i(t)} \\ &= \frac{30\angle 30^\circ}{2.2\angle 78^\circ} \\ &= 9.125 - j0.134 \end{aligned}$$

Impedance Z is also represented as:

$$Z = R - j\omega C$$

Here,

Resistance is R

Capacitance is C

Angular frequency ω is 30

Now resistance R is given as:

$$Z = R - j\omega C$$

$$9.125 - j0.134 = R - j\omega C$$

$$\Rightarrow R = 9.125 \Omega$$

Hence, resistance R is 9.125Ω

Capacitance C is given as:

$$\begin{aligned}
 Z &= R - j\omega C \\
 9.125 - j0.134 &= R - j\omega C \\
 \Rightarrow -j\omega C &= -j0.134 \\
 C &= \frac{0.134}{30} \\
 &= 4.467 \text{ mF}
 \end{aligned}$$

Hence, capacitance C is 4.467 mF

P10.4-9

Solution:

The impedance between nodes a and b is given by

$$18 + j(10)(2.5) = 18 + j25 = 30.8 \angle 54.2^\circ$$

To find the impedance between nodes b and c we first find the impedance of the capacitor:

$$-j \frac{1}{(10)(0.004)} = -j \frac{1}{0.04} = -j25$$

then

$$\frac{9(-j25)}{9 - j25} = \frac{-j225}{26.57 \angle -70.2^\circ} = \frac{225 \angle -90^\circ}{26.57 \angle -70.2^\circ} = 8.47 \angle -19.8^\circ \Omega$$

The impedance between nodes c and d is given by


$$\begin{aligned}
 \frac{(5)(j(10)(0.88))}{5 + j(10)(0.8)} - j \frac{1}{(10)(0.005)} &= \frac{j40}{5 + j8} - j \frac{1}{0.05} = \frac{j40}{5 + j8} \left(\frac{5 - j8}{5 - j8} \right) - j20 \\
 &= \frac{320 + j200}{25 + 64} - j20 \\
 &= 3.60 + j2.25 - j20 = 3.60 - j17.75 \Omega
 \end{aligned}$$

So

$$A = 30.8 \text{ V}, B = 8.47 \Omega, a = 3.57 \Omega \text{ and } b = -17.75 \Omega.$$


P10.4-10

Solution:

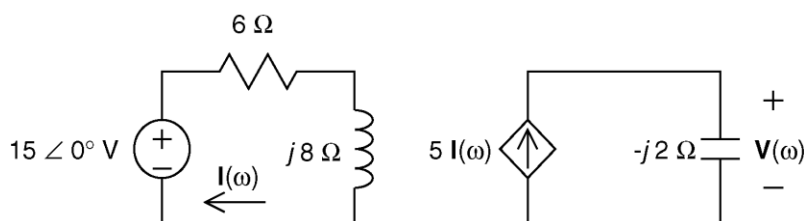

P 10.4-11

Solution:

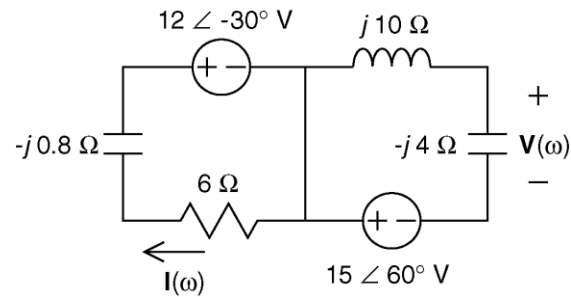

P 10.4-12

Solution:

$$Z = \frac{V}{-I} = \frac{10 \angle 40^\circ}{-2 \times 10^{-3} \angle -165^\circ} = -5000 \angle 205^\circ \Omega = 4532 + j2113 = R + j\omega L$$


$$\text{so } \underline{R = 4532 \Omega} \text{ and } \underline{L = \frac{2113}{\omega} = \frac{2113}{2 \times 10^6} = 1.057 \text{ mH}}$$

Section 10.5 Series and Parallel Impedances

P10.5-1

Solution:

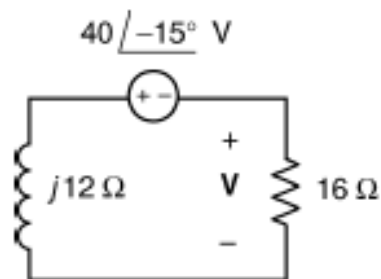Represent the circuits in the frequency domain using phasors and impedances:



$$\text{Using voltage division: } V = -\frac{16}{16 + j12} (40 \angle -15^\circ) = \frac{16 \angle 180^\circ}{20 \angle 36.9^\circ} (40 \angle -15^\circ) = 32 \angle 128.1^\circ \text{ V}$$


In the time domain

$$v(t) = 32 \cos(250t - 57.9^\circ) \text{ V}$$

P10.5-2


Solution:

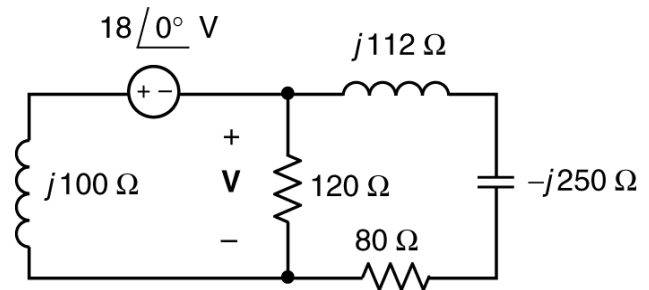Represent the circuit in the frequency domain:




Replace the series impedances at the right of the circuit by an equivalent impedance
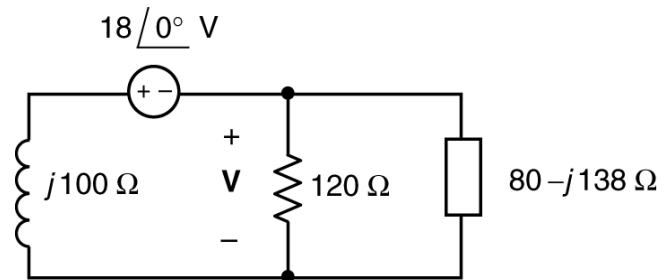
$$\mathbf{Z}_s = j112 + (-j250) + 80 = 80 - j138 \, \Omega$$



Replace the parallel impedances at right of the circuit by an equivalent impedance
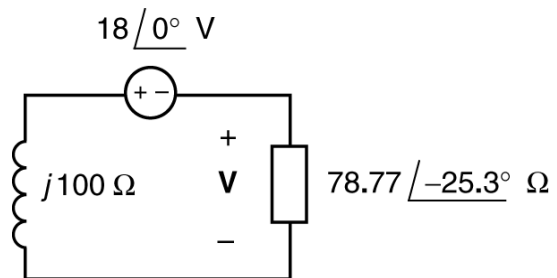
$$\begin{aligned} \mathbf{Z}_p &= \frac{(80 - j138)120}{80 - j138 + 120} = \frac{(80 - j138)120}{200 - j138} \\ &= \frac{(159.51 \angle -59.9^\circ)120}{242.99 \angle -34.6^\circ} \\ &= 78.77 \angle 25.3^\circ \, \Omega \end{aligned}$$



Using voltage division

$$\mathbf{V} = -\frac{78.77 \angle -25.3^\circ}{j100 + 78.77 \angle -25.3^\circ} 18 \angle 0^\circ = -\frac{78.77 \angle -25.3^\circ}{97.325 \angle 42.97^\circ} 18 \angle 0^\circ = 14.57 \angle 111.73^\circ \, \text{V}$$


In the time domain

$$v(t) = 14.57 \cos(800t + 111.7^\circ) \, \text{V}$$

(checked using LNAP)

P10.5-3**Solution:**

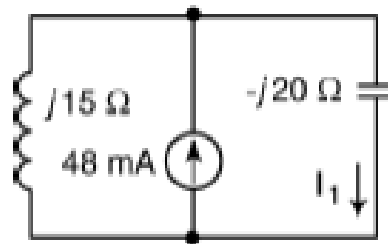Represent the circuits in the frequency domain using phasors and impedances:




Using current division

$$\mathbf{I}_1 = \frac{j15}{j15 - j20} (48 \angle 0^\circ) = \frac{15}{-5} (48 \angle 0^\circ) = 144 \angle 180^\circ \text{ mA}$$

In the time domain

$$i_1(t) = 144 \cos(25t + 180^\circ) \text{ mA}$$

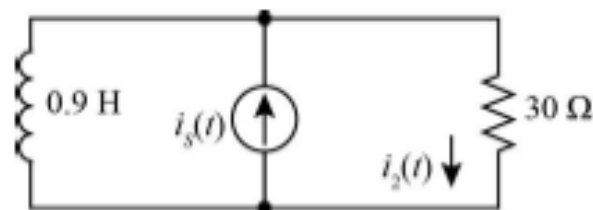P10.5-4**Solution:**In order to find current $i_2(t)$ proceed as follows:Now current $i_2(t)$ as per Figure 1 is as follows:

$$i_2(t) = \frac{i_s(t)}{R + j34.2}$$

Here,


Source Current $i_s(t)$ is $72 \cos(38t) \text{ mA}$ Resistance R is 30Ω Inductance L is 0.9 H Substitute the corresponding values to obtain $i_2(t)$ as follows:

$$\begin{aligned}
 i_2(t) &= \frac{i_s(t)}{30 + j34.2} \\
 &= \frac{72\angle 0^\circ j(38)(0.9)}{30 + j34.2} \\
 &= \frac{(72\angle 0^\circ)(34.2\angle 90^\circ)}{45.493\angle 48.743^\circ} \\
 &= \frac{2462.4\angle 90^\circ}{45.493\angle 48.743^\circ} \\
 &= 54.13\angle 41.257^\circ \\
 &= 54.13\cos(38t + 41.257) \text{ A}
 \end{aligned}$$

Hence, current $i_2(t)$ is $\boxed{54.13\cos(38t + 41.257) \text{ mA}}$

P10.5-5

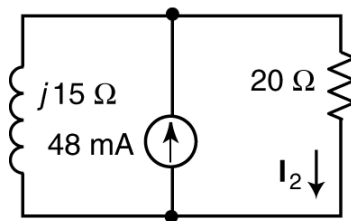Solution: Represent the circuits in the frequency domain using phasors and impedances:



Using current division

$$\mathbf{I}_2(\omega) = \frac{j15}{20 + j15} (48\angle 0^\circ) = \frac{15\angle 90^\circ}{25\angle 36.9^\circ} (48\angle 0^\circ) = 28.8\angle 53.1^\circ \text{ mA}$$

In the time domain $i_2(t) = 28.8\cos(25t + 53.1^\circ) \text{ mA}$

P10.5-6**Solution:**Consider Z_1 :

$$R_1 - j\frac{1}{20C} = 15.3\angle -24.1^\circ = 14 - j6.25 \Rightarrow R_1 = 14\ \Omega \text{ and } C = \frac{1}{20(6.25)} = 0.008\text{ F} = 8\text{ mF}$$

Next consider Z_2 :

$$\frac{1}{\frac{1}{R_2} + \frac{1}{j20L}} = 14.4\angle 53.1^\circ \Rightarrow \frac{1}{R_2} + \frac{1}{j20L} = \frac{1}{14.4\angle 53.1^\circ} = \frac{1}{14.4}\angle -53.1^\circ = 0.05556 - j0.04167$$

Equating coefficients gives

$$R_2 = \frac{1}{0.05556} = 18\ \Omega \text{ and } L = \frac{1}{20(0.04167)} = 1.2\text{ H}$$

Next, consider the voltage divider:


$$\begin{aligned} A\angle 31.5^\circ &= \frac{14.4\angle 36.9^\circ}{15.3\angle -24.1^\circ + 14.4\angle 36.9^\circ} (15\angle 0^\circ) = \frac{(15)(14.4)\angle 36.9^\circ}{(14 - j6.25)(11.52 + j8.64)} \\ &= \frac{216\angle 36.9^\circ}{25.52 + j2.39} \\ &= \frac{216\angle 36.9^\circ}{25.63\angle 5.4^\circ} = 8.43\angle 31.5^\circ\text{ V} \end{aligned}$$

In the time domain, $v(t) = 8.43 \cos(20t + 31.5^\circ)\text{ V}$.

P 10.5-7

Solution:

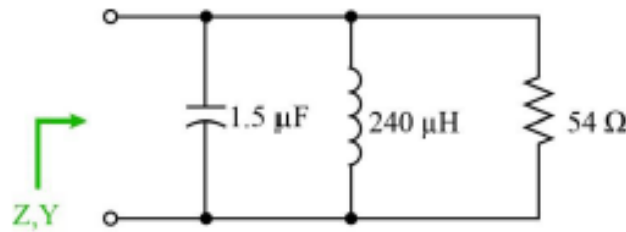In order to determine the impedance and admittance proceed as follows:



As per the figure shown in loop 1 above the impedance Z is given as follows:

$$\begin{aligned} Z &= R \parallel X_L \parallel X_C \\ &= R \parallel 2\pi f(L) \parallel 2\pi f(C) \end{aligned}$$

Here,

Inductance L is $240 \mu\text{H}$

Capacitance C is $1.5 \mu\text{F}$

Frequency f is 15 kHz

Resistance R is 54Ω

Substitute the corresponding values to obtain Z as follows:

$$\begin{aligned} Z &= R \parallel 2\pi f(L) \parallel 2\pi f(C) \\ \frac{1}{Z} &= \frac{1}{R} + j\frac{1}{X_L} - jX_C \\ &= \frac{1}{54 \Omega} + j\left[\frac{1}{2\pi(15 \text{ kHz})(240 \mu\text{H})} - 2\pi(15 \text{ kHz})(1.5 \mu\text{F})\right] \\ &= 0.02 - j7.10 \\ Z &= \frac{1}{0.02 - j7.10} \\ &= 3.97 \times 10^{-4} + j0.14 \Omega \end{aligned}$$

Admittance Y is given as follows:

$$Y = \frac{1}{Z}$$


$$= 0.02 - j7.10 \text{ S}$$

Hence, the admittance Y is $\boxed{0.02 - j7.10 \text{ S}}$

P 10.5-9

Solution:

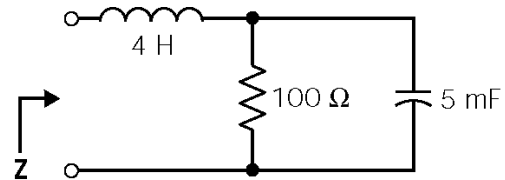
Replace series and parallel capacitors by an equivalent capacitor and series inductors by an equivalent inductor:



Then

$$Z = j\omega 4 + \frac{100 \frac{1}{j\omega(5 \times 10^{-3})}}{100 + \frac{1}{j\omega(5 \times 10^{-3})}} = j\omega 4 + \frac{100 \left(-j \frac{200}{\omega} \right)}{100 + \left(-j \frac{200}{\omega} \right)} = j\omega 4 + \frac{-j \frac{200}{\omega}}{1 - j \frac{2}{\omega}} \times \frac{1 + j \frac{2}{\omega}}{1 + j \frac{2}{\omega}}$$

$$Z = j\omega 4 + 100 \frac{\frac{4}{\omega^2} - j \frac{2}{\omega}}{1 + \frac{4}{\omega^2}} = j\omega 4 + 100 \frac{4 - j2\omega}{4 + \omega^2} = \frac{400}{4 + \omega^2} + j \left(4\omega - \frac{200\omega}{4 + \omega^2} \right)$$

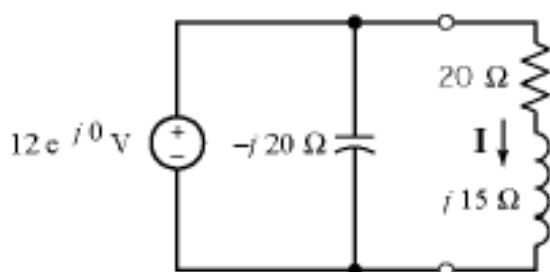P 10.5-10**Solution:**

$$j(2\pi \cdot 796)(3 \cdot 10^{-3}) = j15 \, \Omega$$

$$\mathbf{I} = \frac{12}{20 + j15} = 0.48 \angle -37^\circ \text{ A}$$

$$i(t) = 0.48 \cos(2\pi \cdot 796t - 37^\circ) \text{ A}$$

P 10.5-11**Solution:**


$$\mathbf{Z}_1 = R = 8 \, \Omega, \quad \mathbf{Z}_2 = j3L, \quad \mathbf{I} = B \angle -51.87^\circ \text{ and } \mathbf{I}_s = 2 \angle -15^\circ \text{ A}$$

$$\frac{\mathbf{I}}{\mathbf{I}_s} = \frac{B \angle -51.87^\circ}{2 \angle -15^\circ} = \frac{\mathbf{Z}_1}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{8}{8 + j3L} = \frac{8 \angle 0^\circ}{\sqrt{8^2 + (3L)^2} \angle \tan^{-1}\left(\frac{3L}{8}\right)}$$

Equate the magnitudes and the angles.

$$\text{angles: } +36.87 = +\tan^{-1}\left(\frac{3L}{8}\right) \Rightarrow \underline{L=2 \text{ H}}$$

$$\text{magnitudes: } \frac{8}{\sqrt{64+9L^2}} = \frac{B}{2} \Rightarrow \underline{B=1.6}$$

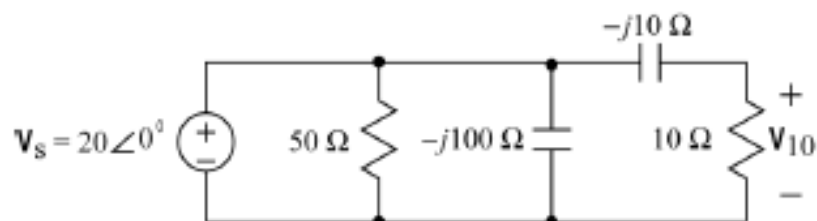P 10.5-12**Solution:**


$$\begin{aligned} \mathbf{V}_{10} &= \mathbf{V}_s \left(\frac{10}{10 - j10} \right) \\ &= 20 \angle 0^\circ \left(\frac{10}{10\sqrt{2} \angle -45^\circ} \right) \\ &= 10\sqrt{2} \angle 45^\circ \end{aligned}$$

$$v_{10}(t) = 10\sqrt{2} \cos(100t + 45^\circ) \text{ V}$$

P 10.5-13

Solution:

(a)

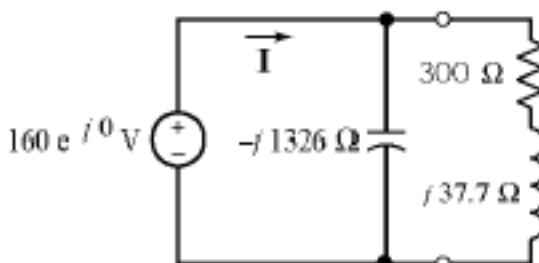


$$\mathbf{I} = \frac{160 \angle 0^\circ}{\frac{(-j1326)(300+j37.7)}{-j1326 + 300+j37.7}} = \frac{160 \angle 0^\circ}{303 \angle -5.9^\circ}$$

$$= 0.53 \angle 5.9^\circ \text{ A}$$

$$\underline{i(t) = 0.53 \cos(120\pi t + 5.9^\circ) \text{ A}}$$

(b)

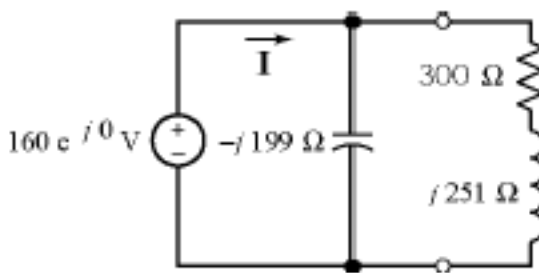

$$\mathbf{I} = \frac{160 \angle 0^\circ}{\frac{(-j199)(300+j251)}{-j199+300+j251}} = \frac{160 \angle 0^\circ}{256 \angle -59.9^\circ}$$

$$= 0.625 \angle 59.9^\circ \text{ A}$$

$$\underline{i(t) = 0.625 \cos(800\pi t + 59.9^\circ) \text{ A}}$$

P 10.5-14

Solution:

In order to find the steady state current $i(t)$ proceed as follows:

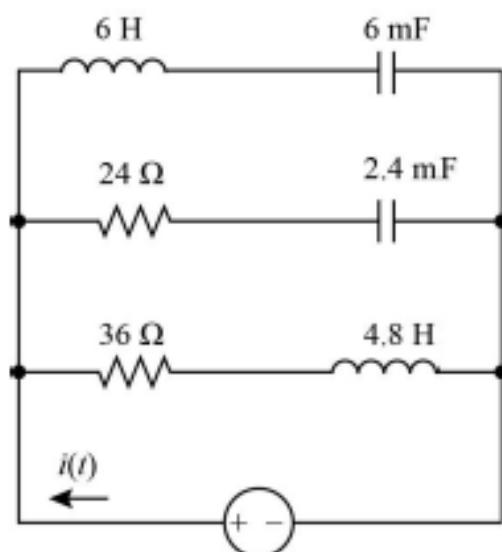


Figure 1: Depicts the circuit

As per Figure 1 the steady state current $i(t)$ is as follows:

$$i(t) = \frac{v(t)}{R + j(\omega)(L)}$$

Here,

Voltage $v(t)$ is $6\cos(12t + 45^\circ)$ V

Resistance R is $36\ \Omega$

Inductance L is 4.8 H

Angular frequency ω is 12 Hz


Substitute the corresponding values to obtain $i(t)$ as follows:

$$\begin{aligned} i(t) &= \frac{v(t)}{36 + j(R)(L)} \\ &= \frac{6\angle 45^\circ}{36 + j(12)(4.8)} \\ &= \frac{6\angle 45^\circ}{36 + j57.6} \\ &= \frac{6\angle 45^\circ}{67.925\angle 57.995^\circ} \\ &= 0.0883\angle -12.995^\circ \\ &= 88.3\cos(12t - 12.995^\circ) \text{ A} \end{aligned}$$

Hence, the steady state current $i(t)$ is $\boxed{88.3\cos(12t - 12.995^\circ) \text{ A}}$

P10.5-15**Solution:**

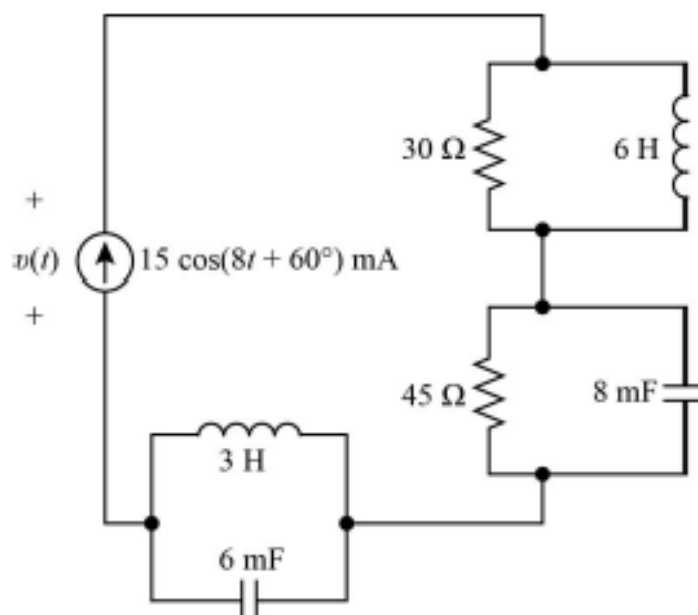In order to determine the steady state voltage $v(t)$ proceed as follows:



As per the figure above, for the circuit to have a steady state voltage the reactance due to the capacitors and the inductors combined must be zero.

Only the net resistance R_{net} is applicable and is given as:

$$\begin{aligned} R_{\text{net}} &= (30 + 45) \, \Omega \\ &= 75 \, \Omega \end{aligned}$$

$$\text{Current } i(t) = 15 \cos(8t + 60^\circ) \, \text{mA}$$


So the steady state voltage $v(t)$ is given as:

$$\begin{aligned} v(t) &= i(t) R_{\text{net}} \\ &= 15 \cos(8t + 60^\circ) \, \text{mA} (75 \, \Omega) \\ &= 75(15 \cos)(8t + 60^\circ) \, \text{mV} \end{aligned}$$

Hence, steady state voltage $v(t)$ is $\boxed{75(15 \cos(8t + 60^\circ)) \text{mV}}$

P10.5-16**Solution:**

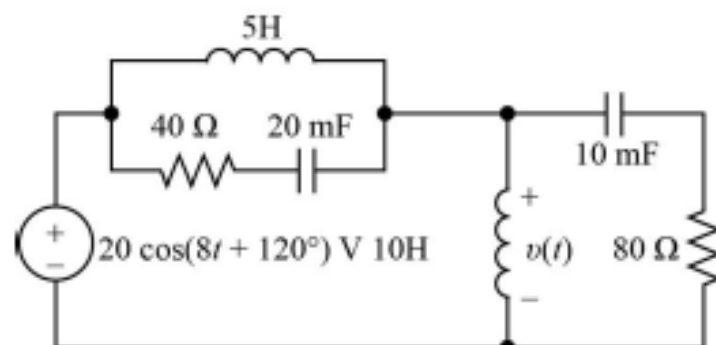In order to determine the steady state voltage $v(t)$ proceed as follows:



As per the figure above, for the circuit has the angular frequency $\omega = 8$

The reactance for inductance 5 H is $[j\omega L = j(8)(5 \text{ H})] = j40 \, \Omega$

The reactance for capacitance 20 mF is $\left[\frac{1}{j\omega C} = \frac{1}{j(8)(20 \text{ mF})} \right] = -j6.125 \, \Omega$

So the net reactance Z_1 is as follows:

$$\begin{aligned} Z_1 &= 40 \parallel 40 - j6.125 \\ &= 20 - j6.125 \, \Omega \end{aligned}$$

As per the figure above, for the circuit has the angular frequency $\omega = 8$

The reactance for inductance 10H is $[j\omega L = j(8)(10 \text{ H})] = j80 \Omega$

The reactance for capacitance 10 mF is $\left[\frac{1}{j\omega C} = \frac{1}{j(8)(10 \text{ mF})} \right] = j12.5 \Omega$

So the net reactance Z_2 is as follows:

$$\begin{aligned} Z_2 &= 80 \parallel 80 - j12.5 \\ &= 46.73 + j40.57 \Omega \end{aligned}$$

Current $i(t)$ is given as:

$$\begin{aligned} i(t) &= \frac{120}{Z_1 + Z_2} \\ &= \frac{120}{23.365 + j20.285 + 46.73 + j40.57} \\ &= -0.076365 + j0.13227 \text{ A} \end{aligned}$$

Voltage $v_2(t)$ across impedance Z_2 is as follows:

$$\begin{aligned} v_2(t) &= i(t)Z_2 \\ &= -0.076365 + j0.13227 \text{ A} [46.73 + j40.57 \Omega] \\ &= -8.9346 + j3.0827 \text{ V} \end{aligned}$$

Now the steady state voltage $v(t)$ is given as follows:

$$\begin{aligned} v(t) &= -8.9346 + j3.0827 \text{ V} \\ &= 9.45 \text{ V} \end{aligned}$$

Hence, the steady state voltage $v(t)$ is $\boxed{9.45 \text{ V}}$

P 10.5-17

Solution:

In order to find the steady state response $i_1(t)$ proceed as follows:

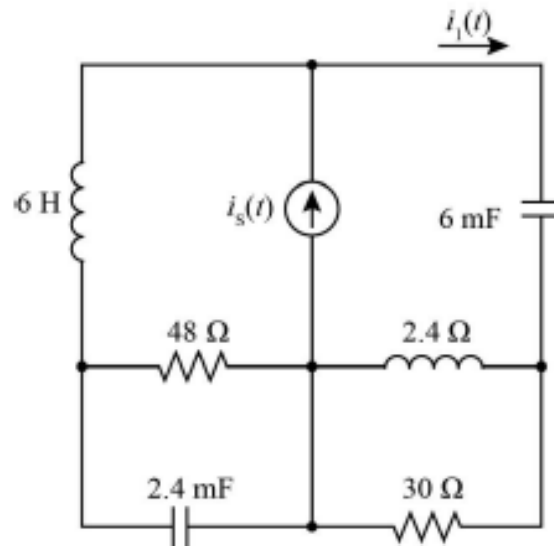


Figure 1: Depicts the circuit

The equivalent circuits are as follows:

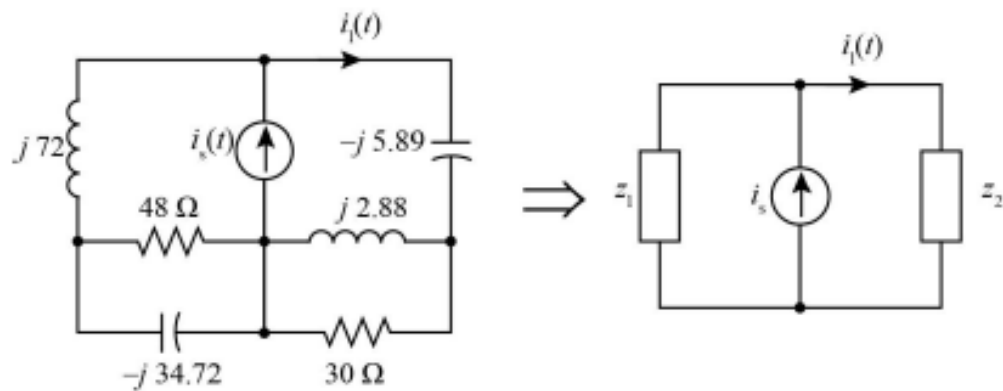


Figure 2: Depicts the equivalent circuit

Source current signal $i_s(t) = 30 \cos(12t + 30^\circ) \text{ mA}$

Here, the angular frequency $\omega = 12$

Inductance L in Laplace domain is $j\omega L$

Capacitance C in Laplace domain is $\frac{1}{j\omega C}$

Impedance Z_1 as per Figure 2 is given as follows:

$$\begin{aligned} Z_1 &= j72 + 48 \parallel -j34.72 \\ &= 16.49 + j49.2 \end{aligned}$$

Impedance Z_2 as per Figure 2 is given as follows:

$$\begin{aligned} Z_2 &= -j3.89 + 30 \parallel -j28.8 \\ &= 14.4 + j11.61 \end{aligned}$$

Now as per the current division rule:

$$\begin{aligned} \bar{i}_1 &= \bar{i}_s \frac{Z_1}{Z_1 + Z_2} \\ &= 30 \angle 30^\circ \frac{16.49 + j49.2}{14.4 + j11.61} \\ &= 84.15 \angle 62.59^\circ \end{aligned}$$


So the steady state response $i_1(t)$ is $\boxed{84.15 \cos(12t + 62.59^\circ) \text{ mA}}$

P10.5-18

Solution:

$$\begin{aligned} \text{(a)} \quad i(t) &= \frac{80 + 80}{40 + (80 + 80)} 0.024 = 19.2 \text{ mA} \\ v(t) &= \frac{80}{80 + 80} \times (40 \parallel (80 + 80)) 0.024 = \frac{1}{2} (32) (0.024) = 0.384 \text{ V} \end{aligned}$$

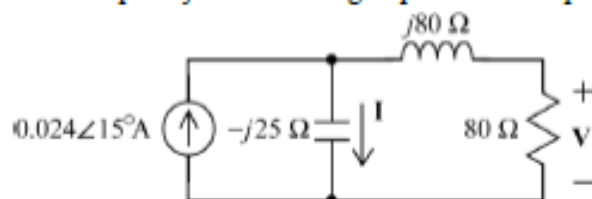(b) Represent the circuit in the frequency domain using impedances and phasors.



$$\mathbf{I} = \frac{80 + j80}{-j25 + (80 + j80)} \times 0.024 \angle 15^\circ = 0.028 \angle 25.5^\circ \text{ A}$$

$$\mathbf{V} = \frac{80}{80 + j80} \times [-j25 \parallel (80 + j80)] \times 0.024 \angle 15^\circ = 0.494 \angle -109.5^\circ \text{ V}$$

So $i(t) = 28 \cos(10t + 25.5^\circ) \text{ mA}$

and $v(t) = 0.494 \cos(10t - 109.5^\circ) \text{ V}$

(checked: LNAP 8/1/04)

P 10.5-19

Solution:

Represent the circuit in the frequency domain using phasors and impedances. The impedance capacitor is $\frac{1}{j(100)(0.5 \times 10^{-6})} = -j20,000$. When the switch is closed

$$17.89 \angle -26.6^\circ = \mathbf{V} = \frac{-j20,000}{R_2 - j20,000} \times 20 \angle 0^\circ$$

Equating angles gives

$$-26.6^\circ = -90^\circ - \tan^{-1} \left(\frac{-20,000}{R_2} \right) \Rightarrow R_2 = \frac{-20,000}{\tan(-63.4)} = 10015 \Omega$$

When the switch is open

$$14.14 \angle -45^\circ = \mathbf{V} = \frac{-j20,000}{R_1 + R_2 - j20,000} \times 20 \angle 0^\circ$$

Equating angles gives

$$-45^\circ = -90^\circ - \tan^{-1} \left(\frac{-20,000}{R_1 + R_2} \right) \Rightarrow R_1 + R_2 = \frac{-20,000}{\tan(-45^\circ)} = 20,000$$

So

$$R_1 = 20,000 - 10015 = 9985 \Omega$$

(checked: LNAP 8/2/04)

P10.5-20

Solution:


(a) Using KCL and then KVL gives

$$20 = 50i(t) + 40(5i(t)) \Rightarrow i(t) = \frac{20}{250} = 80 \text{ mA}$$

Then

$$v(t) = 40(5i(t)) = 200(0.08) = 16 \text{ V}$$

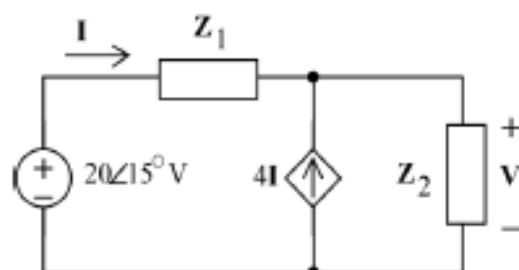(b) Represent the circuit in the frequency domain using phasors and impedances.



Where
$$Z_1 = 40 + j(10)3 + \frac{1}{j(10)(0.005)} = 40 + j10 = 41.23\angle 26.6^\circ \Omega$$

And
$$Z_2 = j(10)2 \parallel 10 = 8 + j4 = 8.944\angle 26.6^\circ \Omega$$

Using KCL and then KVL gives

$$20\angle 15^\circ = Z_1 I + 5Z_2 I \Rightarrow I = 0.234\angle -5.6^\circ \text{ A}$$

Then

$$V = Z_2 (5I) = 10.47\angle 21^\circ \text{ A}$$

so

$$i(t) = 0.234 \cos(10t - 5.6^\circ) \text{ A}$$


and

$$v(t) = 10.47 \cos(10t + 21^\circ) \text{ V}$$


(checked: 8/3/04)

P 10.5-21**Solution:**

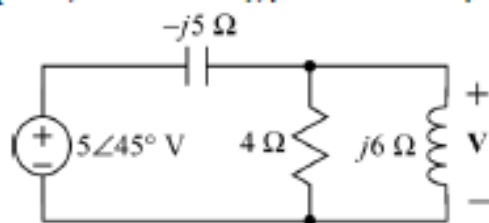Represent the circuit in the frequency domain using phasors and impedances.


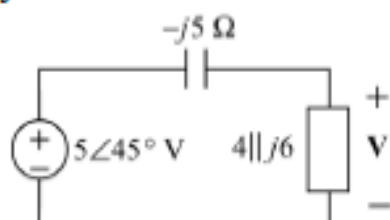
$$4 \parallel j6 = \frac{4(j6)}{4 + j6} = \frac{24 \angle 90^\circ}{7.2 \angle 56^\circ} = 3.33 \angle 34^\circ = 2.76 + j1.86 \Omega$$




Using voltage division

$$V = \frac{3.33 \angle 34^\circ}{-j5 + 2.76 + j1.86} \times 5 \angle 45^\circ = \frac{3.33 \angle 34^\circ}{2.76 - j3.14} \times 5 \angle 45^\circ = \frac{3.33 \angle 34^\circ}{4.18 \angle -48^\circ} \times 5 \angle 45^\circ = 3.98 \angle 127^\circ \text{ V}$$

The corresponding voltage in the time domain is

$$v(t) = 3.98 \cos(2t + 127^\circ) \text{ V}$$

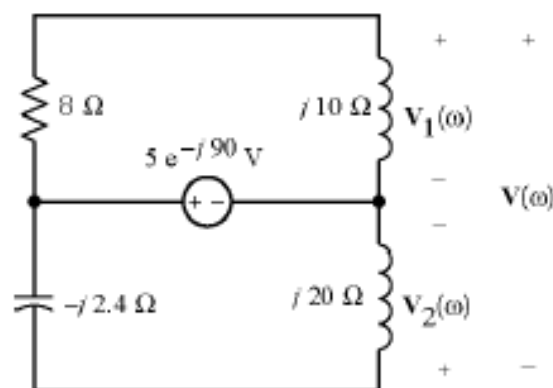P10.5-22**Solution:**

$$V_1(\omega) = \frac{j10}{8 + j10} 5e^{-j90} = 3.9e^{-j51} \text{ V}$$


$$V_2(\omega) = \frac{j20}{j20 - j2.4} 5e^{-j90} = 5.68e^{-j90} \text{ V}$$

$$V(\omega) = V_1(\omega) - V_2(\omega) = 3.9e^{-j51} - 5.68e^{-j90} = 3.58e^{j47} \text{ V}$$

Answer: $v(t) = 3.58 \cos(5t + 47.2^\circ) \text{ V}$

P10.5-23

Solution:

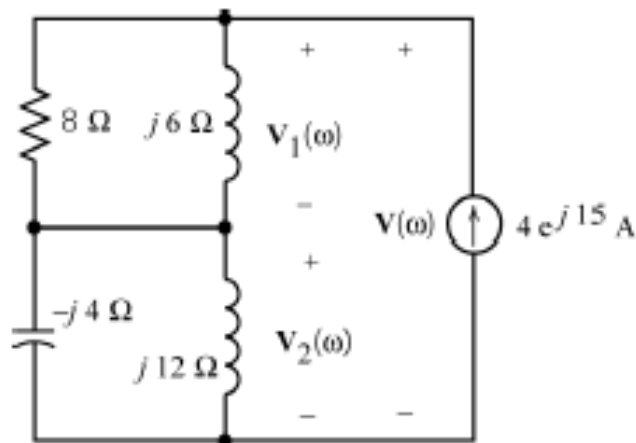

$$V_1(\omega) = \frac{8(j6)}{8+j6} 4e^{j15} = 19.2e^{j68} \text{ V}$$

$$V_2(\omega) = \frac{j12(-j4)}{j12-j4} 4e^{j15} = 24e^{-j75} \text{ V}$$


$$V(\omega) = V_1(\omega) + V_2(\omega) = 14.4e^{-j22} \text{ V}$$

Answer: $v(t) = 14.4 \cos(3t - 22^\circ) \text{ V}$

Section 10.6 Mesh and Node Equations

P10.6-1

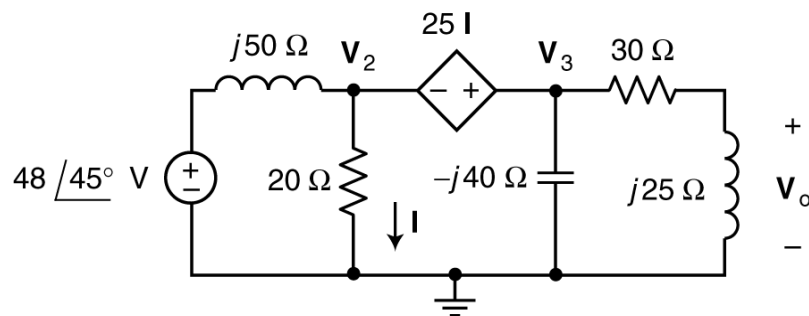Solution: Represent the circuit in the frequency domain as



The node voltages are $48\angle 45^\circ = V_1$, V_2 , V_3 and V_o . Express the dependent source voltage in terms of the node voltages:

$$V_3 - V_2 = 25I = 25\left(\frac{V_2}{20}\right) \Rightarrow V_3 = 2.25 V_2$$

Apply KCL to the supernode corresponding to the CCVS to get

$$\frac{48\angle 45^\circ - \mathbf{V}_2}{j50} = \frac{\mathbf{V}_2}{20} + \frac{\mathbf{V}_3 - \mathbf{V}_o}{30} + \frac{\mathbf{V}_3}{-j40}$$

$$\frac{48\angle 45^\circ}{j50} = \frac{\mathbf{V}_2}{j50} + \frac{\mathbf{V}_2}{20} + \frac{\mathbf{V}_3 - \mathbf{V}_o}{30} + \frac{\mathbf{V}_3}{-j40}$$

$$\frac{48\angle 45^\circ}{j50} = \left(\frac{1}{j50} + \frac{1}{20} \right) \mathbf{V}_2 + \left(\frac{1}{30} + \frac{1}{-j40} \right) \mathbf{V}_3 - \frac{1}{30} \mathbf{V}_o$$

$$\frac{48\angle 45^\circ}{j50} = \left(\frac{1}{j50} + \frac{1}{20} \right) \mathbf{V}_2 + \left(\frac{1}{30} + \frac{1}{-j40} \right) 2.25 \mathbf{V}_2 - \frac{1}{30} \mathbf{V}_o$$

$$\frac{48\angle 45^\circ}{j50} = \left(\frac{1}{j50} + \frac{1}{20} + \frac{2.25}{30} + \frac{2.25}{-j40} \right) \mathbf{V}_2 - \frac{1}{30} \mathbf{V}_o$$

Apply KCL at the right node of the 30 Ω resistor to get

$$\frac{\mathbf{V}_3 - \mathbf{V}_o}{30} = \frac{\mathbf{V}_o}{j25} \Rightarrow 0 = \left(-\frac{1}{30} \right) 2.25 \mathbf{V}_2 + \left(\frac{1}{30} + \frac{1}{j25} \right) \mathbf{V}_o$$

In matrix form

$$\begin{bmatrix} \frac{1}{j50} + \frac{1}{20} + \frac{2.25}{30} + \frac{2.25}{-j40} & -\frac{1}{30} \\ -\frac{2.25}{30} & \frac{1}{30} + \frac{1}{j25} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{V}_o \end{bmatrix} = \begin{bmatrix} \frac{48\angle 45^\circ}{j50} \\ 0 \end{bmatrix}$$

Solving, perhaps using MATLAB,

$$\begin{bmatrix} \mathbf{V}_2 \\ \mathbf{V}_o \end{bmatrix} = \begin{bmatrix} 10.18\angle -44.6^\circ \\ 14.67\angle 5.6^\circ \end{bmatrix} \text{ V}$$

P10.6-2

Solution:

Writing Node equations:

$$\frac{12\angle 45^\circ - \mathbf{V}_b}{j30} = \frac{\mathbf{V}_b}{20 - j25} + \frac{\mathbf{V}_b - \mathbf{V}_c}{15 - j30}$$

$$\frac{\mathbf{V}_b - \mathbf{V}_c}{15 - j30} + \frac{12\angle 45^\circ - \mathbf{V}_c}{40 + j20} = \frac{\mathbf{V}_c}{j40}$$

Rearranging:

$$\frac{12\angle 45^\circ}{j30} = \left(\frac{1}{j30} + \frac{1}{20-j25} + \frac{1}{15-j30} \right) \mathbf{V}_b - \left(\frac{1}{15-j30} \right) \mathbf{V}_c$$

$$\frac{12\angle 45^\circ}{40+j20} = - \left(\frac{1}{15-j30} \right) \mathbf{V}_b + \left(\frac{1}{15-j30} + \frac{1}{40+j20} + \frac{1}{j40} \right) \mathbf{V}_c$$

In matrix from:

$$\begin{bmatrix} \frac{1}{j30} + \frac{1}{20-j25} + \frac{1}{15-j30} & -\frac{1}{15-j30} \\ -\frac{1}{15-j30} & \frac{1}{15-j30} + \frac{1}{40+j20} + \frac{1}{j40} \end{bmatrix} \begin{bmatrix} \mathbf{V}_b \\ \mathbf{V}_c \end{bmatrix} = \begin{bmatrix} \frac{12\angle 45^\circ}{j30} \\ \frac{12\angle 45^\circ}{40+j20} \end{bmatrix}$$

Solving using MATLAB:

$$\mathbf{V}_b = 7.69\angle -19.8^\circ \text{ and } \mathbf{V}_c = 10.18\angle 7.7^\circ \text{ V}$$

Checked using LNAPAC

P10.6-3

Solution:

Mesh 1:

$$(40+j15)\mathbf{I}_1 + (25-j50)(\mathbf{I}_1 - \mathbf{I}_3) - 48\angle 75^\circ = 0$$

$$(65-j35)\mathbf{I}_1 - (25-j50)\mathbf{I}_3 = 48\angle 75^\circ$$

Mesh 2:

$$48\angle 75^\circ + (-j50)(\mathbf{I}_2 - \mathbf{I}_3) + (32+j16)\mathbf{I}_2 = 0$$

$$(32-j34)\mathbf{I}_2 + j50\mathbf{I}_3 = -48\angle 75^\circ$$

Mesh 3:

$$j40\mathbf{I}_3 - (-j50)(\mathbf{I}_2 - \mathbf{I}_3) - (25-j50)(\mathbf{I}_1 - \mathbf{I}_3) = 0$$

$$(-25+j50)\mathbf{I}_1 + j50\mathbf{I}_2 + (25-j160)\mathbf{I}_3 = 0$$

In matrix form:


$$\begin{bmatrix} 65-j35 & 0 & -25+j50 \\ 0 & 32-j34 & +j50 \\ -25+j50 & +j50 & 25-j60 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 48\angle 75^\circ \\ -48\angle 75^\circ \\ 0 \end{bmatrix}$$

Solving using MATLAB:

$$\mathbf{I}_1 = 0.794\angle 111^\circ, \mathbf{I}_2 = 0.790\angle -61.7^\circ \text{ and } \mathbf{I}_3 = 0.229\angle 176^\circ \text{ A}$$

P 10.6-4

Solution:

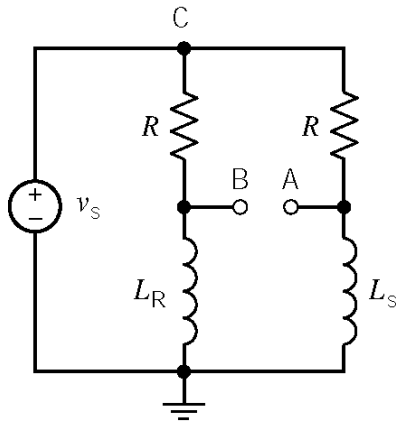

$$v_s = \sin(2\pi \cdot 400t) \text{ V}$$

$$R = 100 \Omega$$

$$L_R = 40 \text{ mH}$$

$$L_S = \begin{cases} 40 \text{ mH} & \text{door opened} \\ 60 \text{ mH} & \text{door closed} \end{cases}$$

With the door open $|\mathbf{V}_A - \mathbf{V}_B| = 0$ since the bridge circuit is balanced.

With the door closed $\mathbf{Z}_{L_R} = j(800\pi)(0.04) = j100.5 \Omega$ and $\mathbf{Z}_{L_S} = j(800\pi)(0.06) = j150.8 \Omega$.

The node equations are:

$$\text{KCL at node B: } \frac{\mathbf{V}_B - \mathbf{V}_C}{R} + \frac{\mathbf{V}_B}{\mathbf{Z}_{L_R}} = 0 \Rightarrow \mathbf{V}_B = \frac{j100.5}{j100.5 + 100} \mathbf{V}_C$$

$$\text{KCL at node A: } \frac{\mathbf{V}_A - \mathbf{V}_C}{R} + \frac{\mathbf{V}_A}{\mathbf{Z}_{L_S}} = 0$$

$$\text{Since } \mathbf{V}_C = |\mathbf{V}_s| = 1 \text{ V} \quad \mathbf{V}_B = 0.709 \angle 44.86^\circ \text{ V} \text{ and } \mathbf{V}_A = 0.833 \angle 33.55^\circ \text{ V}$$


Therefore

$$\begin{aligned} \mathbf{V}_A - \mathbf{V}_B &= 0.833 \angle 33.55^\circ - 0.709 \angle 44.86^\circ = (0.694 + j0.460) - (0.503 + j0.500) = 0.191 - j0.040 \\ &= 0.195 \angle -11.83^\circ \text{ V} \end{aligned}$$

P 10.6-5

Solution:

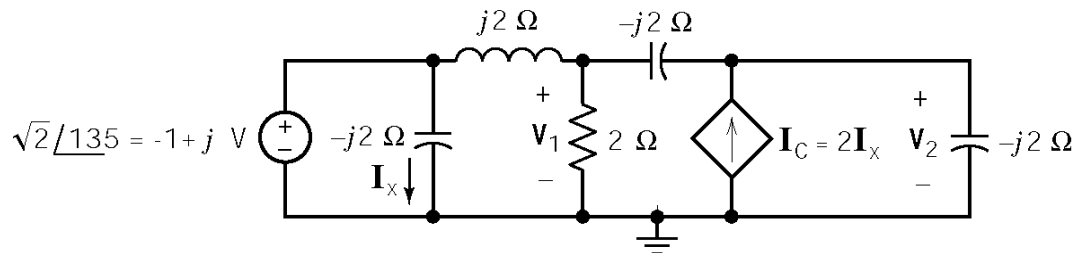Represent the circuit in the frequency domain



$$\text{The node equations are: } \frac{\mathbf{V}_1 - (-1 + j)}{j2} + \frac{\mathbf{V}_1}{2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j2} = 0$$

$$\frac{\mathbf{V}_2 - \mathbf{V}_1}{-j2} + \frac{\mathbf{V}_2}{-j2} - \mathbf{I}_C = 0$$

Also, expressing the controlling signal of the dependent source in terms of the node voltages yields

$$\mathbf{I}_x = \frac{-1+j}{-2j} \Rightarrow \mathbf{I}_C = 2\mathbf{I}_x = 2\left[\frac{-1+j}{-2j}\right] = -1-j \text{ A}$$

Solving these equations yields


$$\mathbf{V}_2 = \frac{-3-j}{1+j2} = \sqrt{2} \angle -135^\circ \text{ V} \Rightarrow v(t) = v_2(t) = \sqrt{2} \cos(40t - 135^\circ) \text{ V}$$

(checked: LNAP 7/19/04)

P10.6-6

Solution

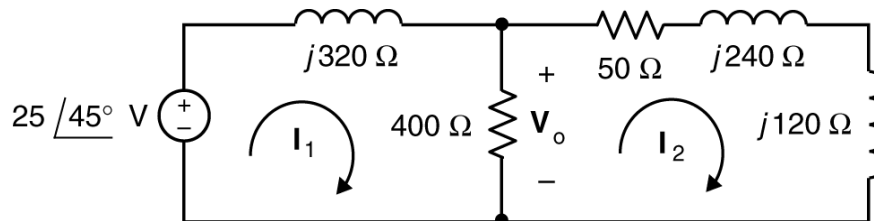Represent the circuit in the frequency domain:



Apply KVL to mesh 1: $j320\mathbf{I}_1 + 400(\mathbf{I}_1 - \mathbf{I}_2) - 25\angle 45^\circ = 0$

Apply KVL to mesh 2: $50\mathbf{I}_2 + j240\mathbf{I}_2 + j120\mathbf{I}_2 - 400(\mathbf{I}_1 - \mathbf{I}_2) = 0$

In matrix form:
$$\begin{bmatrix} 400 + j320 & -400 \\ -400 & 450 + j360 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 25\angle 45^\circ \\ 0 \end{bmatrix}$$

Solving using MATLAB:
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 47.5\angle -24.6^\circ \\ 33.0\angle -63.3^\circ \end{bmatrix} \text{ mA}$$

Using Ohm's Law $\mathbf{V}_o = 400(\mathbf{I}_1 - \mathbf{I}_2) = 12\angle 18.8^\circ \text{ V}$


In the time domain $i_1(t) = 47.5 \cos(40t - 24.6^\circ) \text{ mA}$, $i_2(t) = 33 \cos(40t - 63.3^\circ) \text{ mA}$

and $v_o(t) = 12 \cos(40t + 18.8^\circ) \text{ V}$

P10.6-7

Solution

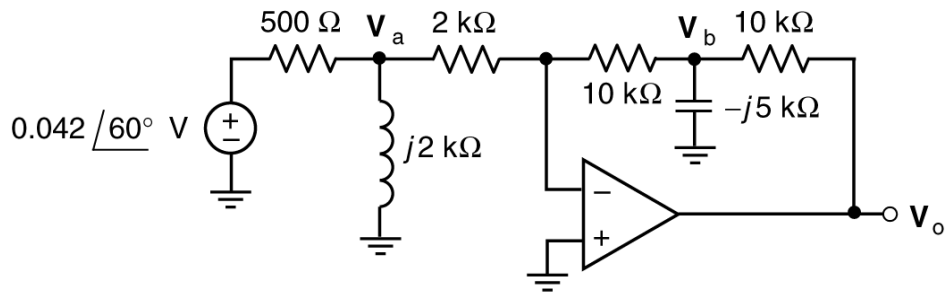Represent the circuit in the frequency domain:



Apply KCL at the top node of the inductor, node a:

$$\frac{0.042\angle 60^\circ - \mathbf{V}_a}{500} = \frac{\mathbf{V}_a}{j2000} + \frac{\mathbf{V}_a}{2000} \Rightarrow \mathbf{V}_a = \frac{4}{5-j}(0.042\angle 60^\circ)$$

Apply KCL at the inverting input node of the op amp:

$$\frac{\mathbf{V}_a}{2000} + \frac{\mathbf{V}_b}{10,000} = 0 \Rightarrow \mathbf{V}_b = -5\mathbf{V}_a$$

Apply KCL at the top node of the capacitor, node b:

$$\frac{\mathbf{V}_b}{10,000} + \frac{\mathbf{V}_b}{-j5000} + \frac{\mathbf{V}_b - \mathbf{V}_o}{20,000} = 0 \Rightarrow \mathbf{V}_o = (3 + j4)\mathbf{V}_b$$

Combining these results we get:


$$\mathbf{V}_o = (3 + j4)(-5) \frac{4}{5-j}(0.042\angle 60^\circ) = \frac{(5\angle 53.1^\circ)(20\angle -180^\circ)}{5.1\angle -11.3^\circ}(0.042\angle 60^\circ) = 0.8235\angle -55.6^\circ$$

In the time domain $v_o(t) = 832.5 \cos(800t - 55.6^\circ) \text{ mV}$

P 10.6-8

Solution:

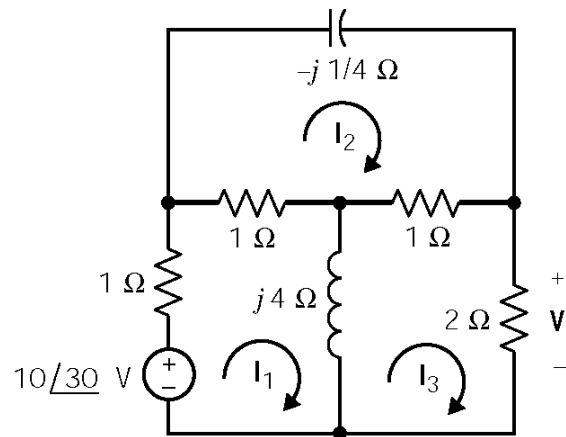Represent the circuit in the frequency domain:



The mesh equations are:

$$\begin{bmatrix} (2+j4) & -1 & -j4 \\ -1 & (2+1/j4) & -1 \\ -j4 & -1 & (3+j4) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10\angle 30^\circ \\ 0 \\ 0 \end{bmatrix}$$

Using Cramer's rule yields


$$\mathbf{I}_3 = \frac{2+j8}{12+j22.5} (10\angle 30^\circ) = 3.225\angle 44^\circ \text{ A}$$

Then $\mathbf{V} = 2 \mathbf{I}_3 = 2(3.225\angle 44^\circ) = 6.45\angle 44^\circ \text{ V} \Rightarrow v(t) = 6.45 \cos(10^5 t + 44^\circ) \text{ V}$

(checked: LNAP 7/19/04)

P 10.6-9

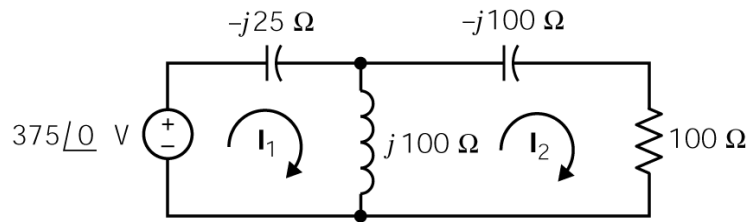Solution: Represent the circuit in the frequency domain:



Mesh Equations:

$$j75\mathbf{I}_1 - j100\mathbf{I}_2 = 375$$

$$-j100\mathbf{I}_1 + (100 + j100)\mathbf{I}_2 = 0$$

Solving for \mathbf{I}_2 yields $\mathbf{I}_2 = 4.5 + j1.5 = 3\angle 53.1^\circ \text{ A} \Rightarrow i_2(t) = 3\cos(400t + 53.1^\circ) \text{ A}$

(checked: LNAP 7/19/04)

P 10.6-10

Solution

(a)

The node equations are

$$\frac{24 - v_a}{40} = \frac{v_a - v_b}{20} + \frac{v_a}{15}$$


$$\frac{24 - v_b}{25} + \frac{v_a - v_b}{20} = \frac{v_b}{50}$$

or

$$\begin{bmatrix} \frac{1}{40} + \frac{1}{20} + \frac{1}{15} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{1}{25} + \frac{1}{20} + \frac{1}{50} \end{bmatrix} \begin{bmatrix} v_a \\ v_b \end{bmatrix} = \begin{bmatrix} \frac{24}{40} \\ \frac{24}{25} \end{bmatrix}$$

Solving using MATLAB gives $v_a = 8.713 \text{ V}$ and $v_b = 12.69 \text{ V}$

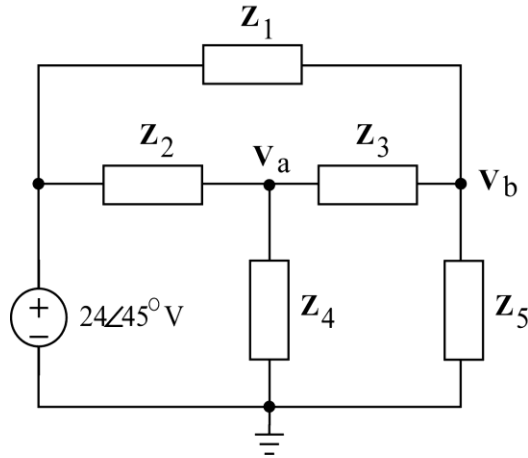(b) Use phasors and impedances to represent the circuit in the frequency domain as



where

$$\mathbf{Z}_1 = 25 + j(20)4 = 25 + j80 = 83.82\angle 72.7^\circ \Omega$$

$$\mathbf{Z}_2 = \left(40 \square \frac{1}{j(20)(0.004)} \right) + j(20)5 = 3.56 + j88.6 = 88.68\angle 87.7^\circ \Omega$$

$$\mathbf{Z}_3 = 20 \Omega$$

$$\mathbf{Z}_4 = 15 + j(20)2 = 15 + j40 = 42.72\angle 69.4^\circ$$

$$\mathbf{Z}_5 = j(20)3 + \frac{1}{j(20)(0.005)} = j50 = 50\angle 90^\circ \Omega$$

The node equations are

$$\frac{24\angle 45^\circ - \mathbf{V}_a}{\mathbf{Z}_2} = \frac{\mathbf{V}_a}{\mathbf{Z}_4} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3}$$

$$\frac{24\angle 45^\circ - \mathbf{V}_b}{\mathbf{Z}_1} + \frac{\mathbf{V}_a - \mathbf{V}_b}{\mathbf{Z}_3} = \frac{\mathbf{V}_b}{\mathbf{Z}_5}$$

$$\begin{bmatrix} \frac{1}{\mathbf{Z}_2} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_4} & -\frac{1}{\mathbf{Z}_3} \\ -\frac{1}{\mathbf{Z}_3} & \frac{1}{\mathbf{Z}_1} + \frac{1}{\mathbf{Z}_3} + \frac{1}{\mathbf{Z}_5} \end{bmatrix} \begin{bmatrix} \mathbf{V}_a \\ \mathbf{V}_b \end{bmatrix} = \begin{bmatrix} \frac{24\angle 45^\circ}{\mathbf{Z}_2} \\ \frac{24\angle 45^\circ}{\mathbf{Z}_1} \end{bmatrix}$$

Solving using MATLAB gives

$$\mathbf{V}_a = 7.89\angle 44.0^\circ$$

$$\mathbf{V}_b = 8.45\angle 45.1^\circ$$

So


$$v_a(t) = 7.89 \cos(20t + 44^\circ) \text{ V}$$

$$v_b(t) = 8.45 \cos(20t + 45.1^\circ) \text{ V}$$

(checked: LNAP 8/3/04)

P 10.6-11**Solution:**

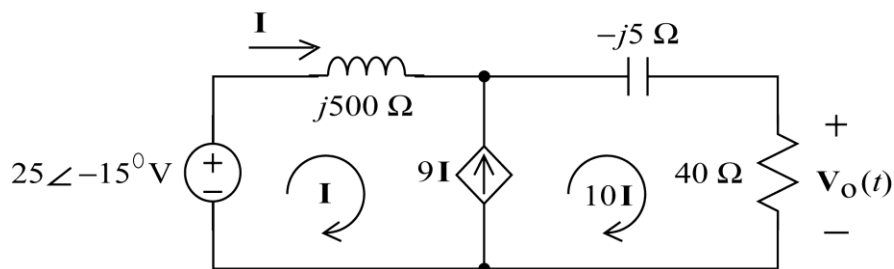Represent the circuit in the frequency domain using impedances and phasors.



The mesh currents are \mathbf{I} and $10\mathbf{I}$. Apply KVL to the supermesh corresponding to the dependant current source to get

$$(j500)\mathbf{I} + (-j5)(10\mathbf{I}) + 40(10\mathbf{I}) - 25\angle -15^\circ = 0$$

So
$$\mathbf{I} = \frac{25\angle -15^\circ}{400 + j450} = 0.04152\angle -63.37^\circ \text{ A}$$

The output voltage is
$$\mathbf{V} = 40(10\mathbf{I}) = 16.61\angle -63.37^\circ \text{ V}$$

So
$$v(t) = 16.61\cos(100t - 63.37^\circ) \text{ V}$$

(checked: LNAP 8/3/04)

P 10.6-12**Solution:**

Represent the circuit in the frequency domain using phasors and impedances. Apply KVL to the center mesh to get

$$0.8394\angle 138.5^\circ = \mathbf{I} = \frac{8\angle 210^\circ - 30\angle -15^\circ}{R + j10L} \Rightarrow R + j10L = 35 + j25 = 35 + j(10)2.5$$

So
$$R = 35 \Omega \quad \text{and} \quad L = 2.5 \text{ H}$$

(checked: LNAP 8/3/04)

P 10.6-13**Solution:**

Represent the circuit in the frequency domain using phasors and impedances. Apply KCL at the top node of R and L to get

$$\frac{(50\angle -75^\circ) - \mathbf{V}}{j40} + \frac{35\angle 100^\circ - \mathbf{V}}{40} = \frac{\mathbf{V}}{R + j\omega L}$$

$$\Rightarrow \frac{50\angle -75^\circ}{40\angle 90^\circ} + \frac{35\angle 110^\circ}{40} = \left(\frac{1}{j40} + \frac{1}{40} + \frac{1}{R} - j\frac{1}{20L} \right) \mathbf{V}$$

Using the given equation for $v(t)$ we get

$$21.25\angle -168.8^\circ = \mathbf{V} = \frac{1.587\angle 161.7^\circ}{0.025(1-j) + \frac{1}{R} - j\frac{1}{20L}}$$

Then $\frac{1}{R} - j\frac{1}{20L} = \frac{1.587\angle 161.7^\circ}{21.25\angle -168.8^\circ} - 0.025(1-j) = 0.04 - j0.01176$


Finally $R = \frac{1}{0.04} = 25 \Omega$ and $L = \frac{1}{20(0.01176)} = 4.25 \text{ H}$

(checked: LNAP 8/3/04)

P 10.6-14

Solution:

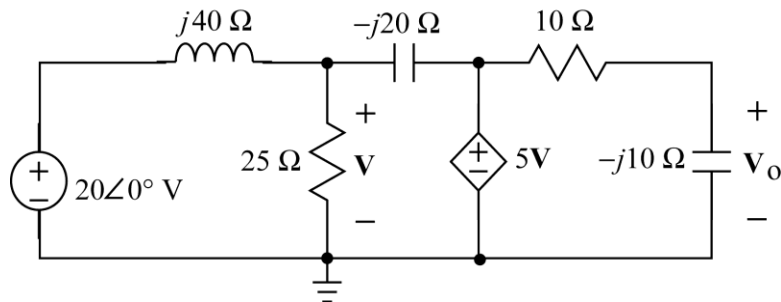Represent the circuit in the frequency domain using phasors and impedances.



$$\frac{20\angle 0^\circ - \mathbf{V}}{j40} = \frac{\mathbf{V}}{25} + \frac{\mathbf{V} - 5\text{V}}{-j20}$$

The node equations are

$$\frac{5\text{V} - \mathbf{V}_o}{10} = \frac{\mathbf{V}_o}{-j10}$$

$$\begin{bmatrix} \frac{1}{25} - j\frac{1}{5} - j\frac{1}{40} & 0 \\ -\frac{1}{2} & \frac{1}{10} + j\frac{1}{10} \end{bmatrix} \begin{bmatrix} \mathbf{V} \\ \mathbf{V}_o \end{bmatrix} = \begin{bmatrix} -j0.5 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0.04 - j0.225 & 0 \\ -0.50 & 0.10 + j0.10 \end{bmatrix} \begin{bmatrix} \mathbf{V} \\ \mathbf{V}_o \end{bmatrix} = \begin{bmatrix} -j0.5 \\ 0 \end{bmatrix}$$

Solving gives $\mathbf{V} = 2.188 \angle -10.1^\circ \text{ V}$ and $\mathbf{V}_o = 7.736 \angle -55.1^\circ \text{ V}$

So $v_o(t) = 7.736 \cos(5t - 55.1^\circ) \text{ V}$

(checked: LNAP 8/4/04)

P 10.6-15

Solution:


(a) Use KVL to see that the voltage across the 8Ω resistor is $20i(t) - 4i(t) = 16i(t)$.

Apply KCL to the supernode corresponding to the dependent voltage source to get

$$0.036 = i(t) + \frac{16i(t)}{8} = 3i(t)$$

so $i(t) = 12 \text{ mA}$

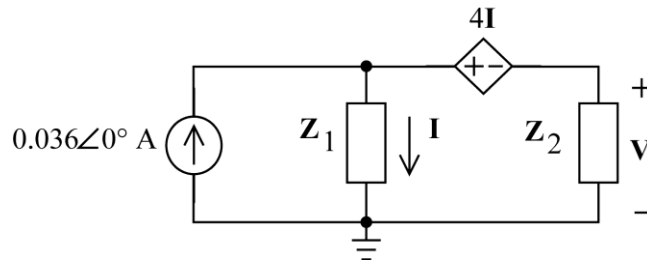(b) Represent the circuit in the frequency domain using phasors and impedances.



$$\mathbf{Z}_1 = 20 + \frac{1}{j(25)(0.002)} = 20 - j20 \Omega$$

where

$$\mathbf{Z}_2 = j50 + \left(15 \square \frac{1}{j(25)(0.004)} \right) = 43.3 \angle 83.9^\circ \Omega$$

Use KVL to get

$$\mathbf{V} = \mathbf{Z}_1 \mathbf{I} - 4\mathbf{I} = (\mathbf{Z}_1 - 4) \mathbf{I}$$

Then apply KCL to the supernode corresponding to the dependent source to get

$$0.036 \angle 0^\circ = \mathbf{I} + \frac{(\mathbf{Z}_1 - 4) \mathbf{I}}{\mathbf{Z}_2} = \left(\frac{\mathbf{Z}_1 + \mathbf{Z}_2 - 4}{\mathbf{Z}_2} \right) \mathbf{I}$$

so
$$\mathbf{I} = \frac{\mathbf{Z}_2 (0.036 \angle 0^\circ)}{\mathbf{Z}_1 + \mathbf{Z}_2 - 4} = 50.4 \angle 35.7^\circ \text{ mA}$$

so
$$i(t) = 50.4 \cos(25t + 35.7^\circ) \text{ mA}$$

(checked: LNAP 8/4/04)

10.6-16


Solution:

Represent the circuit in the frequency domain using phasors and impedances. The mesh currents are

$$\mathbf{I}_1 = 0.080 \angle 0^\circ \text{ A}$$

and
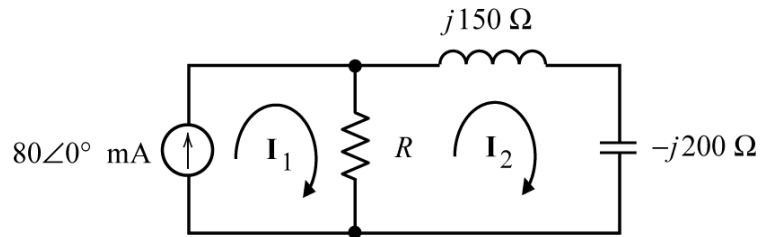
$$\mathbf{I}_2 = 0.06656 \angle 33.7^\circ \text{ A}$$



Apply KVL to the right to get

$$(j150 - j200)(0.06656 \angle 33.7^\circ) + R(0.06656 \angle 33.7^\circ - 0.080 \angle 0^\circ) = 0$$


$$(-j50)(0.06656 \angle 33.7^\circ) + R(0.044376 \angle 123.7^\circ) = 0$$

$$R = \frac{(50 \angle 90^\circ)(0.06656 \angle 33.7^\circ)}{0.044376 \angle 123.7^\circ} = 74.9955 \approx 75 \Omega$$

MATLAB, 11/20/09

P10.6-17

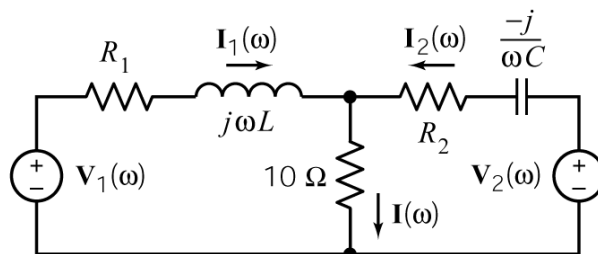
Solution: Represent the circuit in the frequency domain using impedances and phasors:



$$\begin{aligned}
 \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 = 0.744\angle -118^\circ + 0.5405\angle 100^\circ = (-0.349 - j0.657) + (-0.094 + j0.532) \\
 &= (-0.349 - 0.094) + j(-0.657 + 0.532) \\
 &= -0.443 - j0.125 \\
 &= 0.460\angle -164^\circ
 \end{aligned}$$

In the time domain $i(t) = 460 \cos(2t - 164^\circ) \text{ mA}$

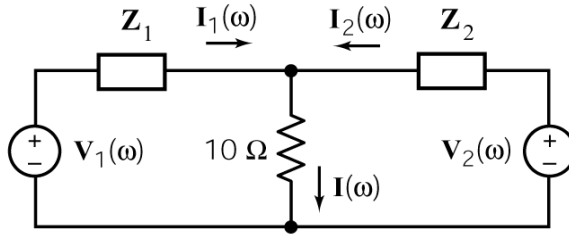Replacing series impedances by equivalent impedances gives



$$\mathbf{Z}_1 = R_1 + j\omega L$$

and

$$\mathbf{Z}_2 = R_2 - j\frac{1}{\omega C}$$

From KVL

$$\begin{aligned}
 \mathbf{Z}_1 \mathbf{I}_1 + 10\mathbf{I} - \mathbf{V}_1 &= 0 \Rightarrow \mathbf{Z}_1 = \frac{\mathbf{V}_1 - 10\mathbf{I}}{\mathbf{I}_1} = \frac{12\angle -90^\circ - 10(0.460\angle -164^\circ)}{0.744\angle -118^\circ} \\
 &= \frac{-j12 - 10(-0.443 - j0.125)}{0.744\angle -118^\circ} \\
 &= \frac{4.43 - j10.75}{0.744\angle -118^\circ} = \frac{11.63\angle -67.6^\circ}{0.744\angle -118^\circ} \\
 &= 15.63\angle 50.4^\circ \\
 &= 10 + j12 \Omega
 \end{aligned}$$

and

$$\begin{aligned}
 -\mathbf{Z}_2 \mathbf{I}_2 + \mathbf{V}_2 - 10\mathbf{I} &= 0 \Rightarrow \mathbf{Z}_2 = \frac{\mathbf{V}_2 - 10\mathbf{I}}{\mathbf{I}_2} = \frac{5\angle 90^\circ - 10(0.460\angle -164^\circ)}{0.5405\angle 100^\circ} \\
 &= \frac{j5 - 10(-0.443 - j0.125)}{0.5405\angle 100^\circ} \\
 &= \frac{4.43 + j6.25}{0.5405\angle 100^\circ} = \frac{7.66\angle 54.7^\circ}{0.5405\angle 100^\circ} \\
 &= 14.14\angle -55.3^\circ \\
 &= 10 - j10 \Omega
 \end{aligned}$$


Next $10 + j12 = R_1 + j\omega L = R_1 + j2L \Rightarrow R_1 = 10 \Omega \text{ and } L = \frac{12}{2} = 6 \text{ H}$

and $10 - j10 = R_2 - j\frac{1}{\omega C} = R_2 - j\frac{1}{2C} \Rightarrow R_2 = 10 \Omega$ and $C = \frac{1}{2(10)} = 0.05 \text{ F}$



Section 10.7 Thevenin and Norton Equivalent Circuits

P10.7-1

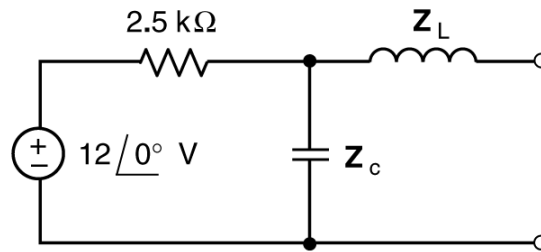Solution: Represent the circuit in the frequency domain as



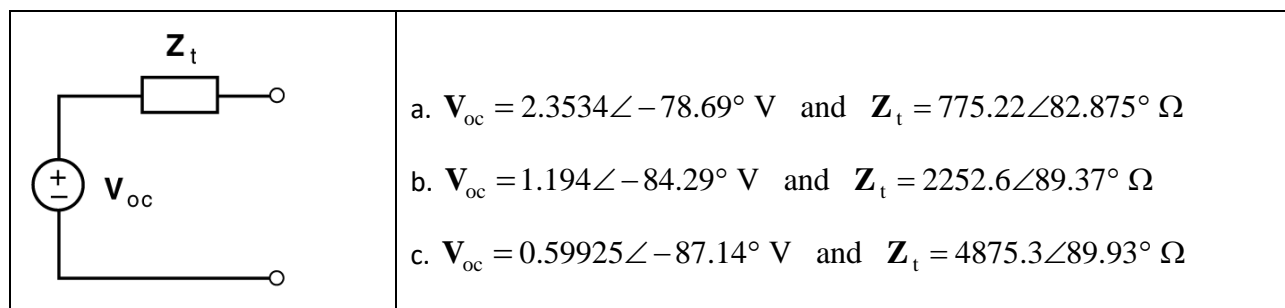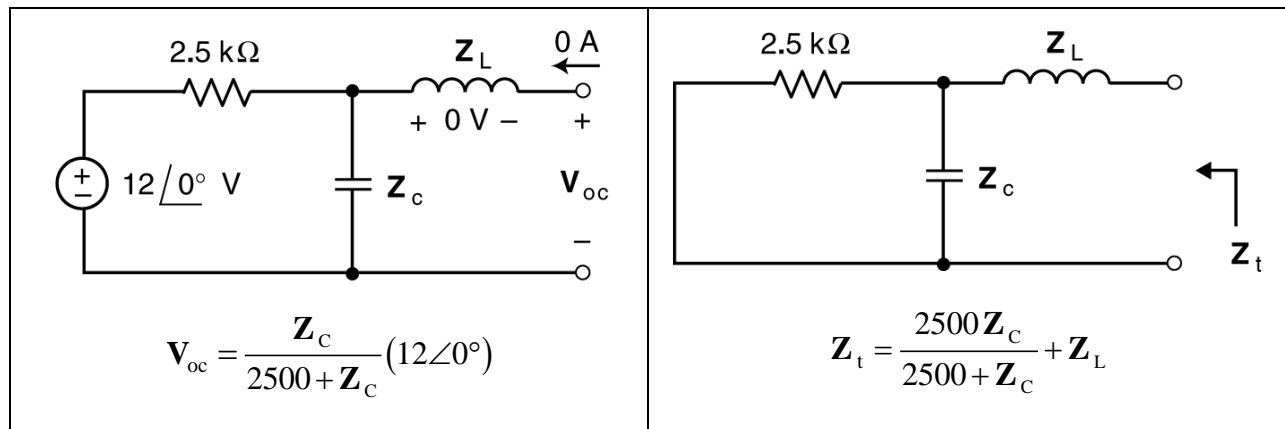
Determine the open circuit voltage and Thevenin impedance:



The Thevenin Equivalent Circuit changes whenever the input frequency changes.


P 10.7-2

Solution:

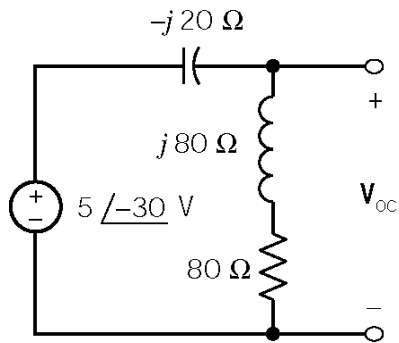

Find V_{oc} :

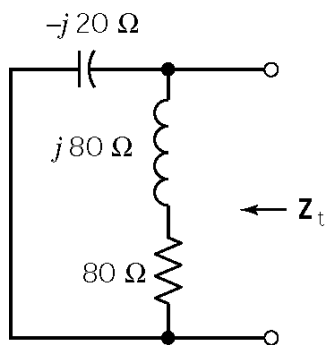
$$\begin{aligned} V_{oc} &= (5 \angle -30^\circ) \left(\frac{80 + j80}{80 + j80 - j20} \right) \\ &= (5 \angle -30^\circ) \left(\frac{80\sqrt{2} \angle -45^\circ}{100 \angle 36.90^\circ} \right) \\ &= 4\sqrt{2} \angle -21.9^\circ \text{ V} \end{aligned}$$



Find Z_t :

$$Z_t = \frac{(-j20)(80 + j80)}{-j20 + 80 + j80} = 23 \angle -81.9^\circ \Omega$$

The Thevenin equivalent is

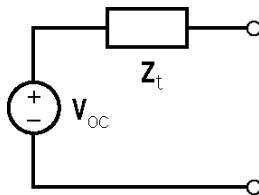


P 10.7-3

Solution:

First, determine V_{oc} :

The node equation is:
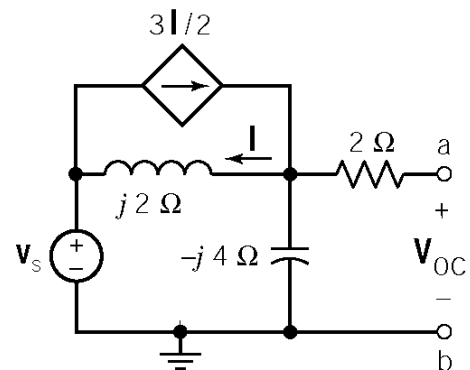
$$\frac{V_{oc}}{-j4} + \frac{V_{oc} - (6 + j8)}{j2} - \frac{3}{2} \left(\frac{V_{oc} - (6 + j8)}{j2} \right) = 0$$



$$\mathbf{V}_{oc} = 3 + j4 = 5 \angle 53.1^\circ \text{ V}$$

$$\mathbf{V}_s = 10 \angle 53^\circ = 6 + j8 \text{ V}$$


Next, determine \mathbf{I}_{sc} :

The node equation is:

$$\frac{\mathbf{V}}{2} + \frac{\mathbf{V}}{-j4} + \frac{\mathbf{V} - (6 + j8)}{j2} - \frac{3}{2} \left[\frac{\mathbf{V} - (6 + j8)}{j2} \right] = 0$$


$$\mathbf{V} = \frac{3 + j4}{1 - j}$$
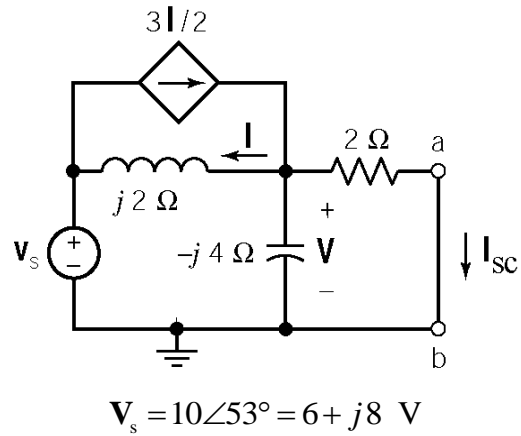
$$\mathbf{I}_{sc} = \frac{\mathbf{V}}{2} = \frac{3 + j4}{2 - j2}$$



The Thevenin impedance is $\mathbf{Z}_T = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = 3 + j4 \left(\frac{2 - j2}{3 + j4} \right) = 2 - j2 \ \Omega$

The Thevenin equivalent is

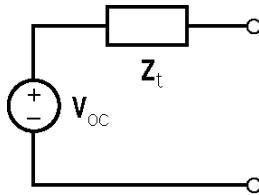

(checked: LNAP 7/18/04)

P10.7-4

Solution:


$$\mathbf{Y} = \mathbf{G} + \mathbf{Y}_L + \mathbf{Y}_C$$

$$\mathbf{Y} = \mathbf{G} \text{ when } \mathbf{Y}_L + \mathbf{Y}_C = 0 \text{ or } \frac{1}{j\omega L} + j\omega C = 0$$

$$\omega_o = \frac{1}{\sqrt{LC}}, f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{39.6 \times 10^{-15}}}$$



$$= 0.07998 \times 10^7 \text{ Hz} = 800 \text{ kHz}$$

(80 on the dial of the radio)

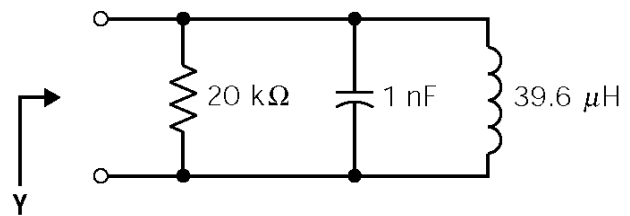


P 10.7-5


Solution:

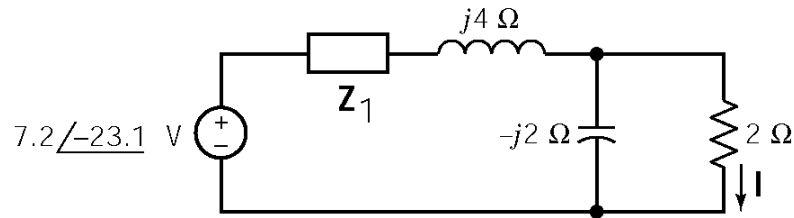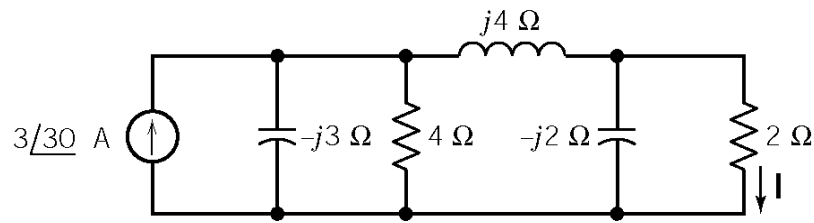
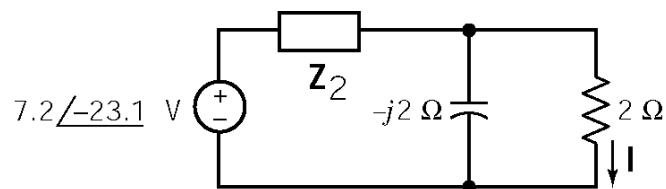
$$\begin{aligned} \mathbf{Z}_1 &= \frac{(-j3)(4)}{-j3+4} = 2.4 \angle -53.1^\circ \Omega \\ &= 1.44 - j1.92 \Omega \end{aligned}$$


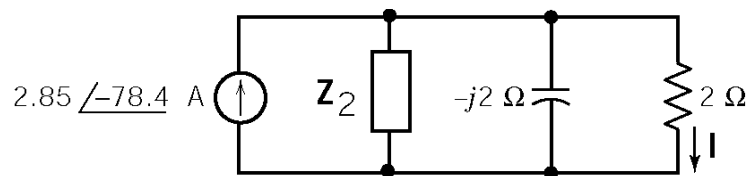
$$\begin{aligned} \mathbf{Z}_2 &= \mathbf{Z}_1 + j4 \\ &= 1.44 + j2.08 \\ &= 2.53 \angle 55.3^\circ \Omega \end{aligned}$$






$$\begin{aligned} \mathbf{Z}_3 &= 3.51 \angle -37.9^\circ \Omega \\ &= 2.77 - j2.16 \Omega \end{aligned}$$

$$\mathbf{I} = (2.85 \angle -78.4^\circ) \left(\frac{3.51 \angle -37.9^\circ}{2.77 - j2.16 + 2} \right) = (2.85 \angle -78.4^\circ) \frac{(3.51 \angle -37.9^\circ)}{(5.24 \angle -24.4^\circ)} = 1.9 \angle -92^\circ \text{ A}$$


(checked: LNAP 7/18/04)

P 10.7-6

Solution:

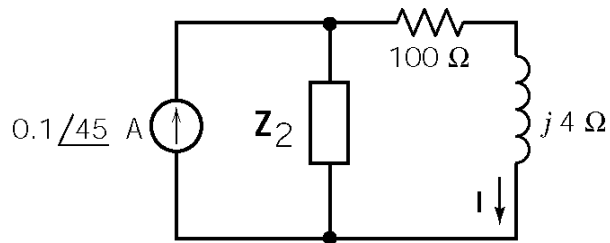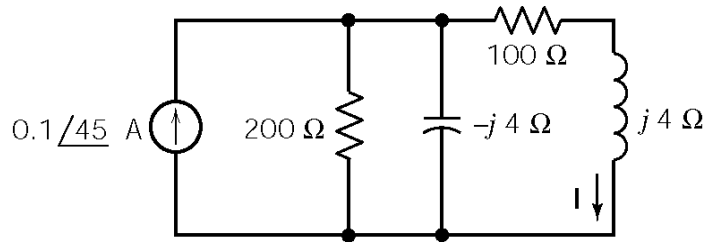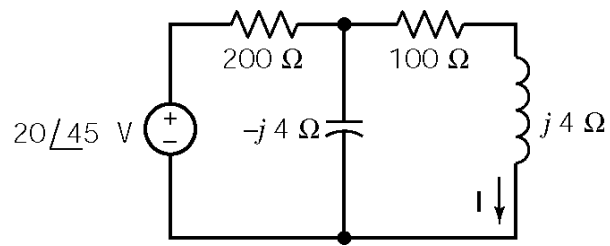
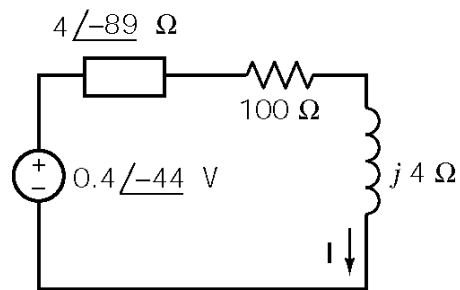
$$\mathbf{Z}_2 = \frac{(200)(-j4)}{200 - j4} = 4\angle -88.8^\circ \Omega$$




$$\mathbf{I} = \frac{0.4\angle -44^\circ}{-4j + 100 + j4} = 4\angle -44^\circ \text{ mA}$$

$$i(t) = 4 \cos(25000t - 44^\circ) \text{ mA}$$

P10.7-7


Solution:

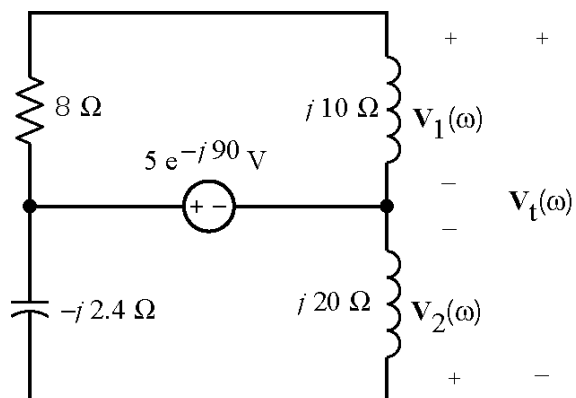

$$V_1 = \frac{j10}{8 + j10} 5e^{-j90} = 3.9e^{-j51}$$

$$V_2 = \frac{j20}{j20 - j2.4} 5e^{-j90} = 5.68e^{-j90}$$
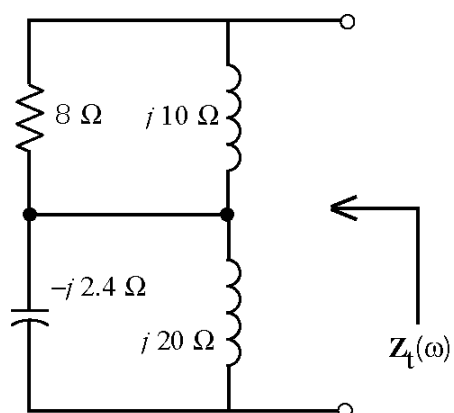
$$V_t = V_1 - V_2 = 3.9e^{-j51} - 5.68e^{-j90} = 3.58e^{j47}$$



$$Z_t = \frac{8(j10)}{8 + j10} + \frac{-j2.4(j20)}{-j2.4 + j20} = 4.9 + j1.2$$

Section 10.8 Superposition

P 10.8-1


Solution:

(a) Represent the circuit in the frequency domain as



Use superposition *in the frequency domain* to write

$$\begin{aligned} \mathbf{V}_o &= -\frac{100}{100 + j150}(12\angle 0^\circ) + 100\frac{j150}{100 + j150}(0.1\angle 0^\circ) \\ &= \frac{-1200 + j1500}{100 + j150} = 10.66\angle 72.35^\circ \end{aligned}$$


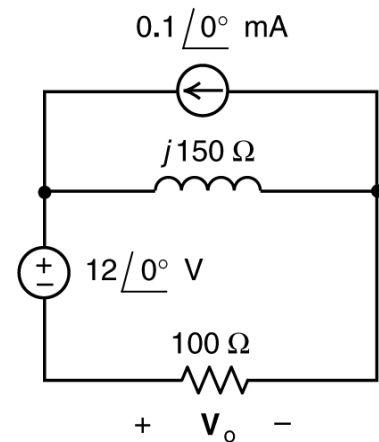
In the time domain $v_o(t) = 10.66\cos(400t + 72.35^\circ) \text{ V}$



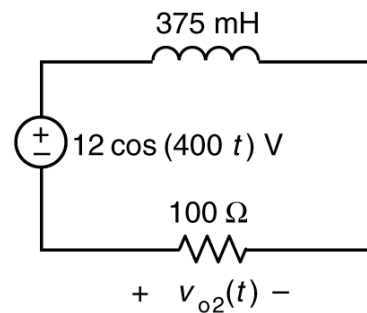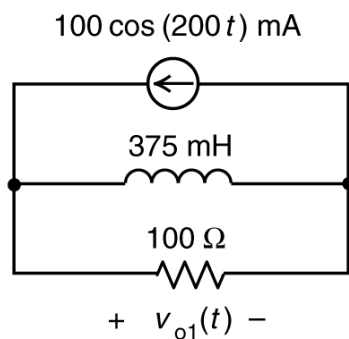(b) Use superposition *in the time domain*. These circuits can be used to find the part of v_o caused by the current source and the part of v_o caused by the voltage source.



In the frequency domain:

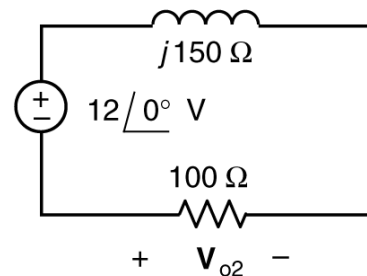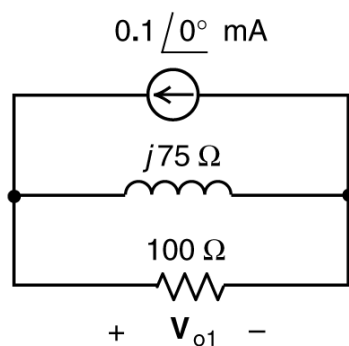

$$\mathbf{V}_{o1} = 100\frac{j75}{100 + j75}(0.1\angle 0^\circ) = 6\angle 53.1^\circ \text{ V}$$

$$\mathbf{V}_{o2} = -\frac{100}{100 + j150}(12\angle 0^\circ) = 6.656\angle 123.7^\circ \text{ V}$$

In the time domain


$$v_{o1}(t) = 6 \cos(200t + 53.1^\circ) \text{ V and } v_{o2}(t) = 6.656 \cos(400t + 123.7^\circ) \text{ V}$$

and

$$v_o(t) = v_{o1}(t) + v_{o2}(t) = 6 \cos(200t + 53.1^\circ) + 6.656 \cos(400t + 123.7^\circ) \text{ V}$$

P 10.8-2


Use superposition *in the time domain*:

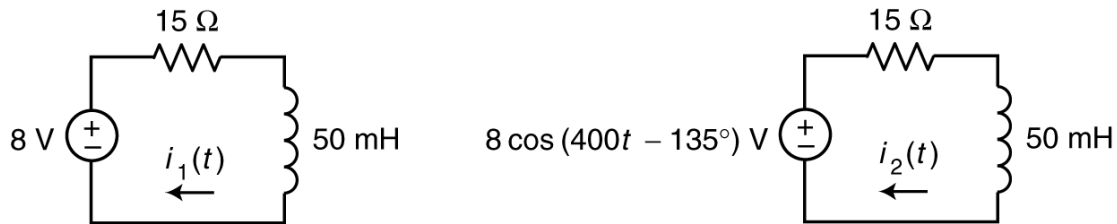

An inductor in a dc circuit acts like a short circuit so:

$$i_1(t) = \frac{8}{15} = 0.533 \text{ A}$$

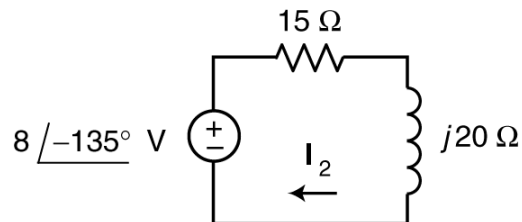Represent the right circuit the frequency domain:



$$\mathbf{I}_2 = \frac{8 \angle -135^\circ}{15 + j20} = 0.32 \angle -188^\circ \text{ A}$$

In the time domain

$$i_2(t) = 0.32 \cos(400t - 188^\circ) \text{ A}$$

and

$$i(t) = i_1(t) + i_2(t) = 0.533 + 0.32 \cos(400t - 188^\circ) \text{ A}$$

P 10.8-3

Solution:


Use superposition in the time domain. Let

$$i_{s1}(t) = 36 \cos(25t) \text{ mA} \quad \text{and} \quad i_{s2}(t) = 48 \cos(50t + 45^\circ) \text{ mA}$$

We will find the response to each of these inputs separately. Let $i_i(t)$ denote the response to $i_{si}(t)$ for $i = 1, 2$. The sum of the two responses will be $i(t)$, i.e.

$$i(t) = i_1(t) + i_2(t)$$

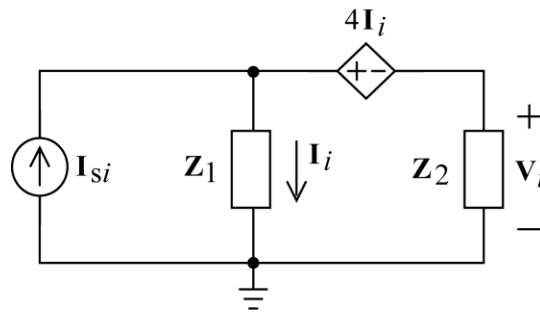Represent the circuit in the frequency domain as



Use KVL to get

$$V_i = Z_i I_i - 4I_i$$

Apply KCL to the supernode corresponding to the dependent voltage source.

$$I_{si} = I_i + \frac{V_i}{Z_2} = \frac{Z_1 + Z_2 - 4}{Z_2} I_i$$

or

$$I_i = \frac{Z_2 I_{si}}{Z_1 + Z_2 - 4}$$

Consider the case $i = 1$: $i_{s1}(t) = 26 \cos(25t) \text{ mA}$.

Here $\omega = 25 \text{ rad/s}$ and

$$I_{si} = 36 \angle 0^\circ \text{ mA}$$

$$Z_1 = 20 + \frac{1}{j(25)(0.002)} = 20 - j20 \, \Omega$$

$$Z_2 = j50 + \left(15 \parallel \frac{1}{j(25)(0.004)} \right) = 43.3 \angle 83.9^\circ \, \Omega$$

and

$$I_1 = 50.4 \angle 35.7^\circ \text{ mA}$$

so

$$i(t) = 50.4 \cos(25t + 35.7^\circ) \text{ mA}$$

Next consider $i = 2 : i_{s2} = 48 \cos(50t + 45^\circ) \text{ mA}$.

Here $\omega = 50 \text{ rad/s}$ and

$$\mathbf{I}_{s2} = 48 \angle 45^\circ \text{ mA}$$

$$\mathbf{Z}_1 = 20 + \frac{1}{j(50)(0.002)} = 20 - j10 \, \Omega$$

$$\mathbf{Z}_2 = j100 + \left(15 \parallel \frac{1}{j(50)(0.004)} \right) = 95.5 \angle 89.1^\circ \, \Omega$$

(Notice that \mathbf{Z}_1 and \mathbf{Z}_2 change when ω changes.)

$$\mathbf{I}_2 = 52.5 \angle 55.7^\circ \text{ mA}$$

so

$$i_2(t) = 52.5 \cos(50t + 55.7^\circ) \text{ mA}$$

Finally, using superposition in the time domain gives


$$i(t) = 50.4 \cos(25t + 35.7^\circ) + 52.5 \cos(50t + 55.7^\circ) \text{ mA}$$

(checked: LNAP 8/7/04)

P 10.8-4

Solution:

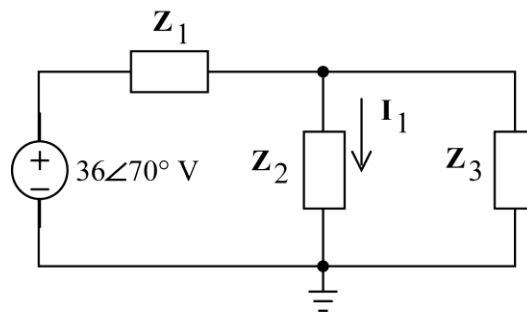Use superposition in the time domain. Let $i_1(t)$ be the part of $i(t)$ due to $v_{s1}(t)$ and $i_2(t)$ be the part of $i(t)$ due to $v_{s2}(t)$. To determine $i_1(t)$, set $v_{s2}(t) = 0$. Represent the resulting circuit in the frequency domain to get



where

$$\mathbf{Z}_1 = 20 + j80 = 82.46 \angle 76^\circ \Omega$$

$$\mathbf{Z}_2 = 10 + (j40 \parallel 15) = 23.15 + j4.93 = 23.67 \angle 12^\circ \Omega$$

$$\mathbf{Z}_3 = 20 + \frac{1}{j(20)(0.005)} = 20 - j10 = 22.36 \angle -26.6^\circ \Omega$$


Next, using Ohm's law and current division gives

$$\mathbf{I}_1 = \frac{30 \angle 70^\circ}{\mathbf{Z}_1 + (\mathbf{Z}_2 \parallel \mathbf{Z}_3)} \times \frac{\mathbf{Z}_3}{\mathbf{Z}_2 + \mathbf{Z}_3} = \frac{\mathbf{Z}_3 (30 \angle 70^\circ)}{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_1 \mathbf{Z}_3} = 0.182 \angle -17.6^\circ \text{ A}$$

so

$$i(t) = 0.182 \cos(20t - 17.6^\circ) \text{ A}$$

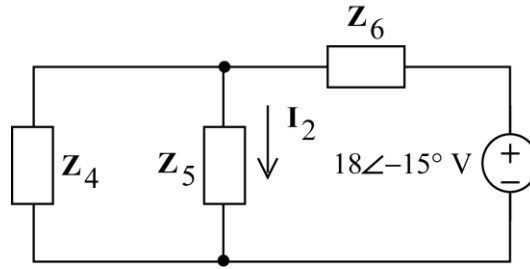To determine $i_2(t)$, set $v_{s1}(t) = 0$. Represent the resulting circuit in the frequency domain to get



where

$$\mathbf{Z}_4 = 20 + j40 = 44.72 \angle 63.4^\circ \Omega$$

$$\mathbf{Z}_5 = 10 + (j20 \parallel 15) = 19.6 + j7.2 = 20.88 \angle 20.2^\circ \Omega$$

$$\mathbf{Z}_6 = 20 + \frac{1}{j(10)(0.005)} = 20 - j20 = 28.28 \angle -45^\circ \Omega$$

Next, using Ohm's law and current division gives

$$\mathbf{I}_2 = \frac{18 \angle -15^\circ}{\mathbf{Z}_6 + (\mathbf{Z}_4 \parallel \mathbf{Z}_5)} \times \frac{\mathbf{Z}_4}{\mathbf{Z}_4 + \mathbf{Z}_5} = \frac{\mathbf{Z}_1 (18 \angle -15^\circ)}{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_1 \mathbf{Z}_3} = 0.377 \angle 18^\circ \text{ A}$$

so

$$i_2(t) = 0.377 \cos(10t + 18^\circ) \text{ A}$$


Using superposition,

$$i(t) = i_1(t) + i_2(t) = 0.182 \cos(20t - 17.6^\circ) + 0.377 \cos(10t + 18^\circ) \text{ A}$$

(checked: LNAP 8/8/04)

P 10.8-5


Solution:

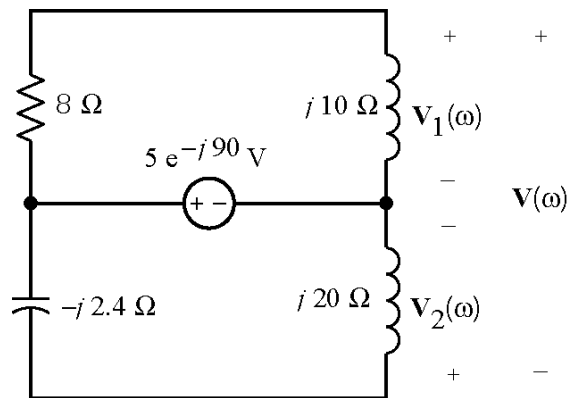

$$\mathbf{V}_1(\omega) = \frac{j10}{8 + j10} 5e^{-j90} = 3.9e^{-j51}$$

$$\mathbf{V}_2(\omega) = \frac{j20}{j20 - j2.4} 5e^{-j90} = 5.68e^{-j90}$$
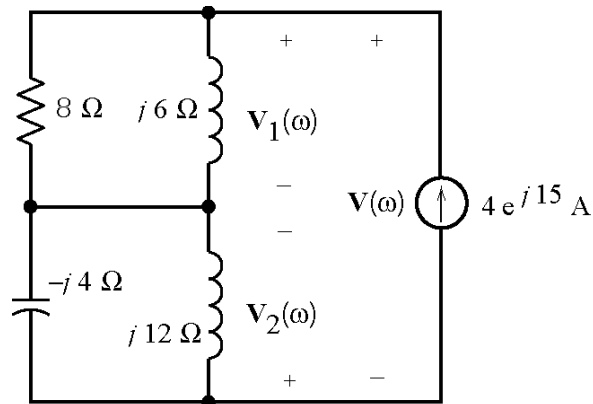
$$\mathbf{V}(\omega) = \mathbf{V}_1(\omega) - \mathbf{V}_2(\omega) = 3.9e^{-j51} - 5.68e^{-j90} = 3.58e^{j47}$$



$$\mathbf{V}_1(\omega) = \frac{8(j6)}{8 + j6} 4e^{j15} = 19.2e^{j68}$$

$$\mathbf{V}_2(\omega) = \frac{j12(-j4)}{j12 - j4} 4e^{j15} = 24e^{-j75}$$


$$\mathbf{V}(\omega) = \mathbf{V}_1(\omega) + \mathbf{V}_2(\omega) = 14.4e^{-j22}$$

Using superposition: $v(t) = 3.58 \cos(5t + 47^\circ) + 14.4 \cos(3t - 22^\circ) \text{ V}$.

P 10.8-6

Solution:

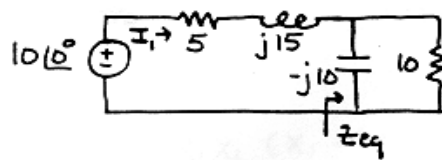Use superposition. First, find the response to the voltage source acting alone:



$$\mathbf{Z}_{eq} = \frac{-j10 \cdot 10}{10 - j10} = 5(1 - j) \Omega$$


Replacing the parallel elements by the equivalent impedance. Then write a mesh equation :

$$-10 + 5 \mathbf{I}_1 + j15 \mathbf{I}_1 + 5(1-j) \mathbf{I}_1 = 0 \Rightarrow \mathbf{I}_1 = \frac{10}{10+j10} = 0.707 \angle -45^\circ \text{ A}$$

Therefore:

$$i_1(t) = 0.707 \cos(10t - 45^\circ) \text{ A}$$

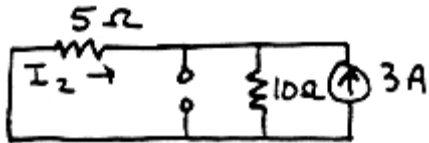Next, find the response to the dc current source acting alone:



Current division: $I_2 = -\frac{10}{15} \times 3 = -2 \text{ A}$


Using superposition:

$$i(t) = 0.707 \cos(10t - 45^\circ) - 2 \text{ A}$$

Section 10-9: Phasor Diagrams

P 10.9-1


Solution:

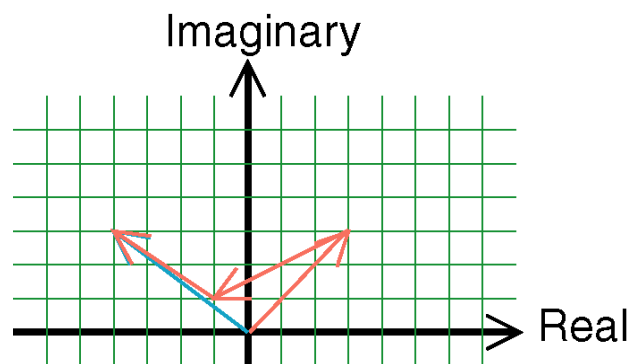

$$\mathbf{V} = \mathbf{V}_1 - \mathbf{V}_2 + \mathbf{V}_3^* = (3 + j3) - (4 + j2) + (-3 - j2)^* = -4 + j3$$

P 10.9-2

Solution:

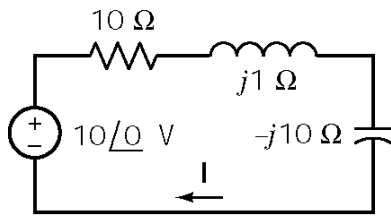


$$\mathbf{I} = \frac{10\angle 0^\circ}{10 + j1 - j10} = 0.74\angle 42^\circ \text{ A}$$

$$\mathbf{V}_R = R\mathbf{I} = 7.4\angle 42^\circ \text{ V}$$

$$\mathbf{V}_L = \mathbf{Z}_L\mathbf{I} = (1\angle 90^\circ)(0.74\angle 42^\circ) = 0.74\angle 132^\circ \text{ V}$$

$$\mathbf{V}_C = \mathbf{Z}_C\mathbf{I} = (10\angle -90^\circ)(0.74\angle 42^\circ) = 7.4\angle -48^\circ \text{ V}$$

$$\mathbf{V}_S = 10\angle 0^\circ \text{ V}$$

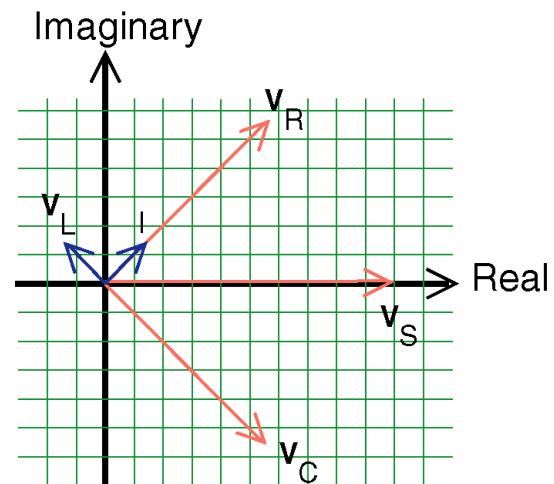


Section 10.10 Op Amps in AC Circuits

P 10.10-1

Solution:

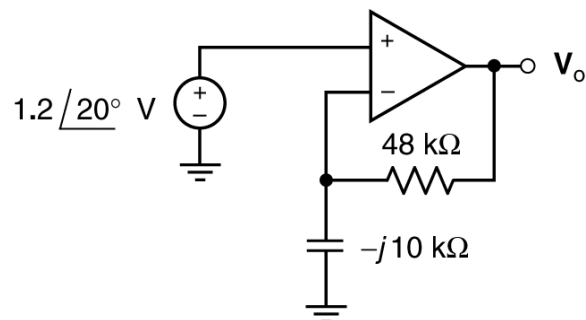Represent the circuit in the frequency domain as



Recognizing this circuit as a noninverting amplifier, we can write

$$\mathbf{V}_o = \left(1 + \frac{48}{-j10} \right) (1.2\angle 20^\circ) = (1 + j4.8)(1.2\angle 20^\circ) = 5.88\angle 98^\circ \text{ V}$$

In the time domain


$$v_o(t) = 5.88 \cos(400t + 98^\circ) \text{ V}$$

(Checked using LNAPAC 3/15/12)

P 10.10-2

Solution:

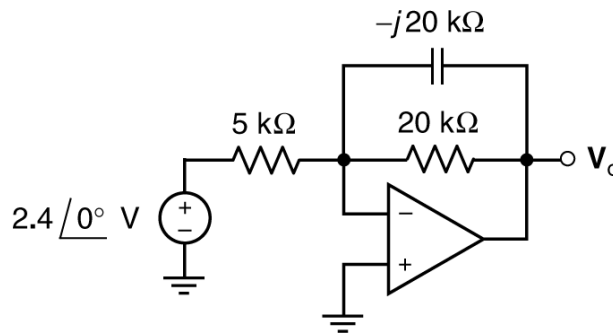Represent the circuit in the frequency domain as



Recognizing this circuit as an inverting amplifier, we can write

$$\mathbf{V}_o = \left(-\frac{20 \parallel -j20}{5} \right) (2.4 \angle 0^\circ) = \left((1 \angle 180^\circ) \frac{14.14 \angle -45^\circ}{5} \right) (2.4 \angle 0^\circ) = 6.788 \angle 135^\circ \text{ V}$$

In the time domain


$$v_o(t) = 6.788 \cos(500t + 135^\circ) \text{ V}$$

(Checked using LNAPAC 3/15/12)

P 10.10-3

Solution:

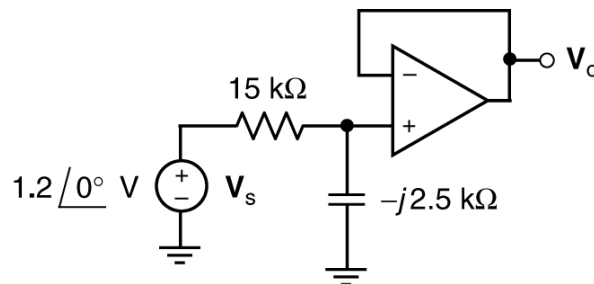Represent the circuit in the frequency domain as



Recognizing this circuit as a voltage divider followed by a voltage follower, we can write

$$\mathbf{V}_o = \left(\frac{-j2.5}{15 - j2.5} \right) (1.2 \angle 0^\circ) = \left(\frac{2.5 \angle -90^\circ}{15.2 \angle -9.46^\circ} \right) (1.2 \angle 0^\circ) = 0.1974 \angle -80.54^\circ \text{ V}$$

In the time domain


$$v_o(t) = 0.1974 \cos(400t - 80.54^\circ) \text{ V}$$

(Checked using LNAPAC 3/15/12)

P 10.10-4

Solution:

Label the nodes:

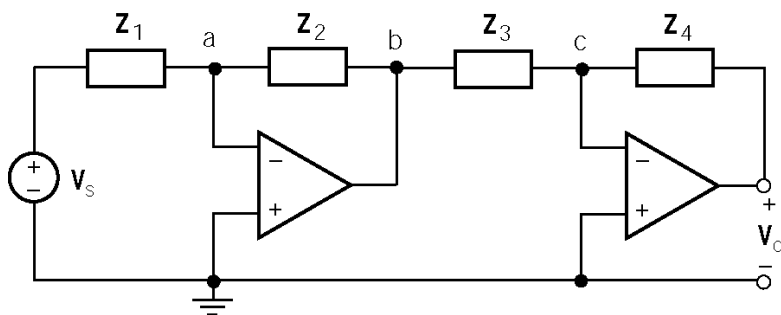

The ideal op amps force $V_a = 0$ and $V_c = 0$.

Apply KCL at node a to get

$$V_b = \frac{Z_2}{Z_1 + Z_2} V_s$$

Apply KCL at node c to get

$$V_o = \frac{Z_4}{Z_3 + Z_4} V_b$$

Therefore

$$\frac{V_o}{V_s} = \frac{Z_4}{Z_3 + Z_4} \times \frac{Z_2}{Z_1 + Z_2}$$

P 10.10-5

Solution:

Label a node voltage as \mathbf{V}_a in each of the circuits.

In both circuits, we can apply KCL at the node between \mathbf{Z}_3 and \mathbf{Z}_4 to get

$$\mathbf{V}_o = \frac{\mathbf{Z}_4}{\mathbf{Z}_3 + \mathbf{Z}_4} \mathbf{V}_a$$

In (a)

$$\begin{aligned} \mathbf{V}_a &= \frac{\mathbf{Z}_2 \parallel (\mathbf{Z}_3 + \mathbf{Z}_4)}{\mathbf{Z}_1 + \mathbf{Z}_2 \parallel (\mathbf{Z}_3 + \mathbf{Z}_4)} \mathbf{V}_s \\ &= \frac{\mathbf{Z}_2 (\mathbf{Z}_3 + \mathbf{Z}_4)}{\mathbf{Z}_1 (\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4) + \mathbf{Z}_2 (\mathbf{Z}_3 + \mathbf{Z}_4)} \mathbf{V}_s \end{aligned}$$

so

$$\frac{\mathbf{V}_a}{\mathbf{V}_s} = \frac{\mathbf{Z}_2 \mathbf{Z}_4}{\mathbf{Z}_1 (\mathbf{Z}_2 + \mathbf{Z}_3 + \mathbf{Z}_4) + \mathbf{Z}_2 (\mathbf{Z}_3 + \mathbf{Z}_4)}$$

In (b)

$$\mathbf{V}_a = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}_s$$


so

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{\mathbf{Z}_4}{\mathbf{Z}_3 + \mathbf{Z}_4} \times \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2}$$


P 10.10-6

Solution:

The network function of the circuit is

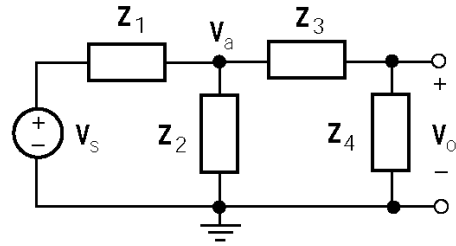

(a)

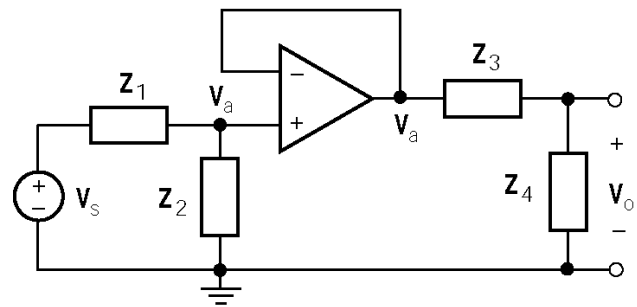

(b)

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = \left(1 + \frac{R_2}{1000}\right) \frac{\frac{1}{j\omega C}}{R_1 + \frac{1}{j\omega C}} = \frac{1 + \frac{R_2}{1000}}{1 + j\omega C R_1} = \frac{1 + \frac{R_2}{1000}}{1 + j10^{-3} R_1}$$

Converting the given input and output sinusoids to phasors gives

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{5 \angle 71.6^\circ}{2}$$

Consequently

$$\frac{5 \angle 71.6^\circ}{2} = \frac{1 + \frac{R_2}{1000}}{1 + j10^{-3} R_1}$$

Equating angles gives

$$71.6^\circ = -\tan^{-1}(10^{-3} R_1) \Rightarrow R_1 = \tan(71.6^\circ) \times 10^3 = 3006 \, \Omega$$


Equating magnitudes gives

$$\frac{5}{2} = \frac{1 + \frac{R_2}{1000}}{\sqrt{1 + (10^{-3} R_1)^2}} = \frac{1 + \frac{R_2}{1000}}{\sqrt{1 + (10^{-3} \times 3006)^2}} \Rightarrow R_2 = \left(\frac{5}{2} \sqrt{10} - 1\right) \times 10^3 = 6906 \, \Omega$$

P 10.10-7

Solution:

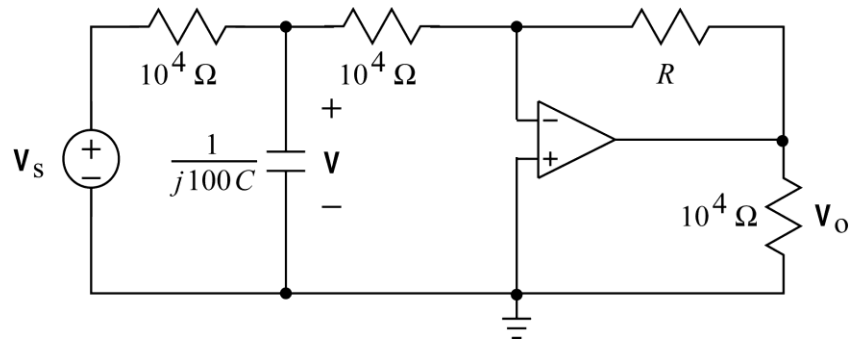Represent the circuit in the frequency domain as



Apply KCL at the top node of the impedance of the capacitor to get

$$\frac{\mathbf{V}_s - \mathbf{V}}{10^4} = \frac{\mathbf{V}}{\frac{1}{j100C}} + \frac{\mathbf{V}}{10^4} \Rightarrow \frac{1}{2}\mathbf{V}_s = (1 + j(5 \times 10^5)C)\mathbf{V}$$

Apply KCL at the inverting node of the op amp to get

$$\frac{\mathbf{V}}{10^4} + \frac{\mathbf{V}_o}{R} = 0 \Rightarrow \mathbf{V}_o = -\frac{R}{10^4}\mathbf{V}$$

so

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{-\frac{R}{2 \times 10^4}}{1 + j(5 \times 10^5)C}$$

Converting the input and output sinusoids to phasors gives

$$\frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{8 \angle 135^\circ}{4 \angle 0^\circ} = 2 \angle 135^\circ$$

so

$$2 \angle 135^\circ = \frac{-\frac{R}{2 \times 10^4}}{1 + j(5 \times 10^5)C} = \frac{\frac{R}{2 \times 10^4}}{\sqrt{1 + [(5 \times 10^5)C]^2}} \angle 180^\circ - \tan^{-1}((5 \times 10^5)C)$$

Equating angles gives


$$135^\circ = 180^\circ - \tan^{-1}((5 \times 10^5)C) \Rightarrow C = \frac{\tan(45^\circ)}{5 \times 10^5} = 2 \times 10^{-6} = 2 \mu\text{F}$$

Next, equating magnitudes gives

$$2 = \frac{\frac{R}{2 \times 10^4}}{\sqrt{1 + (5 \times 10^5)(2 \times 10^{-6})}} = \frac{\frac{R}{2 \times 10^4}}{\sqrt{2}} \Rightarrow R = 10^4 = 10 \text{ k}\Omega$$

P 10.10-8

Solution:

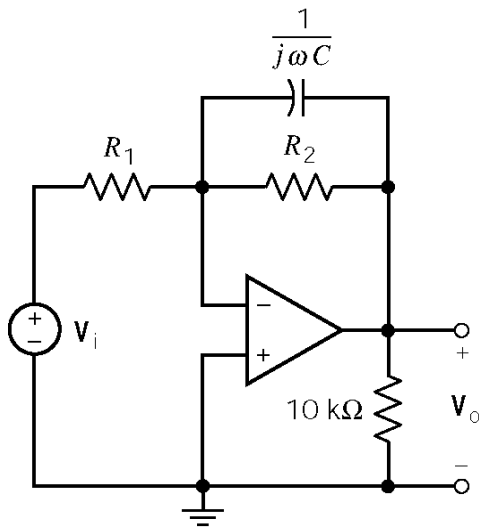

$$R_2 \left\| \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega CR_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = -\frac{\frac{R_2}{1 + j\omega CR_2}}{R_1} = -\frac{\frac{R_2}{R_1}}{1 + j\omega CR_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\frac{R_2}{R_1}}{\sqrt{1 + (\omega CR_2)^2}} e^{j(180 - \tan^{-1} \omega CR_2)}$$

In this case the angle of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be 104° so $CR_2 = \frac{\tan(180^\circ - 104^\circ)}{1000} = 0.004$ and the

magnitude of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be $\frac{8}{2.5}$ so $\frac{\frac{R_2}{R_1}}{\sqrt{1+16}} = \frac{8}{2.5} \Rightarrow \frac{R_2}{R_1} = 13.2$. One set of values


that satisfies these two equations is $C = 0.2 \mu\text{F}$, $R_1 = 1515 \Omega$, $R_2 = 20 \text{ k}\Omega$.

Section 10.11 The Complete Response

P10.11-1

Solution:

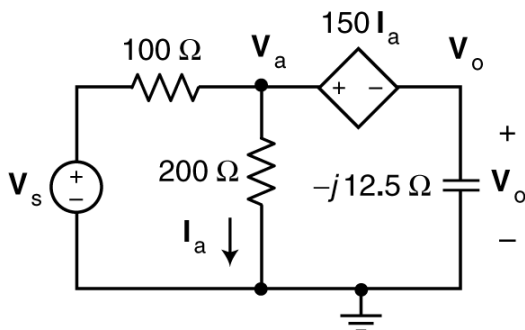Before the switch closes the circuit is represented in the frequency domain as



Express the dependent source voltage in terms of the node voltages:

$$150 I_a = V_a - V_o$$

Using Ohm's law

$$150 \frac{V_a}{200} = V_a - V_o$$

so

$$\mathbf{V}_o = \frac{1}{4} \mathbf{V}_a$$

Apply KCL to the supernode corresponding to the dependent source to get

$$\frac{\mathbf{V}_s - \mathbf{V}_a}{100} = \frac{\mathbf{V}_a}{200} + \frac{\mathbf{V}_o}{-j12.5} \Rightarrow \mathbf{V}_o = \frac{-j12.5}{100} \mathbf{V}_s - \left(\frac{-j12.5}{100} + \frac{-j12.5}{200} \right) \mathbf{V}_a$$


$$\mathbf{V}_o = -j0.125(12\angle 0^\circ) + j0.1875(4\mathbf{V}_o)$$

$$\mathbf{V}_o(1 - j0.75) = -j0.125(12\angle 0^\circ) \Rightarrow \mathbf{V}_o = \frac{-j0.125(12\angle 0^\circ)}{1 - j0.75} = 1.2\angle -53.1^\circ \text{ V}$$

The corresponding sinusoid is $1.2 \cos(4000t - 53.1^\circ) \text{ V}$. The initial capacitor voltage is

$$v_o(0) = 1.2 \cos(-53.1^\circ) = 0.7205 \text{ V}.$$

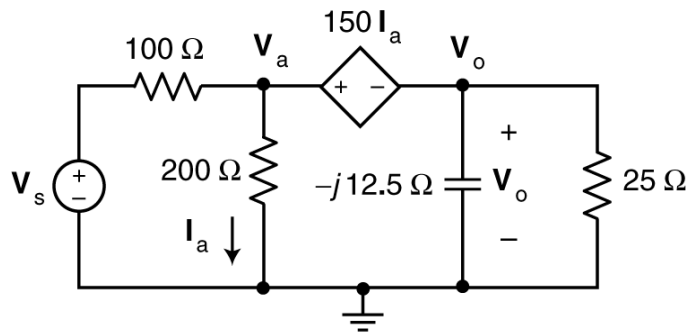The steady state response **after the switch closes** is the forced response. The circuit is represented in the frequency domain as



Express the dependent source voltage in terms of the node voltages:

$$150 I_a = \mathbf{V}_a - \mathbf{V}_o$$

Using Ohm's law

$$150 \frac{\mathbf{V}_a}{200} = \mathbf{V}_a - \mathbf{V}_o$$

so

$$\mathbf{V}_o = \frac{1}{4} \mathbf{V}_a$$

Apply KCL to the supernode corresponding to the dependent source to get

$$\frac{\mathbf{V}_s - \mathbf{V}_a}{100} = \frac{\mathbf{V}_a}{200} + \frac{\mathbf{V}_o}{-j12.5} + \frac{\mathbf{V}_o}{25} \Rightarrow \mathbf{V}_o \left(\frac{1}{-j12.5} + \frac{1}{25} \right) = \frac{1}{100} \mathbf{V}_s - \left(\frac{1}{100} + \frac{1}{200} \right) \mathbf{V}_a$$

Multiply by 200 to get

$$\mathbf{V}_o(8 + j16) = 2(12\angle 0^\circ) - 3(4\mathbf{V}_o) \Rightarrow \mathbf{V}_o = \frac{24}{20 + j16} = 0.937\angle -38.7^\circ \text{ V}$$


The corresponding sinusoid is the forced response:

$$v_f(t) = 0.937 \cos(4000t - 38.7^\circ) \text{ V}$$


The natural response is

$$v_n(t) = k e^{-t/\tau} \text{ V}$$

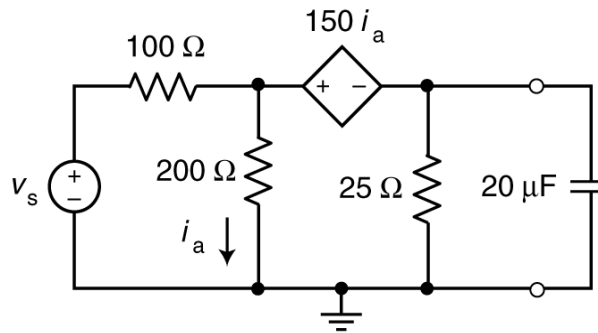To determine the time constant τ we need find to find the Thevenin resistance of the part of the circuit connected to the capacitor after the switch closes. Here's the circuit:



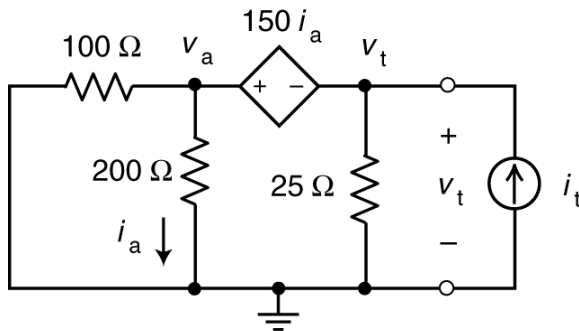The terminals separate the capacitor from the part of the circuit connected to the capacitor. Now (1) remove the capacitor, (2) replace the voltage source by a short circuit to set the input to zero and (3) connect a current source to the terminals to get



The Thevenin resistance is given by

$$R_t = \frac{v_t}{i_t}$$

Express the dependent source voltage in terms of the node voltages to get

$$v_a - v_t = 150 i_a = 150 \frac{v_a}{200} \Rightarrow v_a = 4 v_t$$

Apply KCL to the supernode corresponding to the dependent source to get

$$i_t = \frac{v_a}{100} + \frac{v_a}{200} + \frac{v_t}{25} = \frac{4v_t}{100} + \frac{4v_t}{200} + \frac{v_t}{25} = \frac{v_t}{10} \Rightarrow R_t = \frac{v_t}{i_t} = 10 \Omega$$

The time constant is $\tau = R_t C = 10(20 \times 10^{-6}) = 0.2 \times 10^{-3} = 0.2 \text{ ms}$

The natural response is $v_n(t) = k e^{-t/\tau} = k e^{-5000t} \text{ V}$

The complete response is

$$v_o(t) = 0.937 \cos(4000t - 38.7^\circ) + k e^{-5000t} \text{ V for } t \geq 0$$

Using the initial condition we calculate

$$0.7205 = v_o(0) = 0.937 \cos(-38.7^\circ) + k \Rightarrow k = -0.0108$$


Finally $v_o(t) = 0.937 \cos(4000t - 38.8^\circ) - 0.0108 e^{-5000t} \text{ V for } t \geq 0$

Section 10.12 Using MATLAB to Analyze Electric Circuits

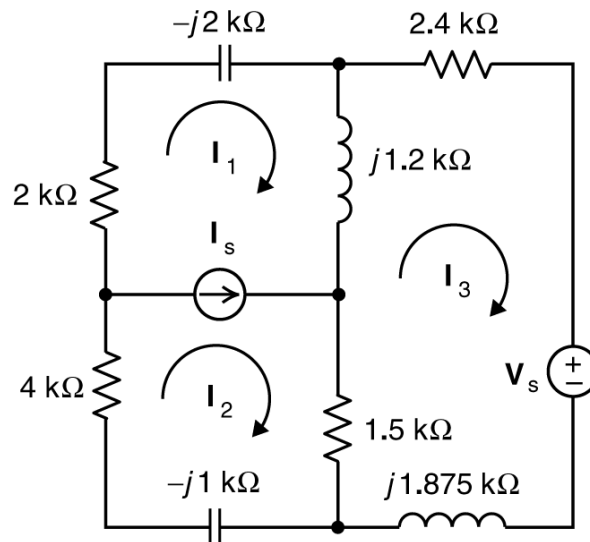10.12-1

Solution:

Represent the circuit in the frequency domain:



Represent the source current in terms of the mesh currents: $\mathbf{I}_2 - \mathbf{I}_1 = \mathbf{I}_s = 0.002 \angle -15^\circ \text{ A}$

Apply KVL to the supermesh corresponding to the current source:

$$(2000 - j2000)\mathbf{I}_1 + j1200(\mathbf{I}_1 - \mathbf{I}_3) + 1500(\mathbf{I}_2 - \mathbf{I}_3) + (4000 - j1000)\mathbf{I}_2 = 0$$

Apply KVL to mesh 3:

$$(2400 + j1875)\mathbf{I}_3 + 1500(\mathbf{I}_3 - \mathbf{I}_2) + j1200(\mathbf{I}_3 - \mathbf{I}_1) = -\mathbf{V}_s = -12 \angle 60^\circ$$

In matrix form:
$$\begin{bmatrix} -1 & 1 & 0 \\ 2000 - j800 & 5500 - j1000 & -1500 - j1200 \\ -j1200 & -1500 & 3900 + j3075 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 0.002 \angle -15^\circ \\ 0 \\ -12 \angle 60^\circ \end{bmatrix}$$


Solving, using MATLAB, gives
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 1.549 \angle -164^\circ \\ 1.039 \angle -65^\circ \\ 2.904 \angle -148^\circ \end{bmatrix} \text{ mA}$$

In the time domain:
$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 1.549 \cos(2500t - 164^\circ) \\ 1.039 \cos(2500t - 65^\circ) \\ 2.904 \cos(2500t - 148^\circ) \end{bmatrix} \text{ mA}$$

P 10.12-2

Solution:

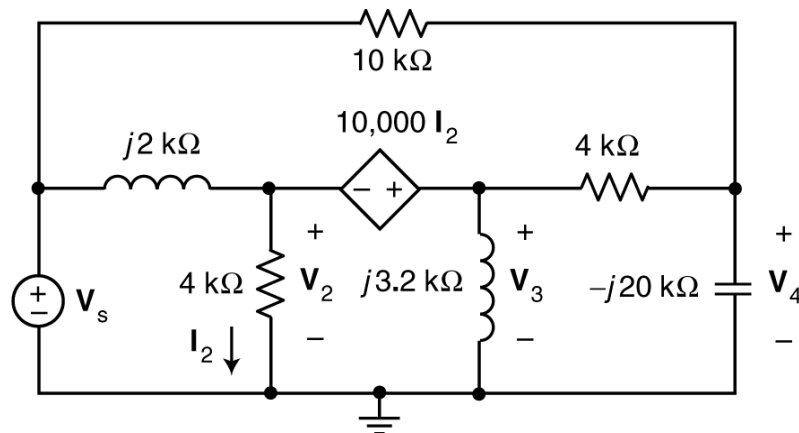Represent the circuit in the frequency domain:



Represent the dependent source voltage in terms of the node voltages currents:

$$\mathbf{V}_3 - \mathbf{V}_2 = 10000 \frac{\mathbf{V}_2}{4000} \Rightarrow \mathbf{V}_3 = 3.5 \mathbf{V}_2$$

Apply KCL to the supernode corresponding to the dependent voltage source:

$$\frac{\mathbf{V}_s - \mathbf{V}_2}{j2000} = \frac{\mathbf{V}_2}{4000} + \frac{\mathbf{V}_3}{j3200} + \frac{\mathbf{V}_3 - \mathbf{V}_4}{4000}$$

Rearranging:
$$\frac{\mathbf{V}_s}{j2000} = \left(\frac{1}{4000} + \frac{1}{j2000} \right) \mathbf{V}_2 + \left(\frac{1}{4000} + \frac{1}{j3200} \right) \mathbf{V}_3 - \left(\frac{1}{4000} \right) \mathbf{V}_4$$

Apply KCL at node 3:
$$\frac{\mathbf{V}_s - \mathbf{V}_4}{10,000} + \frac{\mathbf{V}_3 - \mathbf{V}_4}{4000} = \frac{\mathbf{V}_4}{-j20,000}$$

Rearranging:
$$\frac{\mathbf{V}_s}{10,000} = -\frac{\mathbf{V}_3}{4000} + \left(\frac{1}{4000} + \frac{1}{10,000} + \frac{1}{-j20,000} \right) \mathbf{V}_4$$

In matrix form:
$$\begin{bmatrix} 3.5 & -1 & 0 \\ \frac{1}{4000} + \frac{1}{j2000} & \frac{1}{4000} + \frac{1}{j3200} & -\frac{1}{4000} \\ 0 & -\frac{1}{4000} & \frac{1}{4000} + \frac{1}{10,000} + \frac{1}{-j20,000} \end{bmatrix} \begin{bmatrix} \mathbf{V}_2 \\ \mathbf{V}_3 \\ \mathbf{V}_4 \end{bmatrix} = \begin{bmatrix} 0 \\ \frac{\mathbf{V}_s}{j2000} \\ \frac{\mathbf{V}_s}{10,000} \end{bmatrix}$$

Solving, using MATLAB, gives
$$\begin{bmatrix} \mathbf{V}_2 \\ \mathbf{V}_3 \\ \mathbf{V}_4 \end{bmatrix} = \begin{bmatrix} 3.236 \angle 34^\circ \\ 11.324 \angle 34^\circ \\ 10.798 \angle 29^\circ \end{bmatrix} \text{ V}$$

In the time domain:
$$\begin{bmatrix} v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 3.236 \cos(400t + 34^\circ) \\ 11.324 \cos(400t + 34^\circ) \\ 10.798 \cos(400t + 29^\circ) \end{bmatrix} \text{ V}$$

P 10.12-3

Solution:

Represent the source current in terms of the mesh currents: $\mathbf{I}_1 - \mathbf{I}_2 = 4.2 \angle 30^\circ \text{ A}$

Apply KVL to the supermesh corresponding to the current source:

$$j8(\mathbf{I}_1 - \mathbf{I}_o) + 5[j8(\mathbf{I}_1 - \mathbf{I}_o)] + (4 + j5)\mathbf{I}_2 + (3 - j8)\mathbf{I}_1 = 0$$

Apply KVL to mesh 3: $5\mathbf{I}_o + 6(j8)(\mathbf{I}_1 - \mathbf{I}_o) = 0$


In matrix form:
$$\begin{bmatrix} 1 & -1 & 0 \\ 3 + j40 & 4 + j5 & -j48 \\ -j48 & 0 & 5 + j48 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_o \end{bmatrix} = \begin{bmatrix} 4.2 \angle 30^\circ \\ 0 \\ 0 \end{bmatrix}$$

Solving, using MATLAB, gives
$$\begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_o \end{bmatrix} = \begin{bmatrix} 2.204 \angle 93.1^\circ \\ 3.758 \angle 178^\circ \\ 2.192 \angle 99^\circ \end{bmatrix} \text{ A}$$

P 10.12-4

Solution:

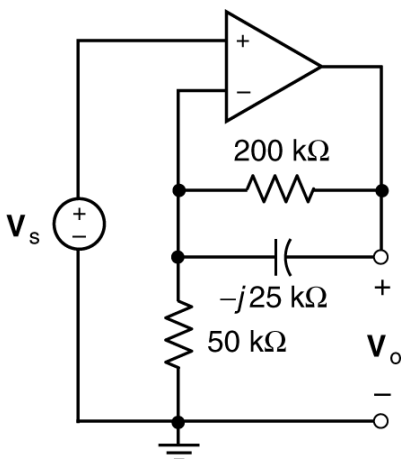Represent the circuit in the frequency domain:



Write a node equation: $\frac{12\angle 60^\circ - V_o}{200,000} + \frac{12\angle 60^\circ - V_o}{-j25,000} + \frac{12\angle 60^\circ}{20,000} = 0$

Rearrange: $\left(\frac{1}{200,000} + \frac{1}{-j25,000} + \frac{1}{20,000} \right) 12\angle 60^\circ = \left(\frac{1}{200,000} + \frac{1}{-j25,000} \right) V_o$

Modify the MATLAB script given in the textbook (and posted on the Student Companion Site for *Introduction to Electric Circuits*):

```
%-----
%           Describe the input voltage source.
%-----

w = 20000;

A = 12;

theta = (pi/180)*60;

Vs = A*exp(j*theta);

%-----
%           Describe the impedances.
%-----

R1=50e3; R2=200e3; zC=-j*25e3;

%-----
%           Calculate the phasor corresponding to the
%           output voltage.
%-----
```

```

Vo=(1/R2 + 1/ZC + 1/R1)*Vs/(1/R2 + 1/ZC);

B = abs(Vo)

phi = angle(Vo)

%-----

%

%-----

T = 2*pi/w;

tf = 2*T; N = 100; dt = tf/N;

t = 0 : dt : tf;

%-----

%      Plot the input and output voltages.

%-----

for k = 1 : 101

    vs(k) = A * cos(w * t(k) + theta);


    vo(k) = B * cos(w * t(k) + phi);

end

plot (t, vs, t, vo)

```

to get the plot:

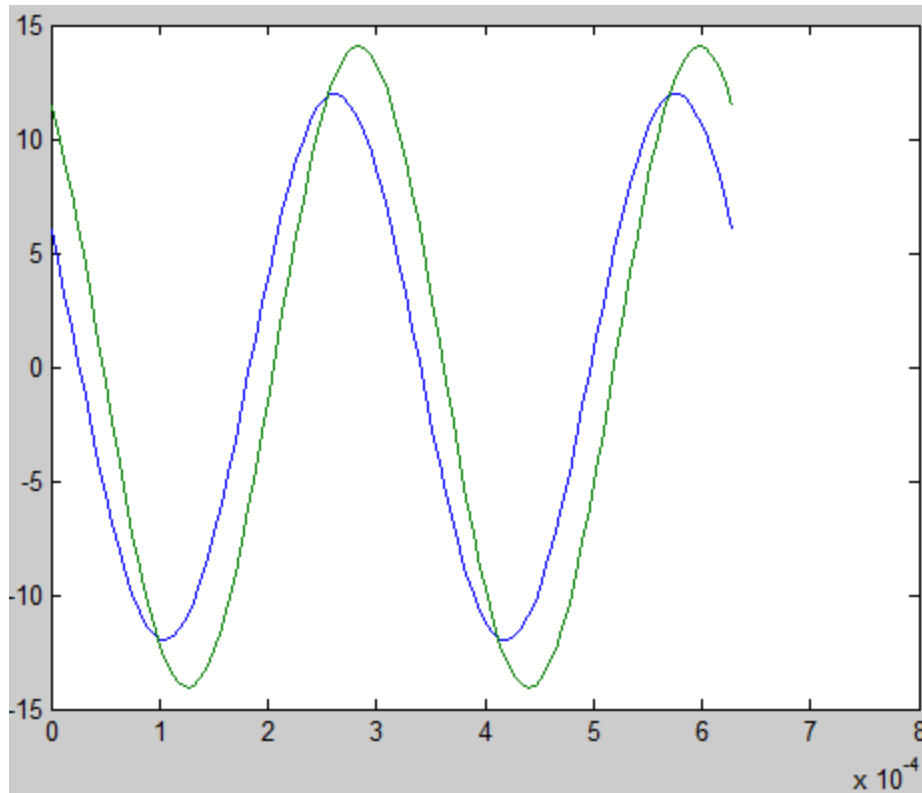

Section 10.14 How Can We Check...?

P 10.14-1

Solution:

Generally, it is more convenient to divide complex numbers in polar form. Sometimes, as in this case, it is more convenient to do the division in rectangular form.

Express \mathbf{V}_1 and \mathbf{V}_2 as: $\mathbf{V}_1 = -j20$ and $\mathbf{V}_2 = 20 - j40$

KCL at node 1:

$$2 - \frac{\mathbf{V}_1}{10} - \frac{\mathbf{V}_1 - \mathbf{V}_2}{j10} = 2 - \frac{-j20}{10} - \frac{-j20 - (20 - j40)}{j10} = 2 + j2 - 2 - j2 = 0$$


KCL at node 2:

$$\frac{\mathbf{V}_1 - \mathbf{V}_2}{j10} - \frac{\mathbf{V}_2}{10} + 3\left(\frac{\mathbf{V}_1}{10}\right) = \frac{-j20 - (20 - j40)}{j10} - \frac{20 - j40}{10} + 3\left(\frac{-j20}{10}\right) = (2 + j2) - (2 - j4) - j6 = 0$$

The currents calculated from \mathbf{V}_1 and \mathbf{V}_2 satisfy KCL at both nodes, so it is very likely that the \mathbf{V}_1 and \mathbf{V}_2 are correct.

P 10.14-2

Solution:

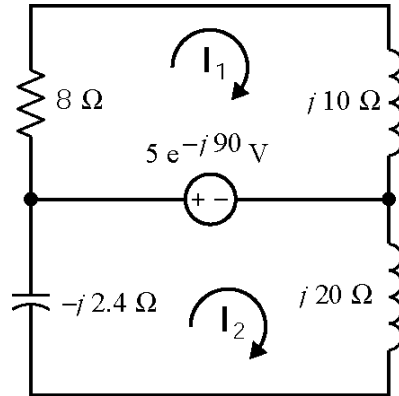

$$\mathbf{I}_1 = 0.390 \angle 39^\circ \text{ and } \mathbf{I}_2 = 0.284 \angle 180^\circ$$

Generally, it is more convenient to multiply complex numbers in polar form. Sometimes, as in this case, it is more convenient to do the multiplication in rectangular form.

Express \mathbf{I}_1 and \mathbf{I}_2 as: $\mathbf{I}_1 = 0.305 + j0.244$ and $\mathbf{I}_2 = -0.284$

KVL for mesh 1:

$$8(0.305 + j0.244) + j10(0.305 + j0.244) - (-j5) = j10 \neq 0$$

Since KVL is not satisfied for mesh 1, the mesh currents are not correct.

Here is a MATLAB file for this problem:

```
Vs = -j*5;

Z1 = 8;

Z2 = j*10;

Z3 = -j*2.4;

Z4 = j*20;

% Mesh equations in matrix form

Z = [ Z1+Z2      0;
      0      Z3+Z4 ];

V = [ Vs;
      -Vs ];

I = Z\V

abs(I)

angle(I)*180/3.14159

% Verify solution by obtaining the algebraic sum of voltages for

% each mesh. KVL requires that both M1 and M2 be zero.
```


$$M1 = -V_s + Z1 \cdot I(1) + Z2 \cdot I(1)$$

$$M2 = V_s + Z3 \cdot I(2) + Z4 \cdot I(2)$$

P 10.14-3

Solution: First, replace the parallel resistor and capacitor by an equivalent impedance
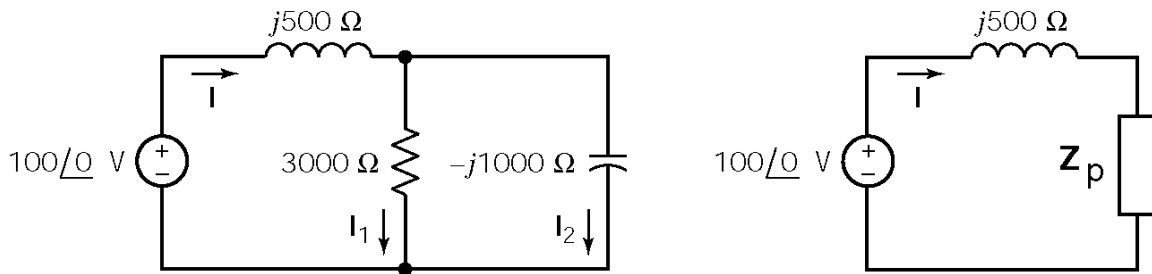
$$Z_p = \frac{(3000)(-j1000)}{3000 - j1000} = 949 \angle -72^\circ = 300 - j900 \Omega$$



The current is given by

$$I = \frac{V_s}{j500 + Z_p} = \frac{100 \angle 0^\circ}{j500 + 300 - j900} = 0.2 \angle 53^\circ \text{ A}$$

Current division yields

$$I_1 = \left(\frac{-j1000}{3000 - j1000} \right) (0.2 \angle 53^\circ) = 63.3 \angle -18.5^\circ \text{ mA}$$

$$I_2 = \left(\frac{3000}{3000 - j1000} \right) (0.2 \angle 53^\circ) = 190 \angle 71.4^\circ \text{ mA}$$

The reported value of I_1 is off by an order of magnitude.

P 10.14-4**Solution:**

Represent the circuit in the frequency domain using phasors and impedances. Use voltage division to get

$$18.3\angle -24^\circ = \frac{\frac{1}{j200C}}{R + \frac{1}{j200C}} \times 20\angle 0^\circ$$

So
$$0.915\angle -24^\circ = \frac{1}{1 + j200CR} = \frac{1}{\sqrt{1 + (200CR)^2}} \angle -\tan^{-1}(200CR)$$

Equating angles gives

$$-24^\circ = -\tan^{-1}(200CR) \Rightarrow 200CR = \tan(24^\circ) = 0.4452$$

The nominal component values cause $200CR = 0.5$. So we expect that the actual component values are smaller than the nominal values.

Try
$$C = 5(1 - 0.10) \times 10^{-6} = 4.5 \mu\text{F}$$

Then
$$R = \frac{0.4452}{200 \times 4.5 \times 10^{-6}} = 494.67 \Omega$$

Since $\frac{500 - 494.67}{500} = 0.01066 = 1.066\%$ this resistance is within 2% of 500Ω . We conclude that the measured angle could have been caused by a capacitance that is within 10% of $5 \mu\text{F}$ and the resistance is within 2% of 500Ω . Let's check the amplitude. We require

$$\frac{1}{\sqrt{1 + (0.4452)^2}} = 0.9136 \approx 0.915$$



So the measured amplitude could also have been caused by the given circuit with $C = 4.5 \mu\text{F}$ and $R = 494.67 \Omega$.

We conclude that the measured capacitor voltage could indeed have been produced by the given circuit with a resistance that is within 2 % of 500Ω and a capacitance that is within 10% of $5 \mu\text{F}$.

PSpice Problems


SP 10-1

Solution:

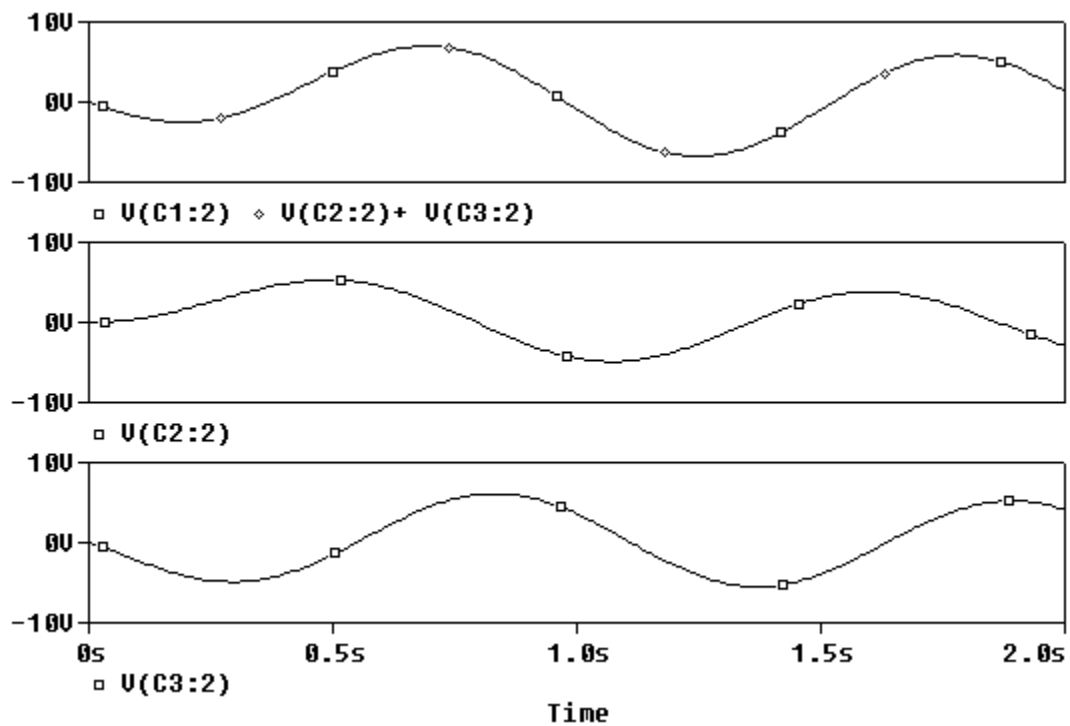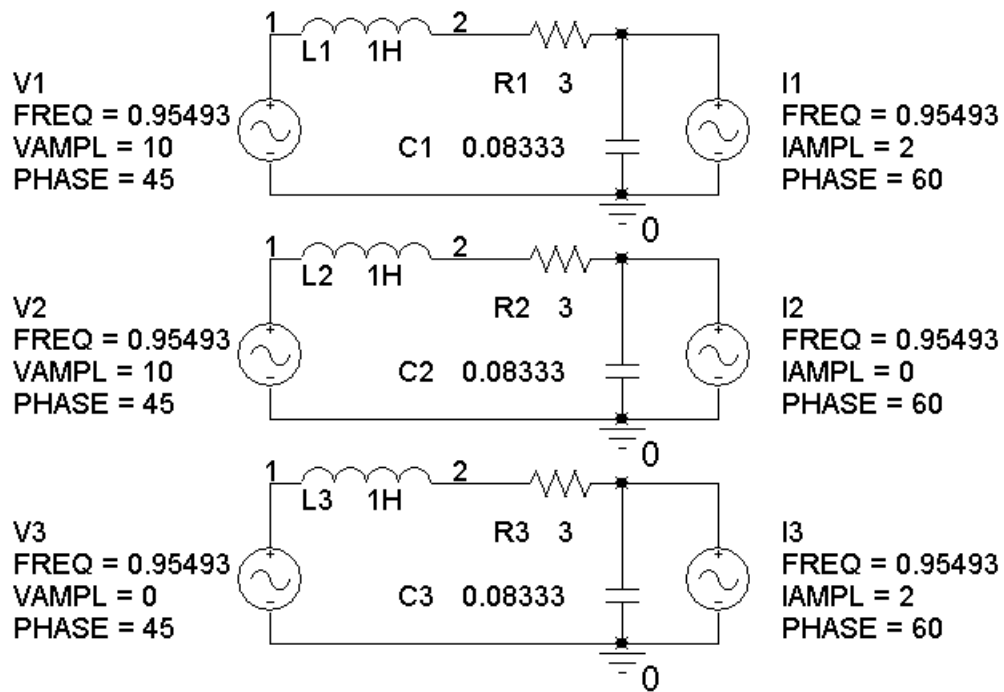



SP 10-2

Solution:

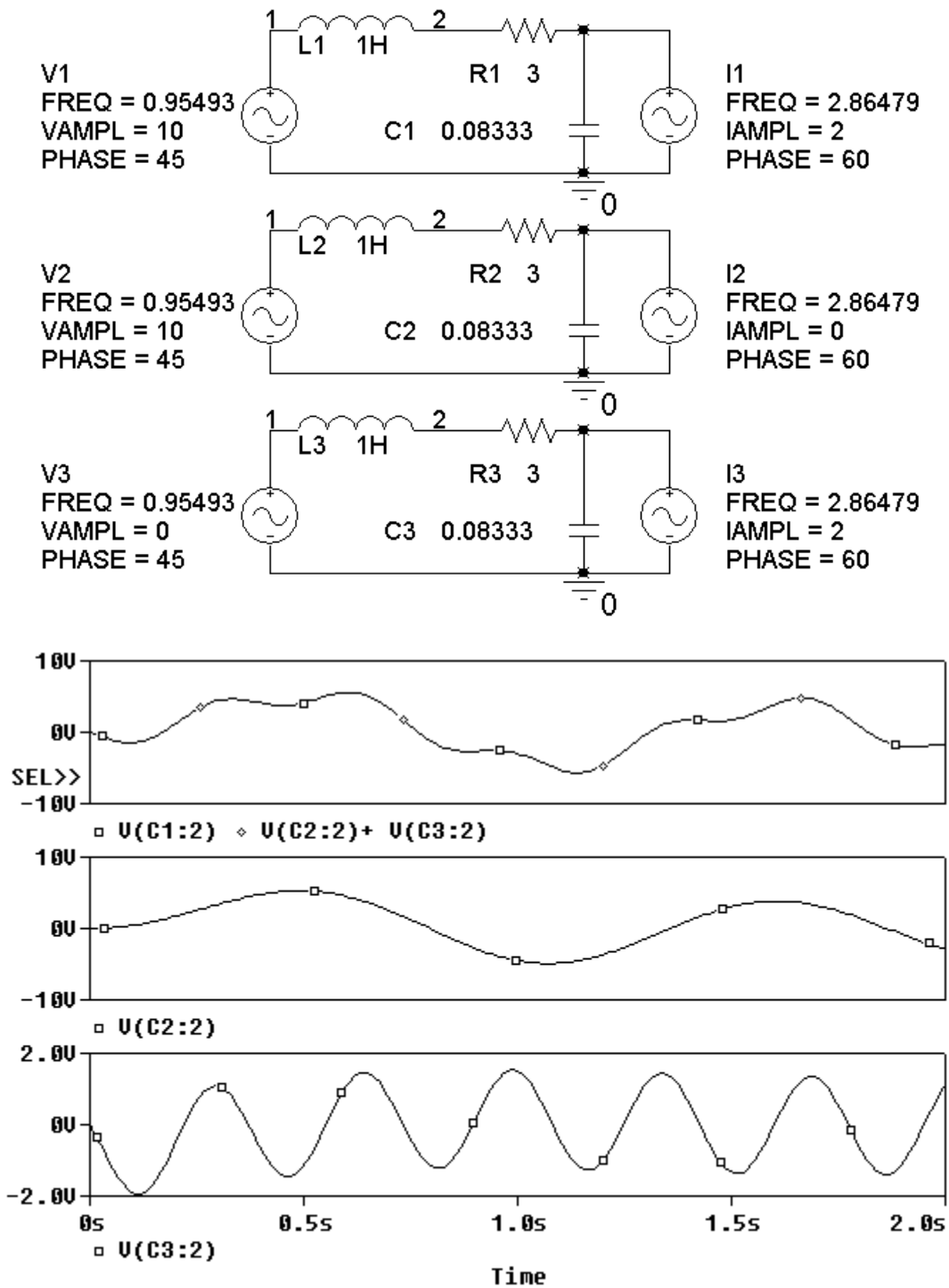

SP 10-3


Solution:

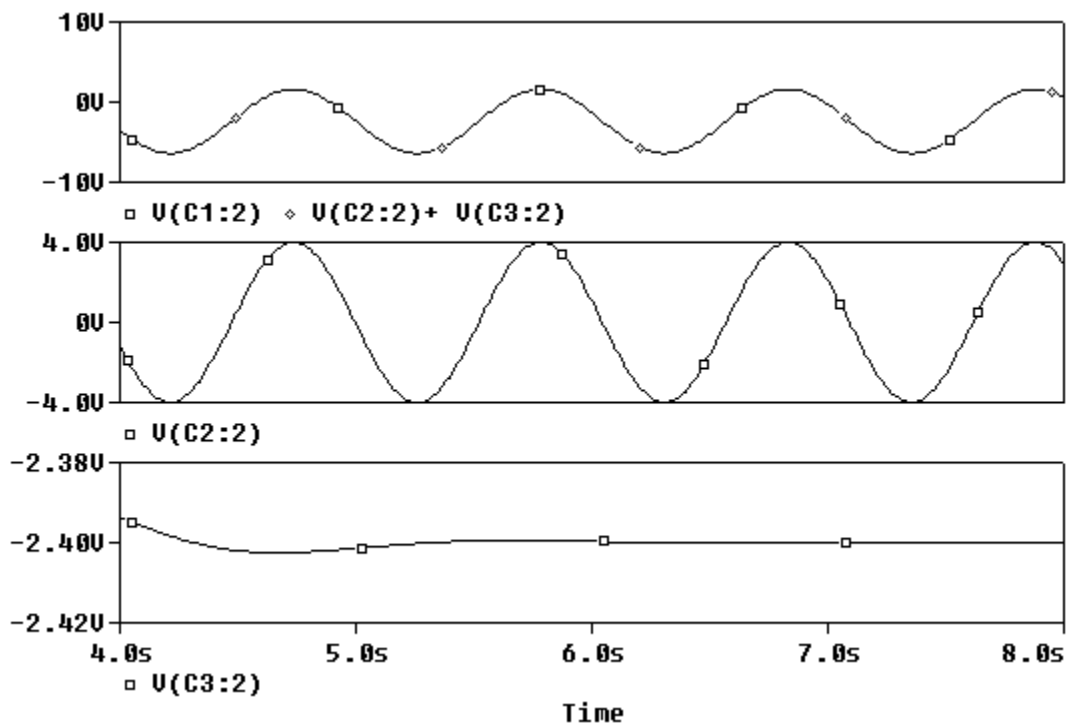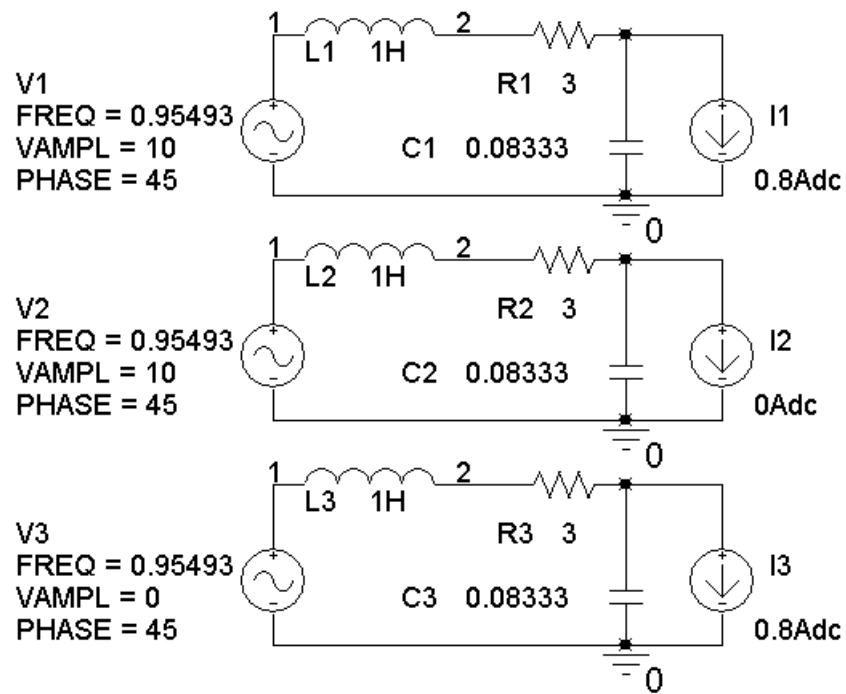


SP 10-4

Solution:

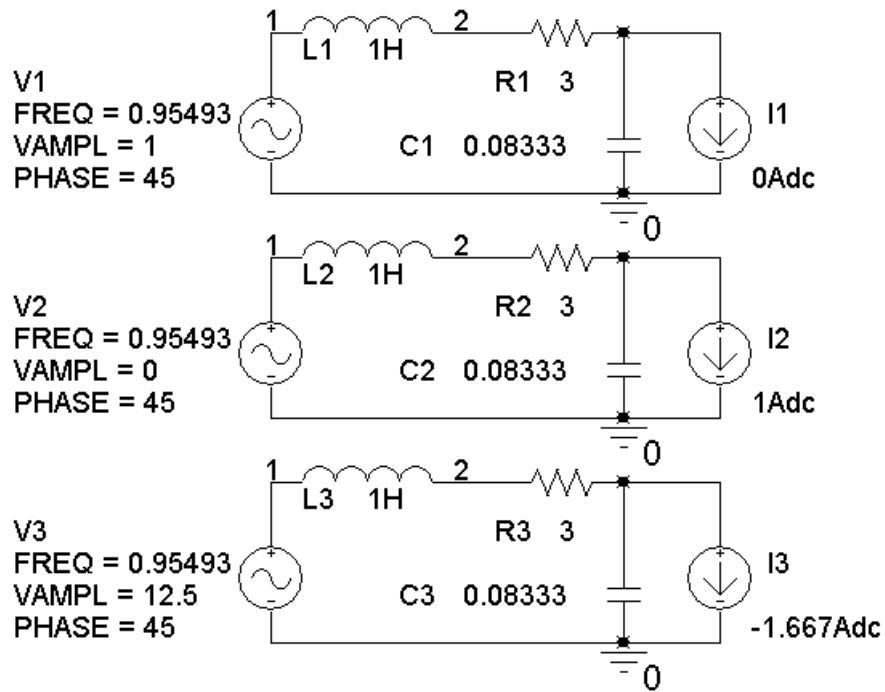The following simulation shows that $k_1 = 0.4$ and $k_2 = -3$ V/A. The required values of V_m and I_m are $V_m = 12.5$ V and $I_m = -1.667$ A.




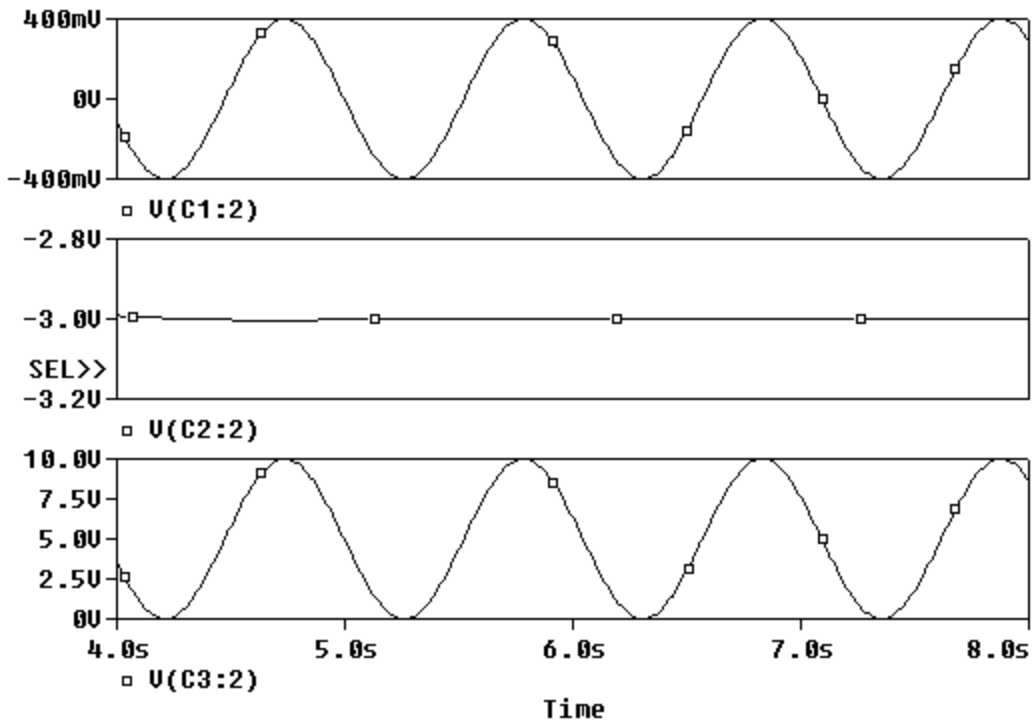

Design Problems

DP 10-1

Solution:

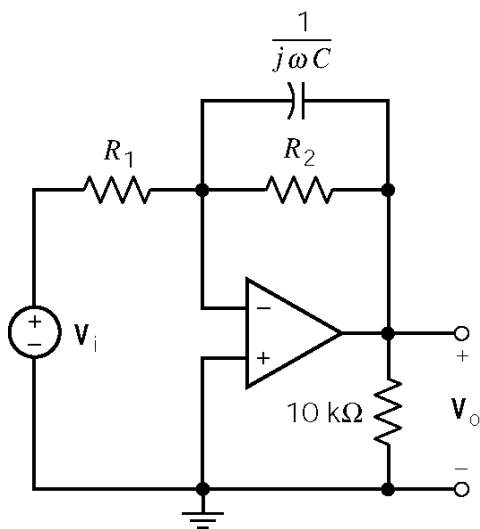

$$R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega CR_2}$$

$$\frac{V_o(\omega)}{V_i(\omega)} = -\frac{\frac{R_2}{1 + j\omega CR_2}}{R_1} = -\frac{\frac{R_2}{R_1}}{1 + j\omega CR_2}$$


$$\frac{V_o(\omega)}{V_i(\omega)} = \frac{\frac{R_2}{R_1}}{\sqrt{1 + (\omega CR_2)^2}} e^{j(180 - \tan^{-1} \omega CR_2)}$$

In this case the angle of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be 104° so $CR_2 = \frac{\tan(180^\circ - 104^\circ)}{1000} = 0.004$ and the

magnitude of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be $\frac{8}{2.5}$ so $\frac{\frac{R_2}{R_1}}{\sqrt{1+16}} = \frac{8}{2.5} \Rightarrow \frac{R_2}{R_1} = 13.2$. One set of values that satisfies these two equations is $C = 0.2 \mu\text{F}$, $R_1 = 1515 \Omega$, $R_2 = 20 \text{ k}\Omega$.

DP 10-2

Solution:

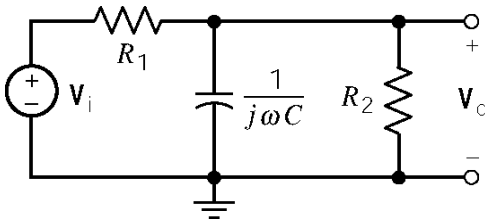

$$R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega CR_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\frac{R_2}{1 + j\omega CR_2}}{R_1 + \frac{R_2}{1 + j\omega CR_2}} = \frac{K}{1 + j\omega CR_p}$$


$$\text{where } K = \frac{R_1}{R_1 + R_2} \text{ and } R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{K}{\sqrt{1 + (\omega CR_p)^2}} e^{-j \tan^{-1} \omega CR_p}$$

In this case the angle of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be -76° so $CR_p = C \frac{R_1 R_2}{R_1 + R_2} = -\frac{\tan(-76^\circ)}{1000} = 0.004$

and the magnitude of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be $\frac{2.5}{12}$ so $\frac{K}{\sqrt{1+16}} = \frac{2.5}{12} \Rightarrow 0.859 = K = \frac{R_2}{R_1 + R_2}$.

One set of values that satisfies these two equations is $C = 0.2 \mu\text{F}$, $R_1 = 23.3 \text{ k}\Omega$, $R_2 = 142 \text{ k}\Omega$.

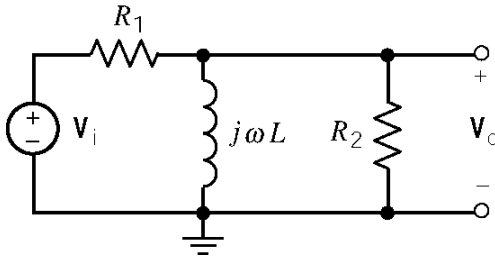DP 10-3**Solution:**

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\frac{j\omega L R_2}{R_2 + j\omega L}}{R_1 + \frac{j\omega L R_2}{R_2 + j\omega L}} = \frac{j\omega \frac{L}{R_1}}{1 + j\omega \frac{L}{R_p}}$$


$$\text{where } R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\omega \frac{L}{R_1}}{\sqrt{1 + \left(\omega \frac{L}{R_p}\right)^2}} e^{j\left(90^\circ - \tan^{-1} \omega \frac{L}{R_p}\right)}$$

In this case the angle of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be 14° so $\frac{L}{R_p} = \frac{L(R_1 + R_2)}{R_1 R_2} = \frac{\tan(90^\circ - 14^\circ)}{40} = 0.1$

and the magnitude of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be $\frac{2.5}{8}$ so $\frac{40 \frac{L}{R_1}}{\sqrt{1 + 16}} = \frac{2.5}{8} \Rightarrow \frac{L}{R_1} = 0.0322$. One set of

values that satisfies these two equations is $L = 1 \text{ H}$, $R_1 = 31 \Omega$, $R_2 = 14.76 \Omega$.

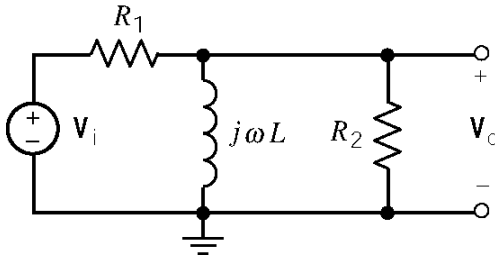DP 10-4**Solution:**

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\frac{j\omega L R_2}{R_2 + j\omega L}}{R_1 + \frac{j\omega L R_2}{R_2 + j\omega L}} = \frac{j\omega \frac{L}{R_1}}{1 + j\omega \frac{L}{R_p}}$$

$$\text{where } R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{\omega \frac{L}{R_1}}{\sqrt{1 + \left(\omega \frac{L}{R_p}\right)^2}} e^{j\left(90 - \tan^{-1} \omega \frac{L}{R_p}\right)}$$


In this case the angle of $\frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$ is specified to be -14° . This requires

$$\frac{L}{R_p} = \frac{L(R_1 + R_2)}{R_1 R_2} = \frac{\tan(90 + 14)}{40} = -0.1$$

This condition cannot be satisfied with positive element values.

DP 10-5

Solution:

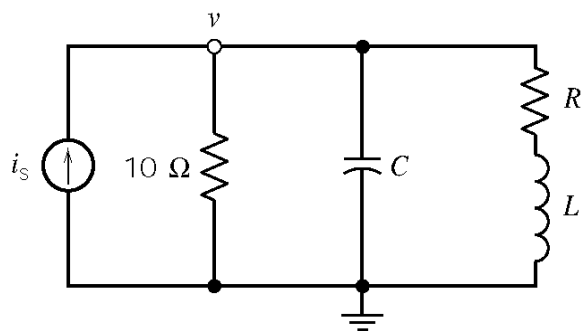

$$\begin{aligned} \mathbf{Z}_1 &= 10 \, \Omega & \mathbf{Y}_1 &= \frac{1}{10} \, \text{S} \\ \mathbf{Z}_2 &= \frac{1}{j\omega C} & \mathbf{Y}_2 &= j\omega C \\ \mathbf{Z}_3 &= R + j\omega L & \mathbf{Y}_3 &= \frac{1}{R + j\omega L} \end{aligned}$$

$$v(t) = 80 \cos(1000t - \theta) \, \text{V} \Rightarrow \mathbf{V} = 80 \angle -\theta \, \text{V}$$

$$i_s(t) = 10 \cos 1000t \, \text{A} \Rightarrow \mathbf{I}_s = 10 \angle 0^\circ \, \text{A}$$

try $\theta = 0^\circ$. Then

$$(80 \angle -\theta) \left[\frac{1}{10} + \frac{1}{R + j\omega L} + j\omega C \right] = 10 \angle 0^\circ \Rightarrow R + 10 - 10\omega^2 LC + j(\omega L + 10\omega RC) = 1.25R + j1.25\omega L$$

Equate real part: $40 - 40\omega^2 LC = R$ where $\omega = 1000 \, \text{rad/sec}$

Equate imaginary part: $40RC = L$

Solving yields $R = 40(1 - 4 \times 10^7 RC^2)$

Now try $R = 20 \, \Omega \Rightarrow 1 - 2(1 - 4 \times 10^7 (20)C^2)$

which yields $C = 2.5 \times 10^{-5} \, \text{F} = 25 \, \mu\text{F}$ so $L = 40RC = 0.02 \, \text{H} = 20 \, \text{mH}$

Now check the angle of the voltage. First

$$\mathbf{Y}_1 = 1/10 = 0.1 \, \text{S}$$

$$\mathbf{Y}_2 = j0.25 \, \text{S}$$

$$\mathbf{Y}_3 = 1/(20 + j20) = .025 - j.025 \, \text{S}$$

then

$$\mathbf{Y} = \mathbf{Y}_1 + \mathbf{Y}_2 + \mathbf{Y}_3 = 0.125, \text{ so } \mathbf{V} = \mathbf{Y}\mathbf{I}_s = (0.125 \angle 0^\circ)(10 \angle 0^\circ) = 1.25 \angle 0^\circ \, \text{V}$$

So the angle of the voltage is $\theta = 0^\circ$, which satisfies the specifications.

DP 10-6

Solution:

Represent the circuit in the frequency domain using phasors and impedances. Using voltage division gives

$$A\angle\theta = \frac{\frac{1}{j1000C}}{R + \frac{1}{j1000C}} \times 10\angle 0^\circ = \frac{10}{1 + j10^3 RC}$$

Equating magnitudes and angles gives

$$A = \frac{10}{\sqrt{1 + 10^6 R^2 C^2}} \Rightarrow RC = \frac{\sqrt{\left(\frac{10}{A}\right)^2 - 1}}{1 + j10^3 RC}$$

and

$$\theta = -\tan^{-1}(10^3 RC) \Rightarrow RC = \frac{\tan(-\theta)}{10^3}$$

$$(a) \quad \theta = -30^\circ \Rightarrow RC = \frac{\tan(30^\circ)}{10^3} = \frac{0.577}{10^3}.$$

Pick $C = 1 \mu\text{F}$, then $R = \frac{0.577}{10^{-6} \times 10^3} = 577 \Omega$ and $A = 8.66 \text{ V}$.

$$(b) \quad A = 5 \text{ V} \Rightarrow RC = \frac{\sqrt{\left(\frac{10}{5}\right)^2 - 1}}{10^3} = \frac{\sqrt{3}}{10^3}.$$

Pick $C = 1 \mu\text{F}$, then $R = \frac{\sqrt{3}}{10^{-6} \times 10^3} = 1732 \Omega$ and $\theta = -60^\circ$.

$$(c) \quad A = 4 \Rightarrow RC = \frac{\sqrt{\left(\frac{10}{4}\right)^2 - 1}}{10^3} = \frac{2.29}{10^3}$$

$$\theta = -60^\circ \quad \Rightarrow \quad RC = \frac{\tan(60^\circ)}{10^3} = \frac{1.73}{10^3}$$

Since RC cannot be both 0.00229 and 0.00173 simultaneously, the specifications cannot be satisfied using this circuit.

$$(d) \quad A = 7.07 \quad \Rightarrow \quad RC = \frac{\sqrt{\left(\frac{10}{7.07}\right)^2 - 1}}{10^3} = 10^{-3}$$

$$\theta = -45^\circ \quad \Rightarrow \quad RC = \frac{\tan(45^\circ)}{10^3} = 10^{-3}$$

Both specifications can be satisfied by taking $R = 1000 \, \Omega$ and $C = 1 \, \mu\text{F}$.