

HW5

1. Perform the subtraction with the following unsigned binary numbers by taking the 2's complement of the subtrahend. (a) $0101 - 0110$, (b) $10110 - 1100$, (c) $1011110 - 1111110$, (d) $101010 - 101$.
2. Repeat Problem 2, assuming the numbers are 2's complement signed numbers. Perform the subtraction and indicate whether overflow occurs.
3. Repeat Problem 3, assuming the numbers are signed-magnitude signed numbers. Perform the subtraction and indicate whether overflow occurs.
4. Design a 4-bit absolute value calculator, $Z=|z|$.
5. Design a 4-bit x 4-bit multiplier using four-bit adders (Ripple-Carry adders) and other logic gates.
6. Use Verilog to design the circuit in problem 5.