

Quiz 4 solution



1. In Figure 1, a constant voltage source of 10 V is applied at $t = 0$ (which means no voltage applied to the circuit at $t < 0$). Given that $i_1(0^-) = 2$ A and $v_4(0^-) = 4$ V. Find all branch voltages (v_1 to v_4) and current (i_1 to i_4) at $t = 0^+$ and $t = \infty$. (20%, each 2.5%)

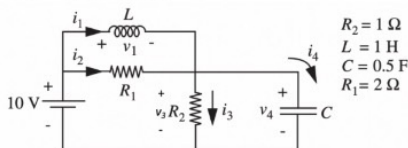


Figure 1.

There is current continuous at inductor

$$i_1(0^+) = i_1(0^-) = 2$$

There is voltage continuous at capacitor

$$v_4(0^+) = v_4(0^-) = 4$$

Use Ohm's law

$$i_2(0^+) = \frac{10 - v_4(0^+)}{R_1} = 3$$

$$v_2(0^+) = 3 \times 2 = 6 = v_1(0^+)$$

And

$$v_4(0^+) = v_3(0^+) = 4$$

Thus,

$$i_3(0^+) = \frac{4}{1} = 4$$

Use KCL

$$i_4(0^+) = i_1(0^+) + i_2(0^+) - i_3(0^+) = 1$$

When $t \rightarrow \infty$, it is steady state, and the inductor is treated as a short while the capacitor is treated as an open.

$$v_1(\infty) = 0 = v_2(\infty)$$

$$i_4(\infty) = 0$$

$$v_4(\infty) = 10 = v_3(\infty)$$

By Ohm's law

$$i_2(\infty) = 0$$

$$i_3(\infty) = \frac{10}{1} = 10$$

Use KCL

$$i_1(\infty) = i_3(\infty) + i_4(\infty) - i_2(\infty) = 10$$

Conclude

Time \ value	i_1	i_2	i_3	i_4	units	v_1	v_2	v_3	v_4	units
0^+	2	3	4	1	A	6	6	4	4	V
∞	10	0	10	0	A	0	0	10	10	V

2. Consider the circuit in Figure 2. Assume the operational amplifier is ideal. Derive the second-order differential equation that shows how the voltage $v_2(t)$ is related to the input voltage $v_3(t)$. (20%)

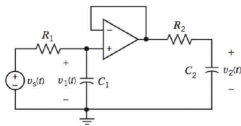


Figure 2.

$$\frac{v_3 - v_1}{R_1} - C_1 \frac{dv_1}{dt} = 0 \Rightarrow \frac{v_1}{R_1} + C_1 \frac{dv_1}{dt} = \frac{v_3}{R_1} \quad \text{--- ①}$$

$$\frac{v_1 - v_2}{R_2} - C_2 \frac{dv_2}{dt} = 0 \Rightarrow \frac{v_2}{R_2} + C_2 \frac{dv_2}{dt} = \frac{v_1}{R_2}$$

$$\Rightarrow v_1 = R_2 C_2 \frac{dv_2}{dt} + v_2 \quad \text{--- ②}$$

$$\text{Substitute ② into ①} \Rightarrow \frac{R_2 C_2}{R_1} \frac{dv_2}{dt} + \frac{v_2}{R_1} + C_1 R_2 C_2 \frac{d^2 v_2}{dt^2} + C_1 \frac{dv_2}{dt} = \frac{v_3}{R_1}$$

$$\Rightarrow v_2'' + \left(\frac{1}{R_1 C_1} + \frac{1}{R_2 C_2} \right) v_2' + \frac{1}{R_1 R_2 C_1 C_2} v_2 = \frac{1}{R_1 R_2 C_1 C_2} v_3 \quad \#$$

Quiz 4

→ KVL:

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{V_C}{LC} = \frac{48}{LC}$$

$$\Rightarrow V_C.p = 48$$

$$V_C.h = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$\text{characteristic eqn: } s^2 + 2800s + 2.5 \times 10^9 = 0$$

$$\Rightarrow s = -1400 \pm 4800j$$

$$V_C = 48 + e^{-1400t} (K_1 \cos(4800t) + K_2 \sin(4800t))$$

$$K_1 = A_1 + A_2 \text{ and } K_2 = jA_1 - jA_2$$

$$\begin{cases} V_C(0) = 48 + K_1 = 0 \\ i_L(0) = C \cdot (-1400K_1 + 4800K_2) = 0 \end{cases} \Rightarrow \begin{cases} K_1 = -48 \\ K_2 = -14 \end{cases}$$

$$\Rightarrow V_C(t) = 48 + e^{-1400t} [-48 \cos(4800t) - 14 \sin(4800t)] \text{ (V)}$$

for $t \geq 0$

✱

4.

$$i_R + i_L + i_C = 0$$

$$R = 200\Omega, L = 50\text{mH}, C = 0.2\mu\text{F}$$

$$\frac{V}{R} + \frac{1}{L} \int_0^t V di + i_L(0) + C \frac{dV}{dt} = 0 \Rightarrow C \frac{d^2 V}{dt^2} + \frac{1}{R} \frac{dV}{dt} + \frac{1}{L} V = 0$$

$$\Rightarrow \frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{1}{LC} V = 0, s^2 + \frac{1}{200 \times 0.2\mu} \frac{dV}{dt} + \frac{V}{50\text{m} \cdot 0.2\mu} = 0$$

$$s^2 + 25000s + 10^8 = 0, \Rightarrow s = -20000 / -5000$$

$$\therefore V(t) = A_1 e^{-20000t} + A_2 e^{-5000t}, V(0) = A_1 + A_2 = 12 \dots \textcircled{1}$$

$$i_L(0) = 30\text{mA}, C \frac{dV}{dt}(t=0) = 30\text{mA}$$

$$-20000A_1 - 5000A_2 = 30 \times 10^{-3} \times \frac{1}{0.2 \times 10^{-6}} = 150000$$

$$A_1 + 0.25A_2 = 7.5 \dots \textcircled{2}$$

solve $\textcircled{1}, \textcircled{2}$, $A_1 = 6, A_2 = 6$

$$V(t) = 6e^{-20000t} + 6e^{-5000t} \quad \text{✱}$$

$$A_1 + A_2 = 12$$

$$-1A_1 + 0.25A_2 = 7.5$$

$$0.75A_2 = 4.5$$

$$A_2 = 6$$

$$A_1 = 6$$