

10920EECS101001 Logic Design

Homework 1

1. (10%) Represent -45 in both the 8-bit signed 1's complement representation, and the 8-bit signed 2's complement representation.
2. (10%) Draw logic diagrams to implement the following Boolean expressions:

$$F = [(u + x')(y' + z)]$$
3. (20%) For the Boolean function $F = xy'z + x'y'z + w'xy + wx'y + wxy$
 - a. Obtain the truth table of F .
 - b. Draw the logic diagram, using the original Boolean expression.
 - c. Use Boolean algebra to simplify the function to a minimum number of literals.
 - d. Obtain the truth table of the function from the simplified expression and show that it is the same as the one in part a.
 - e. Draw the logic diagram from the simplified expression, and compare the total number of gates with the diagram of part b.
4. (20%) Write the Boolean equations and draw the logic diagram of the circuit whose outputs are defined by the following truth table:

Table P2.27

f_1	f_2	a	b	c
1	1	0	0	0
0	1	0	0	1
1	0	0	1	0
1	1	0	1	1
1	0	1	0	0
0	1	1	0	1
1	0	1	1	1

5. (20%) Find the complement of the following expressions. Simplify it to a minimum number of literals:
 - a. $(b + c')(a + c')(b' + c')$
 - b. $w'x' + w(x + y + z)$
6. (20%) Convert each of the following expressions into sum of products and product of sums:
 - a. $(w + xy')(x + y'z)$
 - b. $xy + (w' + y'z')(z' + x'y')$