

Combinational Logic

Chapter 4

Outline


- Introducing combinational circuits
- Design and analysis of combinational circuits
- Iterative systems
 - Arithmetic circuits
 - Magnitude comparators
- Combinational building blocks
 - Decoders
 - Encoders
 - Multiplexers

Combinational Circuits vs Sequential Circuits

- Logic circuits for digital system
 - Combinational circuits
 - consist of logic gates
 - the outputs at any time are determined from only the **present** combination of inputs
 - Sequential circuits
 - contain **memory** elements and logic gates
 - the outputs are a function of the current inputs and the state of the memory elements
 - i.e., the outputs also depend on **past** inputs

Combinational Circuits

 - A combinational circuit
 - 2^n possible combinations of input values



Analysis Procedure

- A combinational circuit
 - make sure that it is combinational not sequential
 - No feedback path

Analysis Example

 


Fig. 3-5 Logic Diagram for Analysis Example

$$T_1 = B'C \quad T_2 = A'B$$

$$F_2 = T_2 + D = A'B + D$$

$$T_3 = A + T_1 = A + B'C$$

$$T_4 = T_2 \oplus D = (A'B) \oplus D = A'BD' + AD + B'D$$

$$F_1 = T_3 + T_4 = A + B'C + A'BD' + AD + B'D = A + B'C + BD' + B'D$$

Design Example 1


- Design a BCD-to-Excess-3 code converter (the *excess-3 code* of a decimal digit p is the binary code of $p+3$).

□ **TABLE 3-1**
Truth Table for Code Converter Example


Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

Design Example 1 (cont'd)


2-level
simplification:

 


$$W = A + BC + BD$$

 
 
$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$



$$Y = CD + \overline{C}\overline{D}$$

 


$$Z = \overline{D}$$

Design Example 1(cont'd)

- The simplified functions
 - $z = D'$
 - $y = CD + C'D'$
 - $x = B'C + B'D + BC'D'$
 - $w = A + BC + BD$
- Further simplification by extraction
 - $T = C + D$
 - $z = D'$
 - $y = CD + C'D' = CD + (C+D)' = CD + T'$
 - $x = B'C + B'D + BC'D' = B'(C+D) + B(C+D)' = B'T + BT'$
 - $w = A + BC + BD = A + B(C+D) = A + BT$

Design Example 1(cont'd)

- The logic diagram

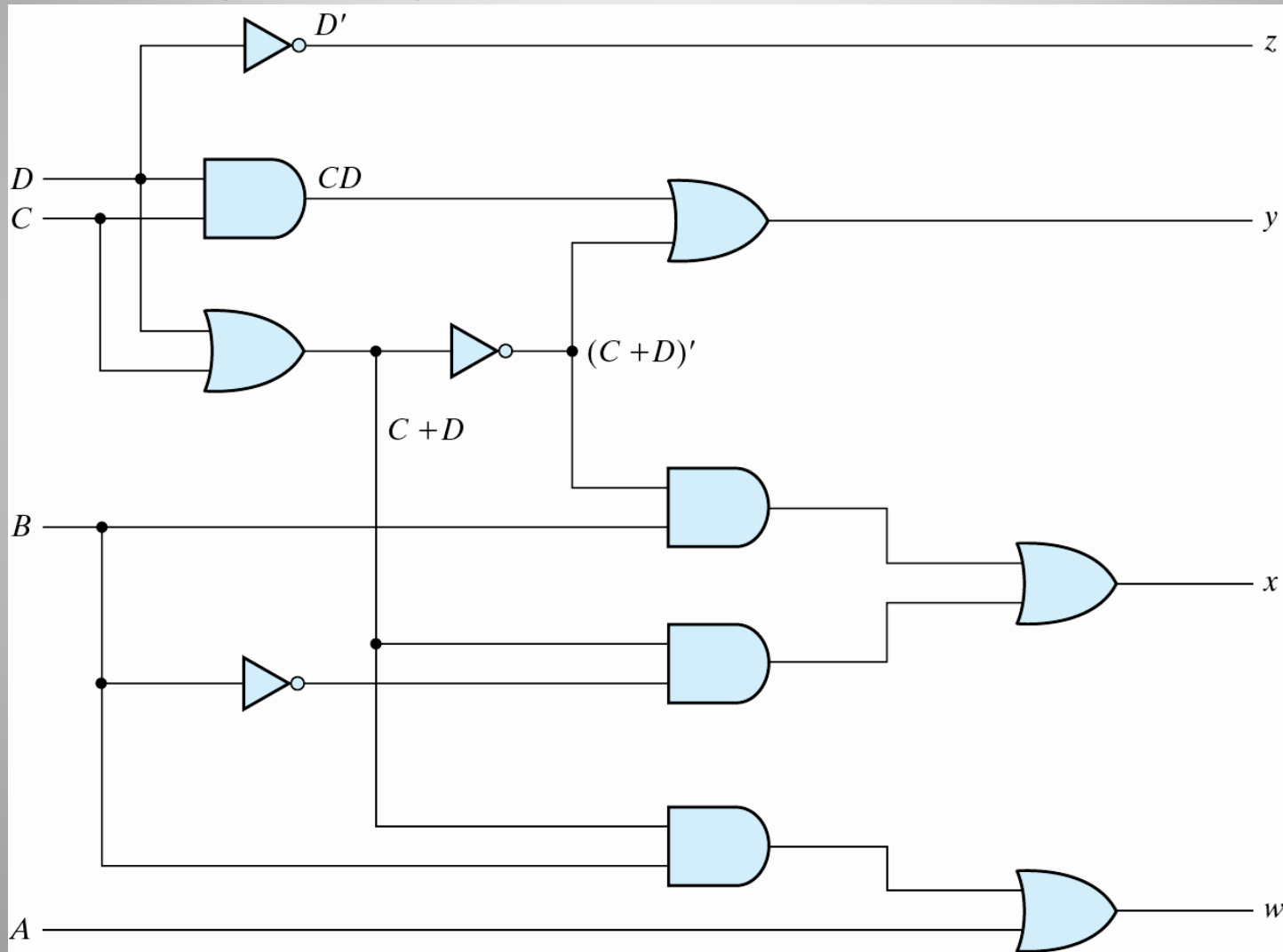

Half Adder

- A half adder performs addition of two bits
 - 2 input bits: x , y
 - 2 output bits: C (carry), S (sum)


Table 4.3
Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Half Adder

- Different implementations


- $S = x'y + xy'$
 $C = xy$

 

 - $S = x'y + xy' = S = x \oplus y$
 $C = xy$



Verilog Description of Half Adder

 

```
// half adder
module HalfAdder(a,b,c,s);
    input a,b ;
    output c,s ;    // carry and sum
    wire s = a ^ b ;
    wire c = a & b ;
endmodule
```

Full Adder

- A full adder is for adding three bits
 - 3 input bits
 - x, y: two significant bits
 - z: the carry bit from the previous lower significant bit
 - 2 output bits: C, S


Table 4.4
Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

SOP Implementation of Full Adder


S:

yz		y			
		00	01	11	10
x	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6
		z			

 

C:

yz		y			
		00	01	11	10
x	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6 1
		z			

 

Alternative Implementation of Full Adder


S:

			y				
	yz		00	01	11	10	
x	0	m_0	m_1	1	m_3	m_2	1
x	1	m_4	m_5	1	m_7	1	m_6

C:

			y				
	yz		00	01	11	10	
x	0	m_0	m_1	m_3	1	m_2	
x	1	m_4	m_5	1	m_7	1	m_6

$$C = xy + xz + xy$$

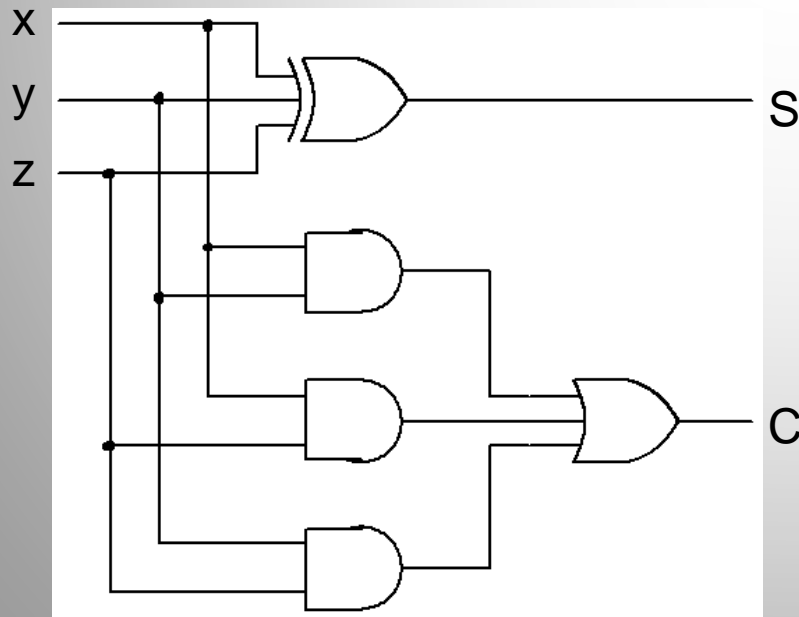

Implementation based on Half Adders

- A full adder can be implemented with two half adders and one OR gate
- $S = x'y'z + x'yz' + xy'z' + xyz = (x \oplus y) \oplus z$
- $C = xy + xz + yz = xy + z(x \oplus y)$

 


Fig. 3-27 Logic Diagram of Full Adder

Full Adder in Verilog

```
// full adder - logical
module FullAdder2(a, b, cin, cout, s);
    input  a, b, cin;
    output cout, s;
    wire   s = a ^ b ^ cin;
    wire   cout = (a & b) | (a & cin) | (b & cin); // majority
endmodule
```

```
// full adder - from half adders
module FullAdder1(a, b, cin, cout, s);
    input a, b, cin;
    output cout, s; // carry and sum
    wire g, p;      // generate and propagate
    wire cp;
    HalfAdder ha1(a, b, g, p);
    HalfAdder ha2(cin, p, cp, s);
    assign cout = g | cp;
endmodule
```


Lesson:

Even very simple functions, like a full adder, can be implemented in many different ways.

Ripple Carry Adder

- Add two n -bit numbers
- Like addition by hand, **progress from least-significant digit to most-significant digit.**
- If a carry is produced in position i , it is added to the operands in position $i+1$.
- A ripple carry adder is formed by cascading n full adders.

e.g.

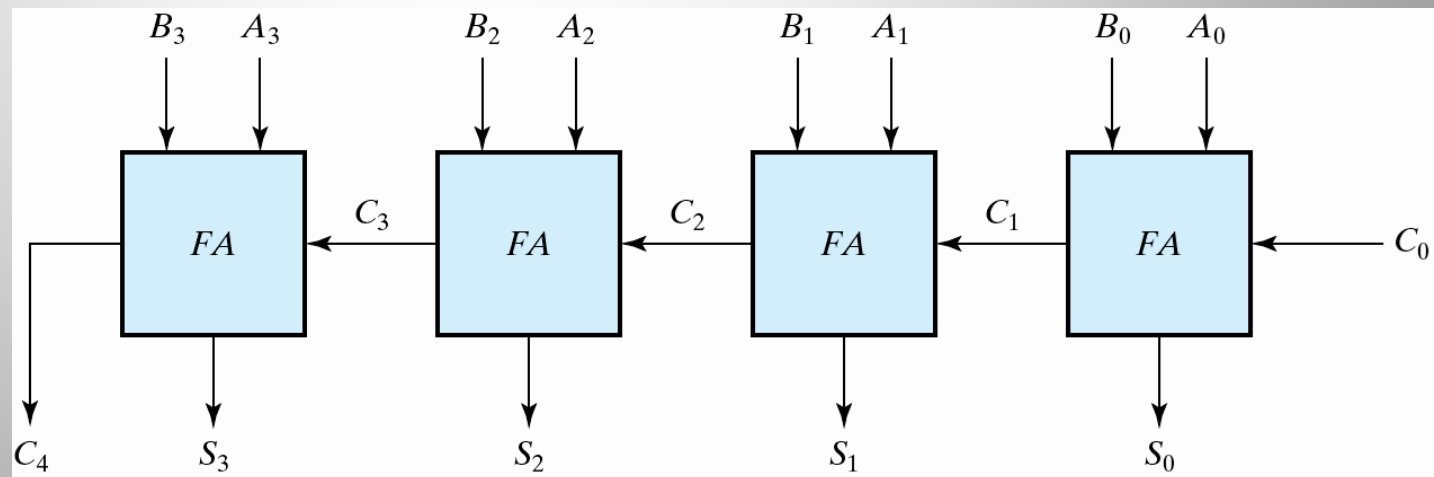

Signed Numbers in 2's Complement

- Recall that in 2's complement scheme
 - $-X$ is obtained by taking the 2's complement of X
 - E.g. $X = 001111 \Rightarrow -X = 110001$

2's Complement Signed Binary Arithmetic

- Addition

— Add the nos. (including the sign bits). Discard any carry out of the sign bit position.

$$\begin{array}{r} +7 \quad 00000111 \\ + +10 \quad 00001010 \\ \hline +17 \quad 00010001 \end{array}$$


$$\begin{array}{r} +7 \quad 00000111 \\ + -10 \quad 11110110 \\ \hline -3 \quad 11111101 \end{array}$$

$$\begin{array}{r} -7 \quad 11111001 \\ + +10 \quad 00001010 \\ \hline +3 \quad (1)00000011 \end{array}$$

$$\begin{array}{r} -7 \quad 11111001 \\ + -10 \quad 11110110 \\ \hline -17 \quad (1)11101111 \end{array}$$

2's Complement Signed Binary Arithmetic

 - Subtraction
 - $A - B = A + (-B)$
 - i.e., $A - B = A + (2\text{'s complement of } B)$
- 4-bit Adder-Subtractor
 - $M=0$, compute $A+B$; $M=1$, compute $A+B'+1 (= A-B)$



Arithmetic Overflow

- Overflow
 - The storage is limited
 - Add two +ve numbers and obtain a -ve number
 - Add two -ve numbers and obtain a +ve number

$$\begin{array}{r}
 +70 \quad 01000110 \\
 + \quad +80 \quad 01010000 \\
 \hline
 +150 \quad 10010110
 \end{array}$$

\uparrow
 Negative!!

$$\begin{array}{r}
 -70 \quad 10111010 \\
 + \quad -80 \quad 10110000 \\
 \hline
 -150 \quad (1)01101010
 \end{array}$$

\uparrow
 Positive!!

$$\text{overflow} = A_{n-1}B_{n-1}S'_{n-1} + A'_{n-1}B'_{n-1}S_{n-1}$$

Alternatively, $\text{overflow} = C_{n-1} \oplus C_n$


Magnitude Comparator

- Compare two numbers
 - outputs: $A > B$, $A = B$, $A < B$
- Design Approaches
 - truth table
 - 2^{2n} entries - too cumbersome for large n
 - use inherent regularity of the problem
 - reduce design efforts
 - reduce human errors

Magnitude Comparator

- Algorithm \rightarrow logic
 - $A = A_3A_2A_1A_0$; $B = B_3B_2B_1B_0$
 - $A=B$ if $A_3=B_3$, $A_2=B_2$, $A_1=B_1$ and $A_0=B_0$
 - equality: $x_i = A_iB_i + A_i'B_i'$
 - $(A=B)$ iff $x_3x_2x_1x_0=1$
 - $(A>B)$ iff $A_3B_3' + x_3A_2B_2' + x_3x_2A_1B_1' + x_3x_2x_1A_0B_0'$
 - $(A<B)$ iff $A_3'B_3 + x_3A_2'B_2 + x_3x_2A_1'B_1 + x_3x_2x_1A_0'B_0$
- Reduce gate count by noting
 - $x_i = A_iB_i + A_i'B_i' = (A_iB_i' + A_i'B_i)'$

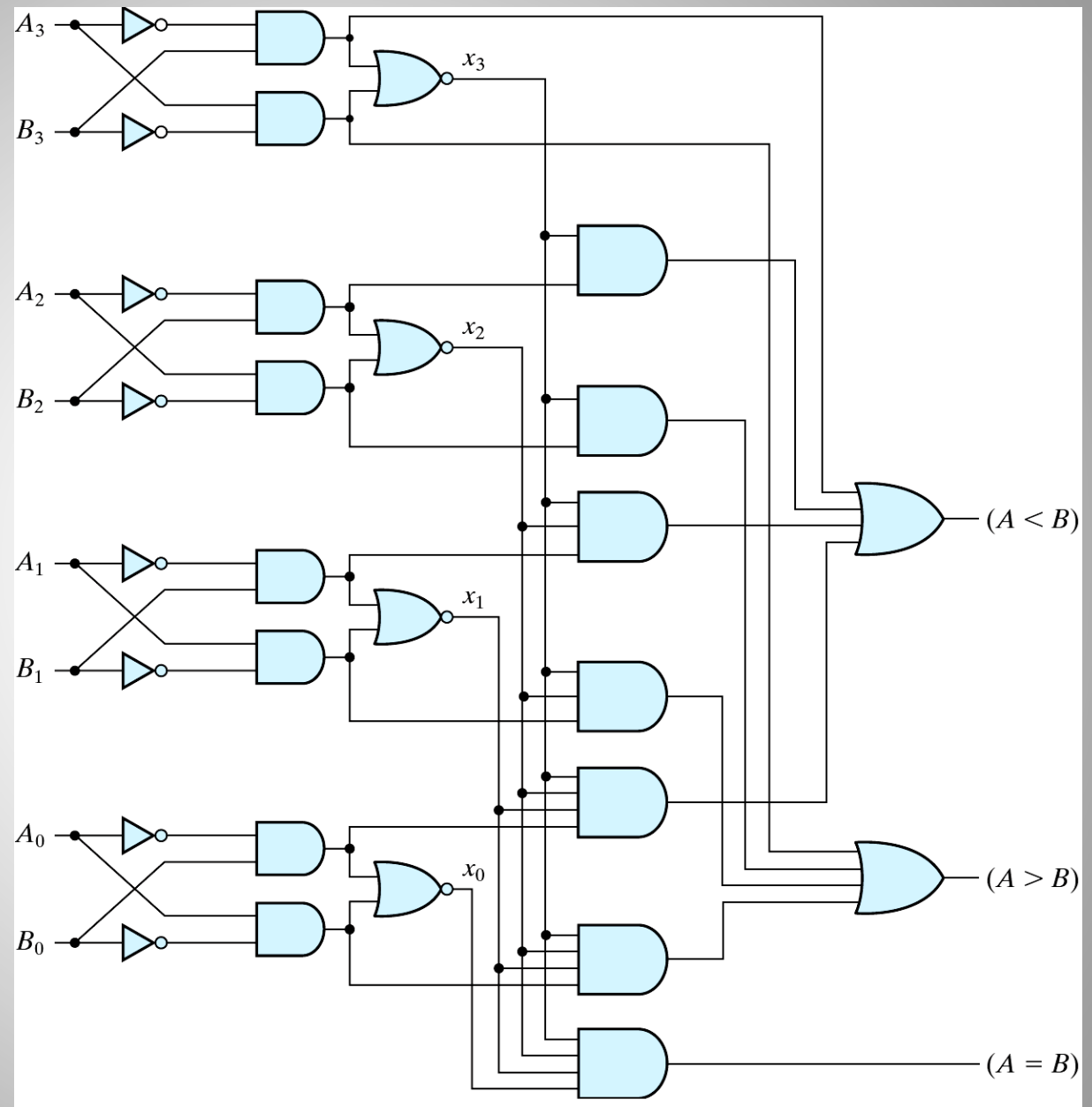Logic diagram of a 4-bit magnitude comparator




Lesson:

From algorithm to logic design e.g.
adders, multipliers, comparators.


Multiplexer

 - A data selector
- 2^n data input lines, n selection lines and one output line
- $b = a[i]$ if $sb = i$




Multiplexer

- e.g. 2-to-1 multiplexer

 


(a) Logic diagram

 

(b) Block diagram

Multiplexer

- e.g. 4-to-1 multiplexer

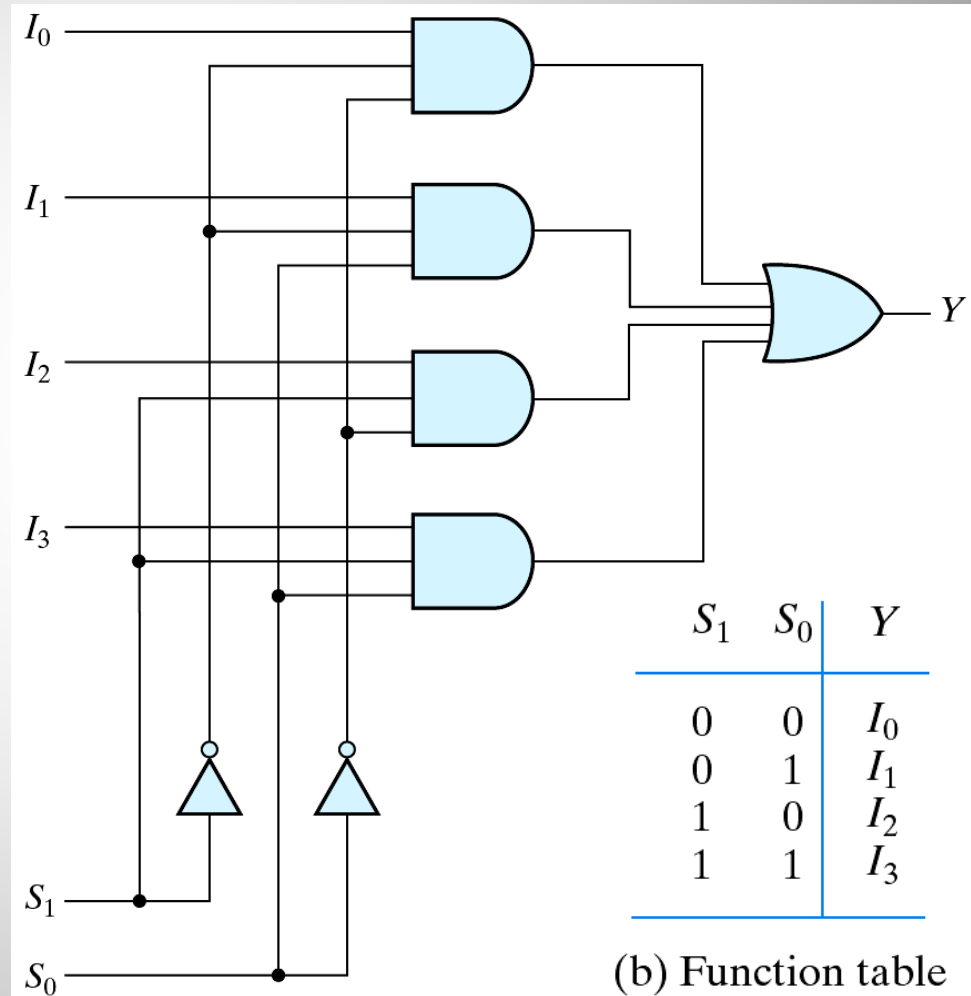


(a) Logic diagram

(b) Function table

Mux Tree

- e.g. A 16-to-1 mux

 

Verilog Description of a 4-to-1 MUX Using case

```
module Mux4to1(a3, a2, a1, a0, sb, b);
    input  a0, a1, a2, a3; // inputs
    input  [1:0]      sb;   // binary select
    output b;
    reg      b;

    always @(*) begin
        case(sb)
            2'b00: b = a0;
            2'b01: b = a1;
            2'b10: b = a2;
            2'b11: b = a3;
            default: b = x;
        endcase
    end
endmodule
```

Using MUX to Implement Boolean Function

- A MUX is a data selector, for a 4x1 MUX:

$$Y = S'_1 S'_0 I_0 + S'_1 S_0 I_1 + S_1 S'_0 I_2 + S_1 S_0 I_3$$

- In general, for a $2^n \times 1$ MUX:

$$Y = \sum m_k I_k$$


- Observation: Any function of n variables can be implemented with a single MUX with $n-1$ selection inputs.

Example 1. $F = X'Y'Z + X'YZ' + XY$

Suppose we use X and Y as the selection inputs S_1 and S_0 , resp., then

X	Y	Z	F	
0	0	0	0	$F = Z$
0	0	1	1	
0	1	0	1	$F = \bar{Z}$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 

(b) Multiplexer implementation

Fig. 3-22 Implementing a Boolean Function with a Multiplexer

Q. How to implement F using Y , Z as the selection inputs?

Example 2. $F(A,B,C,D) = \sum m(1,3,4,11,12,13,14,15)$

Using A, B, and C as the selection inputs S_2, S_1, S_0 :

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	


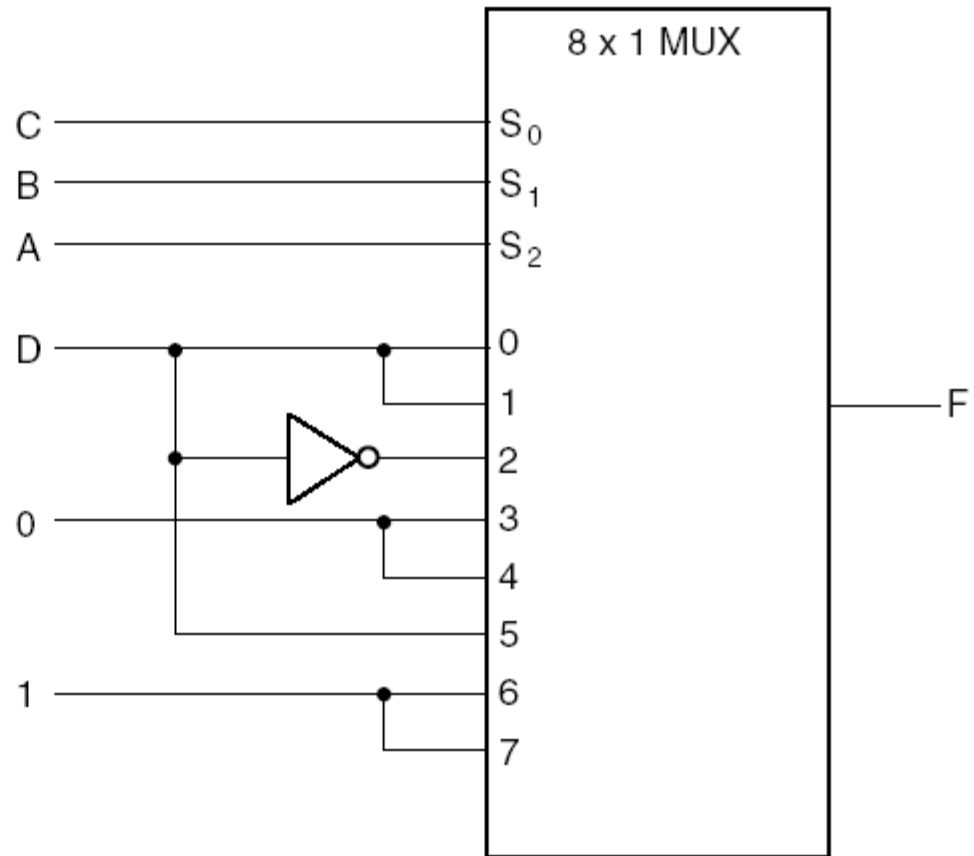


Fig. 3-23 Implementing a Four-Input Function with a Multiplexer


Tri-state Buffer

 - A type of buffer
- Output state: 0, 1, and high-impedance (open circuit)




Example with Tri-State Buffer

- Muxes with tri-state buffers

 

(a) 2-to-1-line mux

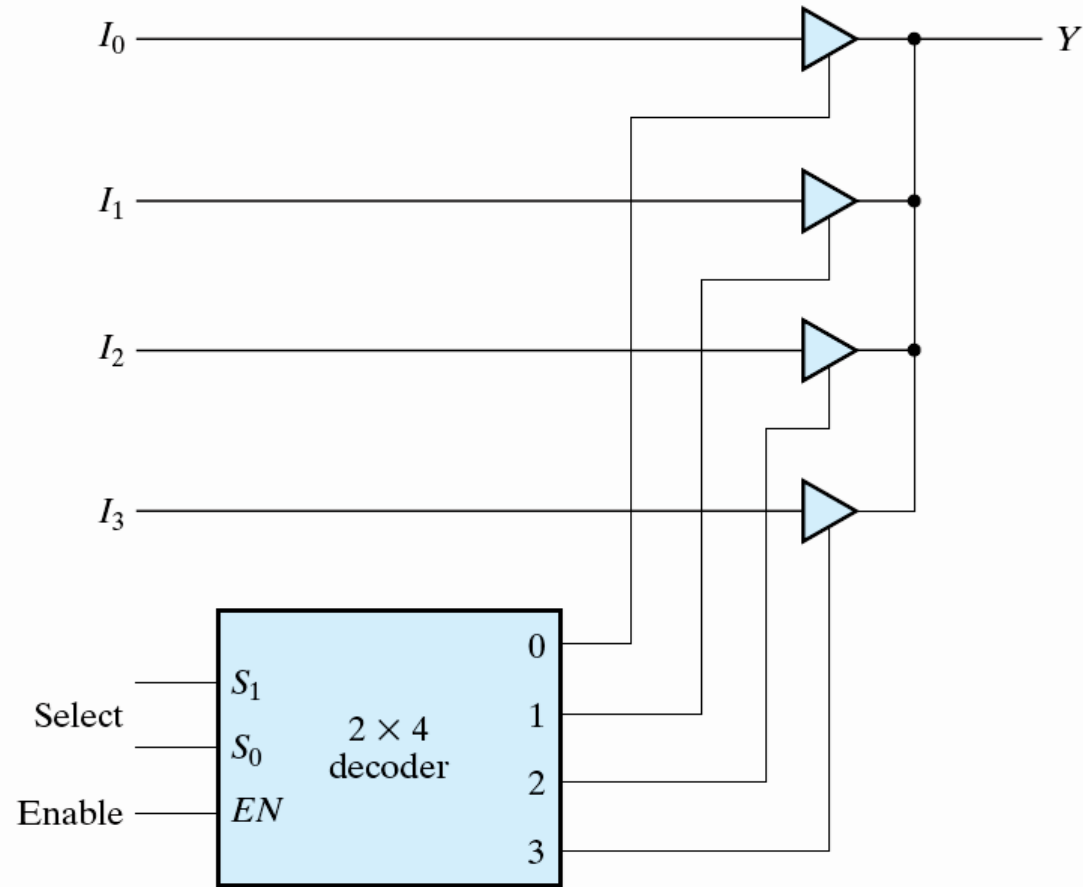

(b) 4-to-1-line mux

Verilog Description of a Binary Adder

```
module binary_adder(a, b, c_in, c_out, sum);  
    parameter k = 4;  
    input  [k - 1:0] a, b;  
    input  c_in;  
    output c_out;  
    output [k - 1:0] sum;  
  
    assign {c_out, sum} = a + b + c_in;  
endmodule
```

Verilog Description of a Magnitude Comparator

```
module magnitude_comparator(a, b, a_lt_b, a_eq_b, a_gt_b);  
    parameter k = 4;  
    input  [k - 1:0] a, b;  
    output a_lt_b, a_eq_b, a_gt_b;  
  
    assign a_lt_b = (a < b);  
    assign a_eq_b = (a == b);  
    assign a_gt_b = (a > b);  
endmodule
```

附錄

Decimal Adder

- Each stage add two BCD digits
 - 9 inputs: two BCD digits and one carry-in
 - 5 outputs: one BCD digit and one carry-out
- Design approaches
 - A truth table with 2^9 entries
 - Use 4-bit binary adders
 - the sum $\leq 9 + 9 + 1 = 19$
 - Need binary to BCD conversion

Convert binary sum to a BCD digit and a carry-out

Table 4.5
Derivation of BCD Adder

Binary Sum					BCD Sum					Decimal
<i>K</i>	<i>Z</i> ₈	<i>Z</i> ₄	<i>Z</i> ₂	<i>Z</i> ₁	<i>C</i>	<i>S</i> ₈	<i>S</i> ₄	<i>S</i> ₂	<i>S</i> ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19


Decimal Adder

- Modifications are needed if result > 9
- result $> 9 \Leftrightarrow K = 1$ or $Z_8Z_4 = 1$ or $Z_8Z_2 = 1$

$$C = K + Z_8Z_4 + Z_8Z_2$$

Add 6 to the binary sum to convert to the correct BCD representation when $C = 1$

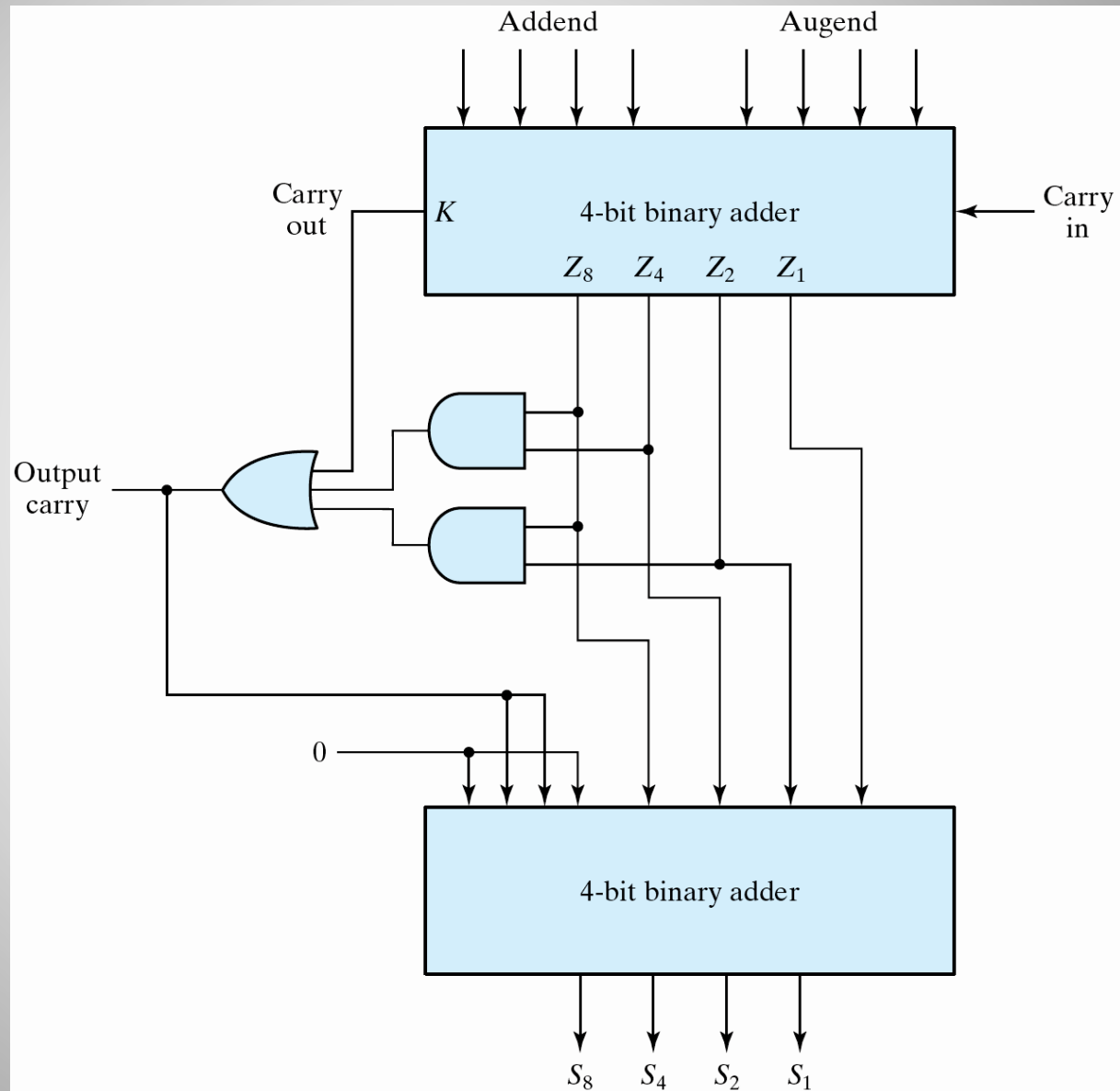Block diagram for one stage of BCD addition




Combinational Building Blocks

- A few types of logic circuit are often used as building blocks in larger design
 - Decoder (binary to one-hot)
 - Encoder (one-hot to binary)
 - Multiplexer (select one of N)

Multi-Bit Notation

- Multi-bit signal or a **bus**

 

- Verilog bit-select (bit-slice) or part-select
 - $b[7:0]$
 - $b[7]$
 - $b[5:3]$

One-Hot Representation

- Represent a set of N elements with N bits
- Exactly one bit is set
- Example – to encode numbers 0-7

Binary	One-hot
000	00000001
001	00000010
010	00000100
...	...
110	01000000
111	10000000

- What operations are simpler with one-hot representation?
With binary?

Decoder

- A n-to-m decoder

- n input variables; up to 2^n output lines
- binary to one-hot decoder

- only one output can be high at any time
- each output corresponds to one valuation of inputs

 


Table 4.6

Truth Table of a Three-to-Eight-Line Decoder

Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃	<i>D</i> ₄	<i>D</i> ₅	<i>D</i> ₆	<i>D</i> ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Verilog Description of Decoder

```
// a - binary input    (n bits wide)
// b - one hot output  (m bits wide)
```

```
module Dec(a, b);
```

```
    parameter n = 2;
```


```
    parameter m = 4;
```

```
    input  [n - 1:0] a;
```

```
    output [m - 1:0] b;
```

```
    wire [m - 1:0] b = 1 << a;
```

```
endmodule
```

 


Parameterized Module

- Instantiate the decoder with default parameters
Dec dec24(a, b);
- Instantiate the decoder overriding the default parameters

Dec #(3, 8) dec38(a, b);


Dec #(.n(4), .m(10)) dec410(a, b);

An implementation
of a 3-to-8 decoder

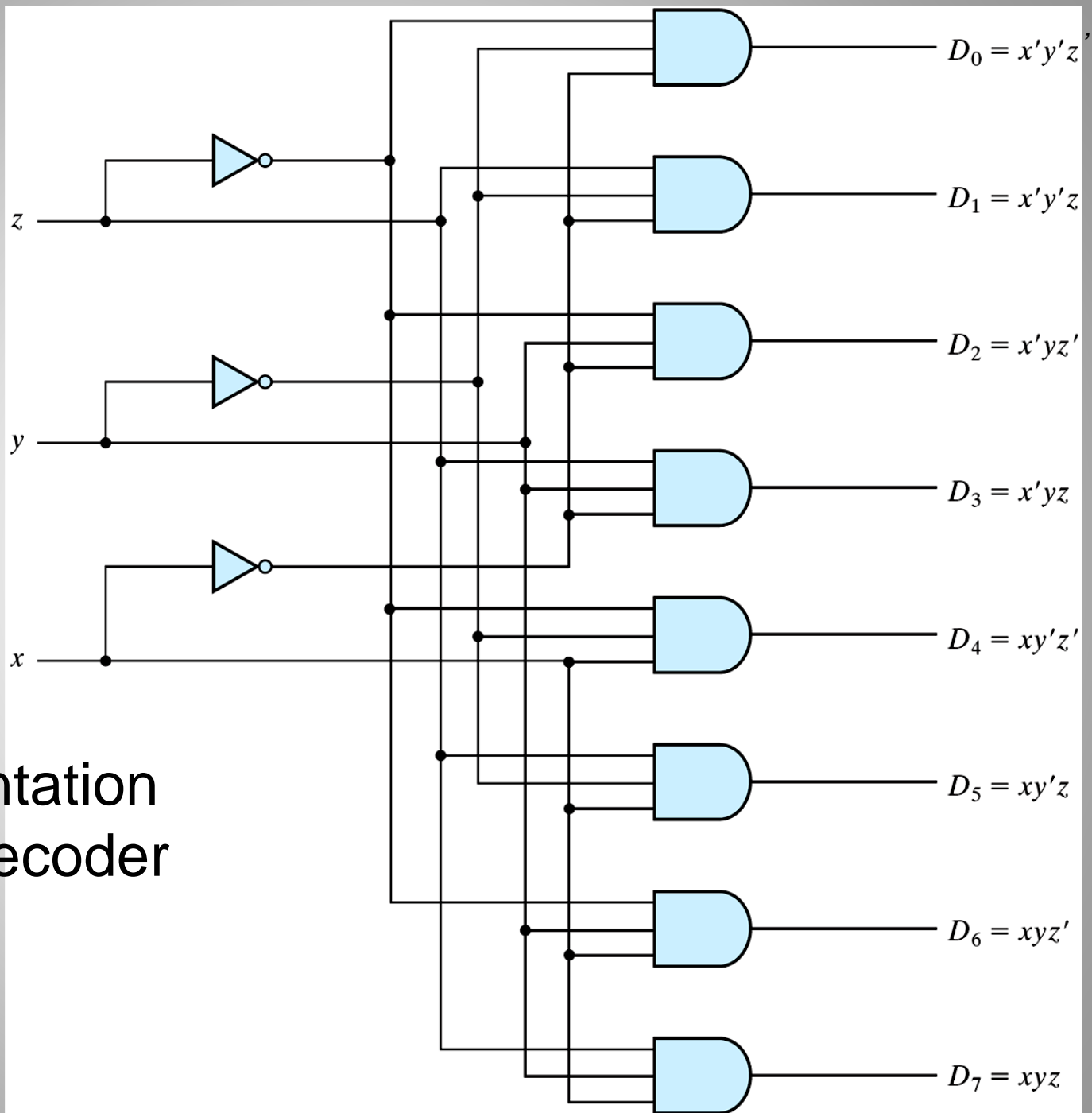


Decoder with Enable Input

inputs			outputs			
E	A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	*	*	0	0	0	0

 


Larger Decoder from Small Ones

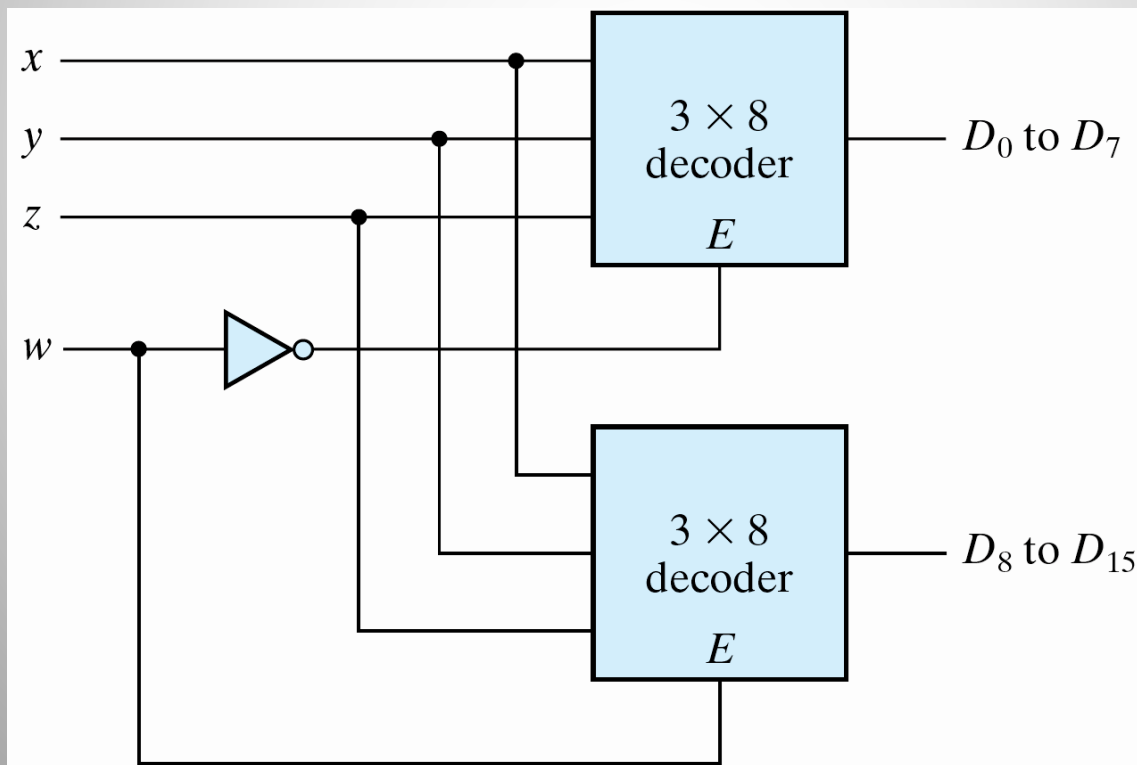- Expansion
 - e.g. A 4-to-16 decoder from two 3-to-8 decoders



Decoder Tree

- A 4-to-16 decoder with enable

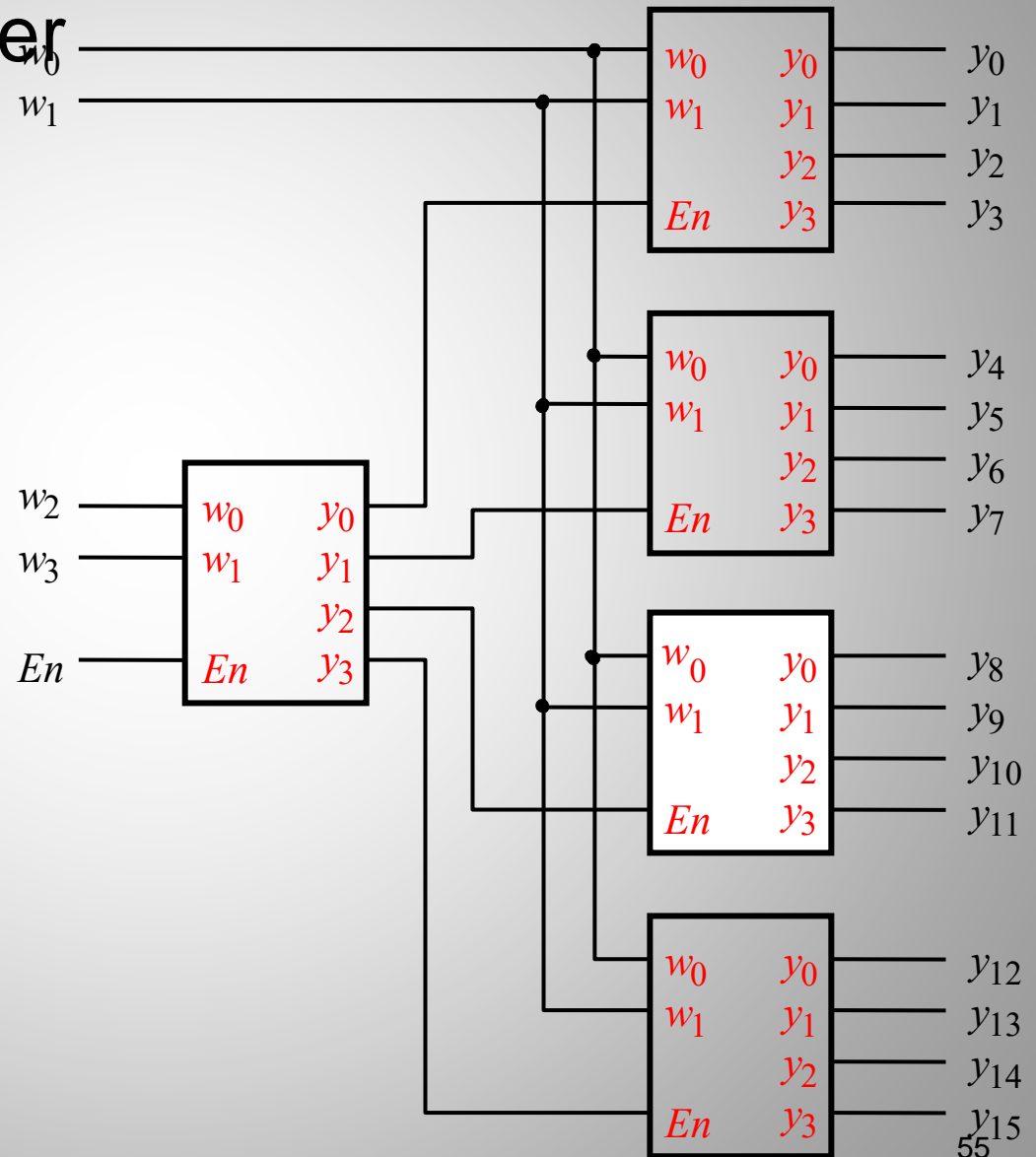

Using Decoder to Implement Boolean Function

- Each output of decoder = a minterm
- May use a decoder and an external OR gate to implement any Boolean function of n input variables
- e.g. Implement a full adder

□ **TABLE 3-8**
Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Table 3-8 Truth Table of Full Adder

Example: Using Decoder to Implement Prime Number Detector

$$f = \sum m(1, 2, 3, 5, 7)$$

in[2:0]	isprime
0 0 0	0
0 0 1	1
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	1
1 1 0	0
1 1 1	1

```
module Primed(in, isprime);  
  input [2:0] in;  
  output      isprime;  
  wire [7:0] b;
```


```
  // compute the output as the OR of  
  // the required minterms
```

```
  wire isprime = b[1] | b[2] | b[3] | b[5] | b[7];
```

```
  // instantiate a 3->8 decoder
```


```
  Dec #(.n(3), .m(8)) d(.a(in), .b(b));
```

```
endmodule
```

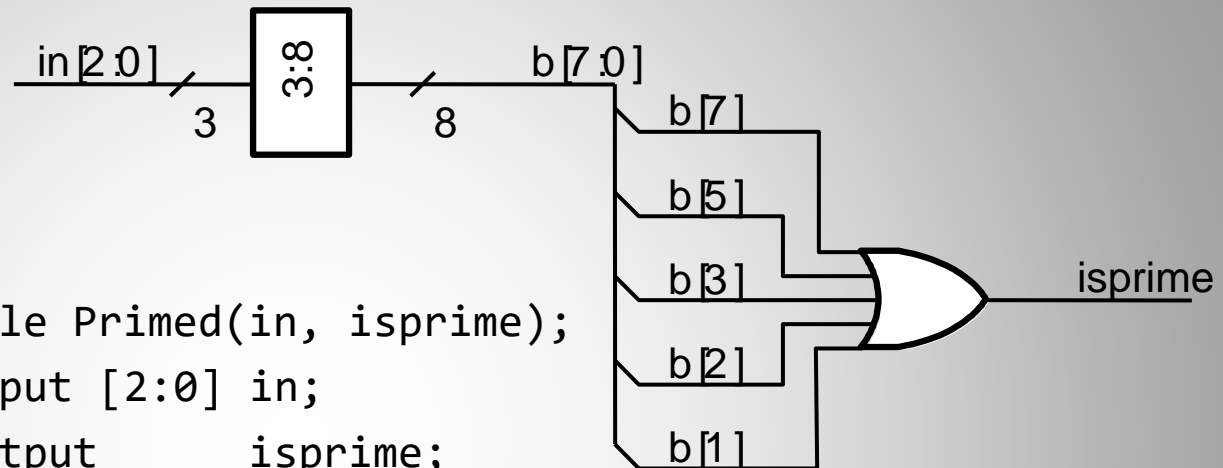

Encoder

 - An encoder provides the **inverse function** of a decoder
- Encoder converts an n -bit one-hot input signal to an m -bit binary-encoded output signal



Encoder

- E.g. 8-to-3 Encoder

Table 4.7
Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$



The encoder can be implemented with three OR gates.

Priority Encoder

- Allows multiple input lines to be asserted
- Higher-numbered input line has higher priority
- e.g. 4-to-2-line priority encoder

□ **TABLE 3-6**
Truth Table of Priority Encoder

Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

Table 3-6 Truth Table of Priority Encoder

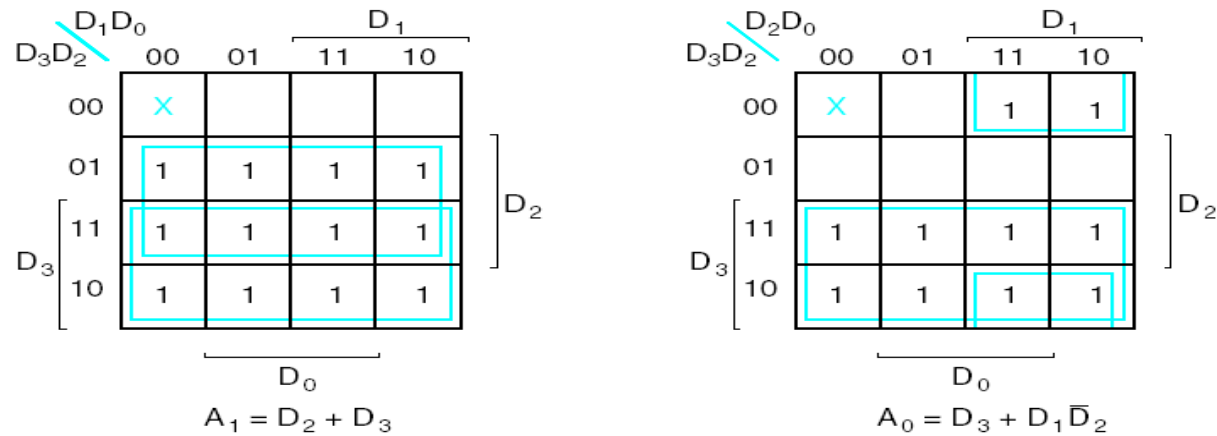


Fig. 3-17 Maps for Priority Encoder

 


Fig. 3-18 Logic Diagram of a 4-Input Priority Encoder