

Synchronous Sequential Logic

Ch.5



Outline

- . Synchronous vs asynchronous sequential circuits
- . Storage elements
 - Latches
 - Flip-flops
- . Mealy and Moore models
- . Analysis of synchronous sequential circuit
- . State diagram and state table
- . Design of synchronous sequential circuit
- . State reduction and assignment


Introduction

- . Combinational circuit
 - contains no memory element
 - outputs determined solely by present inputs
 - does not meet the need of all applications

State Machine Examples

  

Sequential Circuit

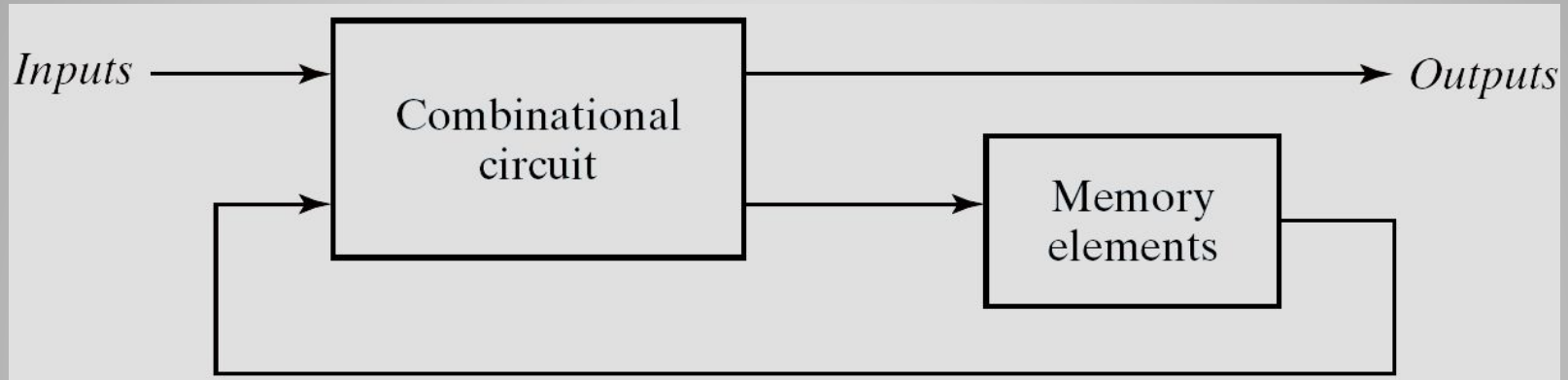


- . Has feedback path
- . *State* of sequential circuit: content of memory elements
- . (inputs, current state) \Rightarrow (outputs, next state)

Synchronous vs Asynchronous

- . Types of sequential circuit
 - *Synchronous*: synchronized by a *clock*, the state of the circuit is updated upon receiving a clock pulse
 - *Asynchronous*: the state of the circuit can be updated at any time when an input change occurs

Synchronous Sequential Circuit

 - Synchronous(clocked) sequential circuit
 - a master-clock generator generates a periodic train of clock pulses
 - the clock pulses are distributed throughout the system to the storage elements
 - most popular





(a) Block diagram



(b) Timing diagram of clock pulses

Storage

- Storage? How?

  

Logic Based Storage

- . We may keep a 0-bit or a 1-bit by re-generating it in a logic loop!


 


Fig. 4-2 Logic Structures for Storing Information

Latches

 - . Latches
 - the most basic storage elements
 - *asynchronous* circuits (have no clock input)
 - flip-flops can be constructed from latches
- . e.g. *SR* latch



(a) Logic diagram



S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

Fig. 4-4 SR Latch with NOR Gates

SR Latch

- . Cross coupling two NOR gates

  


- . Operations

- $(S,R)=(0,0)$: no operation
- $(S,R)=(0,1)$: reset ($Q \leftarrow 0$, the clear state)
- $(S,R)=(1,0)$: set ($Q \leftarrow 1$, the set state)
- $(S,R)=(1,1)$: indeterminate state ($Q=Q'=0$)

S R	Q^+
0 0	Q
0 1	0
1 0	1
1 1	Not allowed

Logic Simulation of SR Latch

 

R changes; then Q; then Q_B

S changes; then Q_B; then Q


 
 


Fig. 4-5 Logic Simulation of SR Latch Behavior

indeterminate
behavior

$\overline{S}\overline{R}$ latch

 - use NAND gates
- set and reset occur with a logic-0 signal





set	reset	Q	Q^+
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	—
0	0	1	—

} inputs not allowed

SR Latch with Control Input

SR latch with control input

- $En = 1$: enabled
- $En = 0$: disabled

  


(a) Logic diagram


En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

D Latch

 

 - Use only a single input D to eliminate the undesirable state
- $Q \leftarrow D$ when $En = 1$
- no change when $En = 0$



(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

(b) Function table


D Latch in Verilog

```
. always @(En, D) begin
    if (En == 1'b1) begin
        Q = D;
    end
end
```


Latch vs Flip-Flop

. Latch

 
- *level triggered*
- “transparent” as long as $EN = 1$
 - state will keep changing if input keeps changing



Latch vs Flip-Flop

. Flip-flop

 - storage element whose state cannot change more than once in a clock cycle
- *edge triggered*
 - state transition happens only on active clock edge
 - eliminate the multiple-transition problem



(a) Block diagram



(b) Timing diagram of clock pulses

Clock Response in Latch and Flip-Flop

Latch

(a) Response to positive level



Flip-flop

(b) Positive-edge response

  (c) Negative-edge response


D Flip-Flop

- . D FF's output changes only at active clock edge
- . Either *positive-* or *negative-edge* triggered




D Flip-Flop	
D	$Q(t + 1)$
0	0
1	1

- . E.g. negative-edge triggered version

 


Negative-edge Triggered *D* Flip-Flop

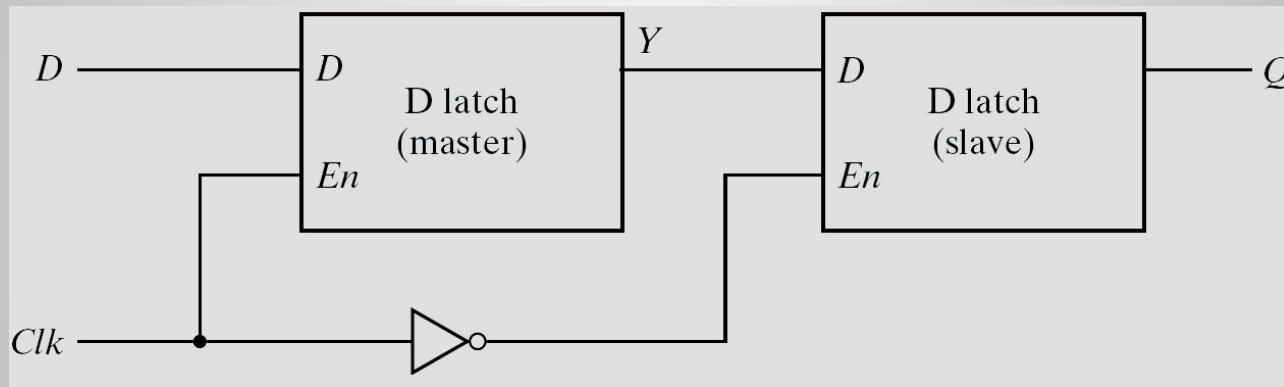
- . Can be formed by two latches + an inverter
 - master latch and slave latch




Operation:

 

Positive-edge Triggered *D* Flip-Flop

 

 (a) Construction from two gated D latches



(b) Time analysis


Flip-Flop Timing Parameters

- . *Setup time* t_s
 - minimum time for which the input data must be stable before the trigger edge
- . *Hold time* t_H
 - minimum time for which the input data must remain stable after the trigger edge
- . *Propagation delay* t_p
 - interval between the trigger edge and the stabilization of the output to its new value

Timing Characteristics of Sequential Circuits


Input D must remain stable during this interval

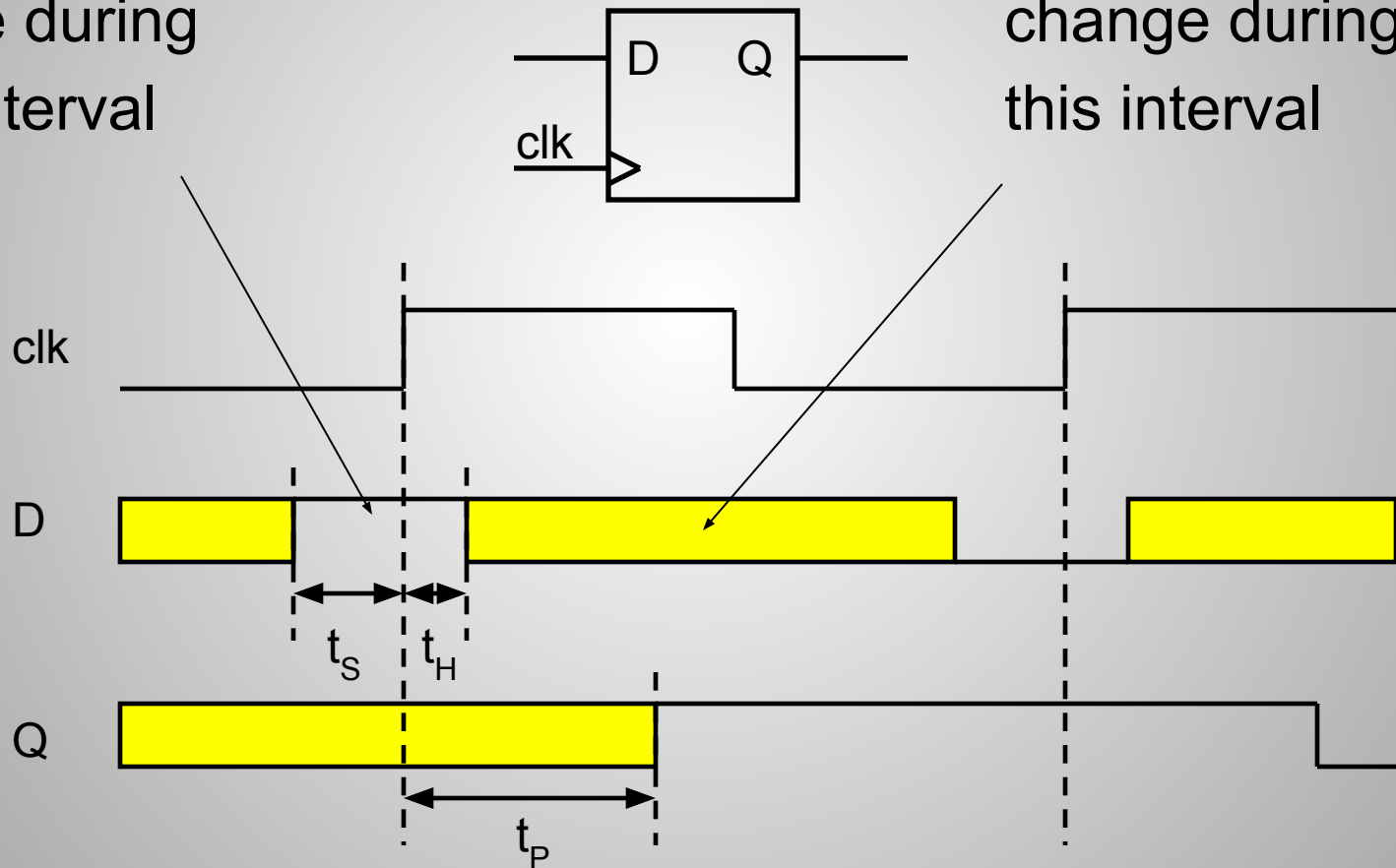Input D can freely change during this interval




Positive-edge Triggered DFF in Verilog
 
```
. reg Q;  
  always @(posedge clk) begin  
    Q <= D;  
  end
```




. Or we usually have DFF with a **reset control**
 
```
reg Q;  
always @(posedge clk, posedge rst) begin  
  if (rst == 1)  
    Q <= 0;  
  else  
    Q <= D;  
end
```



Exercise

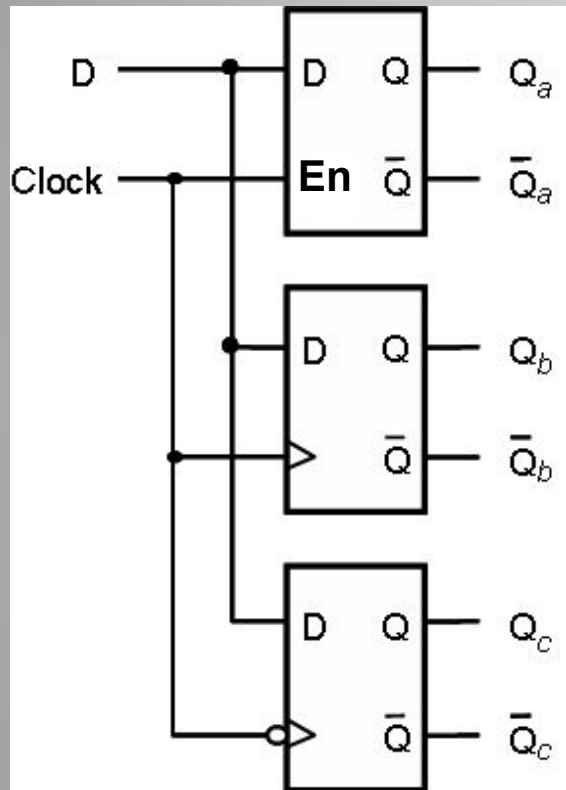


Clock

D

Q_a


Q_b

Q_c

 

Flip-Flops with Inputs: Asynchronous Set/Reset


 
- FFs often have additional inputs to set to an initial state asynchronously
- E.g. *D* flip-flop with *active-low* preset and clear



Ck	<i>D</i>	PreN	ClrN	<i>Q</i> ⁺
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	<i>Q</i> (no change)

Flip-Flops with Additional Inputs: Enable Input

- . E.g. D flip-flop with clock enable

  

- If $CE=0$, disabled, $Q(t+1) = Q$
- If $CE=1$, like a normal D flip-flop, $Q(t+1) = D$
- $Q(t+1) = Q \cdot CE' + D \cdot CE$

Importance of the Sensitivity List

. *D-Register with synchronous clear*

```
module dff_sync_clear(  
input d, clearb, clock,  
output reg q  
);  
always @(posedge clock) begin  
    if (!clearb) q <= 1'b0;  
    else q <= d;  
end  
endmodule
```


. *D-Register with asynchronous clear*

```
module dff_sync_clear(  
input d, clearb, clock,  
output reg q  
);  
always @(negedge clearb or  
posedge clock) begin  
    if (!clearb) q <= 1'b0;  
    else q <= d;  
end  
endmodule
```


If one signal in the sensitivity list uses posedge/negedge, then all signals must.

Use Nonblocking (<=) for Sequential Logic
 
```
always @(posedge clk) begin
    q1 <= in;
    q2 <= q1; // uses old q1
    out <= q2; // uses old q2
end
```


 
```
always @(posedge clk) begin
    q1 = in;
    q2 = q1; // uses new q1
    out = q2; // uses new q2
end
```



Sequential always block style

```
reg [3:0] count1, next_count1;
```

```
always @(posedge clk)
    count1 <= next_count1;
```

```
always @* begin
    if (reset) next_count1 = 0;
    else next_count1 =
        (count1 == 4) ? 0 : count1 + 1;
end
```

```
assign enable1 = (count1 == 4);
```

```
reg [3:0] count2;
```

```
always @(posedge clk) begin
    if (reset) count2 <= 0;
    else count2 <=
        (count2 == 4) ? 0 : count2 + 1;
end
```

```
assign enable2 = (count2 == 4);
```

always block

- . Sequential always block: always @(posedge clock) use “<=“
- . Combinatorial always block: always @* use “=“
- . Results of operators (LHS) inside always block (sequential and combinatorial) must be declared as “reg”
- . Equivalent Verilog

```
reg z;  
always @*  
z = x || y
```

```
Wire z;  
assign z = x && y  
// z not a “reg”
```


Coding Guidelines


- . Ensure your simulation results will match what they synthesized hardware will do:
 - When modeling sequential logic, use nonblocking assignments.
 - When modeling combinational logic with an always block, use blocking assignments.
 - When modeling both sequential and “combinational” logic within the same always block, use nonblocking assignments.
 - Do not mix blocking and nonblocking assignments in the same always block.
 - Do not make assignments to the same variable from more than one always block.

Synchronous Sequential Circuit


- . Also known as *clocked sequential circuit*, or *finite-state machine (FSM)*
- . Current state at time t is stored in a set of flip-flops
- . (input, current state) \Rightarrow (output, next state)
 - next state at time $t+1$ (one clock period after time t) is a Boolean function of the present state and input
 - output is a Boolean function of present state and input

Mealy and Moore Models

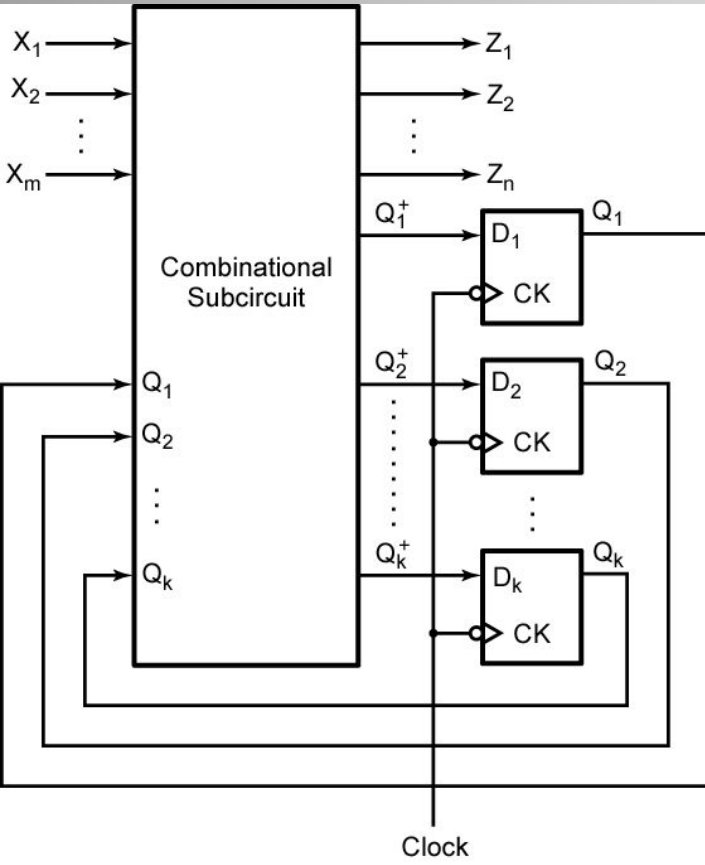- . *Mealy circuit*: sequential circuit for which the output is a function of both present state and input
- . *Moore circuit*: sequential circuit for which the output is a function of present state only



Mealy machine

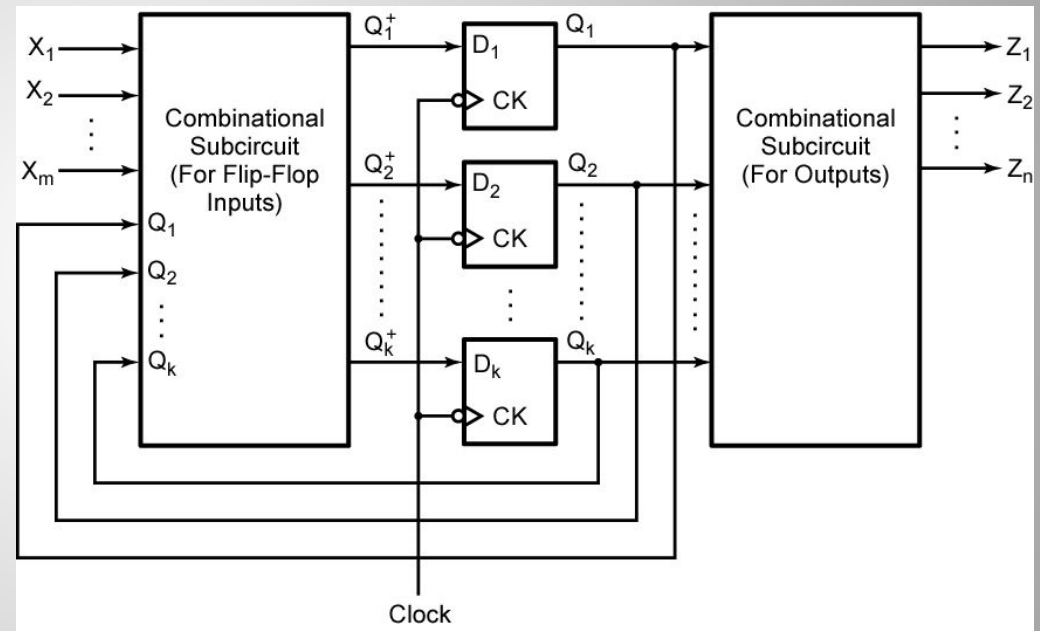

Moore machine

Analysis Example with *D* Flip-Flops

- With *D* flip-flops, the next state can be obtained immediately from the flip-flop input equations:

$$D_A = AX + BX \quad (\text{so } A(t+1) = A(t)X(t) + B(t)X(t))$$

$$D_B = A'X \quad (\text{so } B(t+1) = A'(t)X(t))$$

$$Y = (A + B)X'$$

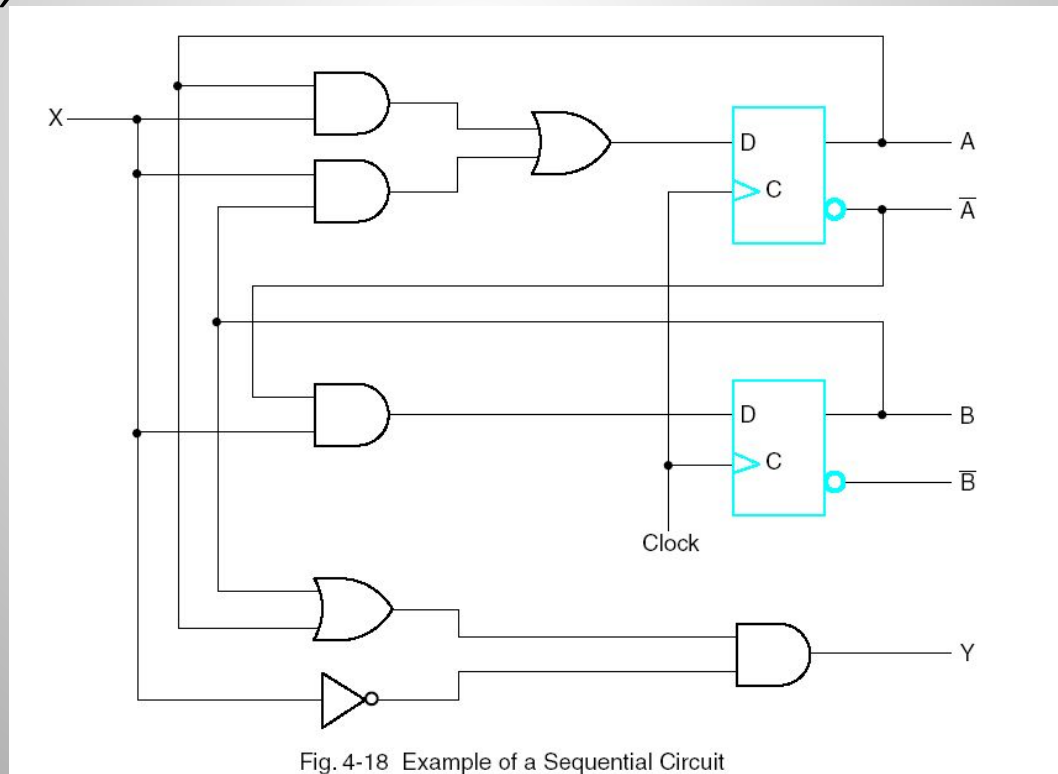


Fig. 4-18 Example of a Sequential Circuit

State Table

- A state table shows the state transitions and outputs in tabular form like below.

□ **TABLE 4-2**
State Table for Circuit of Figure 4-18

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Table 4-2 State Table for Circuit of Figure 4-18

State Table

- An alternative way to draw a state table:

Table 5.3


Second Form of the State Table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

State Diagram


. State transition diagram

 - a circle: a state
- a directed line: transition between the states




input/output

Another Example

 

- . Input equation
 - $D_A = A \oplus x \oplus y$
- . State equation
 - $A(t+1) = A \oplus x \oplus y$
- . Output equation
 - $Z = A$


Present State	Inputs		Next State	Output
A	X	Y	A	Z
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Finding State Diagrams and State Tables

Example. Construct a recognizer that takes one bit at a time and generates an output $Z=1$ when and only when the sequence “1101” is detected at the input. (A typical input sequence and the corresponding output sequence are: $X=00110111001101101$
 $Z=000001000000001001$)

A possible design:

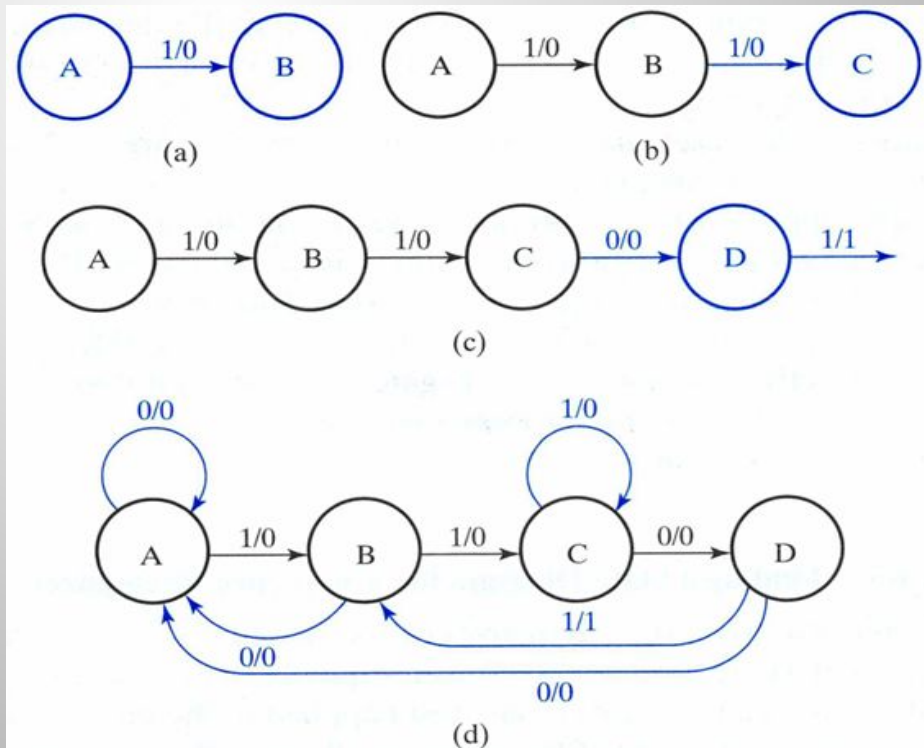

Corresponding state table:

□ **TABLE 4-5**
State Table for State Diagram in Figure 4-21

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

Table 4-5 State Table for State Diagram in Figure 4-21

State names replaced by binary codes:

□ **TABLE 4-7**

Table 4-5 with Names Replaced by Binary Codes

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

Table 4-7 Table 4-5 with Names Replaced by Binary Codes

Remark: There are many different possible binary code assignments which result in final circuit with different complexities.

(Exercise: (i) Complete the design using the above binary code assignment. (ii) Complete the design using another binary code assignment such as 10, 01, 00, 11 for states *A*, *B*, *C*, and *D*, resp.)

State Reduction

- . Two states of a FSM are **equivalent** if the outputs produced for each possible input value are **identical** and the next states for each possible input value are the **same** or **equivalent**
- . Equivalent states may be merged into a single state
- . State reduction through state equivalence can reduce number of flip-flops used


State Reduction Example

Example

— state a a b c d e f f g f g a
 input 0 1 0 1 0 1 1 0 1 0 0
 output 0 0 0 0 0 1 1 0 1 0 0

Table 5.6
State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

 

Equivalent states

- . Equivalent states
 - $g = e$
 - one of them can be removed
- . Reduced state table

Table 5.7
Reducing the State Table


Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Equivalent states

- . New equivalent states
 - $d = f$
 - one of them can be removed
- . State table after further reduction

Table 5.8
Reduced State Table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

 

State Assignment

- . Cost of final circuit depends on state assignment
- . Many possible binary state assignments e.g.

Table 5.9
Three Possible Binary State Assignments

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000

- . *One-hot encoding* uses more FFs but may lead to simpler decoding logic for next state and output

Design Procedure for Sequential Circuit

1. Determine a state diagram or state table
2. State reduction if necessary
3. Assign binary values to the states
 - obtain binary-coded state table
4. Choose the type of flip-flops
 - derive the simplified flip-flop input equations and output equations
5. Obtain the logic diagram

Design Example with D flip-flops

Complete the following design with the given state diagram and the given states to binary codes mapping using *D* flip-flops.

 


Fig. 4-23 State Diagram for Design Example

TABLE 4-8
State Table for Design Example

Present State		Input X	Next State		Output Y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Table 4-8 State Table for Design Example

Deriving the flip-flop input equations and output function:

Output $Y(A,B,X) = \Sigma m(1,5)$

Since D flip-flops are used,

$$D_A(A,B,X) = A(t+1) = \Sigma m(2,4,5,6)$$

$$D_B(A,B,X) = B(t+1) = \Sigma m(1,3,5,6)$$

D_A

		B			
		00	01	11	10
A	0				1
	1	1	1		1

X

D_B

		B			
		00	01	11	10
A	0		1	1	
	1		1		1

X

Y

		B			
		00	01	11	10
A	0		1		
	1		1		

X

Hence, $D_A = AB' + BX'$ $D_B = A'X + B'X + ABX'$

$$Y = B'X$$

Final logic diagram:

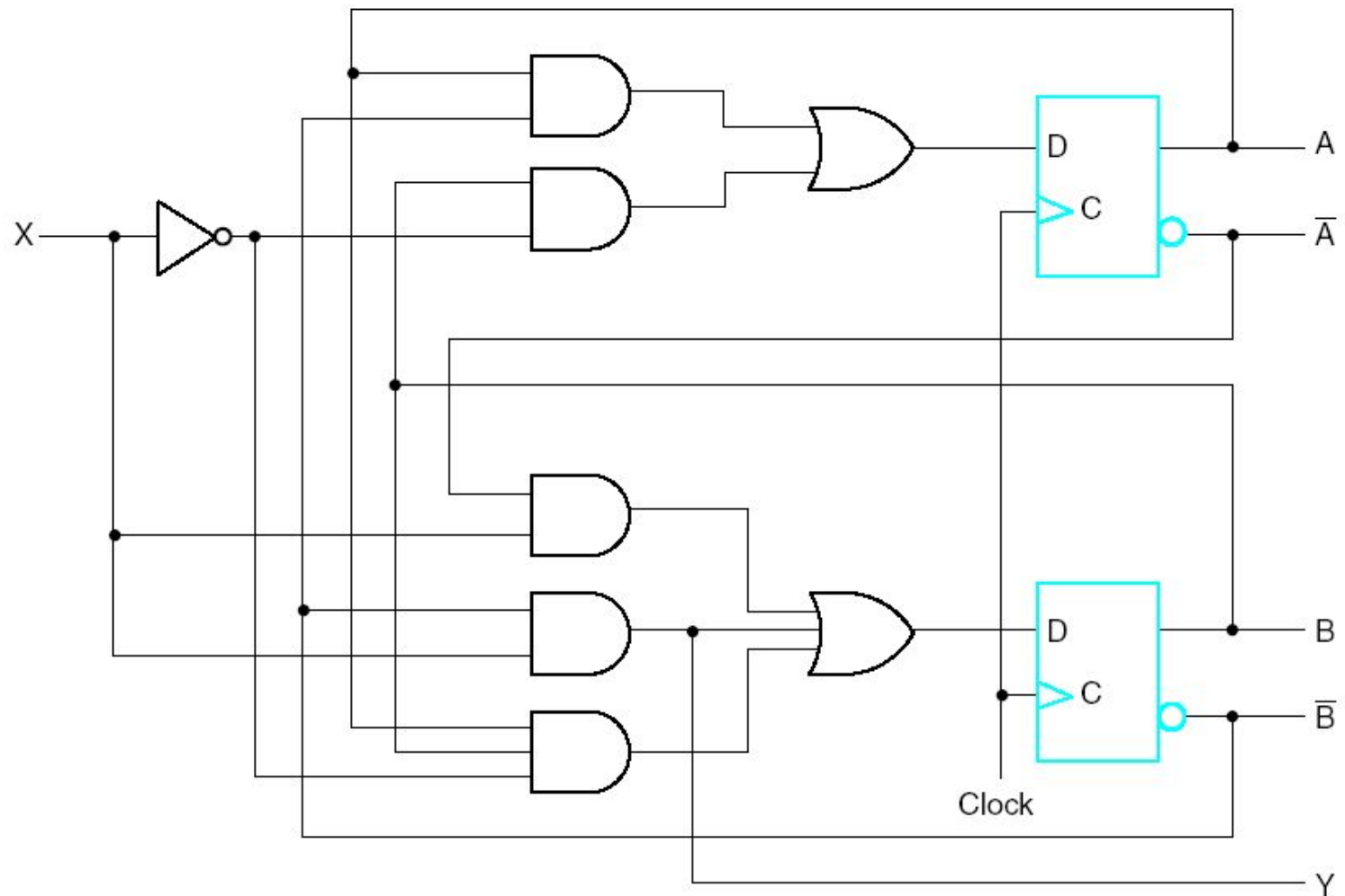


Fig. 4-25 Logic Diagram for Sequential Circuit with D Flip-Flops

Remarks

1. Heuristic State Assignment Guidelines

- i. States having the same next state for a given input should be given adjacent assignments.
 - ii. States that are next states of a single state should be given adjacent assignments.
 - iii. States having the same output for a given input should be given adjacent assignments.
- (2 states are adjacent if they differ in one variable)

Remarks

2. Unused States

- . Unused states can be treated as don't care conditions to simplify the circuit
- . But, for more robust design it may be desirable to specify the next states and/or output values for the unused states upon a malfunction


3. Start State/Reset State

- . A master reset signal is usually provided for initializing the flip-flop states

Remarks

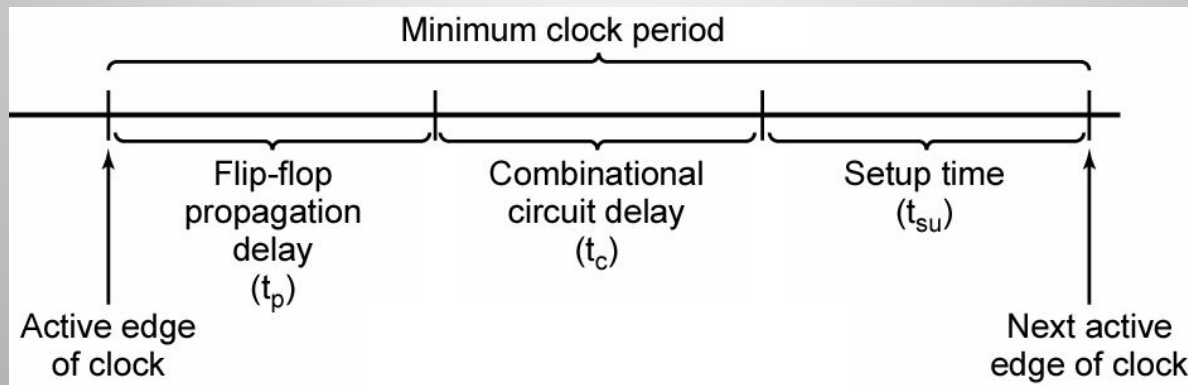4. Timing Issues


- External input changes must be properly timed with respect to active edge to ensure correct operation
- Must give enough time for signals to be transmitted to flip-flop inputs before we sample the flip-flop inputs



 Example: Vending Machine FSM

. Assumptions

- deliver package of gum after 15 cents deposited
- single coin slot for dime(10¢), nickel(5¢)
- no change provided




Vending Machine FSM (cont)

- Possible input sequences

- 3 nickels
- nickel, then dime
- dime, then nickel
- 2 dimes
- 2 nickels, then dime


- Inputs: N, D, reset

- Output: open

 

Vending Machine FSM (cont)

State reduction

 

Present State	Inputs		Next State	Output Open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	X	X
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	X	X
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	X	X
15¢	X	X	0¢	1

reuse states whenever possible

Verilog example


Supplementary Materials

Vending Machine FSM (cont)


Remarks

- . In practice, a vending machine's coin-receptor is a mechanical device and very slow compared to an electronic circuit
- . Inserting a dime (nickel) would cause signal $sense_D$ ($sense_N$) to be asserted for a large number of clock cycles. And there may be an arbitrarily long time between insertion of two consecutive coins (see next page)
- . So, we need to generate a signal $D(N)$ that will be asserted for 1 clock cycle after $sense_D$ ($sense_N$) becomes 1 (see next page)

Vending Machine FSM (cont)

 

(a) Timing diagram

 


(b) Circuit that generates N

Example: Arbiter FSM


- . Control access to a shared resources by different devices in a system
 - Each device provides one input (request) to the arbiter
 - The arbiter provides one output (grant) for each device
 - A device asserts its request signal to request for the resource
 - When the resource is not used, the arbiter selects the highest priority requesting device and asserts its grant signal
 - When a device finished using the resource, it deasserts its request signal
- . E.g. Devices 1 to 3 where device 1 has highest priority, followed by device 2

Arbiter FSM

State diagram

 

Alternative style of state diagram

 

r_i : request signal of device i
 g_i : grant signal for device i

Verilog Code for Arbiter FSM

```
module arbiter (r, Reset, Clock, g);
    input [1:3] r;        // request signals
    input Reset, Clock;
    output wire [1:3] g;   // grant signals
    reg [2:1] state, next;
    parameter Idle = 2'b00, gnt1 = 2'b01, gnt2 = 2'b10, gnt3 = 2'b11;

    // Sequential block
    always @(posedge Clock)
        if (Reset == 1)      state <= Idle;
        else    state <= next;

    // Define output
    assign g[1] = (state == gnt1);
    assign g[2] = (state == gnt2);
    assign g[3] = (state == gnt3);
```

```
// Next state combinational circuit
always @(r, state)
    case (state)
        Idle: casex (r)
            3'b000: next = Idle;
            3'b1xx: next = gnt1;
            3'b01x: next = gnt2;
            3'b001: next = gnt3;
            default: next = Idle;
        endcase
    gnt1: if (r[1]) next = gnt1;
        else next = Idle;
    gnt2: if (r[2]) next = gnt2;
        else next = Idle;
    gnt3: if (r[3]) next = gnt3;
        else next = Idle;
    default: next = Idle;
    endcase
endmodule
```


Verilog Code for FSM

- . There are more than one way to describe a FSM
- . In the sample code above
 - 1st always block introduces flip-flops into the circuit
 - 2nd always block describes the combinational circuit for computing the next state
 - The outputs are defined with conditional assignment statements
- . State transition should use non-blocking assignment (`<=`) as FFs of synchronous sequential circuit are updated concurrently by a common clock

附錄


JK Flip-Flop

 - E.g. Positive-edge triggered JK flip-flop





J	K	$Q(t + 1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	$Q'(t)$

From D flip-flop:

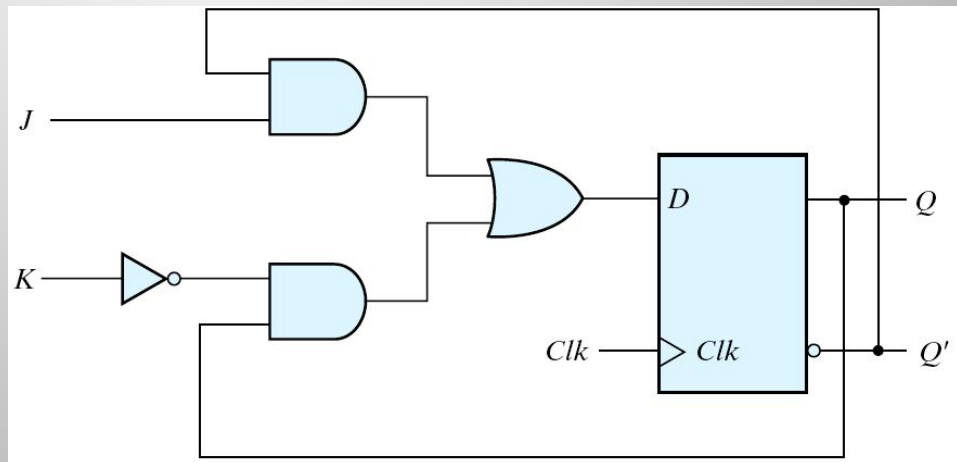


Exercise

  


T Flip-Flop

 - E.g. Positive-edge triggered T flip-flop




T	$Q(t + 1)$
0	$Q(t)$
1	$Q'(t)$

From JK flip-flop:

 

From D flip-flop:

 

Characteristic Table (Next State Table)

- Show the next state as a function of the inputs and present state

Table 5.1
Flip-Flop Characteristic Tables

JK Flip-Flop

<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

D Flip-Flop

<i>D</i>	<i>Q(t + 1)</i>	
0	0	Reset
1	1	Set

T Flip-Flop

<i>T</i>	<i>Q(t + 1)</i>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Characteristic Equation

- . Characteristic equations

- D flip-flop

- $Q(t+1) = D$

- JK flip-flop


- $Q(t+1) = JQ' + K'Q$

- T flop-flop

- $Q(t+1) = T \oplus Q$

Analysis Example with *JK* flip-flops

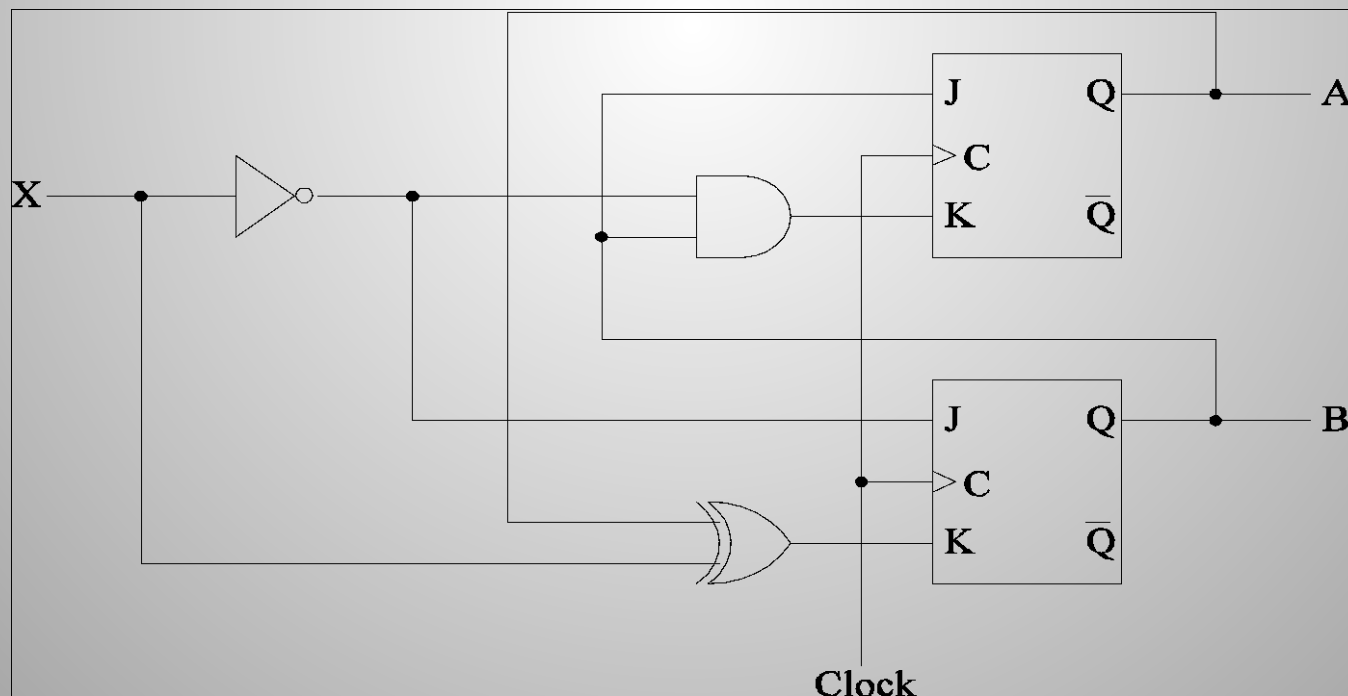- . Obtain the flip-flop input equations in terms of the present state and input variables
- . Use the corresponding flip-flop characteristic table or equation to determine the next state



1. FF input equations:

$$J_A = B, K_A = BX', J_B = X', K_B = A \oplus X$$

2. Compute the next state

Table 5.4

State Table for Sequential Circuit with JK Flip-Flops


Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

. State equations for A and B:

$$A(t+1) = J_A A' + K_A A = BA' + (Bx)'A = A'B + AB' + Ax$$


$$B(t+1) = J_B B' + K_B B = x'B' + (A \oplus x)'B = B'x' + ABx + A'Bx'$$

. State transition diagram

 


Analysis Example with T flip-flops
 
$$\begin{aligned} Q(t+1) &= T \oplus Q \\ &= TQ' + T'Q \end{aligned}$$



(a) Circuit diagram

 

(b) State diagram

. The input and output functions

- $T_A = Bx$
- $T_B = x$
- $y = AB$

. The state equations

- $A(t+1) = (Bx)'A + (Bx)A'$
 $\quad \quad \quad = AB' + Ax' + A'Bx$
- $B(t+1) = x \oplus B$

Table 5.5

State Table for Sequential Circuit with T Flip-Flops

Present State		Input	Next State		Output
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

Design Using JK Flip-Flops or T Flip-Flops

- Need to know the FF input values to bring about the required state change
- Excitation tables for JK flip-flop and T flip-flop:

$Q(t)$	$Q(t = 1)$	J	K	$Q(t)$	$Q(t = 1)$	T
0	0	0	X	0	0	0
0	1	1	X	0	1	1
1	0	X	1	1	0	1
1	1	X	0	1	1	0

(a) *JK* Flip-Flop

(b) *T* Flip-Flop

Design Example with JK flip-flops

Complete the following design with the given state diagram and the given states to binary codes mapping using *JK* flip-flops.

 


Fig. 4-23 State Diagram for Design Example

TABLE 4-8
State Table for Design Example

Present State		Input	Next State		Output
A	B		A	B	Y
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Table 4-8 State Table for Design Example

Deriving the flip-flop input equations and output function:

Output $Y(A,B,X) = \Sigma m(1,5)$


JK flip-flops are used, we derive the required J and K input values:

□ **TABLE 4-11**
State Table with JK Flip-Flop Inputs


Present State		Input	Next State		Flip-Flop Inputs			
A	B	X	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

Table 4-11 State Table with JK Flip-Flop Inputs


$J_A:$

 

$K_A:$

 

$J_B:$

 

$K_B:$

 


Fig. 4-27 Maps for J and K Input Equations

Hence, $J_A = BX'$ $K_A = BX$
 $J_B = X$ $K_B = (A \oplus X)'$
 $Y = B'X$

Final logic diagram:


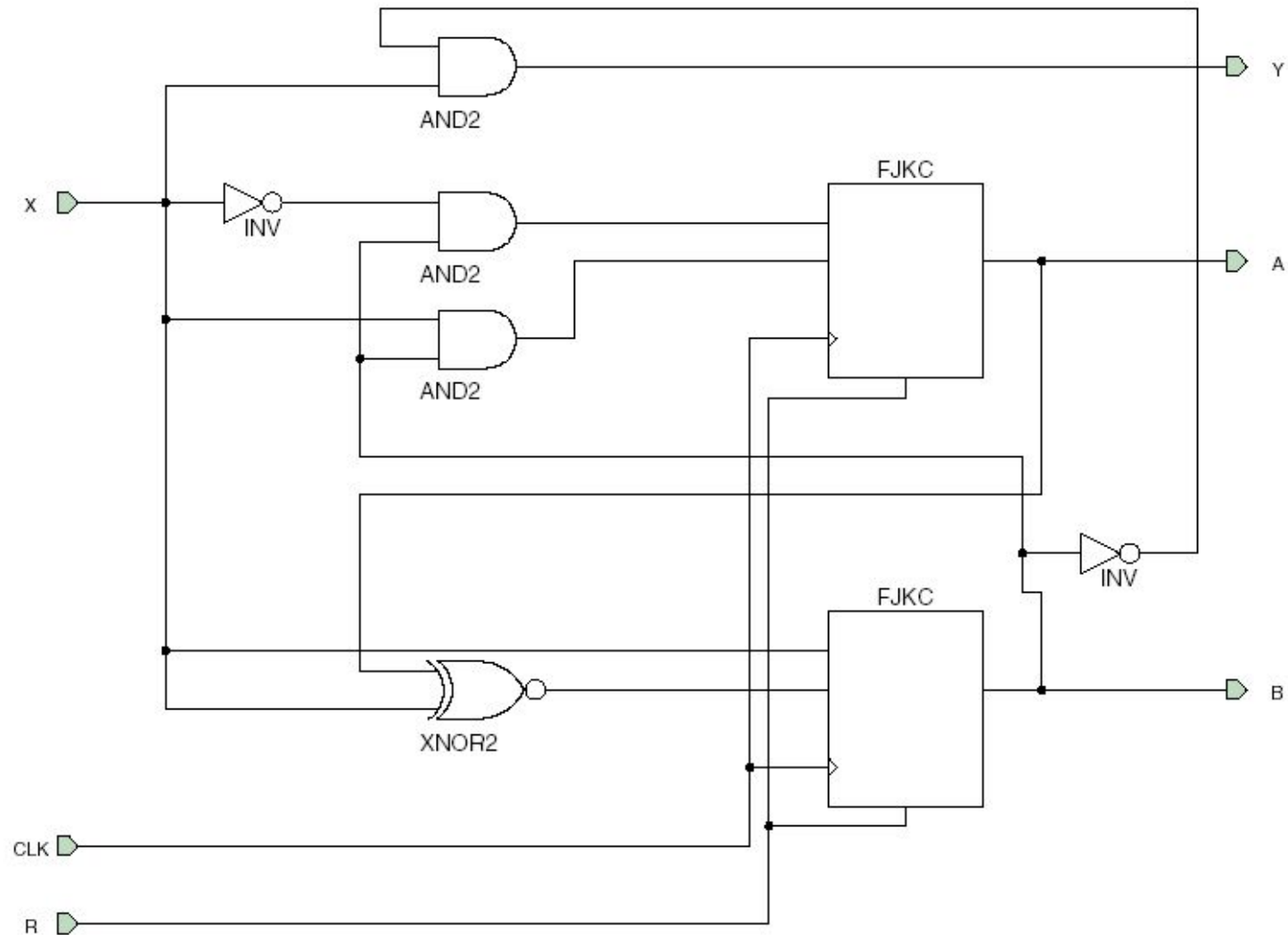


Fig. 4-28 Logic Diagram for Sequential Circuit with *JK* Flip-Flops

Design Example with *T* flip-flops

 - . A n -bit binary counter
 - the state diagram
 - no input (except for the clock)



. The state table and required flip-flop inputs:

Table 5.14
State Table for Three-Bit Counter

Present State			Next State			Flip-Flop Inputs		
A_2	A_1	A_0	A_2	A_1	A_0	T_{A2}	T_{A1}	T_{A0}
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

A_1A_0		A_1			
		00	01	11	10
A_2	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		A_0			

$$T_{A2} = A_1A_0$$

		A_1A_0			
		00	01	11	10
A_2	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		A_0			

$$T_{A1} = A_0$$

		A_1A_0		A_1	
		00	01	11	10
A_2	0	m_0 1	m_1 1	m_3 1	m_2 1
	1 <td>m_4 1</td> <td>m_5 1</td> <td>m_7 1</td> <td>m_6 1</td>	m_4 1	m_5 1	m_7 1	m_6 1
		x			

$$T_{A0} = 1$$


• Logic simplification using the K map

– $T_{A2} = A_1 A_0$

– $T_{A1} = A_0$




– $T_{A0} = 1$

• The logic diagram

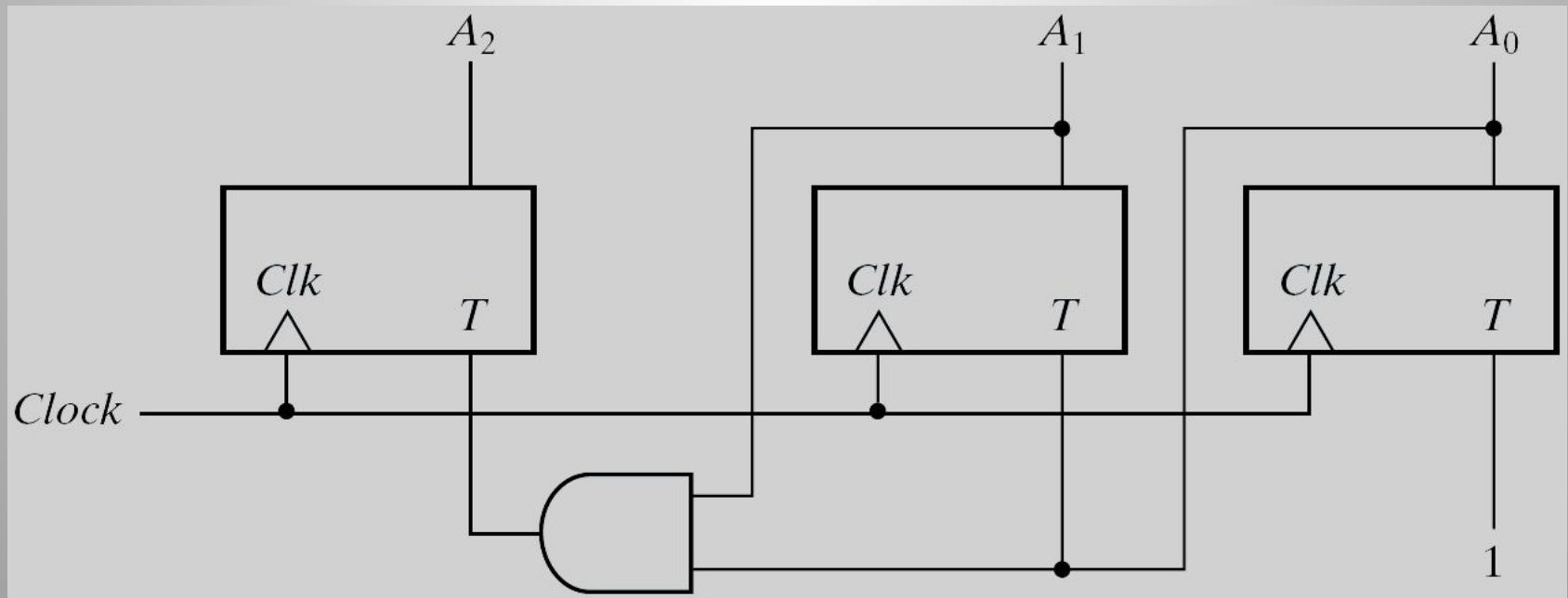

附錄

Sequential networks

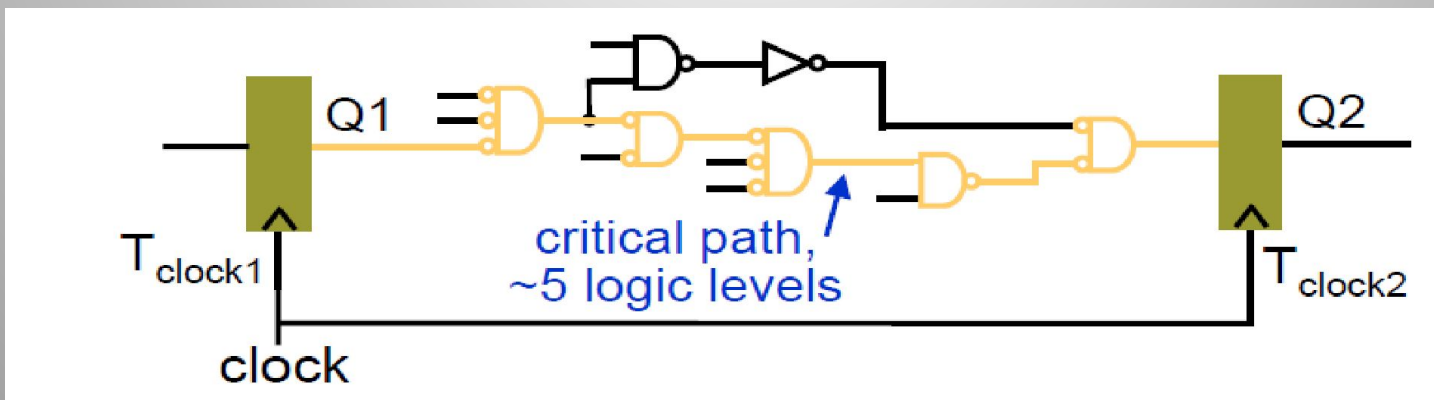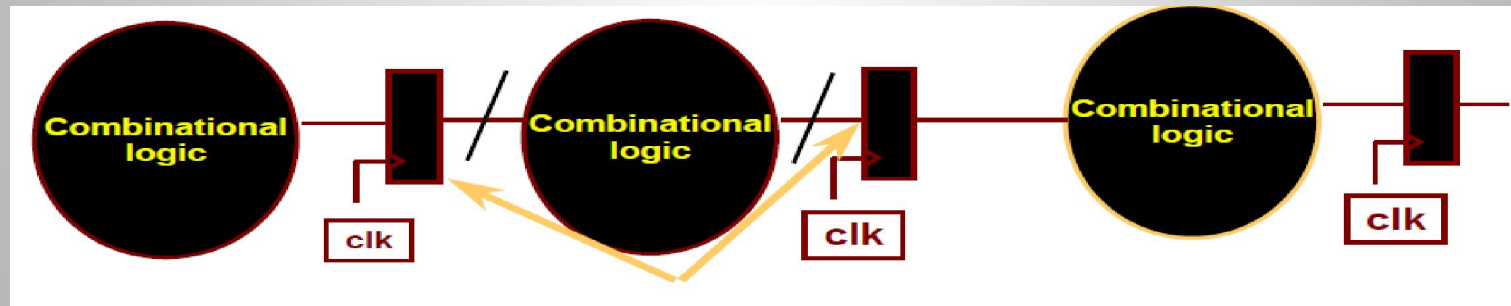 

Test bench

```
. https://verilogguide.readthedocs.io/en/latest/verilog/testbench.html
`timescale 1ns / 1ps
module Lab1_Team5_Comparator_4bits_tb;
    reg [3:0] A,B;
    wire A_lt_B, A_gt_B, A_eq_B;

    Comparator_4bits c(A, B, A_lt_B, A_gt_B, A_eq_B);

    initial begin
        #10 A=4'b1010; B=4'b1010; // edit your own testbench
        $display ("time = %t A = %b , B = %b , A_lt_B=%b,A_gt_B=%b,A_eq_B=%b", $time, A,B,A_lt_B, A_gt_B, A_eq_B);

        #10 A= 4'b0000; B= 4'b1111;
        $display ("time = %t A = %b , B = %b , A_lt_B=%b,A_gt_B=%b,A_eq_B=%b", $time, A,B,A_lt_B, A_gt_B, A_eq_B);

        $finish;
    End

    initial begin $monitor("time = %t, A = %b , B = %b , A_lt_B=%b,A_gt_B=%b,A_eq_B=%b", $time, A,B,A_lt_B, A_gt_B,
    A_eq_B);
    End

endmodule
```