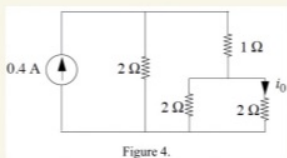



Quiz 2 solution



1.



4.

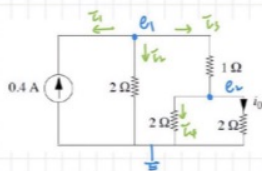

$$\tilde{I}_0 = \frac{e_2}{2}$$

$$\text{KCL @ } e_1: -0.4 + \frac{e_1}{2} + \frac{e_1 - e_2}{1} = 0$$


$$\text{KCL @ } e_2: \frac{e_2 - e_1}{1} + \frac{e_2}{2} + \frac{e_2}{2} = 0$$

$$\Rightarrow e_1 = 0.4 \text{ V}, \quad e_2 = 0.2 \text{ V}$$

$$\Rightarrow \tilde{I}_0 = \frac{0.2}{2} = 0.1 \text{ A} \quad \#$$

2.

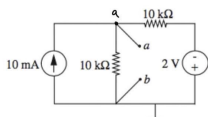
2. Find the Thevenin equivalent circuit of the circuit at terminals a, b, in the following figure. (18%)



KCL at a

$$10 \text{ mA} + \frac{-2 - V_a}{10 \text{ k}} + \frac{-V_a}{10 \text{ k}} = 0$$
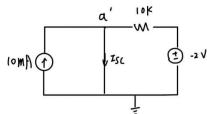
$$\frac{2V_a + 2}{10^4} = 10^{-2} \Rightarrow 2V_a + 2 = 100, \quad V_a = 49 \text{ V} = V_{oc} \quad \#$$




KCL at a'

$$10 \text{ mA} - I_{sc} + \frac{-2}{10 \text{ k}} = 0$$

$$I_{sc} = 10 \text{ mA} - 0.2 \text{ mA} = 9.8 \text{ mA} \quad \#$$


$$R_{TH} = \frac{V_{oc}}{I_{sc}} = 5 \text{ k} \Omega$$

ANS:

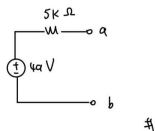


3.

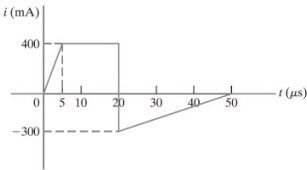3. The current is applied to a capacitor as shown in the following figure. The capacitance of this capacitor is $1 \mu F$. The initial voltage of the capacitor is zero.
- (a) Derive and plot the voltage across the capacitor. (16%)
- (b) Determine the energy stored in the capacitor at $t = 30 \mu s$. (8%)



- a. Function of current at each section :
- $$\begin{cases} 0 \sim 5 : i = 80t \\ 5 \sim 20 : i = 400 \\ 20 \sim 50 : i = -500 + 10t \end{cases}$$
- For capacitor, we have formula $i = C \frac{dv}{dt} \rightarrow V = \frac{1}{C} \int i dt$
- Therefore, function of voltage at each section :
- $$\begin{cases} 0 \sim 5 : V \text{ is quadratic} \\ 5 \sim 20 : V \text{ is linear} \\ 20 \sim 50 : V \text{ is quadratic} \end{cases}$$
- Moreover, we can calculate the area (or integral i) to obtain
- $$\begin{cases} t = 0 \mu s, V = 0 V \\ t = 5 \mu s, V = 1 V \\ t = 20 \mu s, V = 7 V \\ t = 50 \mu s, V = 2.5 V \end{cases}$$

So, we can plot V-t diagram as below :

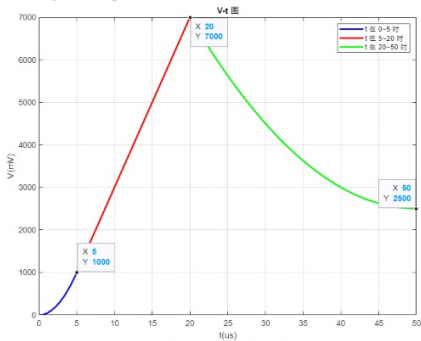


Or solve for the exact function

$$\begin{cases} 0 \sim 5 : V = 40t^2 \\ 5 \sim 20 : V = 400t - 1000 \\ 20 \sim 50 : V = -500t + 5t^2 + 15000 \end{cases}, \text{ where unit} \\ = mV$$

- b.
- $i @ 30 \mu s = -200 \text{ mA}$
- $V @ 30 \mu s = 7 + (-300 - 200) \cdot \frac{10}{2} = 4.5 V$
- energy stored in capacitor : $U = \frac{1}{2} CV^2 = \frac{1}{2} \cdot 1 \mu + 4.5^2 = 10.125 \mu J$

4.

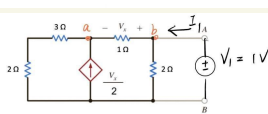

a: $\frac{V_x}{1} + \frac{V_x}{2} = \frac{1-V_x}{5} \Rightarrow V_x = \frac{2}{7} V$

b: $I_1 = \frac{V_x}{1} + \frac{1}{2} = \frac{21}{34} A$

$R_{TH} = \frac{V_1}{I_1} = \frac{1}{\frac{21}{34}} = \frac{34}{21} \Omega = R_N$

equivalent circuit $\Rightarrow \begin{cases} R_N = \frac{34}{21} \Omega \end{cases}$

$I_N = \frac{V_{TH}}{R_{TH}} = \frac{0V}{R_{TH}} = 0 A$

Quiz 2

$$5. \quad \bar{V}_C = C \frac{dV_0}{dt} = \frac{V_S - V_0}{R}$$

$$\Rightarrow RC \frac{dV_0}{dt} + V_0 = V_S$$

① for V_{Op}

$$\text{guess } V_{Op} = V_S$$

$$\Rightarrow RC \frac{dV_0}{dt} + V_S = V_S = V_S \Rightarrow V_{Op} = V_S$$

② for V_{Oh} :

$$RC \frac{dV_{Oh}}{dt} + V_{Oh} = 0$$

$$\text{guess } V_{Oh} = A e^{st}$$

$$\Rightarrow RC \frac{d(Ae^{st})}{dt} + Ae^{st} = 0 \Rightarrow sRC A e^{st} + A e^{st} = 0$$

$$\Rightarrow A(sRC + 1)e^{st} = 0 \Rightarrow s = -\frac{1}{RC} \rightarrow V_{Oh} = A e^{-\frac{t}{RC}}$$

$$\Rightarrow V_0 = V_S + A e^{-\frac{t}{RC}}, t \geq 0$$

$$V_0(t=0) = V_S + A = 1 \rightarrow A = 1 - V_S$$

$$\Rightarrow V_0 = 4 - 3 e^{-\frac{t}{0.01}} \text{ (V)}$$

