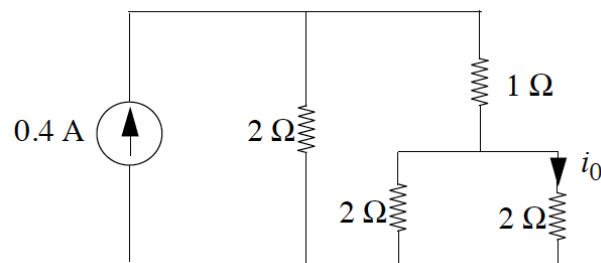


Quiz 2 (Total 100 points)


It is a closed-book, closed-note quiz. Cheating leads to 0% score.

Calculator is allowed. Please show the process of thinking/calculation. Indicate your final answers clearly. Unit is needed if applicable.


1. Find the current i_0 in the following figure. (14%)



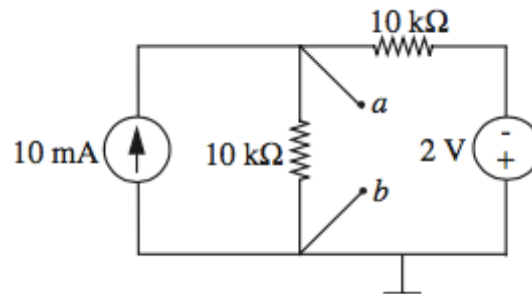
2. Find the Thevenin equivalent circuit of the circuit at terminals a, b, in the following figure. (18%)



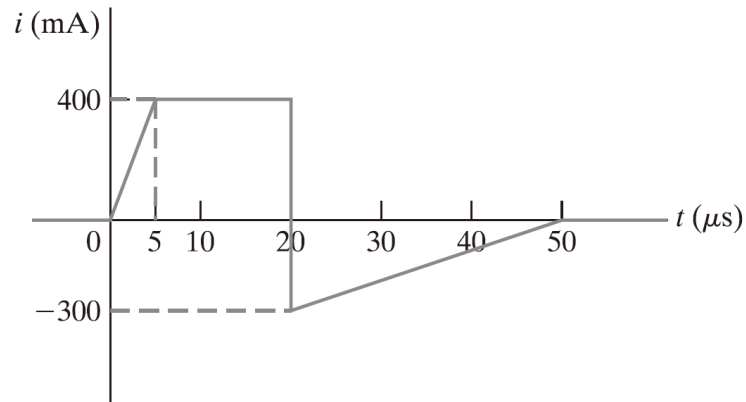3. The current is applied to a capacitor as shown in the following figure. The capacitance of this capacitor is $1\ \mu\text{F}$. The initial voltage of the capacitor is zero.
- (a) Derive and plot the voltage across the capacitor. (16%)
- (b) Determine the energy stored in the capacitor at $t = 30\ \mu\text{s}$. (8%)



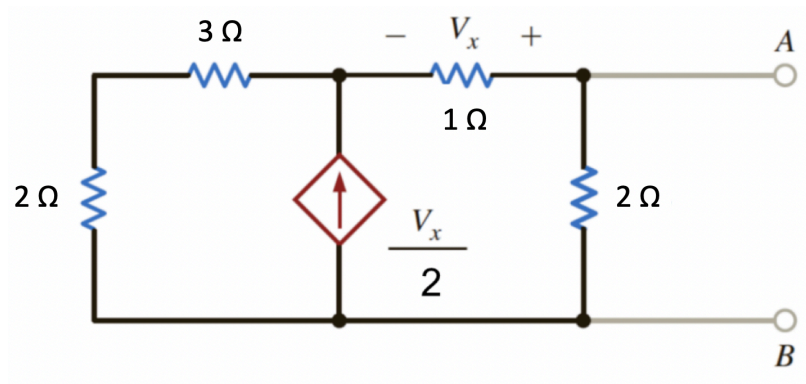4. Find the Norton equivalent circuit of the circuit at terminals A, B, in the following figure. (18%)



5. Analyze the following RC circuit where $R = 10 \text{ k}\Omega$ and $C = 1 \mu\text{F}$. $v_o(t = 0) = 1 \text{ V}$, and the input $v_s(t) = 4 \text{ V}$ for $t \geq 0$. Derive and plot v_o for $t \geq 0$. (26%)

