


國立清華大學

Examples of systems modeled by 1st-order ODEs (Ch3)

Examples :

Example 1 : Series circuit

LR-series circuit

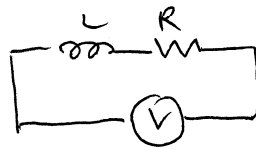

Given $V=12$, $R=10\ \Omega$,
 $L=\frac{1}{2}\text{ H}$, $i(0)=0$

Example 2 : Population dynamics

growth of population :

國立清華大學

But, due to limited resources, at some point, the growth rate will decrease.

For simplicity, let's assume growth rate

Remarks:

① DE with a form of $\frac{dx}{dt} = r x (1 - \frac{x}{K})$ is called
Such DE is commonly shown in a system with

② Features of the